



Exercise: Low Noise Charge Amplifier

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Goal

- In this concluding exercise for the charge amplifier, we want to design a MOS-only (i.e. no more stuff from analogLib..) charge amplifier and determine its noise.
 - Only i_{dc} and v_{dc} sources for bias will be left.
- ‘Specifications’:
 - $C_{det} = 10 \text{ pF}$
 - CR-RC shaper
 - Peaking time $T_{peak} = 100 \text{ ns}$
 - Supply: 1.8 V
 - Power: <5 mW
- For the feedback of the CSA, use the transconductor from exercise 2



The Amplifier

- For the main amplifier, use the following straight cascode design, followed by a source follower:

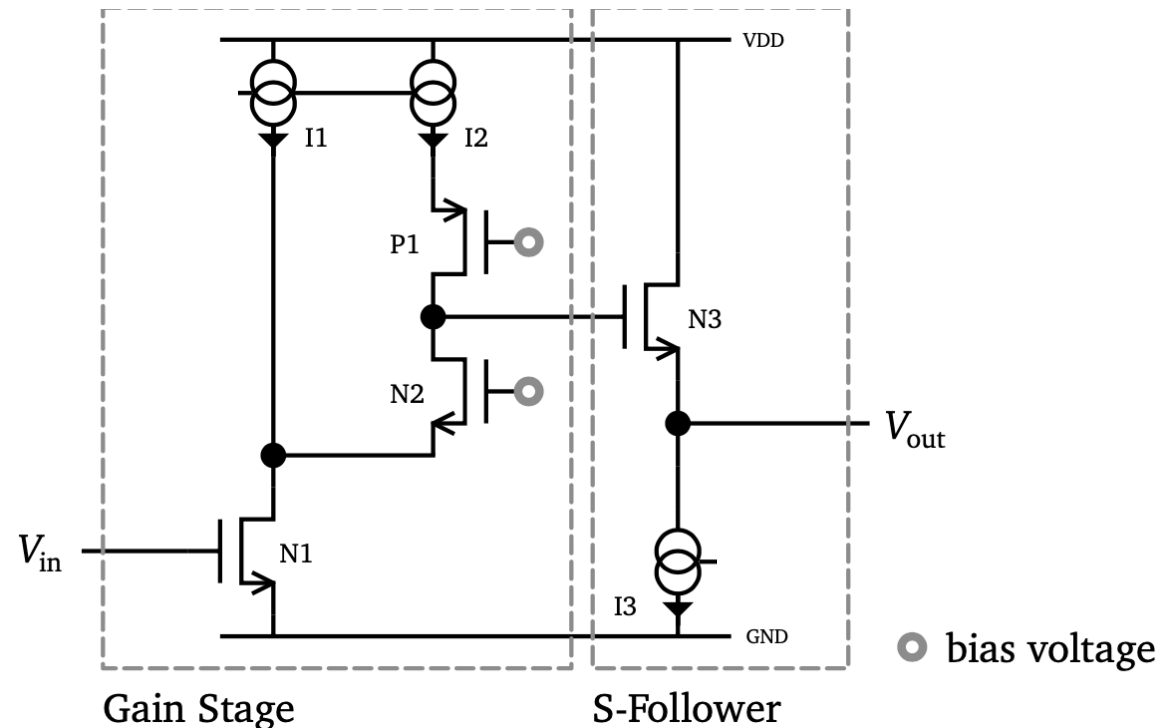


Image taken from PhD of Tim Armbruster




The Amplifier

- Current source I1 provides the major current of input MOS N1. Use $>1\text{mA}$. Make its noise as small as possible (low g_m).
 - The saturation of I1 voltage can be high!
- Input MOS N1 is critical for noise.
 - Increase its g_m . Do not use minimal length
- Cascode N2 must bias N1 into saturation
- I2 provides the current for the gain branch. Use $\sim 1/10$ of the main current. Its output resistance must be high for gain. You may achieve this with cascode P1 (but you can do without).
- The source follower has at least two tasks:
 - Shift the output voltage down so that DC feedback ($V_{\text{out}}=V_{\text{in}}$) is possible
 - Buffer the gain node so that we can put a resistive load (i.e. draw current)
- Bias the source follower with $\sim 100\ \mu\text{A}$



The Shaper

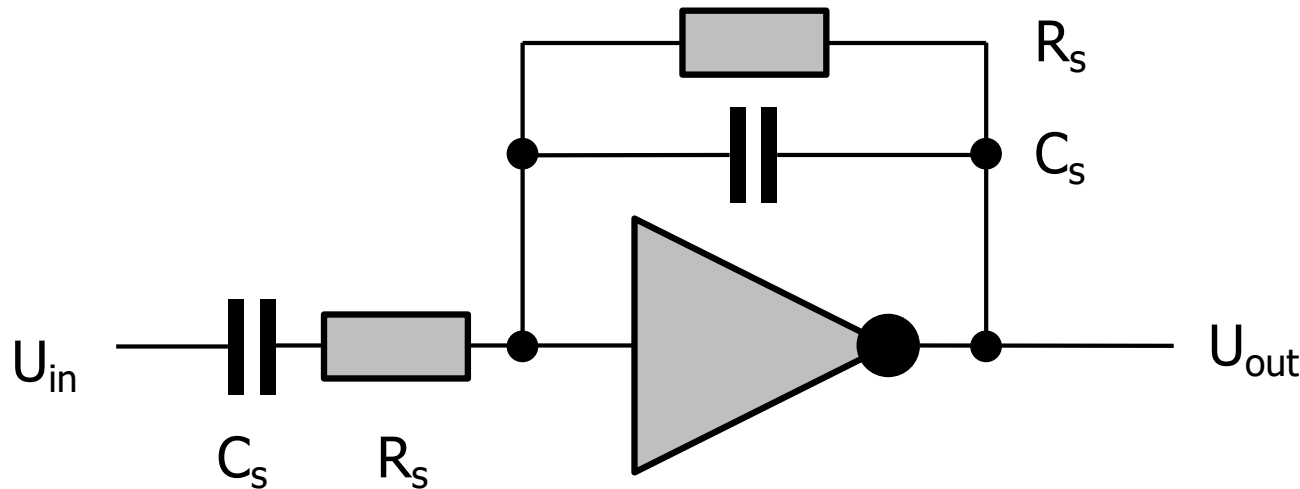- You can use the following simple shaper topology
- The amplifier can be the same as for the CSA, maybe with smaller current.



- Calculate the transfer function. Is it CR-RC?
- Can you change the component value keeping the time constant and CR-RC, but adding (voltage) gain?
- Chose R_s large enough so that it does not load the source follower of the CSA too much!



Comments

- Use C_f as small as possible, but such that the CSA still reaches ‘nearly’ its nominal gain at a larger C_{in} of 30 pF.
- You can try to connect C_f to the node between amplifier and source follower.
- Make the CSA discharge much slower than T_{peak} .
 - (What happens if you discharge too fast? How do the shaper pulses look like? There are tricks to get rid of this effect (‘pole-zero-cancellation’))
- Make sure the cascodes are biased correctly!



Final results

- Inject increasing charges and look at the pulse shapes at the output of the CSA and the shaper
- Check that this does NOT depend a lot on
 - C_{det}
 - The bias current in the amplifier
 - The bias of the source follower
 - The bias current in the shaper
- Determine overall noise at the shaper output (noise integral), referred back to the input (i.e. the ENC)
- Check how the noise depends on
 - C_{det}
 - The bias current in the amplifier
 - The bias current in the shaper
 - ...