



Some BASICS

Voltage, Current, Components and AC behavior,
Bode Plots, Transfer Functions, Thévenin Equivalent,
High-pass and Low-pass filters,...



Prefixes for Units

- For writing down small or large quantities, exponents can be used: $1.5 \times 10^6 \Omega$, $3 \times 10^{-9} A$

- To simplify, **prefixes** in steps of 1000 are used:

• T	Tera	$\times 10^{12}$
• G	Giga	$\times 10^9$
• M	Mega	$\times 10^6$
• k	Kilo	$\times 10^3$
•	1	$\times 10^0$
• m	Milli	$\times 10^{-3}$
• μ (or u)	Mikro	$\times 10^{-6}$
• n	Nano	$\times 10^{-9}$
• p	Piko	$\times 10^{-12}$
• f	Femto	$\times 10^{-15}$
• a	Atto	$\times 10^{-18}$

- Try to learn: ‘Piko \times Kilo = Nano, Milli \times Mega = Kilo,...’




VOLTAGE, CURRENT, KIRCHHOFF'S LAWS




Voltage

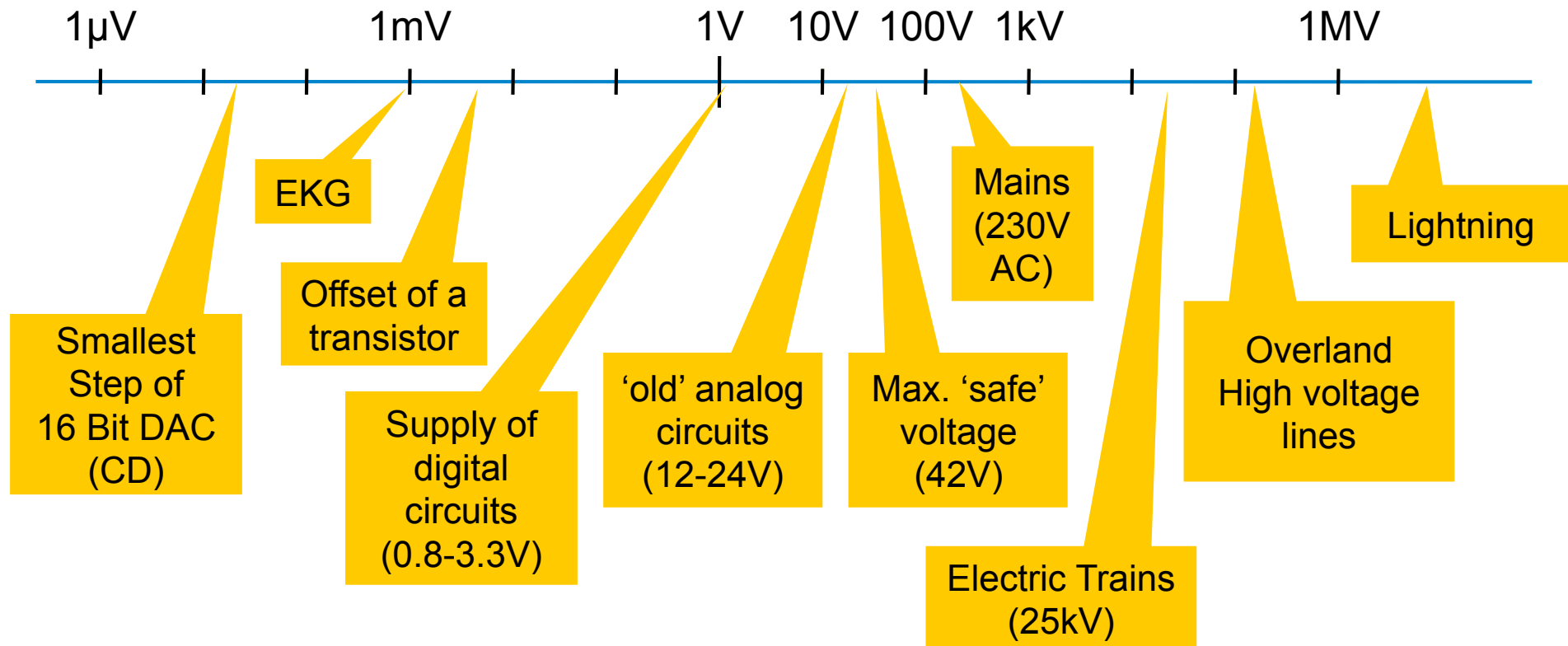- Voltage is the *difference* in electrical potentials, i.e. the energy required to move a unit charge in an electric field
 - This is only well defined in static fields where $\text{rot } \vec{E} = 0$
- Unit: Volt (V)






Ground

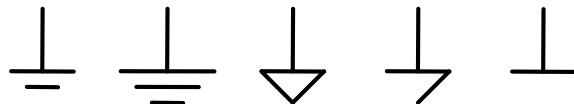- Voltages are really potential **differences**
- To simplify life, we define a **reference potential** to which voltages are referred. We call it '**ground**'
 - i.e. when we say 'net A has 3V', we mean $V_A - V_{\text{GND}} = 3\text{V}$
 - Ground is at 0V by definition
- Common ground symbol are: 
- (Later we may use several grounds, all at 0V, but separated, for digital and analogue circuit parts)



Current

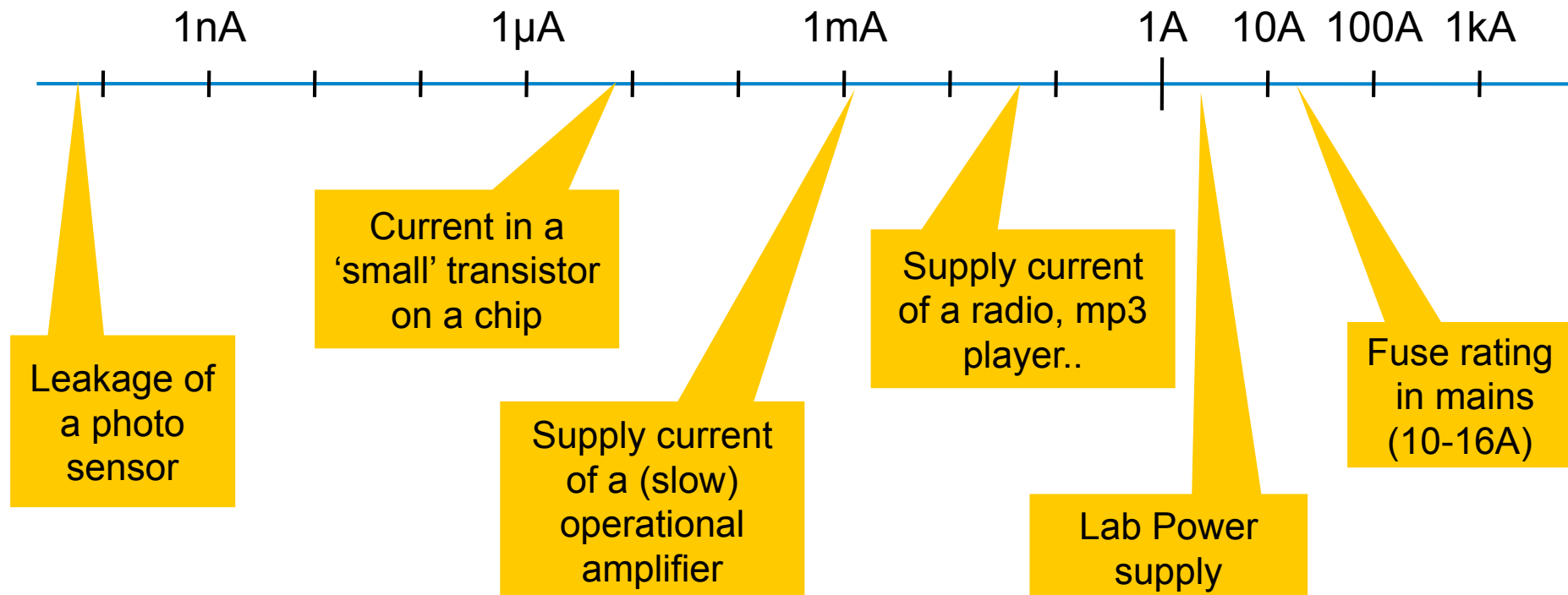- Electric current is the flow (or change) of electric charge
- $i = dQ / dt$
- Unit: Ampere (A)






Kirchhoff's Laws

1. The sum of currents at any node is zero:

$$\sum_{k=1}^n I_k = 0$$

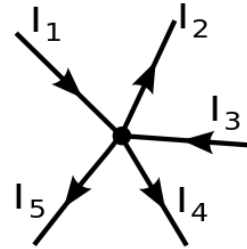

- Follows from charge conservation

2. The sum of voltages in any closed loop is zero:


$$\sum_{k=1}^n U_k = 0$$

The sign of the U_k is fixed by a consistent ordering of the nodes in the loop.

Example:

$$U_1 = U_B - U_A, U_2 = U_C - U_B, \dots$$

$$U_1 + U_2 + U_3 + U_4 = 0$$

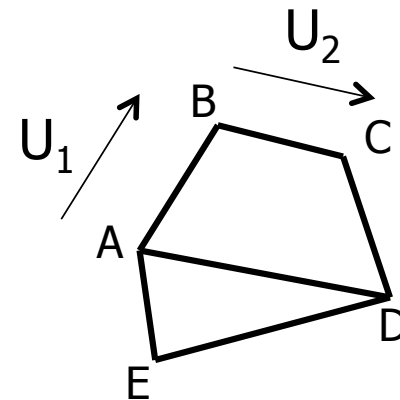

- Follows from energy conservation



RESISTORS & CAPACITORS



Resistors


- A resistor is a 2 terminal device
- When voltage is applied, a current flows
- The current is **proportional** to the voltage (Ohms's law):

$I = U \times G$ G is the **conductivity** (Leitwert) in Siemens [S]
or

$I = U / R$ R is the **resistivity** (Widerstand) in Ohm [Ω]

- G and R describe the same relation. $G = 1/R$, $R = 1/G$


- Symbols:

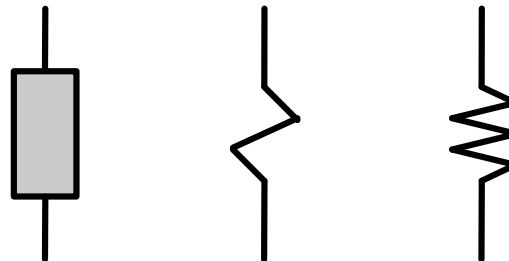

- Note: **Ohm's law is not trivial**. Not all materials are 'ohmic'



Parallel Connection of Resistors

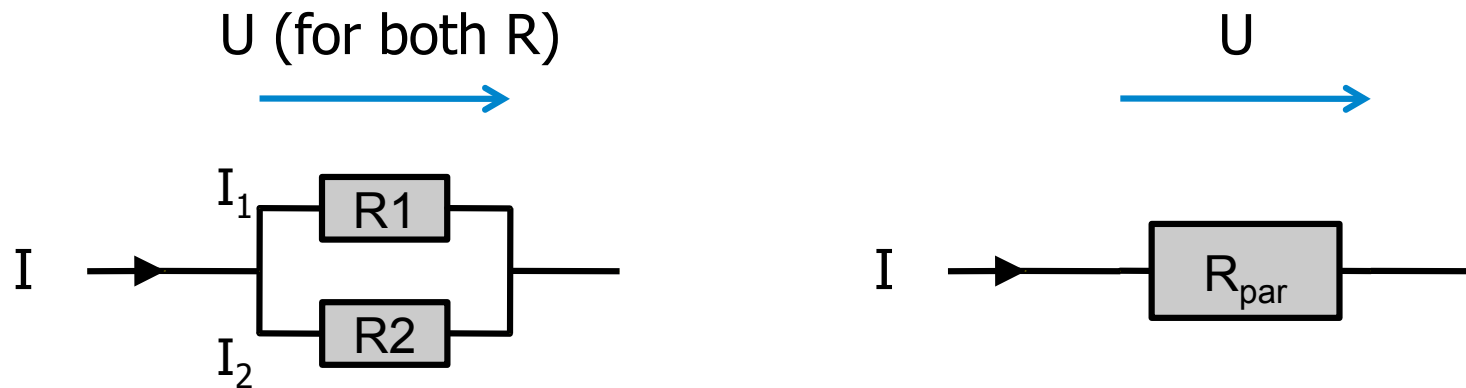


$$I = I_1 + I_2 = G_1 \times U + G_2 \times U = (G_1 + G_2) \times U$$

$$I = G_{\text{par}} \times U$$

$$G_{\text{par}} = G_1 + G_2 \quad \leftrightarrow \quad 1/R_{\text{par}} = 1/R_1 + 1/R_2$$



Series Connection of Resistors

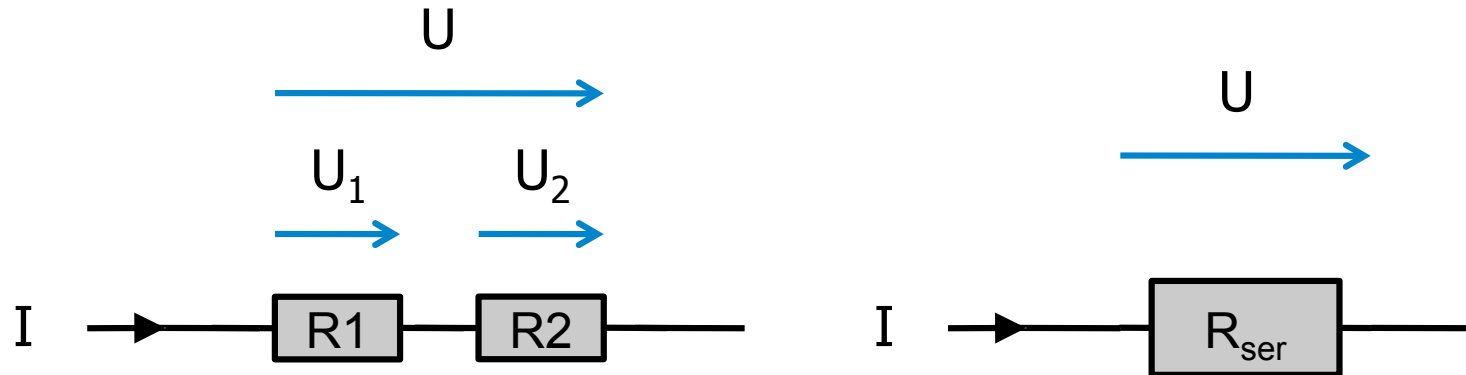

$$U = U_1 + U_2 = I \times R_1 + I \times R_2 = I \times (R_1 + R_2)$$


$$U = I \times R_{\text{ser}}$$

$$R_{\text{ser}} = R_1 + R_2 \quad \leftrightarrow \quad 1/G_{\text{ser}} = 1/G_1 + 1/G_2$$



The Voltage Divider (*without* load current!)

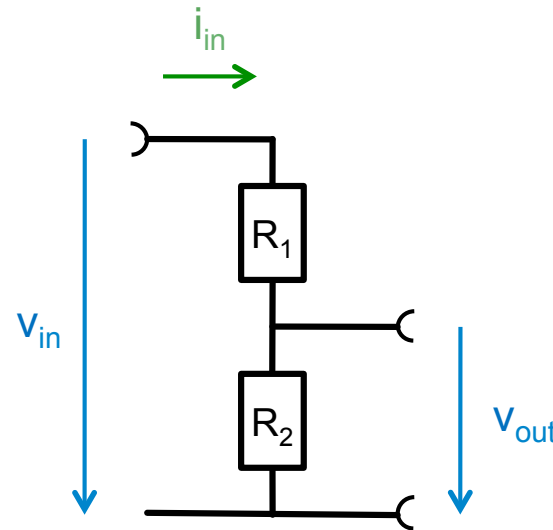- A very common topology is the voltage divider:




- The input current $I_{in} = V_{in} / (R_1 + R_2)$
- This current flows through R_1 and R_2 , i.e. $I_{in} = I_{R1} = I_{R2}$
- On R_2 , it develops a voltage $V_{out} = I_{R2} R_2 = V_{in} R_2 / (R_1 + R_2)$


- Overall: $V_{out} / V_{in} = R_2 / (R_1 + R_2)$



Capacitors

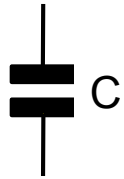

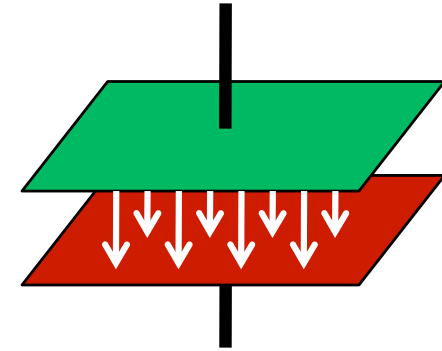- A capacitor can store electrical charge
- Prototype: parallel plate capacitor
 - **Charge Q** on plates generates field (through Gauss' law)
 - Field between plates gives a **voltage V**
- $Q = C \times V$: capacitance is factor between charge and voltage
 - A **large** capacitor can store a **lot** of charge at **low** voltage
- The voltage on a capacitor is given by the current integral:



$$V = \frac{Q}{C} = \frac{1}{C} \int I(t) dt \quad \Leftrightarrow \quad I(t) = C \frac{dV}{dt}$$

- The stored energy is:

$$dE(Q) = V(Q)dQ \Rightarrow E = \int_0^Q V(Q')dQ' = \int_0^Q \frac{Q'}{C}dQ' = \frac{Q^2}{2C} = \frac{1}{2}CV^2$$




Charging a Capacitor

- At constant current I : **linear ramp**:

$$I(t) = I_0 = \text{const}$$

$$\Delta Q(t) = \int_0^t I(t') dt' = \int_0^t I_0 dt = I_0 \times t$$
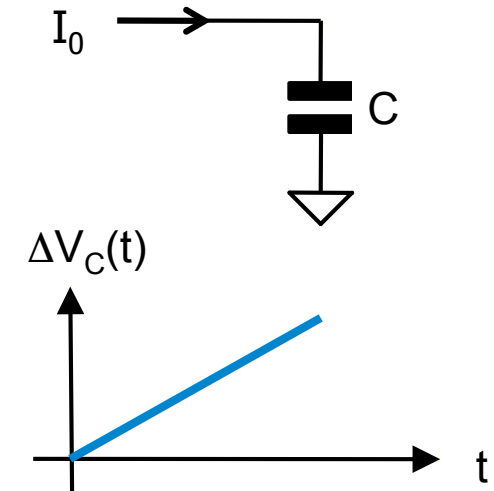
$$\Delta U(t) = \frac{\Delta Q(t)}{C} = \frac{I_0}{C} \times t$$




- Through resistor R : **exponential settling**:

$$I(t) = \frac{U_0 - U(t)}{R}$$

$$\frac{dU(t)}{dt} = \frac{I(t)}{C} = \frac{U_0 - U(t)}{RC}$$
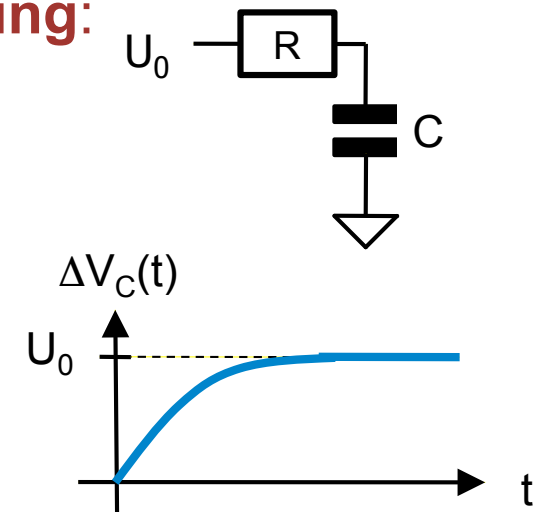
$$\text{Solution : } U(t) = U_0 - U_0 e^{-\frac{t}{RC}}$$






VOLTAGE & CURRENT SOURCES





Voltage Sources

- A voltage source has 2 terminals:

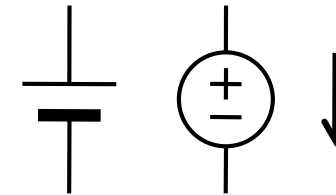

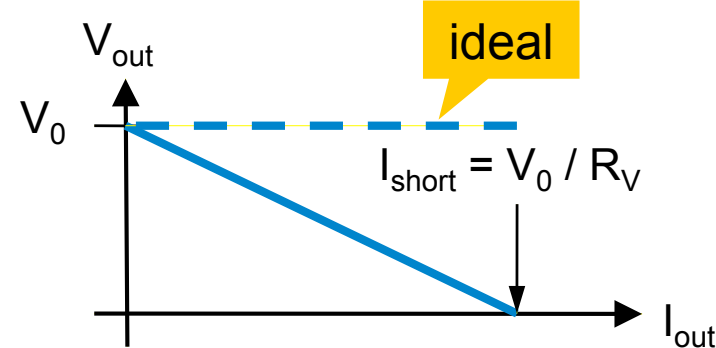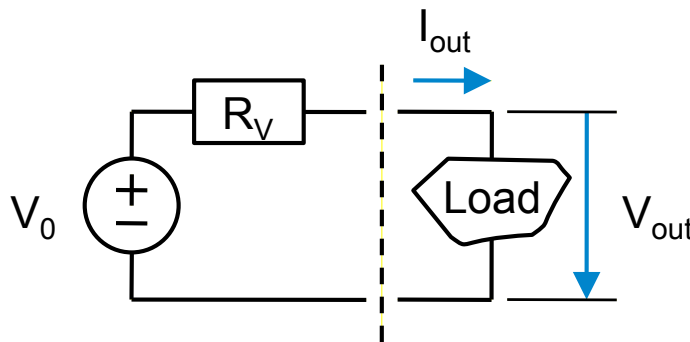- An **ideal** voltage source maintains the voltage for **any** output current ('1000 A')
- The voltage of a **real** source drops with **load current**.
- This is modeled by a **series** resistor (internal resistor, source resistor):




- The **open voltage** is V_0 ($I_{out}=0 \rightarrow$ voltage drop over R_V is 0)
- The **short circuit current** is $I_{short} = V_0 / R_V$
- Note: '**Good**' voltage sources have **low** $R_V \rightarrow 0$





Current Sources

- A current source has 2 terminals:

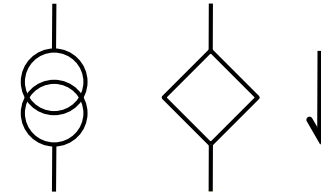

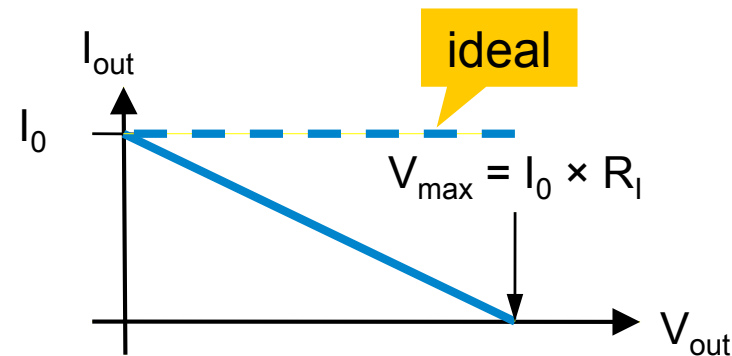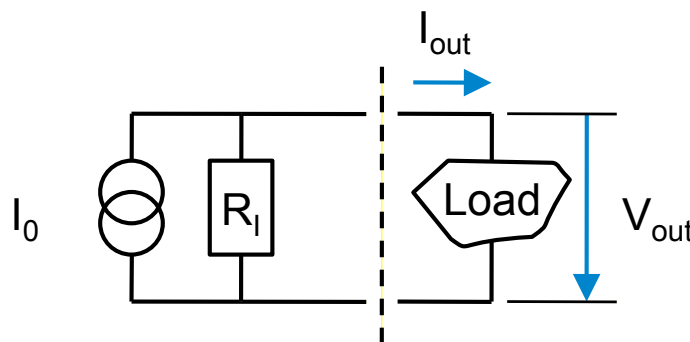- An **ideal** current source maintains the current for **any** output voltage
- The current of a **real** source drops with **load voltage**.
- This is modeled by a **parallel** resistor (internal resistor, source resistor):




- The **short circuit current** is I_0 (no voltage at $R_i \rightarrow$ no current)
- At a voltage of $I_0 \times R_i$ no more current flows (all flows in R_i)
- Note: '**Good**' current sources have **high** $R_i \rightarrow \infty$




Equivalence of U- and I-Source

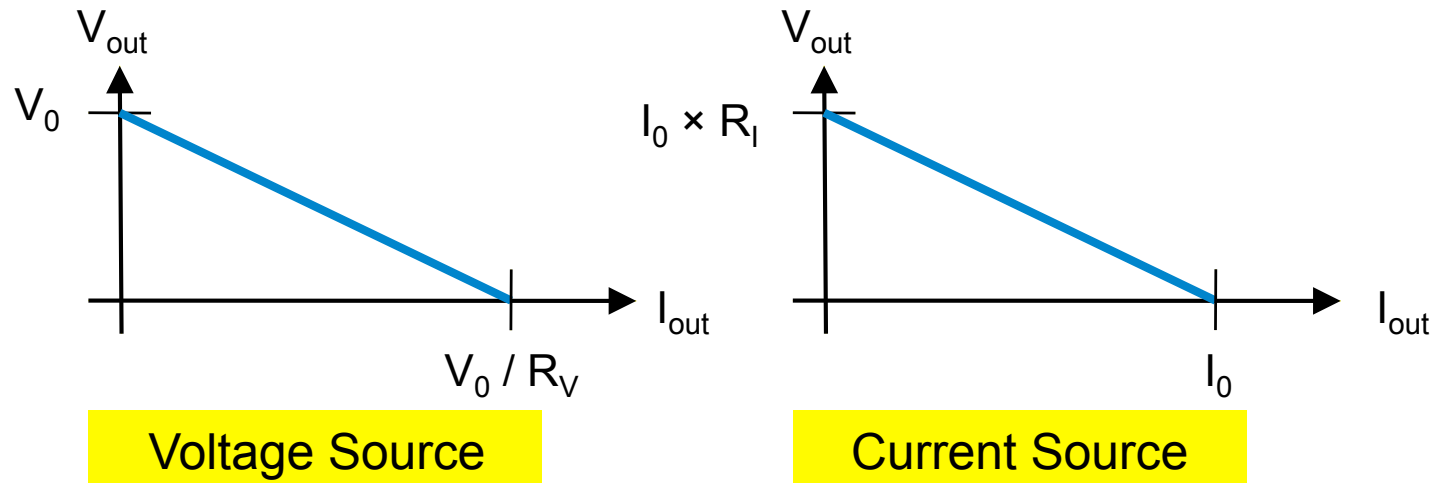- Flip the diagram of the I-source and compare:



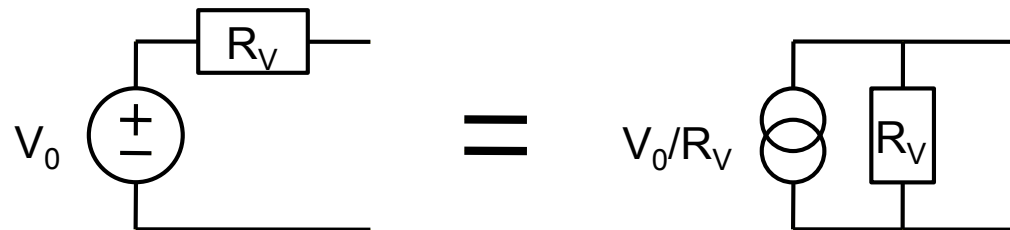- Same shape! Therefore:
- For voltage source with V_0 and R_V , a current source with $I_0 = V_0 / R_V$ and $R_I = V_0 / I_0 = R_V$ behaves the same!






Thévenin's Theorem

Any combination of U-sources, I-sources and resistors behaves like a (real) voltage source with an internal resistor

- This is fairly obvious from the previous page and the linearity of the resistor properties
- Clearly, a current source with internal resistor can also be used

■ Example:

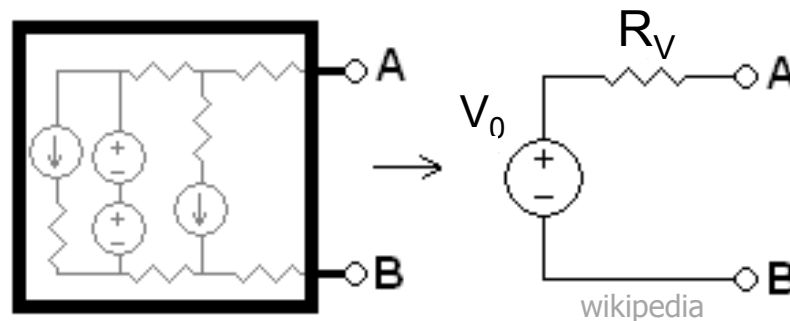


- To find V_0 : calculate the open voltage
- To find R_V : find the short circuit current. Then $R_V = V_0 / I_{\text{short}}$



Thévenin Equivalent of a Voltage Divider

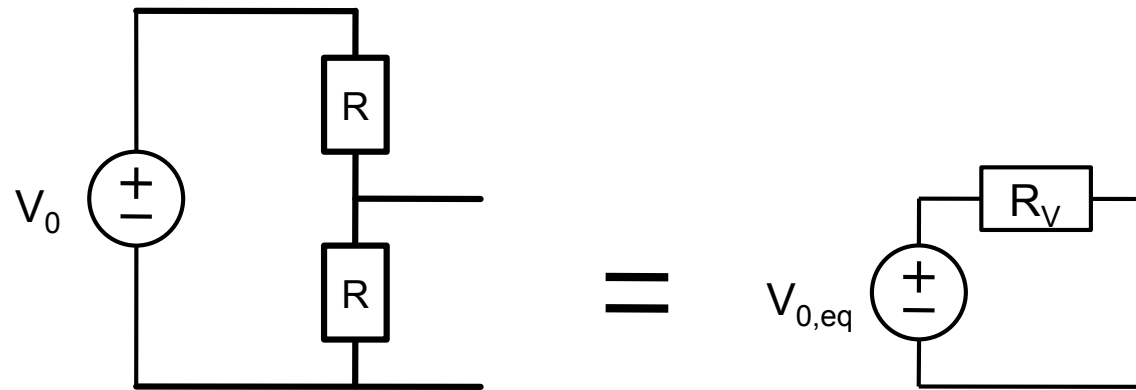- Consider a voltage divider with equal resistors:




- $V_{0,eq} = V_0 / 2$ ($I = V_0 / (2R)$, $V_{0,eq} = R \times I$)
- $I_{short} = V_0 / R \rightarrow R_V = V_{0,eq} / I_{short} = R / 2$


- In general, R_V is the parallel connection of R_1 and R_2



A More Complicated Example - 1

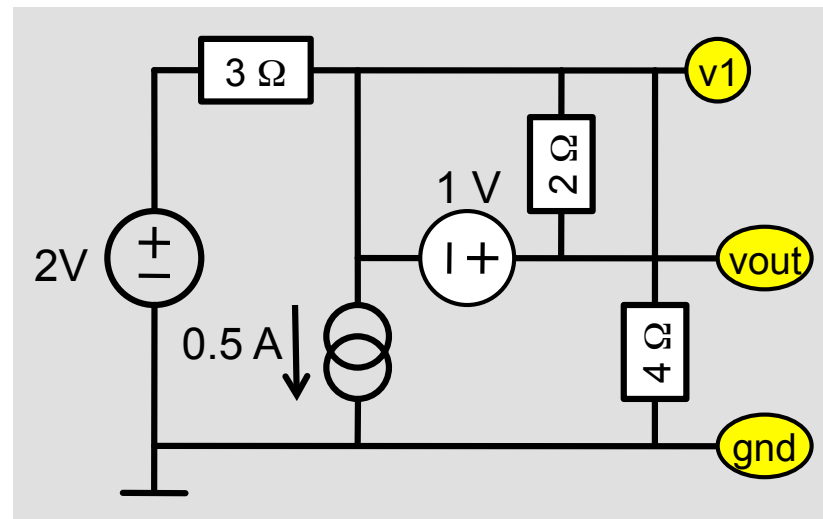


1. Open circuit:

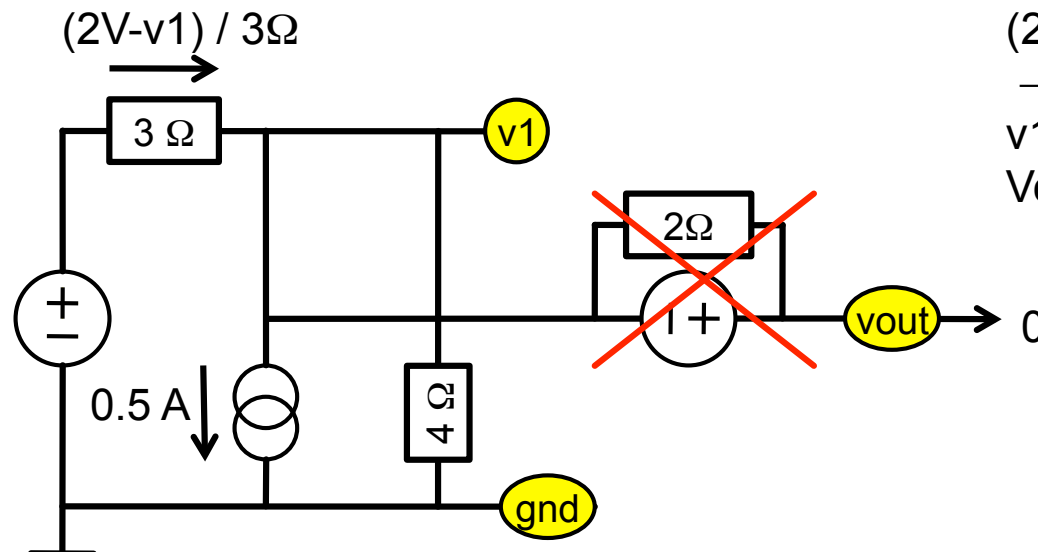


$$\begin{aligned} (2V-v1) / 3\Omega &= 0.5A + v1 / 4\Omega \\ \rightarrow \\ v1 &= 0.285714 V \\ V_{out} &= v1 + 1V = \mathbf{1.285 V = V_0} \end{aligned}$$



A More Complicated Example - 2

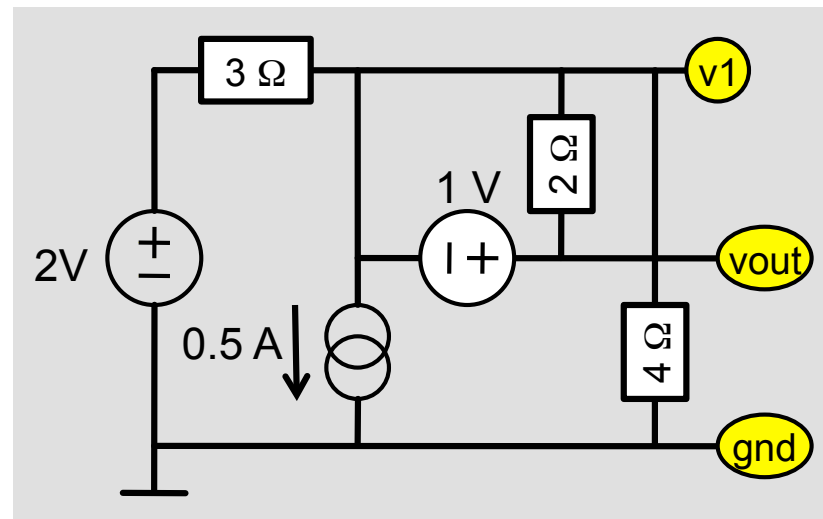

1. Short circuit:

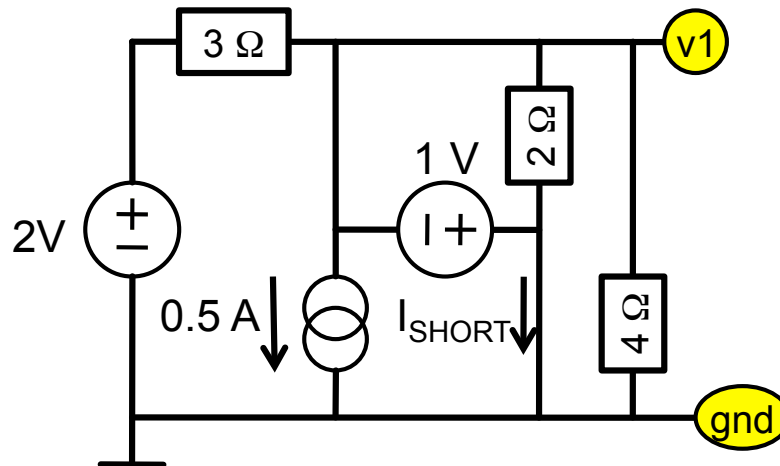

$$(2V - v1) / 3\Omega = 0.5A + v1 / 4\Omega + I_{\text{SHORT}}$$

$$v1 = -1V$$





→

$$I_{\text{SHORT}} = 0.75 A$$

$$R_V = V_0 / I_{\text{SHORT}} = 1.285 V / 0.75 A = 1.71\Omega$$



A More Complicated Example - Simulation

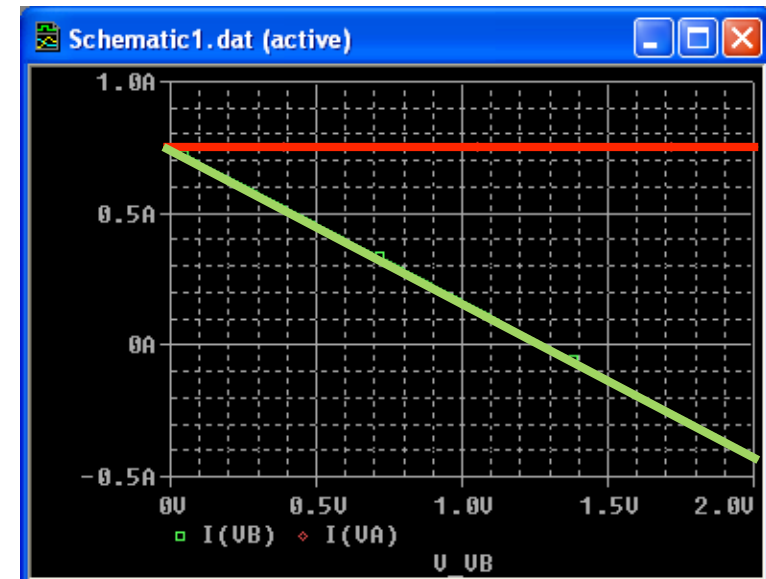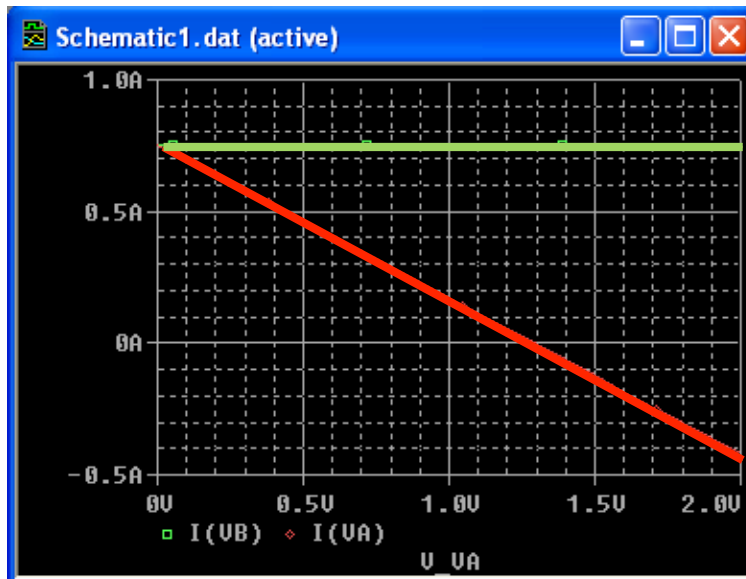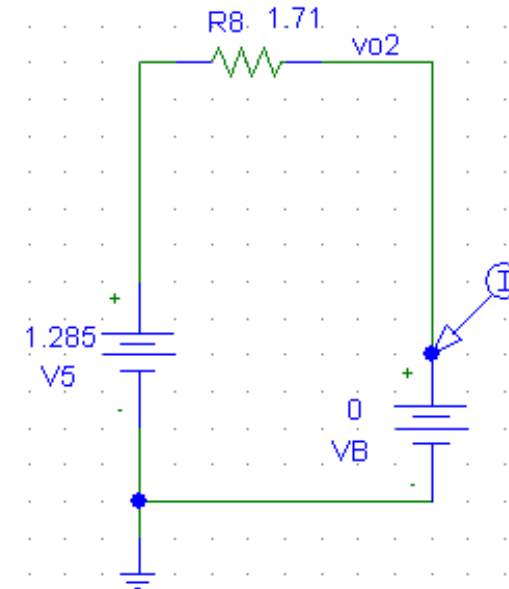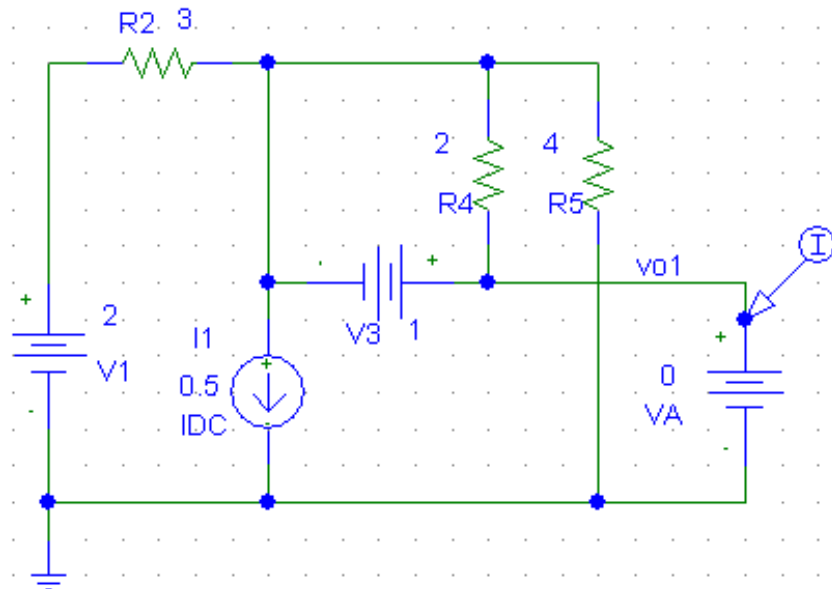





INTERMEZZO: DRAWING SCHEMATICS



Drawing Schematics: Some Rules

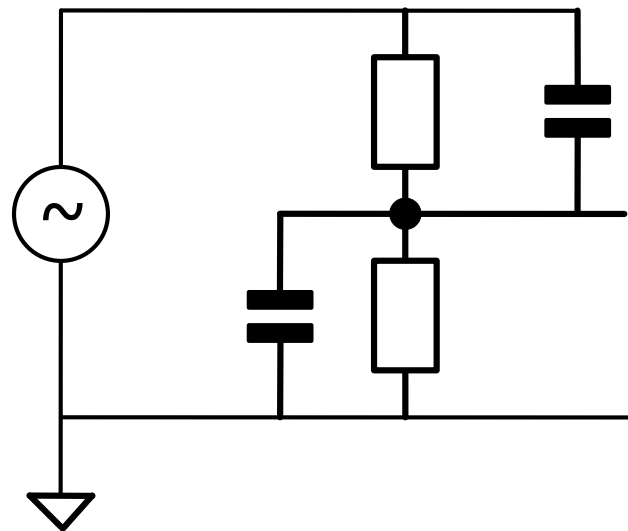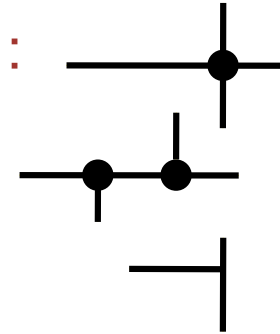
- **Positive** voltages are at the **top**, negative at the bottom
- **Input** signals are at the **left**, **outputs** at the **right**
- Connected **crossings** are marked with a ● :
 - should be avoided
- T-connections do not need a ● :
 - but they can have one...





Example

- A useless circuit...

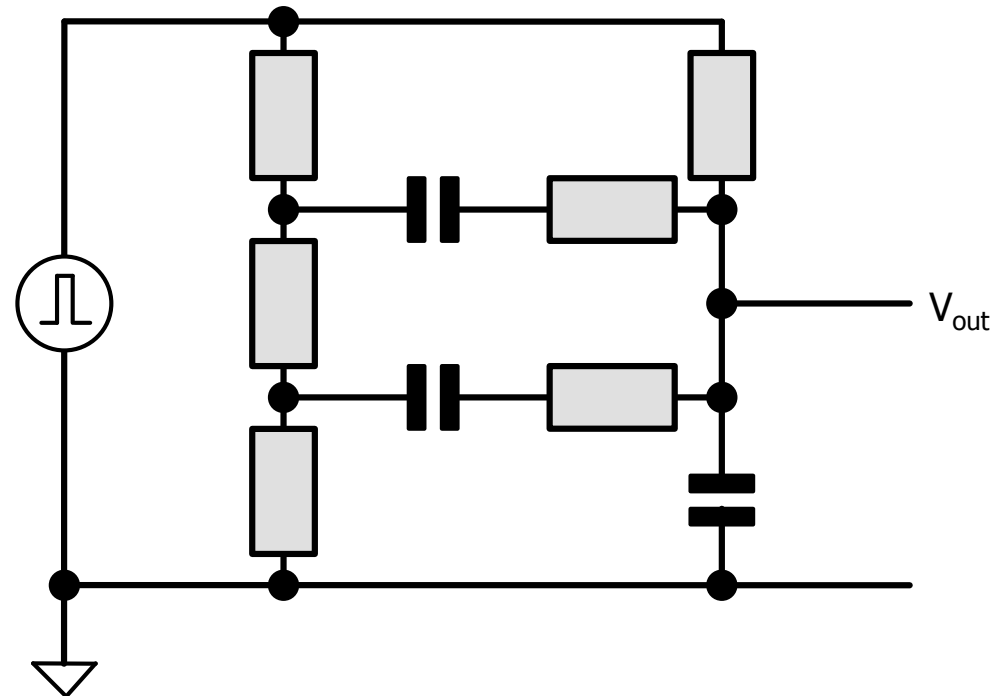




AC BEHAVIOR OF COMPONENTS




AC Behavior of Capacitor

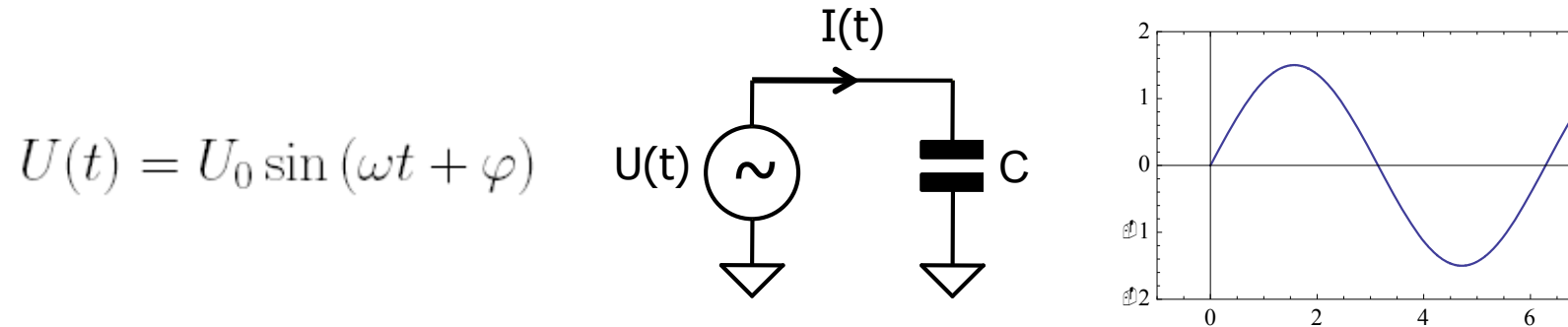- Consider a capacitor driven by a sine wave voltage:



- The current: $I(t) = C \frac{dU(t)}{dt} = C U_0 \omega \cos(\omega t + \varphi)$

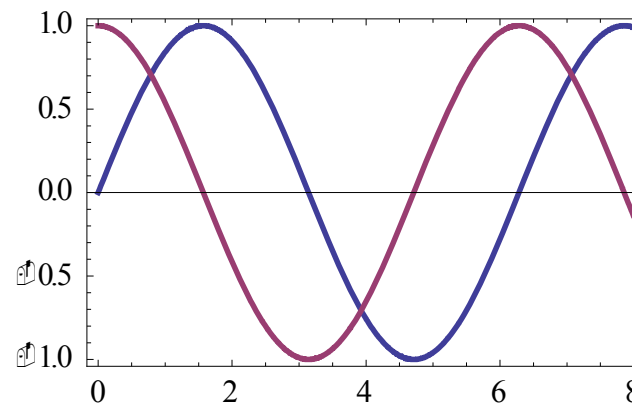is shifted by 90° ($\sin \leftrightarrow \cos$)!






Complex Impedance

- To simplify our calculations, we would like to extend the relation $R = U/I$ to capacitors, using an **impedance** Z_C .
- In order to get the **phase** right, we use **complex** quantities:

$$U(t) = U_0 \sin(\omega t + \varphi) \rightsquigarrow U_0 \cdot e^{i(\omega t + \varphi)} = U_0 [\cos(\omega t + \varphi) + i \sin(\omega t + \varphi)]$$

for voltages and currents.

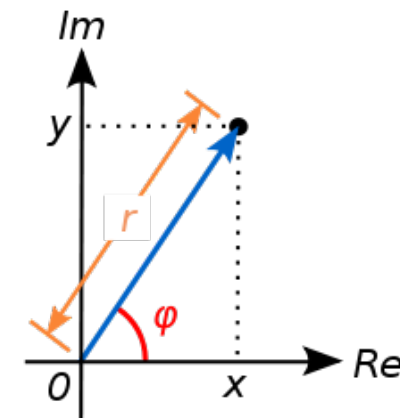- By mixing complex and real parts, we can mix $\sin()$ and $\cos()$ components and therefore influence the phase.
- Note: Often 'j' is used instead of 'i' for the complex unit, because 'i' is used as current symbol...
- Often 's' is used for $i\omega$ (or $j\omega$)






From Complex Values back to Real Quantities


- To find ('back') the **amplitude** of such a complex signal, we calculate the length (**magnitude**) of the complex vector as

$$a = \sqrt{z z^*}$$

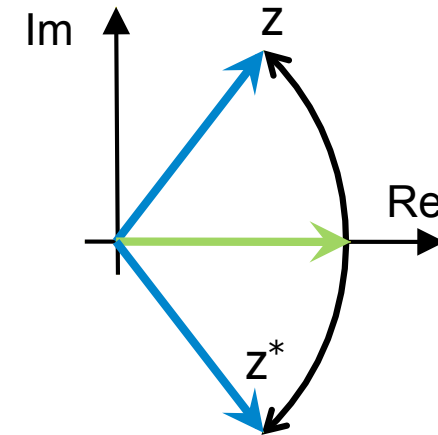

- To get the **phase**, we use real and imaginary parts:
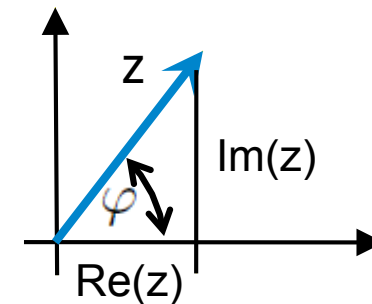
$$\varphi = \text{atan} \left(\frac{\text{Im}(z)}{\text{Re}(z)} \right)$$



Note: this simple formula works only in 2 quadrants. You may have to look at signs of $\text{Re}(z)$ and $\text{Im}(z)$



Complex Impedance of the Capacitor

- We know that

$$I(t) = C \frac{dU(t)}{dt}$$

- With $U(t) = U_0 \cdot e^{i(\omega t + \varphi)}$

we have $I(t) = CU'(t) = C \cdot U_0 \cdot i\omega \cdot e^{i(\omega t + \varphi)}$

- Therefore

$$Z_C = \frac{U(t)}{I(t)} = \frac{1}{i\omega C} = \frac{1}{sC}$$

The impedance of a capacitor becomes very small at high frequencies

- Similar:

$$Z_L = i\omega L = sL$$



Checking this for a Capacitor

- For an input voltage (sine wave of freq. ω) with phase = 0

$$U(t) = U_0 e^{i\omega t}$$

we have

$$I(t) = \frac{U(t)}{Z_C} = U_0 e^{i\omega t} \cdot i\omega C$$

- The amplitude of $I(t)$ is

$$\begin{aligned} |I| &= \sqrt{I(t)I^*(t)} \\ &= \sqrt{U_0 e^{i\omega t} \cdot i\omega C \times U_0 e^{-i\omega t} \cdot (-i)\omega C} \\ &= \sqrt{U_0^2 e^{i\omega t} e^{-i\omega t} \cdot (i\omega C)(-i\omega C)} \\ &= U_0 \omega C \end{aligned}$$

- The phase is:

$$\varphi = \text{atan} \left(\frac{\omega C}{0} \right) = \text{atan}(\infty) = \frac{\pi}{2}$$

- We have dropped the time variant part and the constant U_0



Simplifying even more

- As we have just seen, the $U(t) = U_0 e^{i\omega t}$ propagates trivially to the output.
- We therefore drop this part and just use '1'!



Recipe to Calculate Transfer Functions

- Replace all component by their complex impedances ($1/(sC)$, sL , R)
- Assume a unit signal of '1' at the input


(in reality it is $U(t) = U_0 e^{i\omega t}$)

- Write down all node current equations or current equalities using Kirchhoff's Law (they depend on s)
 - You need N equations for N unknowns
- Solve for the quantity you are interested in (most often V_{out})
- Analyze the result (amplitude / phase / ...)



Example: Low Pass

- Consider

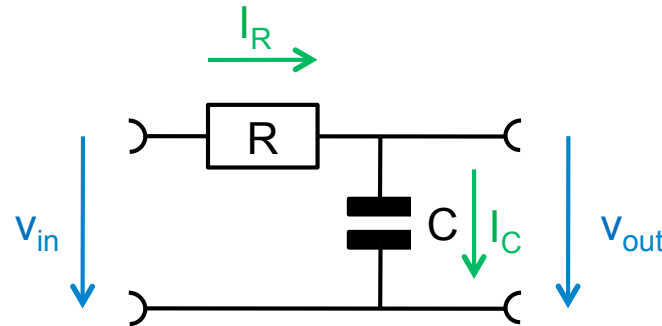

- We have only *one* unknown: v_{out}

- Current equality at node v_{out} : $\frac{V_{in} - V_{out}}{R} = I_R = I_C = v_{out} s C$

- Solve for v_{out} :



$$V_{in} - V_{out} = v_{out} s C R$$

$$V_{in} = v_{out} (1 + s C R)$$

$$\frac{V_{out}}{V_{in}} = H(s) = \frac{1}{1 + s C R}$$



Low Pass as 'complex' voltage divider

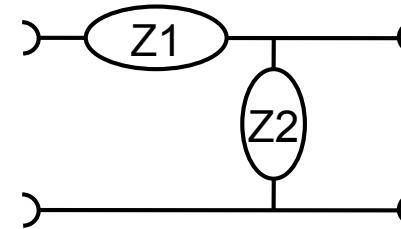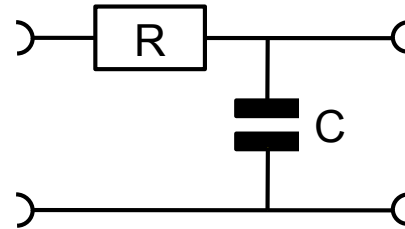

- This is an 'ac' voltage divider with two impedances $Z_1 = R$ and $Z_2 = 1/sC$
- Using the voltage divider formula, we get



$$H(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_2}{Z_2 + Z_1} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sRC} = \frac{1}{1 + i\frac{\omega}{\omega_0}}$$

with $\omega_0 = 1/(RC)$, the 'corner frequency'.



The HIGH Pass

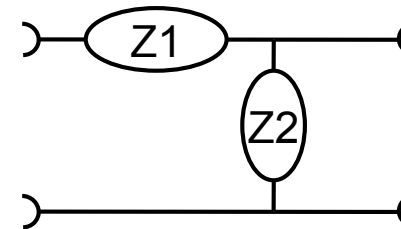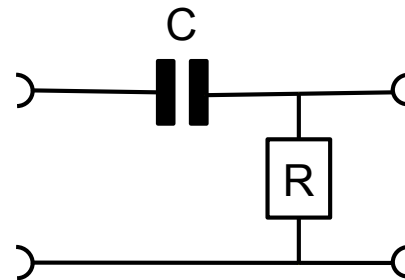
- By exchanging R and C, low frequencies are blocked and high frequencies pass through. This is the High-Pass.



- We get $H_{HP}(s) = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC}$



More Complicated Example

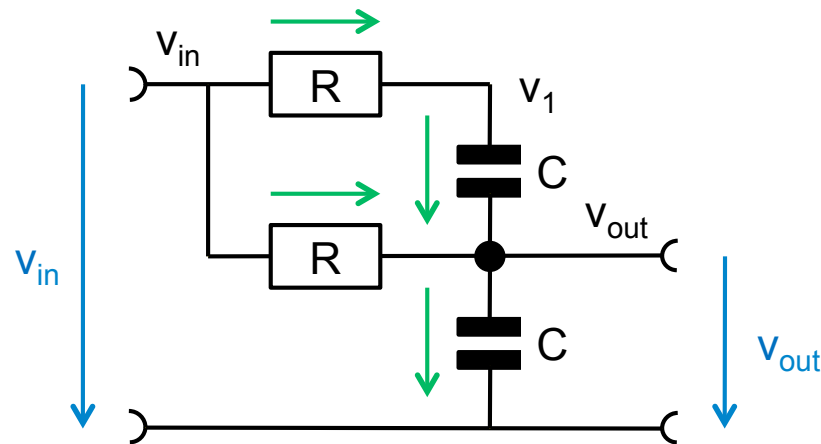

- We have now *two* unknowns: v_1 , v_{out}

$$EQ1 (@v_1) : \frac{v_{in} - v_1}{R} = (v_1 - v_{out})sC$$

$$EQ2 (@v_{out}) : (v_1 - v_{out})sC + \frac{v_{in} - v_{out}}{R} = v_{out} sC$$

- Eliminating v_1 gives:

$$H(s) = \frac{1 + 2RC s}{1 + 3RC s + (RC)^2 s^2}$$




BODE PLOT



Transfer Function

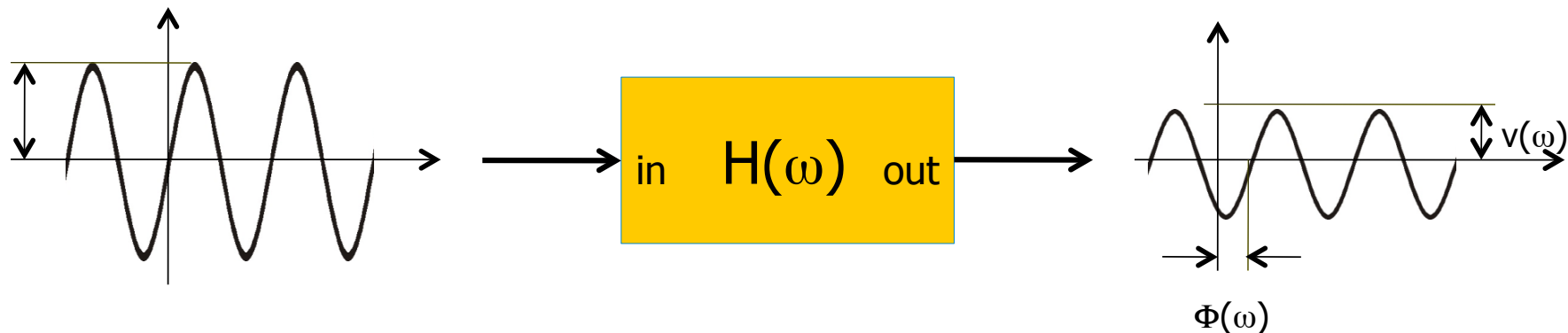- The **transfer function** of a *linear, time invariant* system visualizes how the **amplitude** and **phase** of a sine wave input signal of **constant frequency** ω appears at the output
- The frequency remains unchanged
- The transfer function $H(\omega)$ contains
 - The phase change $\Phi(\omega)$
 - The gain $v(\omega) = \text{amp_in} / \text{amp_out}(\omega)$





Bode Diagram: Definition

- The Bode Plot shows gain (+ phase) of the transfer function
- The frequency (x-axis) is plotted **logarithmically**
- Gain is plotted (y-axis) **logarithmically**, often in **decibel**

• $DB(x) = 20 \log_{10}(x)$:

$\times 10$ +20 dB



$\times 100$ +40 dB

$\times 2$ 6 dB (not exactly!)

$\times 1$ 0 dB

$/ 2$ -6 dB

$/ \sqrt{2}$ -3 dB

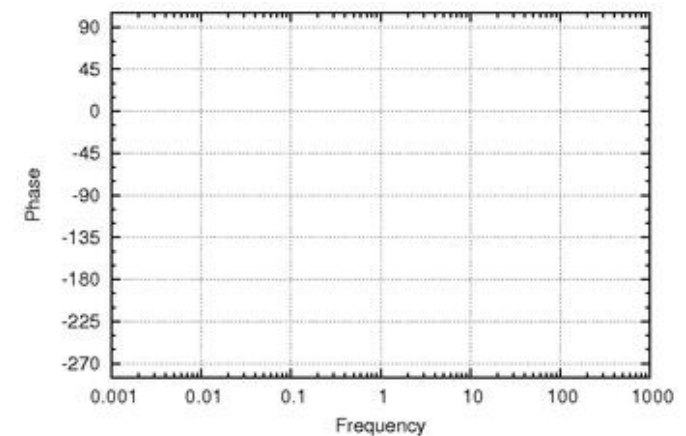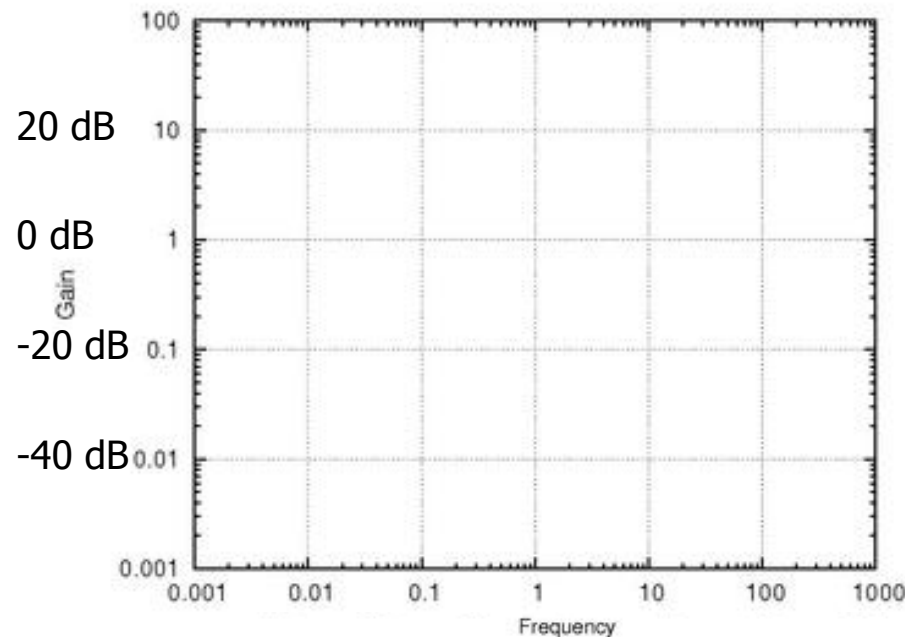

• dBs for multiplied quantities just add !




Bode Diagram: Properties


- Power functions are straight lines:

$$f(x) = x^n \Rightarrow \log[f(x)] = n \log(x)$$


`Plot[x2, {x, 0, 10}]`

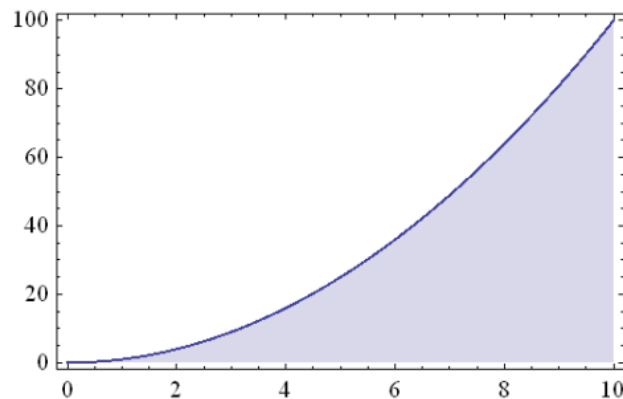


`LogPlot[x2, {x, 0, 10}]`

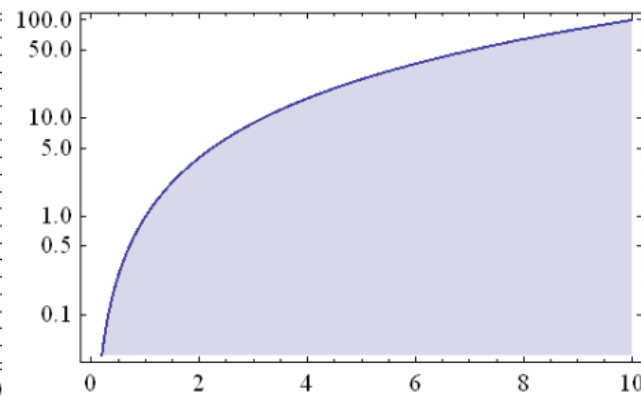

`LogLogPlot[x2, {x, 1, 10}]`

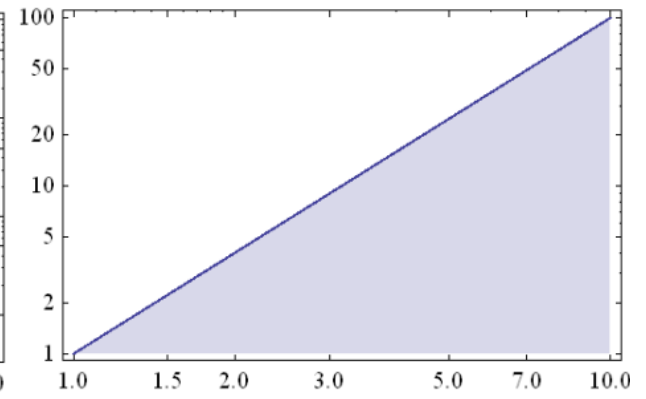
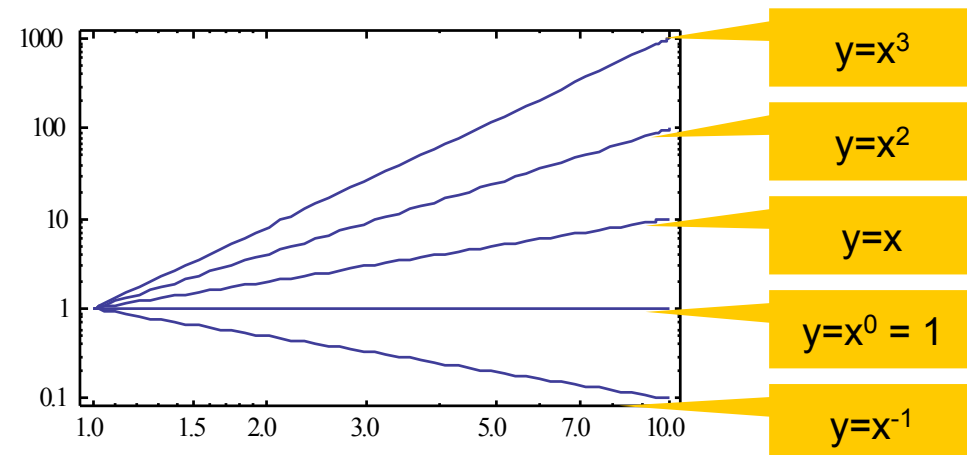
`LogLogPlot[Table[xN, {N, -1, 3}], {x, 1, 10}]`





Bode Diagram: Properties



- $1/x$ function has slope -1:

$$f(x) = \frac{1}{x} = x^{-1} \Rightarrow \log[f(x)] = -1 \log(x)$$

- Multiplied functions are **added** in plot:

$$f = f_1 \cdot f_2 \Rightarrow \log[f] = \log(f_1) + \log(f_2)$$

$f_1=2+x; f_2=x^{-1};$

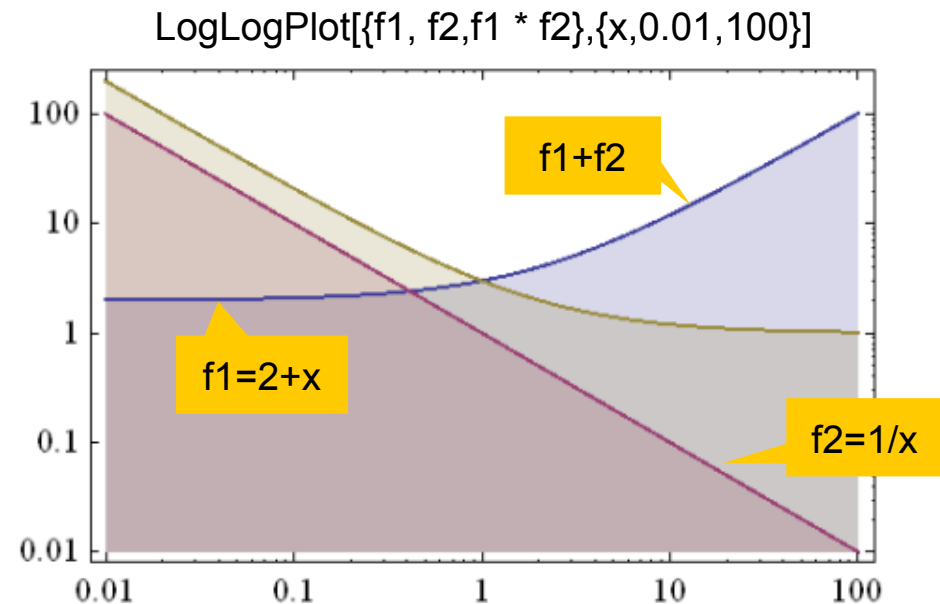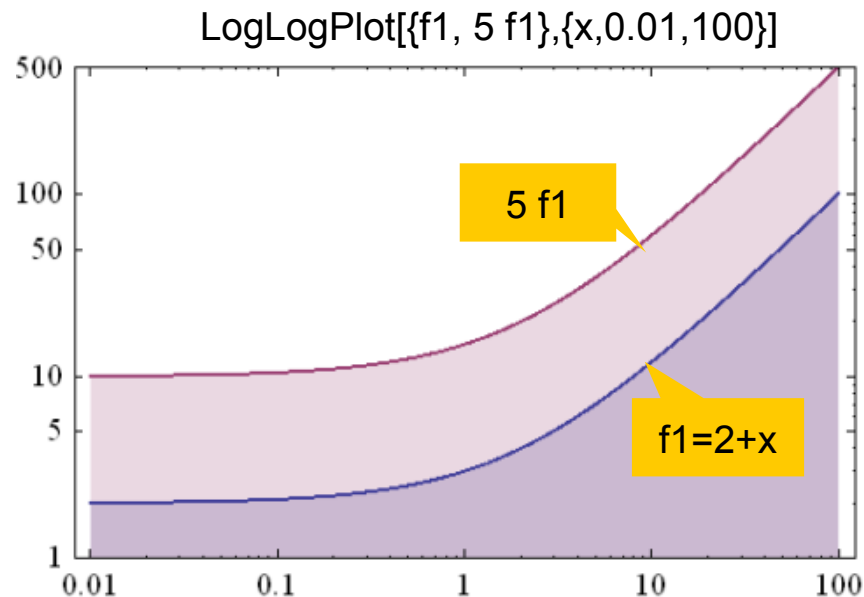



THE LOW PASS FILTER



Analysis of the Low Pass Transfer Function

▪ **Transfer Function:** $H(\omega) = \frac{1}{1 + i\frac{\omega}{\omega_0}}$

▪ **Magnitude:** $v(\omega) = \sqrt{H(\omega)H^*(\omega)} = \frac{1}{\sqrt{(1 + i\frac{\omega}{\omega_0})(1 - i\frac{\omega}{\omega_0})}}$

$$v(\omega) = \frac{1}{\sqrt{(1 + \frac{\omega^2}{\omega_0^2})}}$$

$$\rightarrow 1 \text{ for } \omega \rightarrow 0$$

$$\rightarrow \frac{1}{\sqrt{2}} \text{ for } \omega = \omega_0$$

$$\rightarrow \frac{\omega_0}{\omega} \text{ for } \omega \rightarrow \infty$$


▪ **Phase:** $H(\omega) = \frac{1}{1 + i\frac{\omega}{\omega_0}} = \frac{1}{1 + i\frac{\omega}{\omega_0}} \times \frac{1 - i\frac{\omega}{\omega_0}}{1 - i\frac{\omega}{\omega_0}} = \frac{1 - i\frac{\omega}{\omega_0}}{1 + \frac{\omega^2}{\omega_0^2}}$

$$\varphi = \text{atan} \left(\frac{\text{Im}(H)}{\text{Re}(H)} \right) = -\text{atan} \left(\frac{\omega}{\omega_0} \right)$$

(rad or degree)




Bode Plot of LowPass (Amplitude)

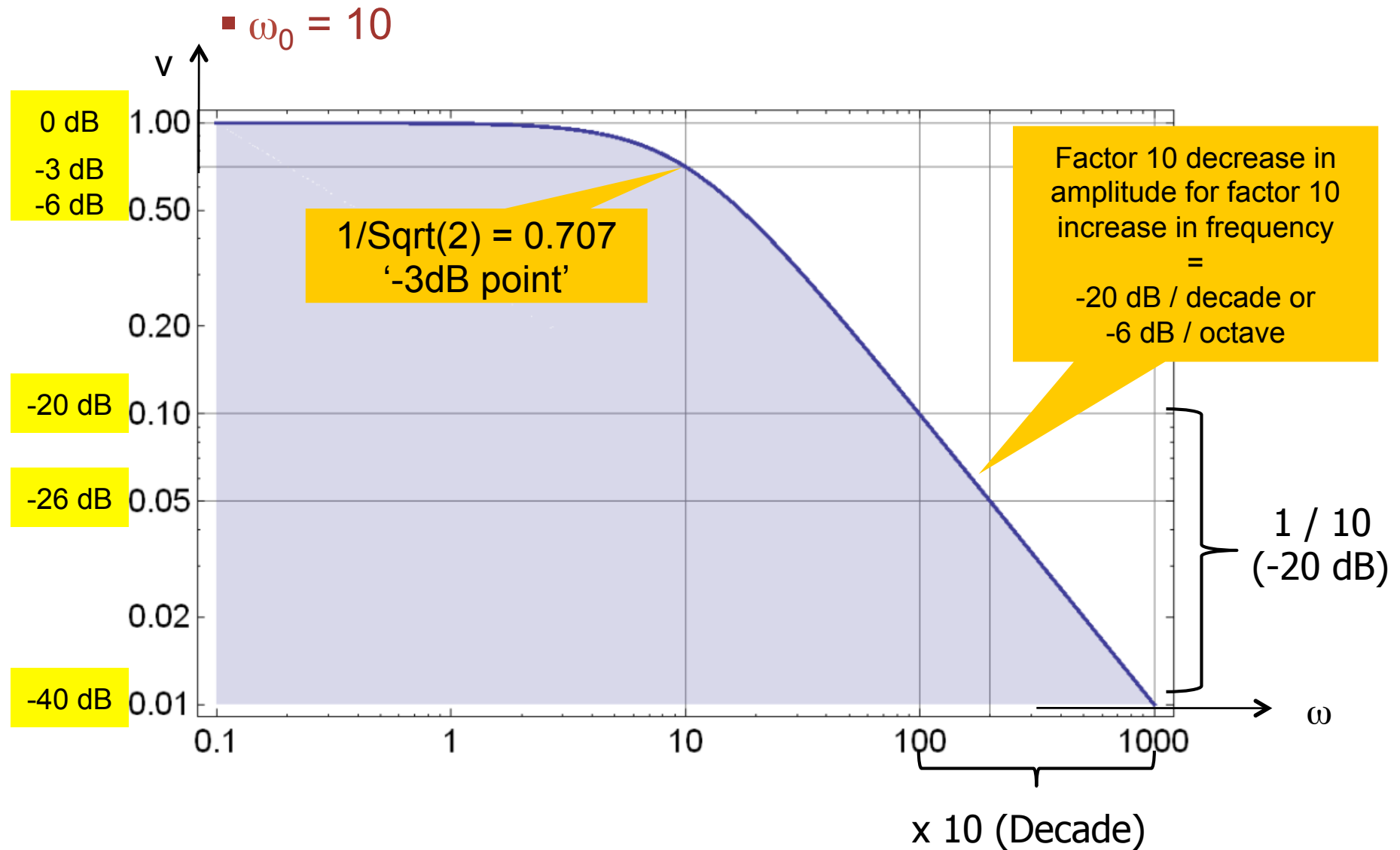



The same in dB

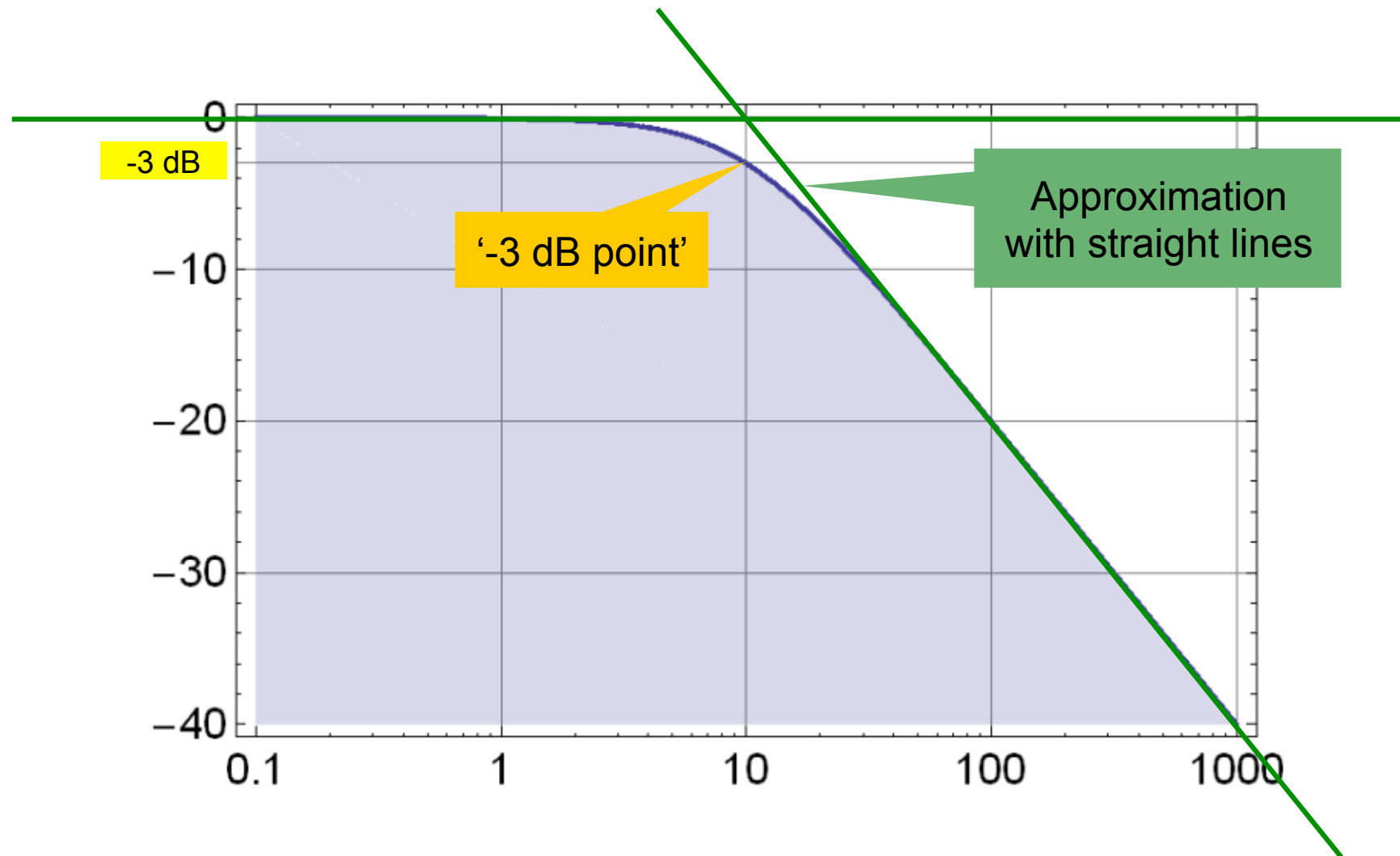




Bode Plot of LowPass (Phase)

■ $\omega_0 = 10$


Phase

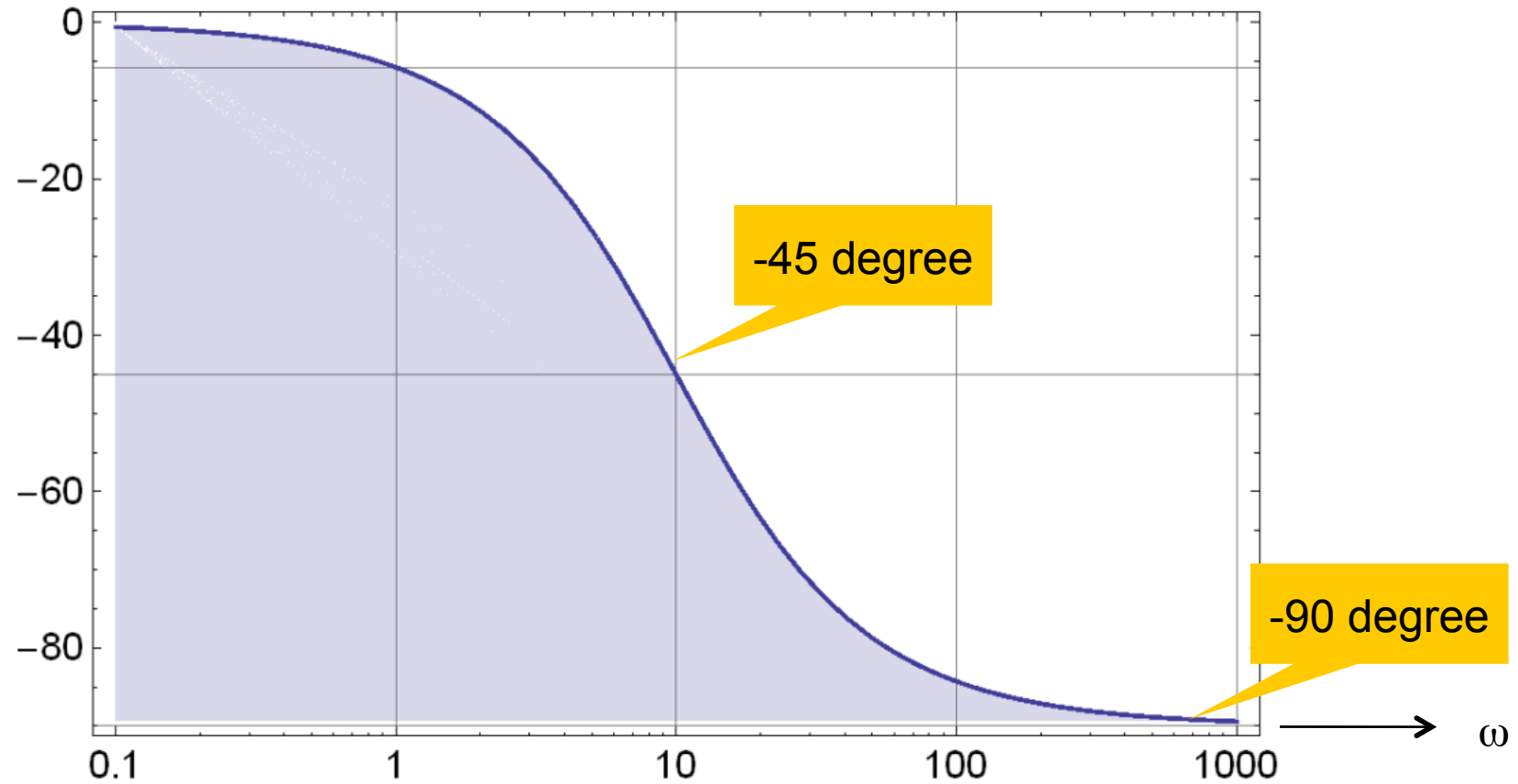





Series Connection of two Low Pass Filters

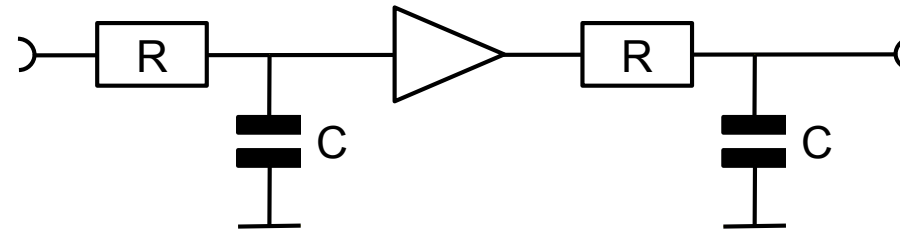- Consider two identical LP filters. A 'unit gain buffer' makes sure that the second LP does not load the first one:



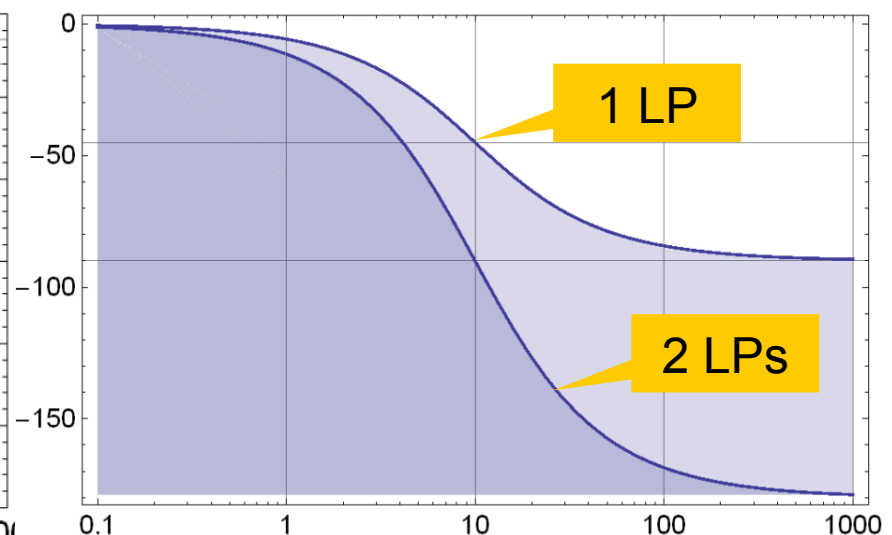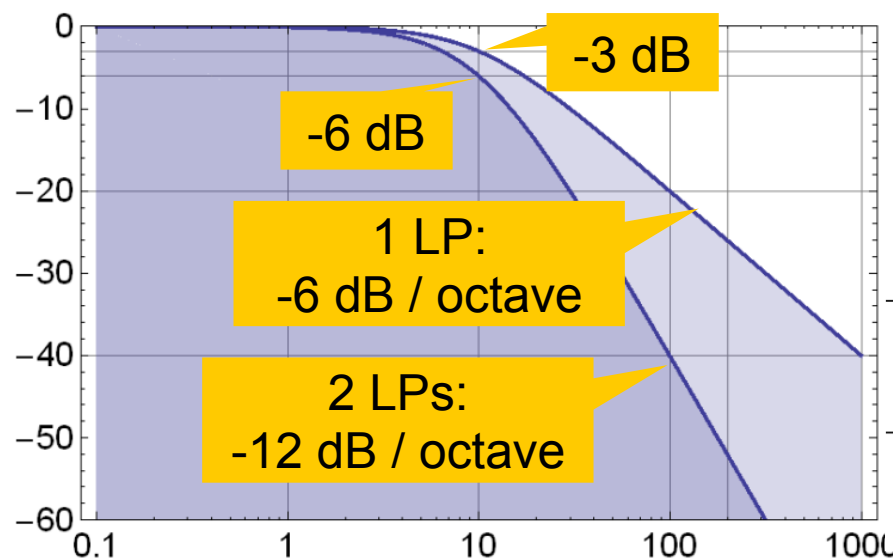- From the properties of the LogLog Plot, the TF of the 2nd order LP is just the sum of two 1st order LPs:






Why bother so much about the low pass ?

- All circuits behave like low-passes (at some frequency)!




Caveat!

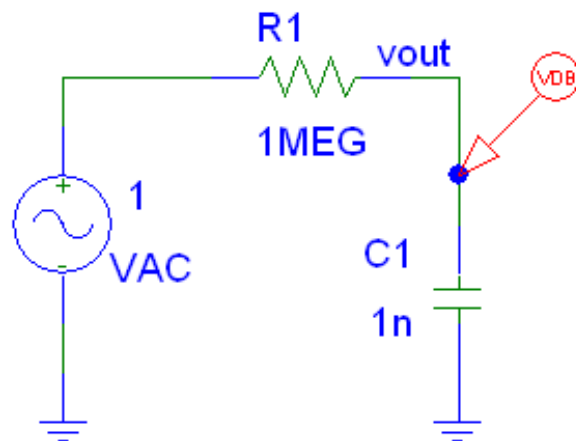- So far, frequency is expressed with ω , i.e. in radian / second
- We have: $\omega = 2 \pi \nu$
- Therefore, the frequencies in Hertz are 2π lower!!!


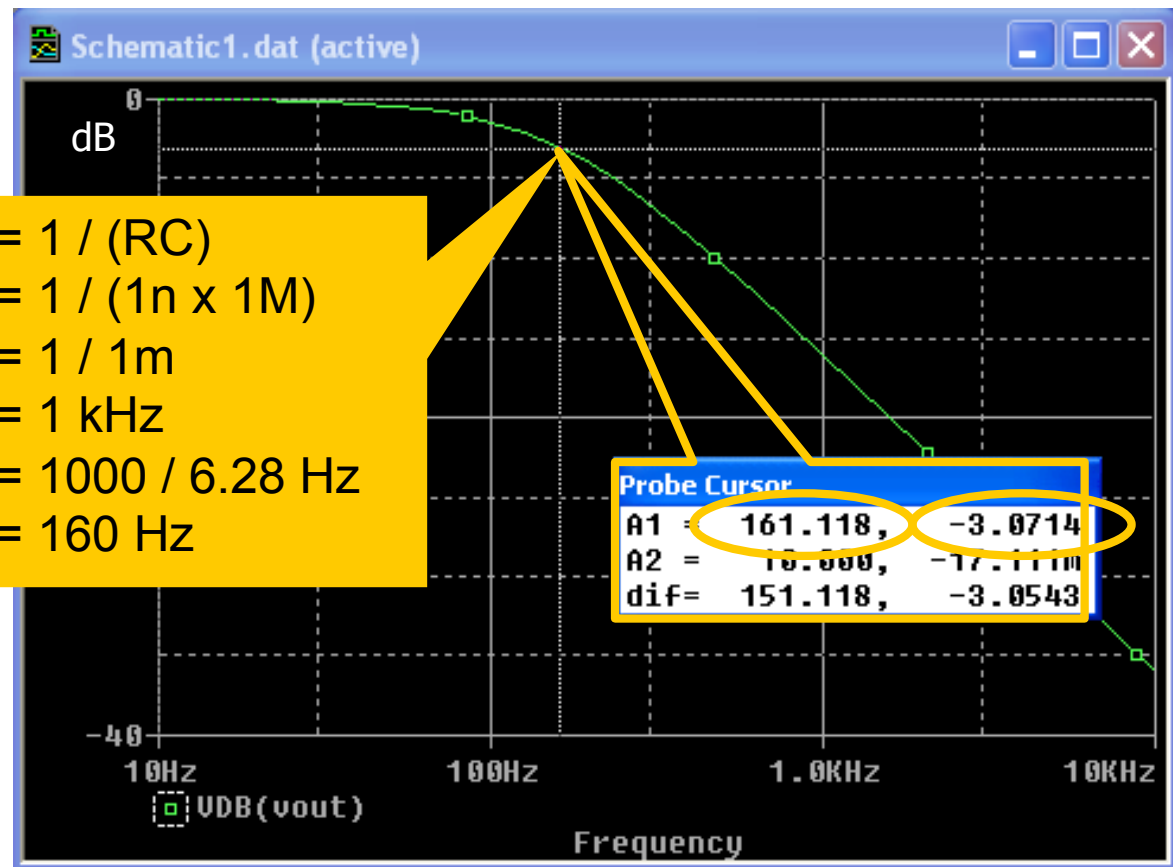
$$\begin{aligned}\omega_0 &= 1 / (RC) \\ &= 1 / (1n \times 1M) \\ &= 1 / 1m \\ &= 1 \text{ kHz} \\ \nu &= 1000 / 6.28 \text{ Hz} \\ &= 160 \text{ Hz}\end{aligned}$$






Low Pass and High Pass

$$\mathbf{LP}[\omega] = \frac{1}{1 + \mathbf{i} \frac{\omega}{\omega_0}}$$

$$\mathbf{HP}[\omega] = \frac{\mathbf{i} \frac{\omega}{\omega_0}}{1 + \mathbf{i} \frac{\omega}{\omega_0}};$$

$$\mathbf{LPgain}(\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

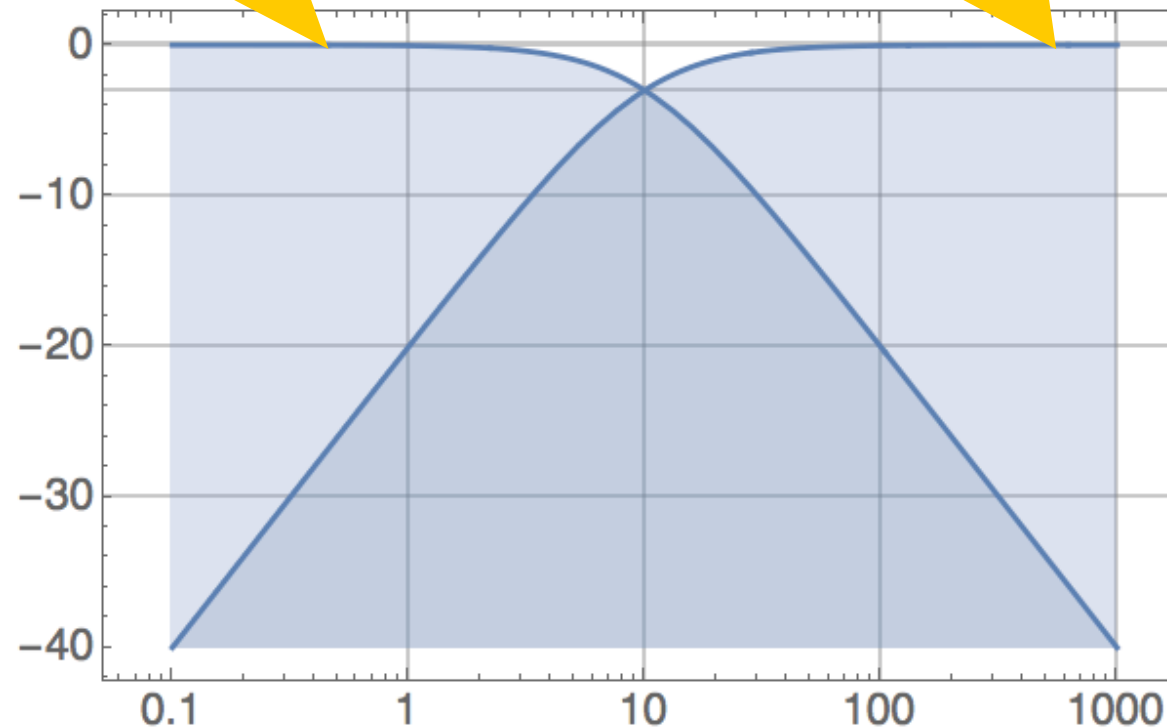
$$\mathbf{HPgain}(\omega) = \frac{\frac{\omega}{\omega_0}}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$






A More Complex Example

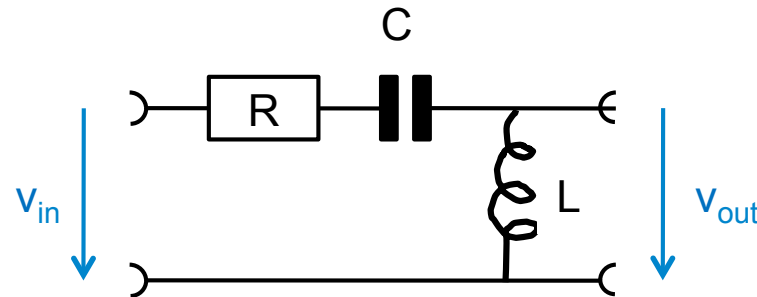- Consider a (High Pass) filter with an inductor:



Mathematica
Demo

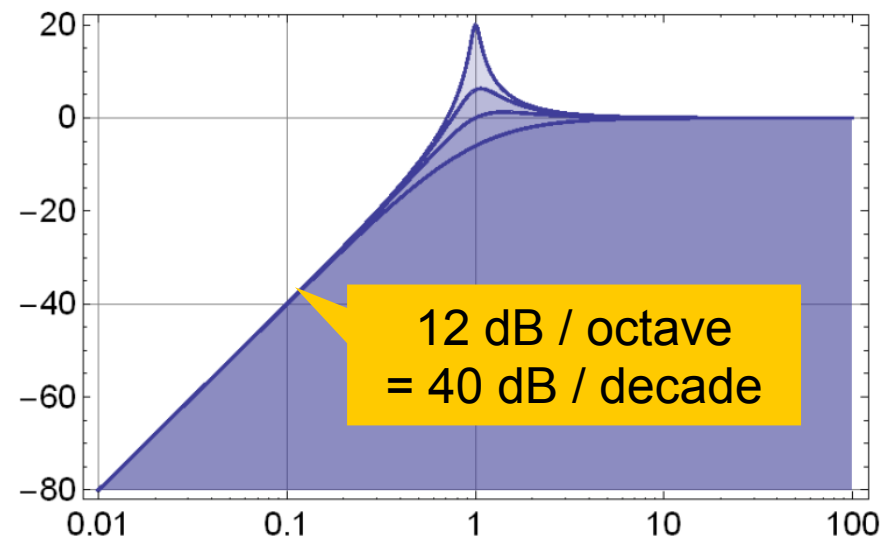
- The transfer function is $H(s) = (C L s^2) / (1 + C R s + C L s^2)$
- It is of 'second order' (s has exponent of 2 in denominator)
- Magnitude:
 $L=C=1$
 $R=0.1, 0.5, 1, 2$
- 'Inductive peaking'






Phase

- Phase has a 'jump'

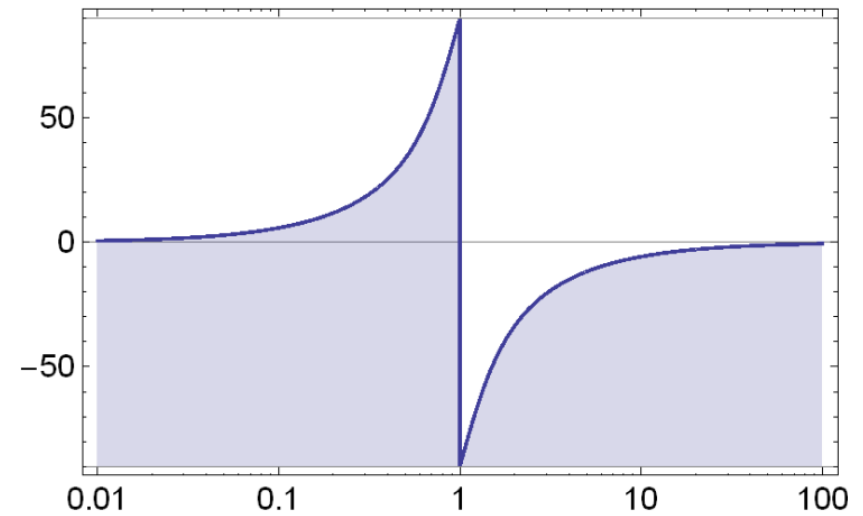

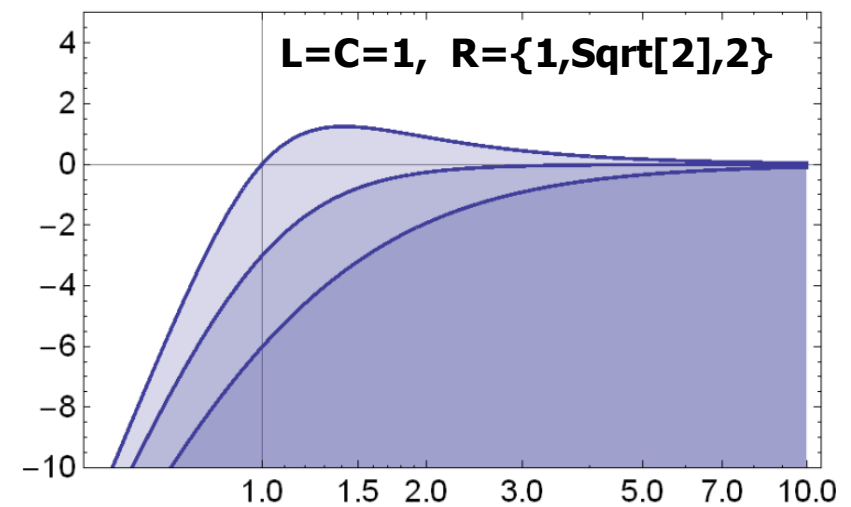- For fun:
 - When is filter steep & flat?






CIRCUIT SIMPLIFICATIONS



Large and Small Values

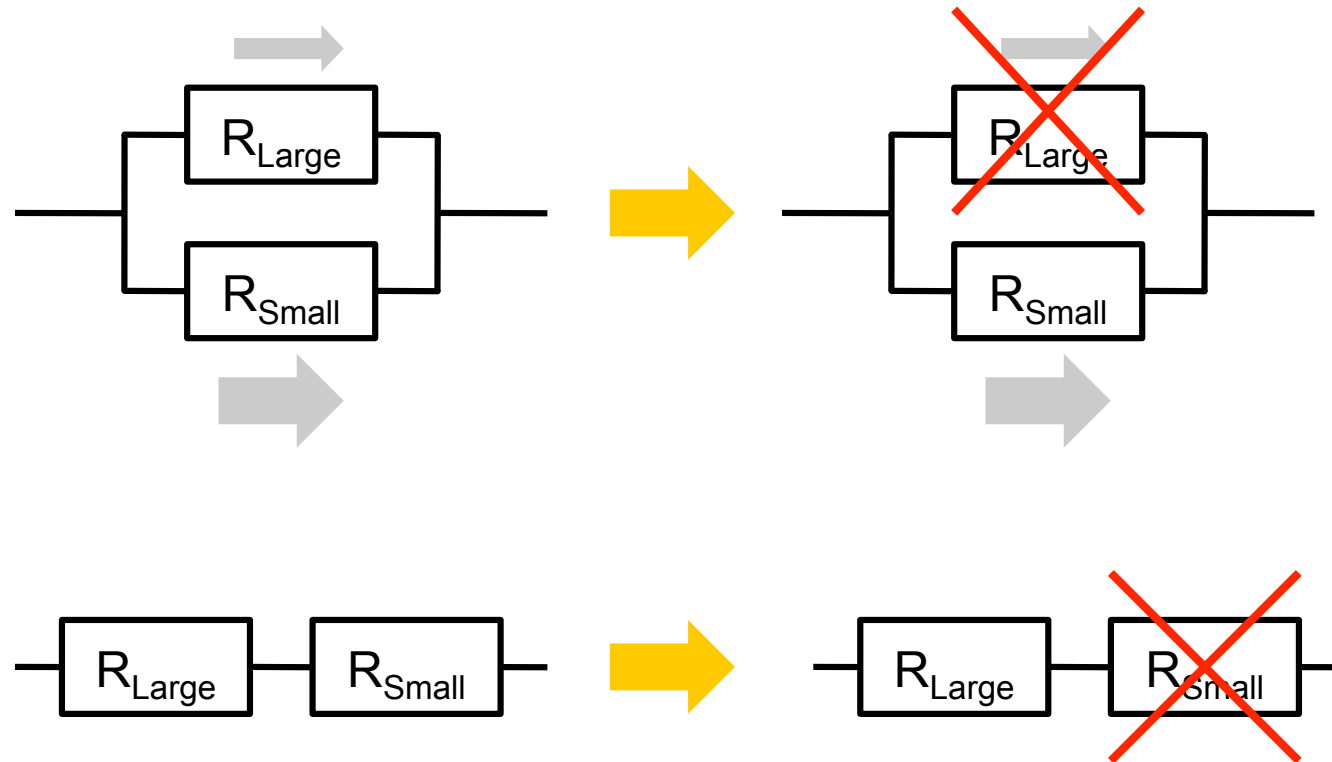
- To roughly understand behavior of circuits, only keep the dominant components:



- Eliminate *larger* or the *smaller* part (depending on circuit!)
- Error \sim ratio of components



The same for Capacitors

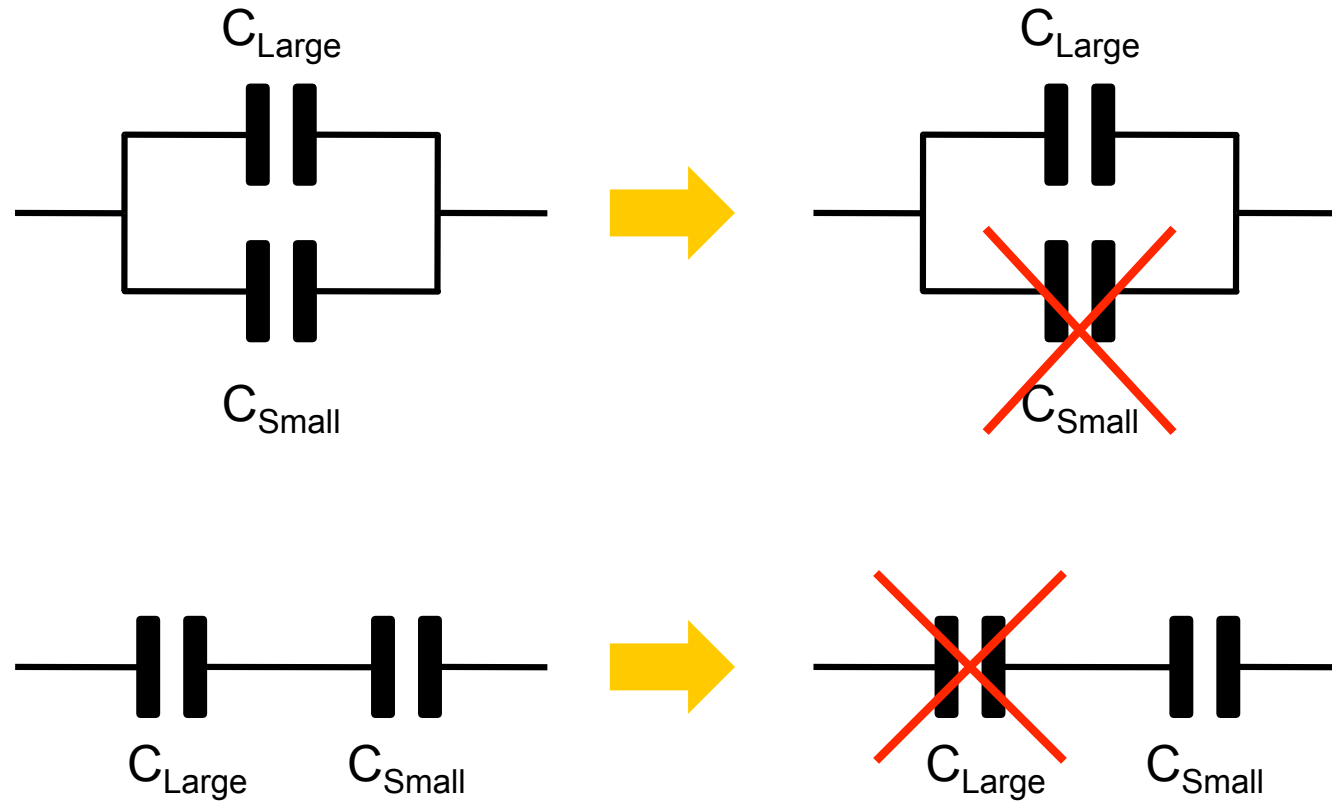



Resistors AND Capacitors

- Behavior depends on frequency ($|Z_C| = 1/(2\pi\nu C)$)

