




FOR FUN: HIGHER ORDER FILTERS




Reminder: One Low Pass

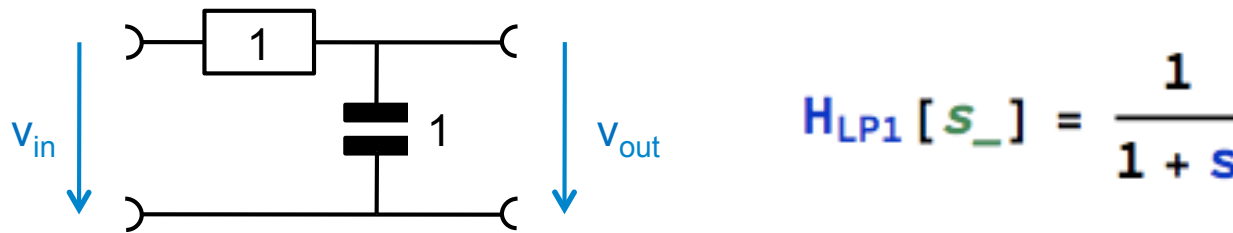- (For simplicity, we use fixed values for R and C, often 1 Ω /F)



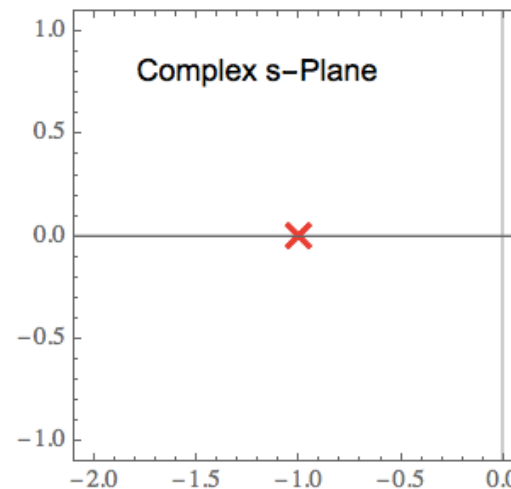- Mathematically, $H_{LP1}[s]$ has a **POLE** at $s = -1$.
- This can be illustrated in the COMPLEX s-Plane:




- This particular pole is real, i.e. it lies on the real axis




Reminder: Cascaded Low Pass Stages

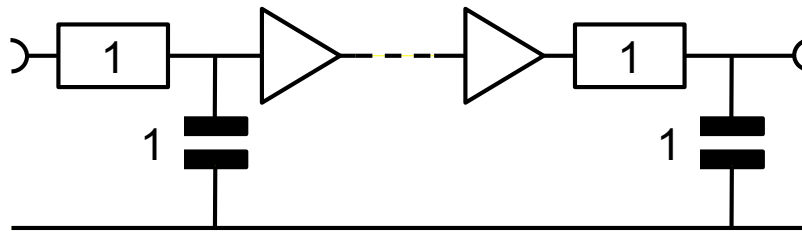- If we cascade N stages *with buffers*, we get



$$H_{LPN}[s] = \frac{1}{(1+s)^N}$$

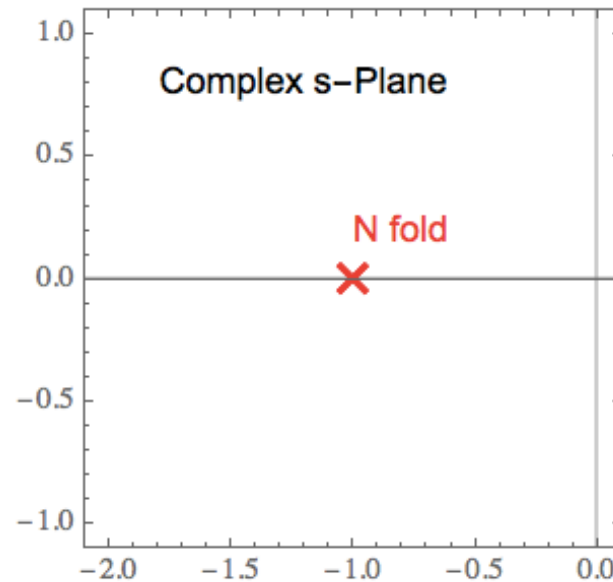
- $H_{LPN}[s]$ has a ***N-fold*** POLE at the same location $s = -1$.






Two Unbuffered Low Pass Stages

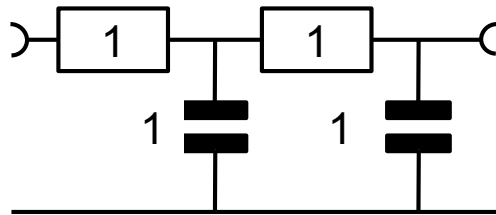- If we cascade two stages *without buffer*, we get



$$H_{LPCasc}[s] = \frac{1}{1 + 3s + s^2}$$

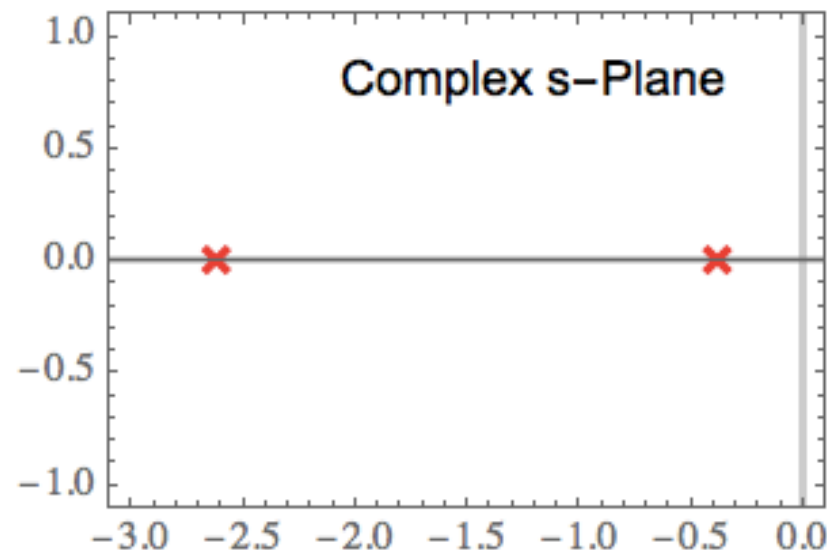- We now have *two different* (still real) poles:




(Their locations depend on the impedance of the second stage)




(Pole Location for Previous Case)

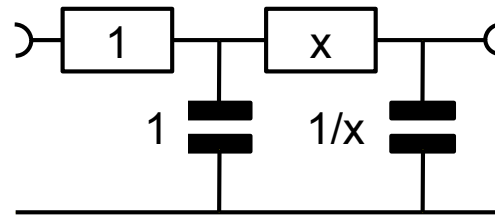- If we modify R,C of the second stage, keeping $RC = 1$, we get



$$H[s_] = \frac{x}{s + x + 2sx + s^2 x}$$

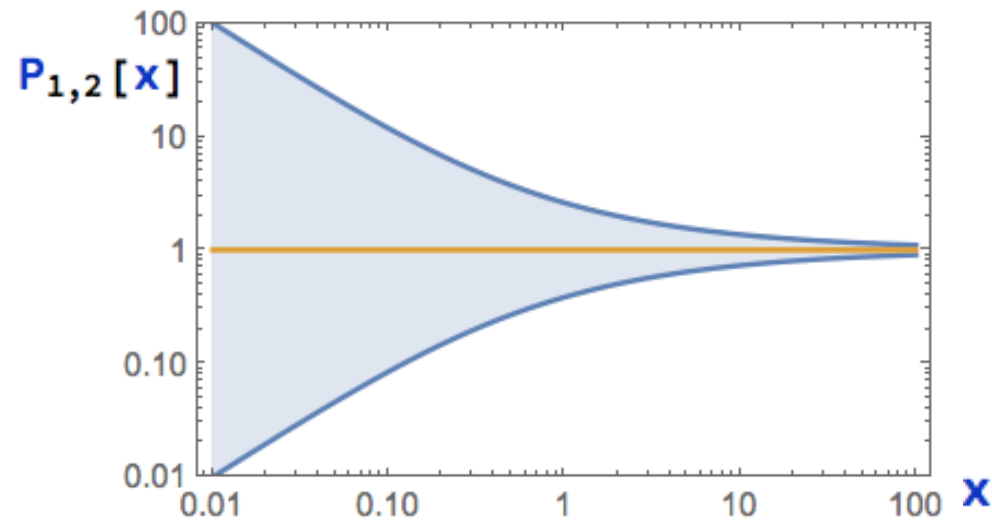- The poles are at $P_{1,2}[x] = \frac{-1 - 2x \pm \sqrt{1 + 4x}}{2x}$




(when x is large, the 2nd LP does not load the 1st)



An Active Filter

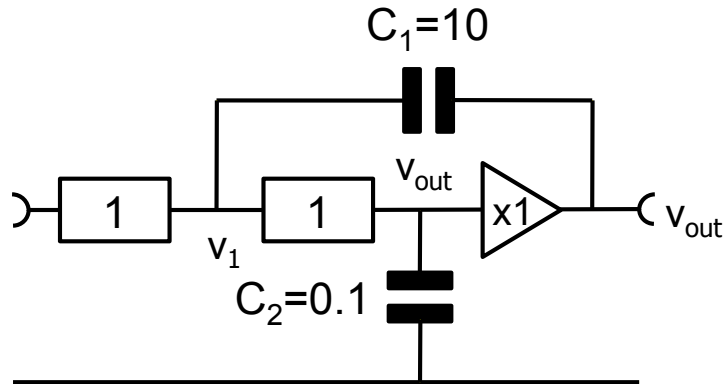- Now consider the following filter ('Sallen and Key')





$$EQ1 = \frac{v_{in} - v_1}{1} = \frac{v_1 - v_{out}}{1} + (v_1 - v_{out}) s 10;$$

$$EQ2 = \frac{v_1 - v_{out}}{1} = v_{out} s \frac{1}{10};$$

$$H[s] = \frac{5}{5 + s + 5 s^2}$$

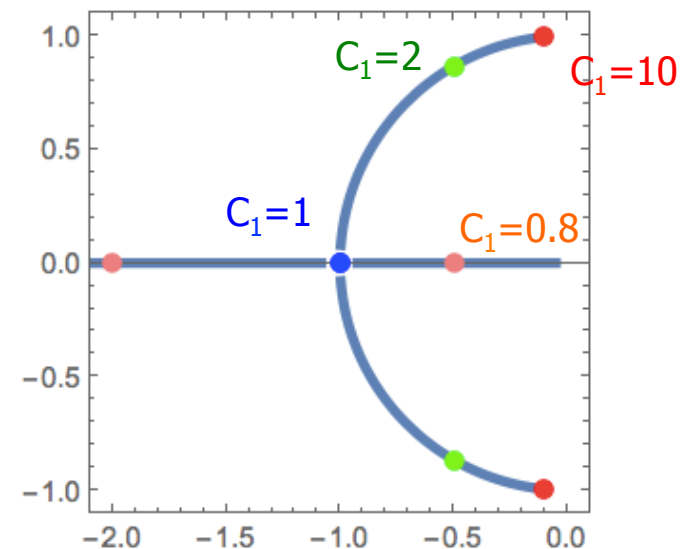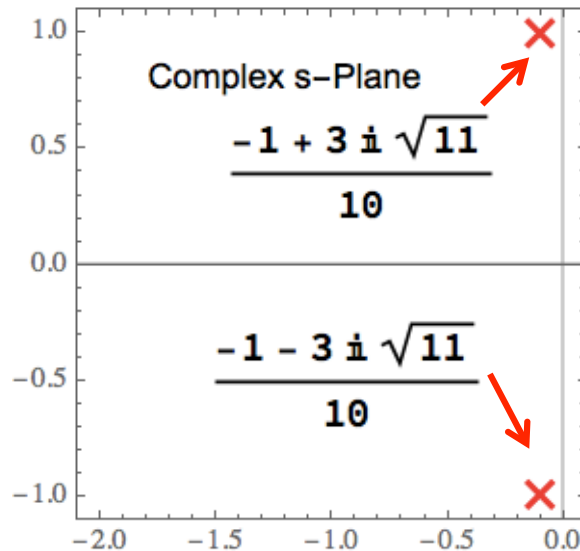
- This transfer function has two **COMPLEX** (conjugate) poles:





Bode Plots of 2nd Order Filters

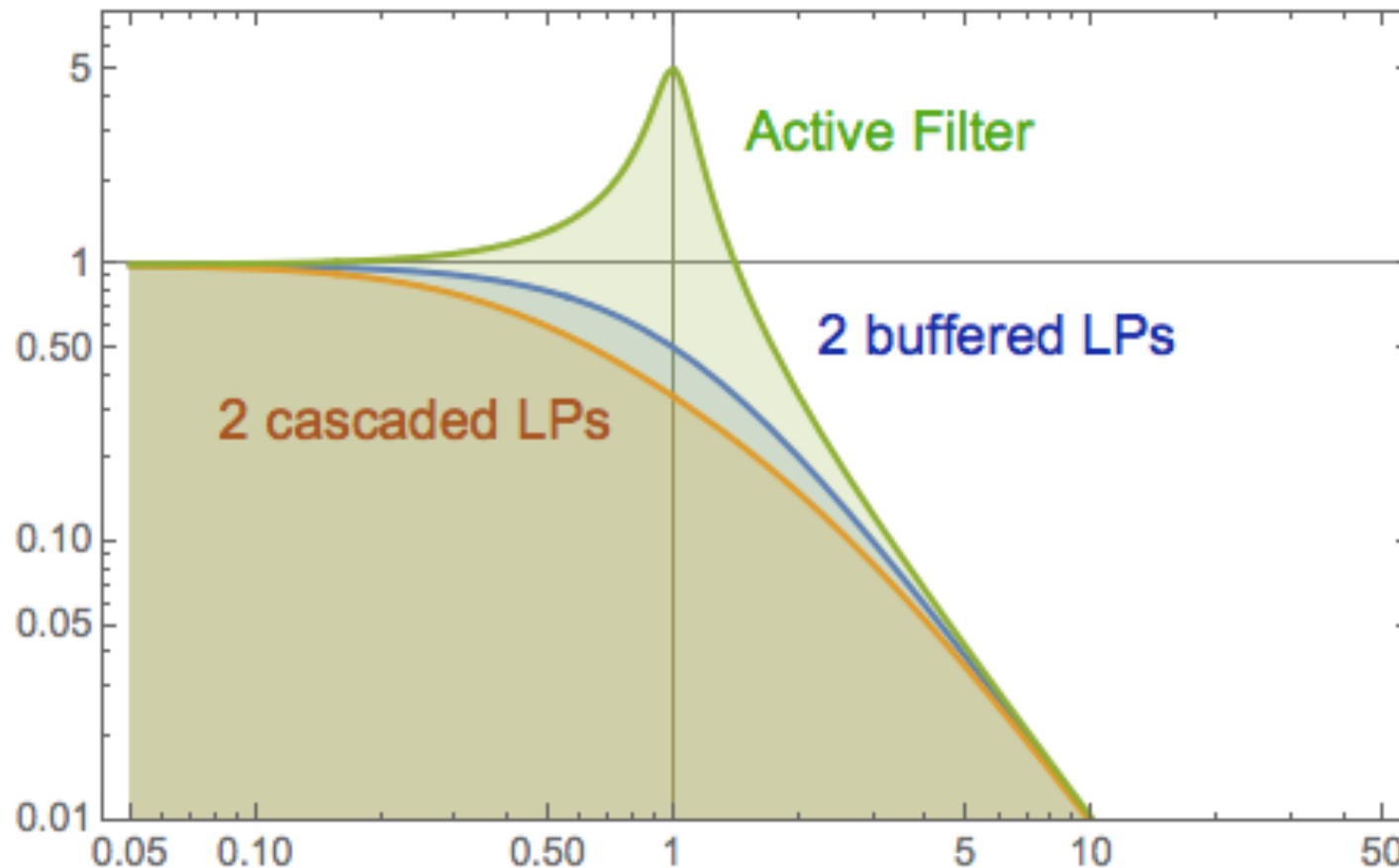- The active filter has an overshoot (for the values chosen)
- This is typical for complex conjugate poles






MAKING STEEP FILTERS



A Steep Low Pass Filter

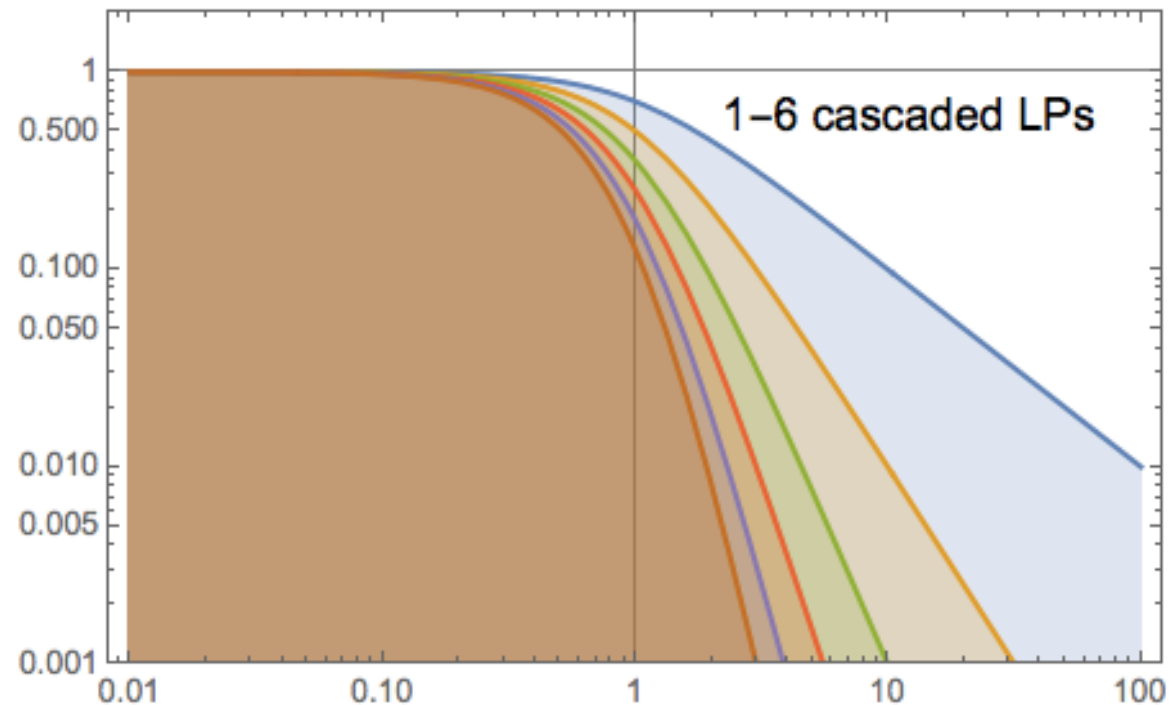- We want to design a higher (N^{th}) order low-pass filter which drops suddenly from **pass band** to **stop band**.
- We know that we roll off with slope $-N$ at the end (for $s \rightarrow \infty$).




- Simple cascaded LPs attenuate by $2^{-N/2}$ at the corner
- Can this be improved ?




Choosing the Poles

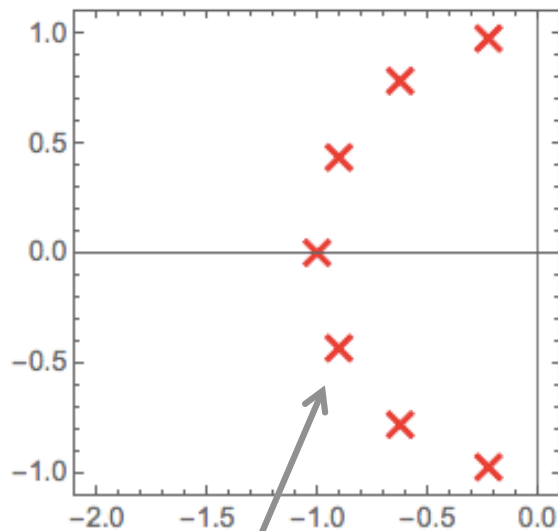- The Idea: Use complex poles and adjust them 'somehow'
- 'Butterworth' arranges poles on circle. Here: 7th order.



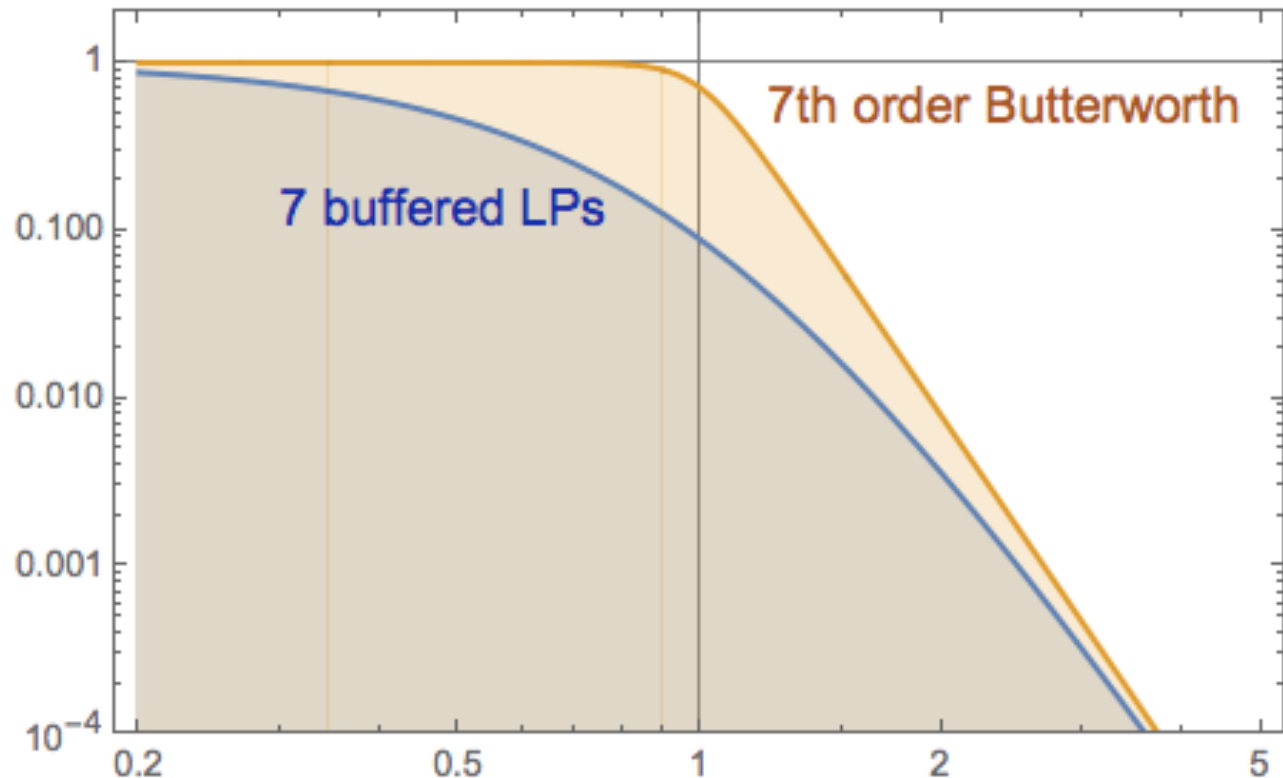It can be shown (easily) that poles on a circle have same corner frequencies.





- Wow! Butterworth attenuation at the corner is only -3dB !



(Decomposing the Butterworth Filter)

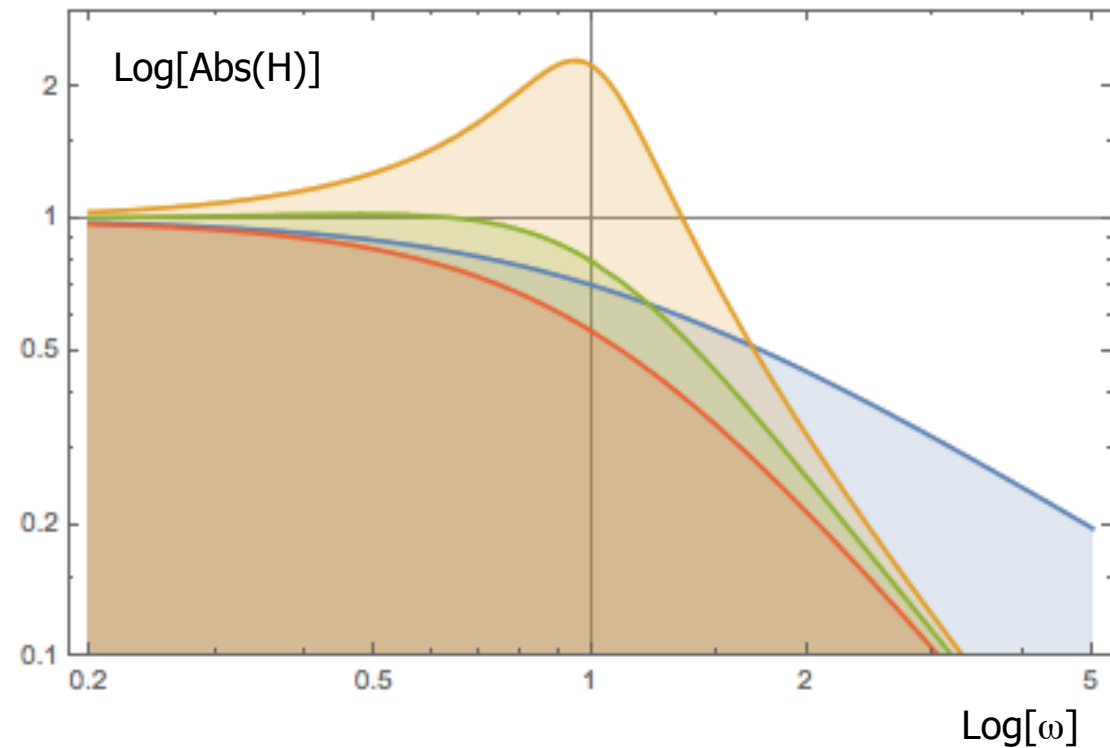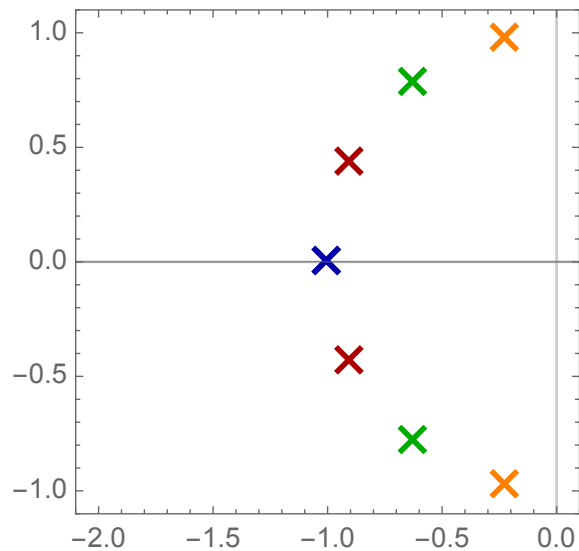
- For $N=7$:
 - One real pole (1st order, blue)
 - 3 conjugate poles (2nd order)





Even Steeper?

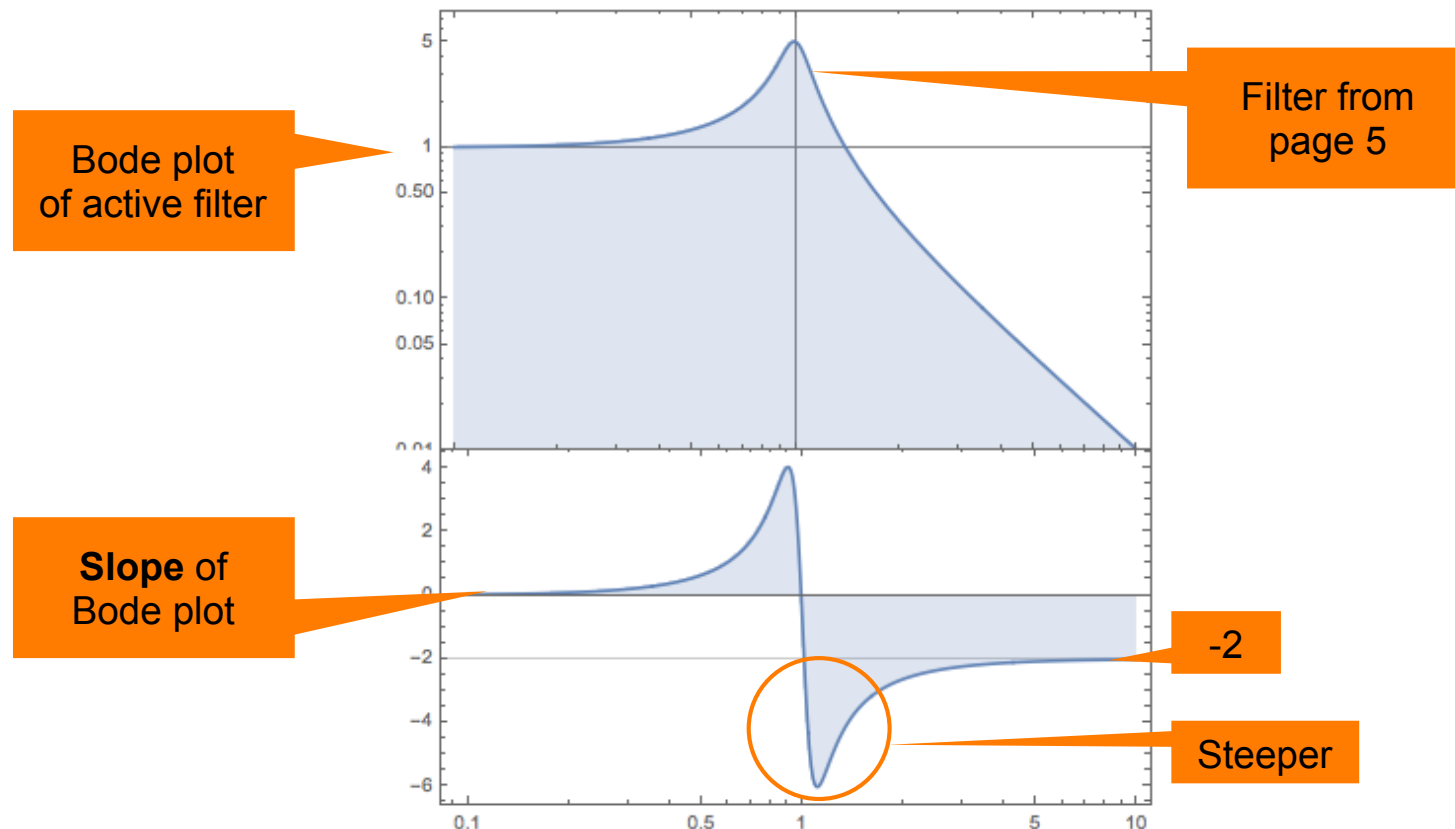- Remember: For large frequencies, we will always roll off with s^{-N} (the order of the filter, i.e. the number of caps)
- But: The 'peaking' for complex poles provides steeper response close to the bandwidth:





Placing the Poles...


- There are obviously MANY possibilities to place the poles...

- Desired filter properties are for instance
 - Flatness/ripple of the response in the pass band
 - Steepness of the drop
 - Ripple in the stop band
 - Response to step signals (overshoots)
 - Phase behavior



- Four main types have evolved:
 - Butterworth: Flat pass band
 - Bessel: No phase shift, no overshoot
 - Chebyshev: Steeper rolloff, but ripple in pass band
 - Elliptic: Even steeper rolloff, but ripple in pass and stop band



The Chebyshev Filter (7th order)

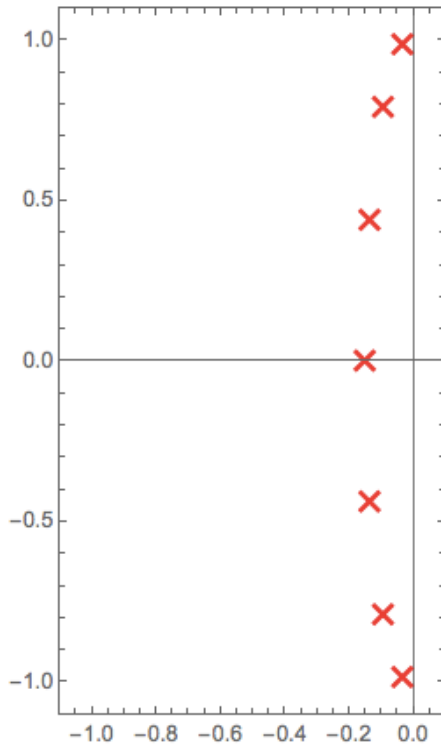

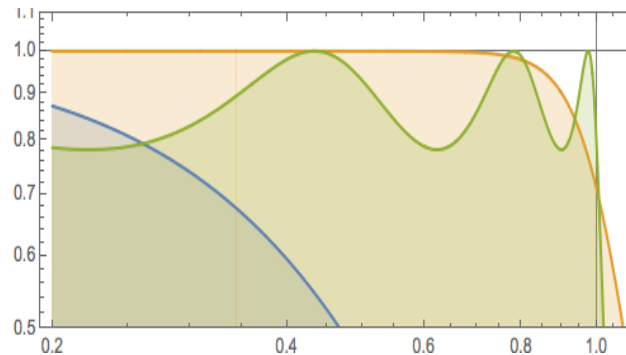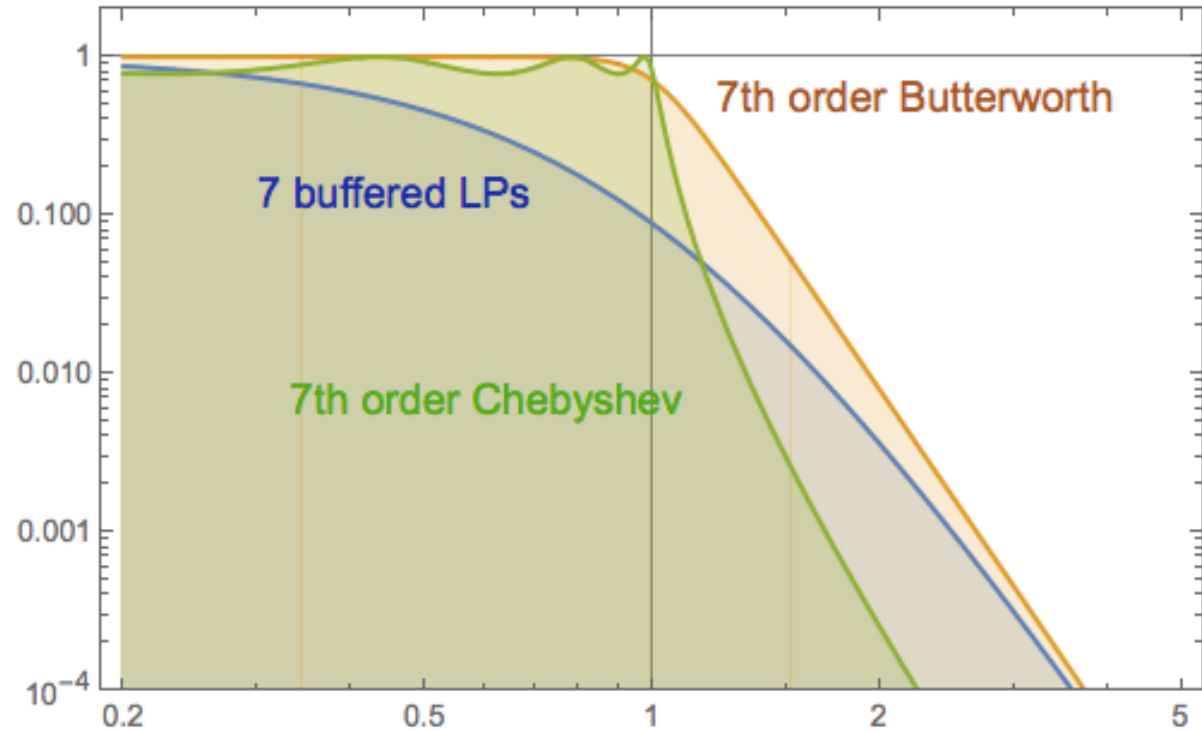Pole location for a 7th order Chebyshev filter (there are others, depending on the desired pass band ripple)



Zoom of pass band showing ripple of Chebyshev and flat response of Butterworth