



# Exercise 1: Thévenin Equivalent & RC-Circuits

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg





# Recommendations

- I strongly recommend to use a mathematical program (Mathematica, Maple, SageMath,..) to solve the exercises
  
- Inspect each result:
  - What happens for  $\omega \rightarrow 0, \infty$  ?
  - What happens if component values go to 0 or  $\infty$ ?


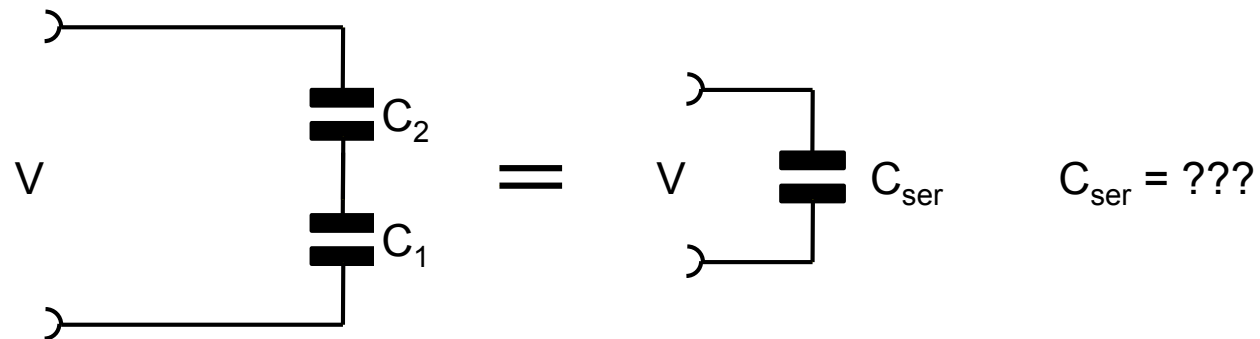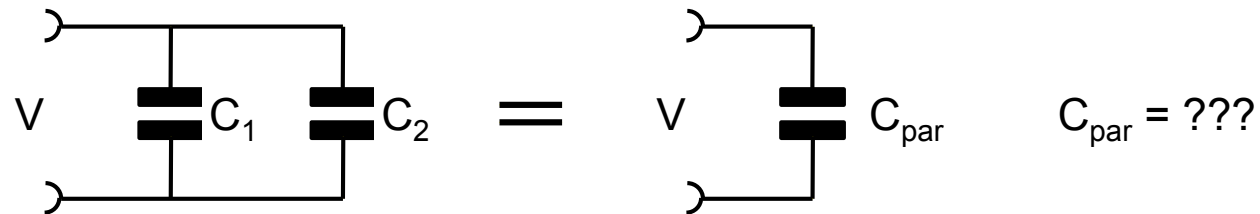
# Exercise 1.0


- Derive the expressions for the series and parallel connection of capacitors using
  - Charge conservation
  - Complex impedance & Kirchhoff's law




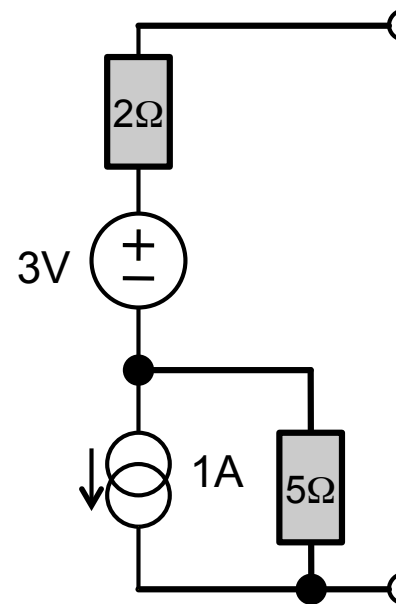
## Exercise 1.1

- Derive the Thévenin Equivalent for the following circuit:




- Try two different methods:
  - Use the Open/Short method with Kirchhoff's rules
  - Convert the I-source part to a voltage source first...


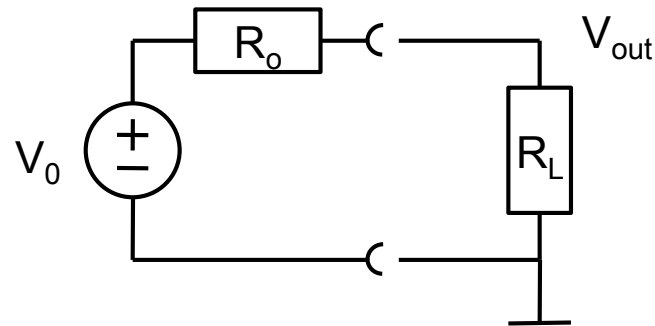
## Exercise 1.2

- A voltage source with voltage  $V_0$  and output resistance  $R_0$  is loaded by a resistor  $R_L$ :




- What is the output voltage  $V_{out}$  ?
- Which current flows in  $R_L$  ?
- What power is dissipated in  $R_L$  ?
  - Check that nothing is dissipated for  $R_L=0$  and  $R_L \rightarrow \infty$
- For which value of  $R_L$  is the dissipation maximized?
  - What is the dissipation?


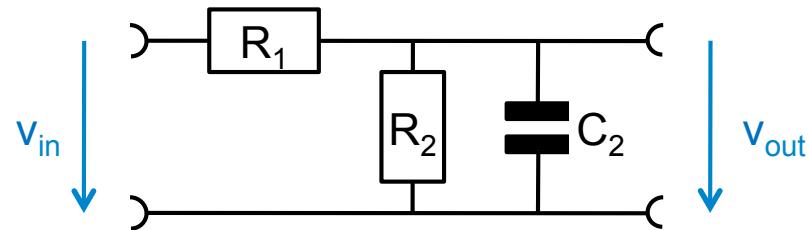
## Exercise 1.3

- Derive the Transfer Function of this circuit:




- Use 3 different approaches:
  - Treat the circuit directly (using Kirchhoff's rule)
  - Consider it as a voltage divider of two Impedances. Use  $R_1$  for  $Z_1$  and the parallel connection of  $R_2$  and  $C_2$  for  $Z_2$
  - Replace the (resistive) voltage divider by its Thévenin equivalent and then add the capacitor
- Make a Bode Plot
  - Describe the difference to the normal Low Pass Filter


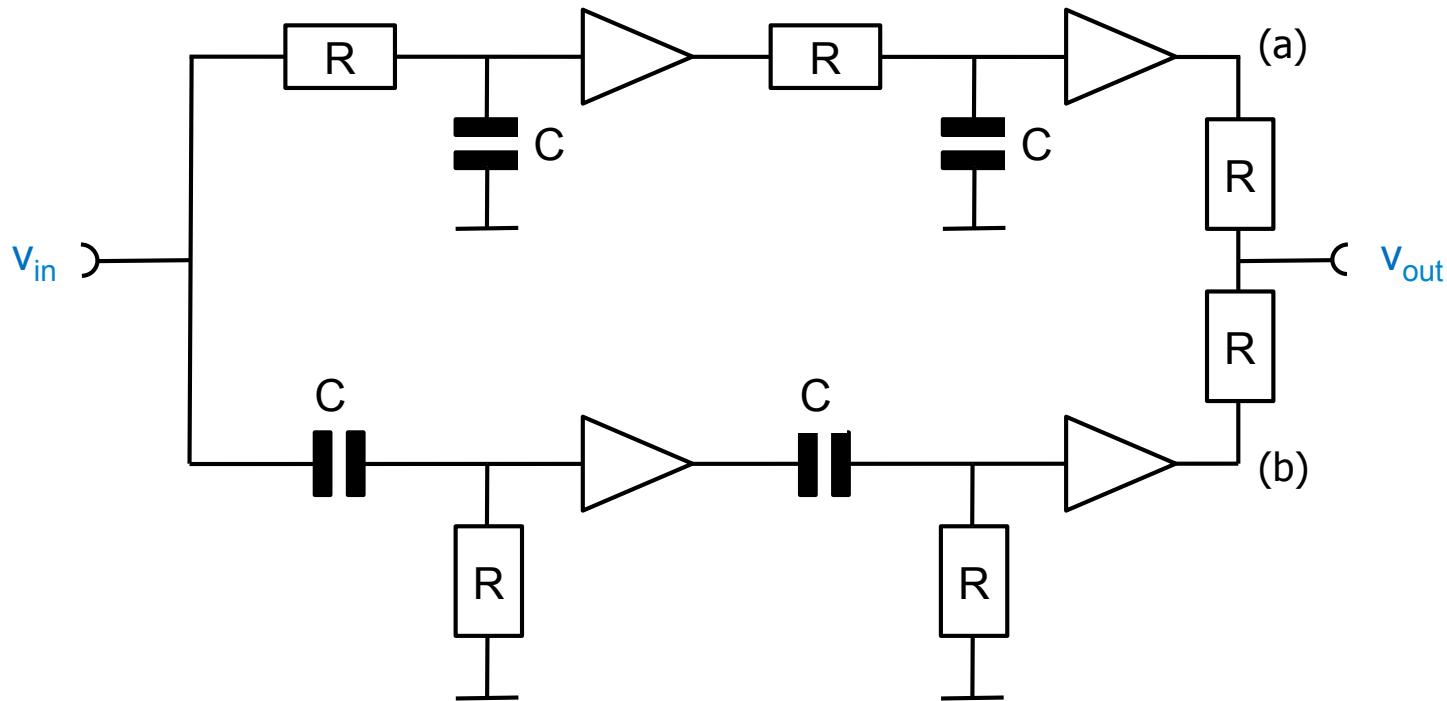
## Exercise 1.4: Notch Filter

- Consider the following circuit made of cascaded High- and Low Pass stages:
  - The resistors at the output just add the signals at (a) and (b)




- What is the output signal at the corner frequency?
  - Explain this by comparing amplitudes *and phases* at (a) and (b)


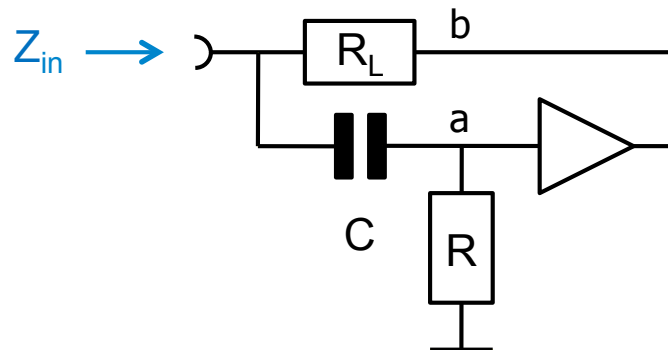
## Exercise 1.5: Gyrator

- A 'Gyrator' can mimic inductive behaviour, while using only resistors, capacitors and amplifiers
- Consider the following circuit:
  - the triangle is a voltage amplifier with gain=1 ('follower'). It forces node b to the potential of node a



- Calculate the input impedance  $Z_{in} = U_{in}/I_{in}$  of the circuit
  - (Use Kirchhoff's law at the input node and node a)
- For frequencies  $< 1/C R_L$ , the denominator can be neglected.
- Compare the result to an inductor in series with  $R_L$ !