



Exercise 4b: Time Domain


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



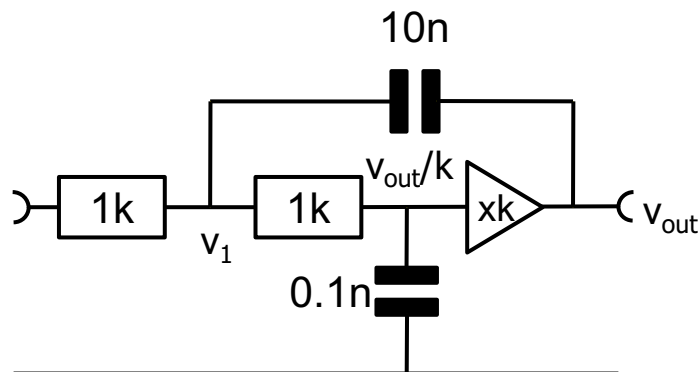Exercise 4b.1

- Derive $H[s]$ for the following active filter.



- For which k do you get a divergence ?
- For $k=1$, derive the step response of the circuit
- Simulate the circuit and compare quantitatively.



Solution 4b.1

■ $H[s]$

$$\text{In[221]:= EQ1} = \frac{v_{in} - v_1}{1} == \frac{v_1 - \frac{v_{out}}{k}}{1} + (v_1 - v_{out}) s 10;$$

$$\text{EQ2} = \frac{v_1 - \frac{v_{out}}{k}}{1} == \frac{v_{out}}{k} s \frac{1}{10};$$

$$\text{In[224]:= \$Assumptions} = k > 0 \ \&\& \ s > 0 \ \&\& \ \omega > 0;$$

▼ In[225]:= `Eliminate[{EQ1, EQ2}, v1] // Simplify`

$$\text{Out[225]= } (5 + 51 s + 5 s^2) v_{out} == 5 k (v_{in} + 10 s v_{out})$$

▼ In[226]:= `Solve[%, vout] // First`

$$\text{Out[226]= } \left\{ v_{out} \rightarrow - \frac{5 k v_{in}}{-5 - 51 s + 50 k s - 5 s^2} \right\}$$

▼ In[227]:= `Hactive[s_, k_] = \frac{vout}{vin} /. % // Simplify`

$$\text{Out[227]= } \frac{5 k}{5 + (51 - 50 k) s + 5 s^2}$$

▼ In[228]:= `Hactive[s, 1]`

$$\text{Out[228]= } \frac{5}{5 + s + 5 s^2}$$



Solution 4b.1


■ **Divergence:** `In[249]:= gpeak = Abs@Hactive[i, k]`

$$\text{Out[249]= } 5 \text{ Abs} \left[\frac{k}{51 - 50 k} \right]$$

`In[253]:= Solve[51 - 50 k == 0, k] // N`

$$\text{Out[253]= } \{ \{ k \rightarrow 1.02 \} \}$$

```
LogLogPlot[{Abs@Hactive[i ω, {0.9, 1, 1.02}]}], {ω, 0.1, 10},  
Frame → True, PlotRange → {Full, {0.01, 50}}, Filling → Axis,  
GridLinesStyle → Directive[Gray, Thin], GridLines → {{1}, {1}}]
```

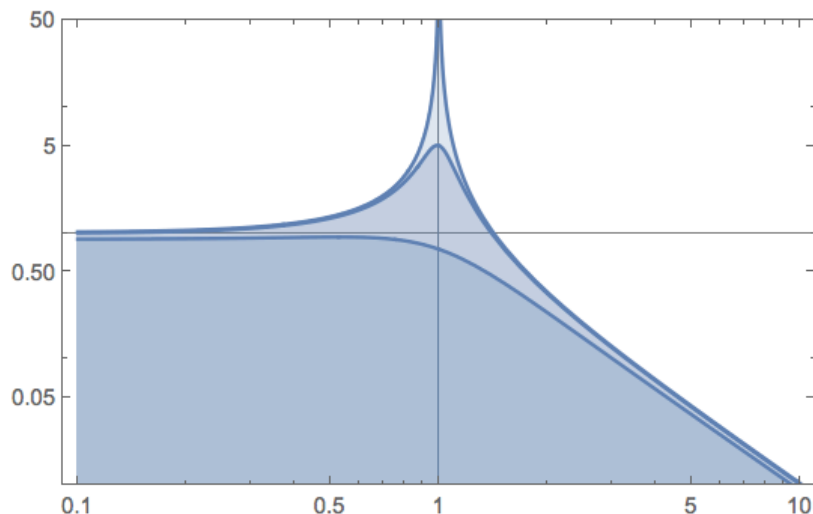




Solution 4b.1

■ Step Response

```
In[322]:= Step1 = InverseLaplaceTransform[ $\frac{H_{\text{active}}[s, 1]}{s}$ , s, t] // Simplify
```

$$\text{Out[322]} = 1 - e^{-t/10} \cos\left[\frac{3\sqrt{11}t}{10}\right] - \frac{e^{-t/10} \sin\left[\frac{3\sqrt{11}t}{10}\right]}{3\sqrt{11}}$$
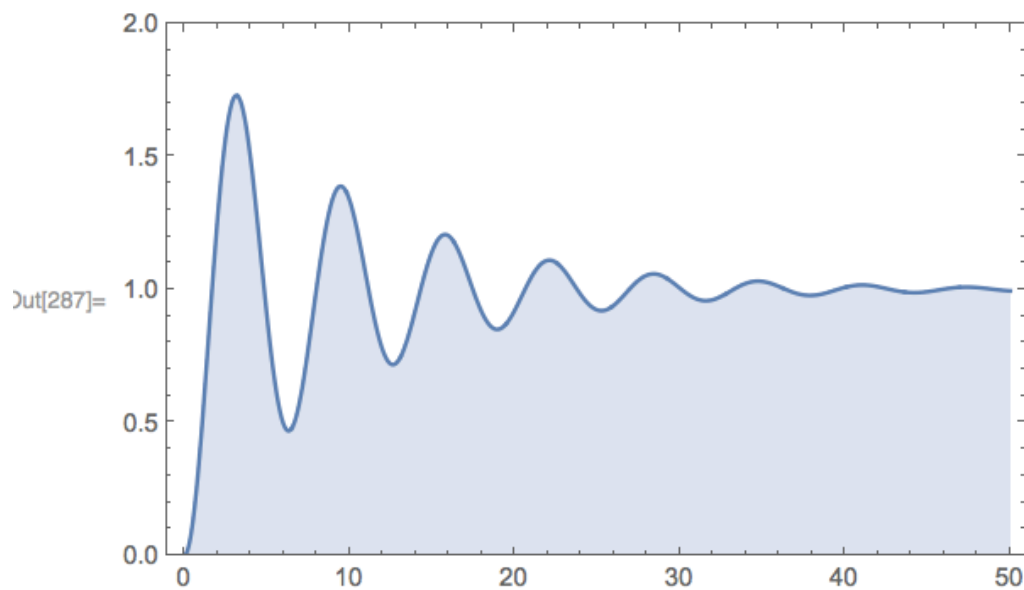
```
In[287]:= Plot[Step1, {t, 0, 50}, PlotRange -> {0, 2}, Frame -> True, Filling -> Axis]
```





Simulation:

