



Exercise 5: Abstract Circuits


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg






Exercise 5.1: voltage controlled current source

- The drain current in a transistor depends on the gate voltage. It can therefore be considered as a **voltage controlled current source** 'vccs'
- In the analogLib, the vccs has a differential input and two outputs of opposite signs:
 $i_1 = G (v_+ - v_-)$, $i_2 = -i_1$
- Set up the following circuit
 - Use a vccs with gain = 100 μS
 - Connect v_- to ground and v_+ to a dc voltage V_{IN}
 - Connect the i_1 and i_2 outputs to $V_{\text{OUT1}} = 1\text{V}$ and $V_{\text{OUT2}} = 1\text{V}$
- Now
 - Sweep V_{IN} (DC sweep, for instance from -1V to 1V) and observe the currents in the output voltage sources. Change the gain of the vccs and observe the effect.
 - Does the output **current** for a given V_{IN} depend on the V_{OUT} ?

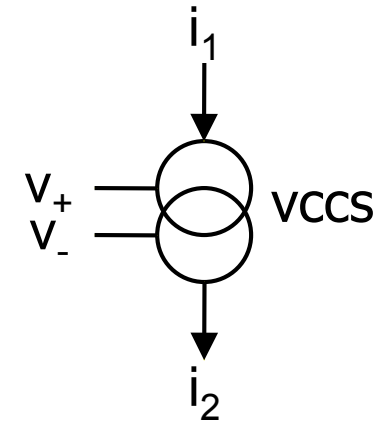



Solution 5.1

 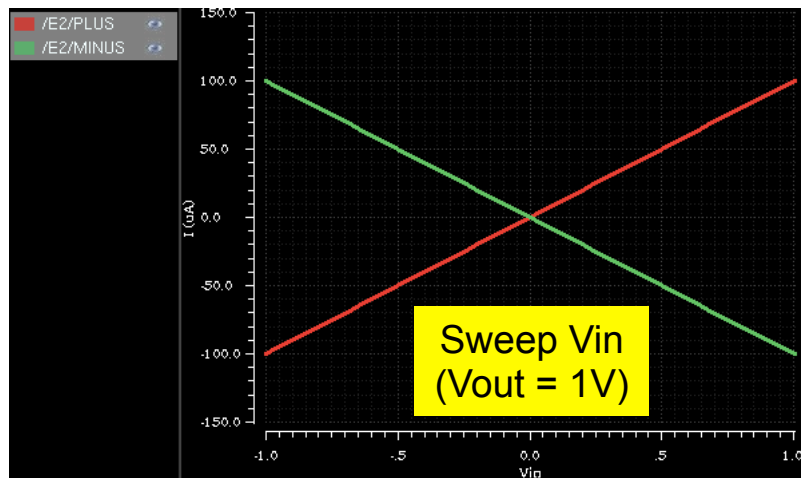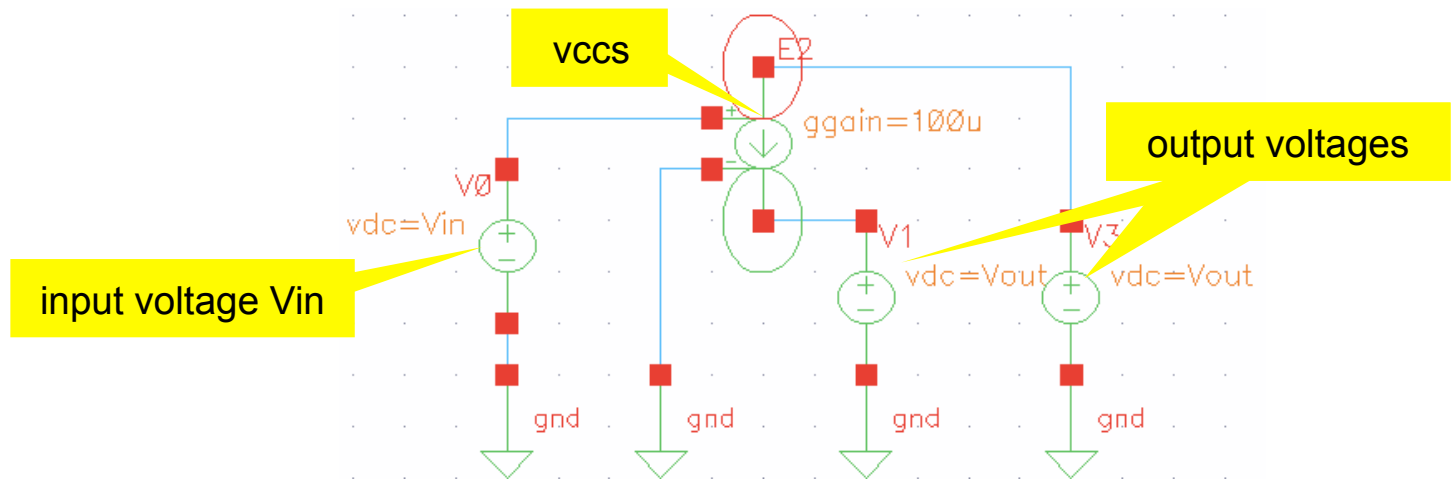

- The output current of these *ideal* sources does not depend on the output voltage



Exercise 5.2: Idealized Amplifier 1

- Implement the following circuit:


- The current from the vccs is sent to a resistor R

- Start with

- $G = 100 \mu\text{S}$
- $R = 2 \text{ k}\Omega$
- $V_0 = 1 \text{ V}$



- Simulate:

- How does v_{OUT} change when v_{IN} changed (e.g. from 0 to 1 V) ?
- Explain (Calculate) ! Write down the current equation at node v_{out} and use $i_{\text{VCCS}} = G v_{\text{in}}$
- What is the gain of the circuit $dV_{\text{OUT}} / dV_{\text{IN}}$?
- Change R and G in your simulation. Is the effect as expected (as calculated)?

 




Solution 5.2

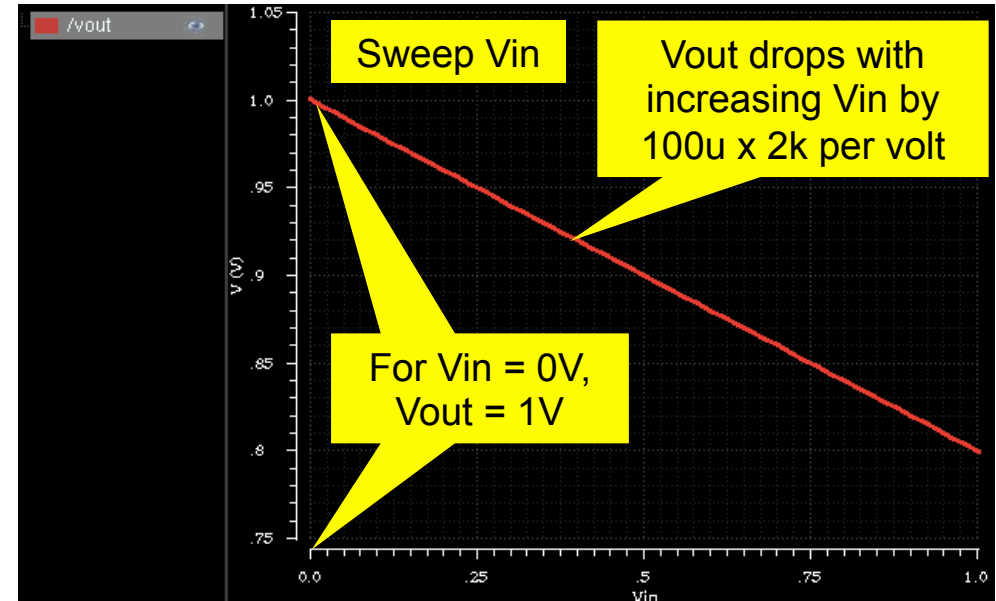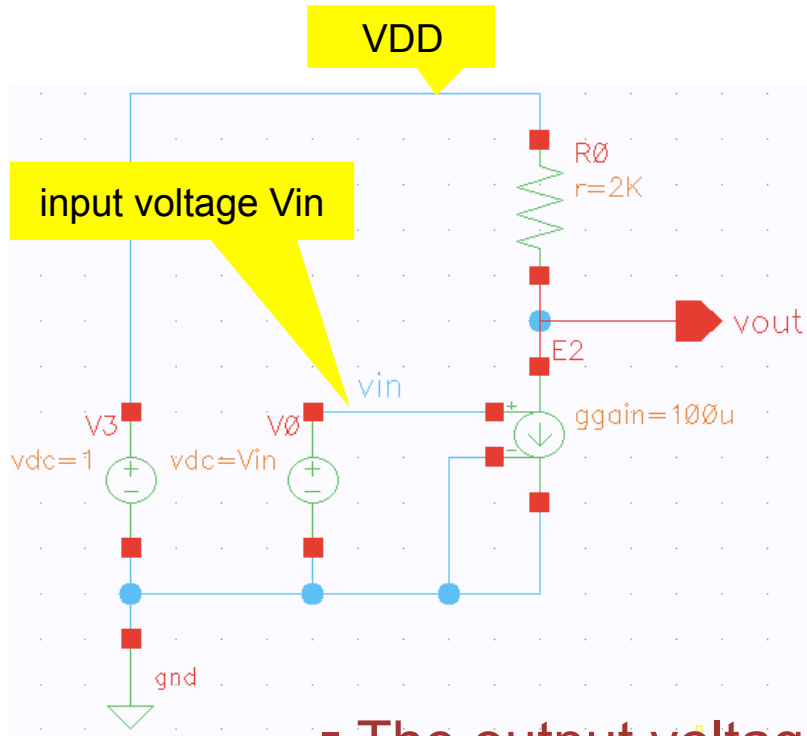



- The output voltage is $V_{out} = VDD - R \times I = VDD - R G V_{in}$
- The gain (slope) is $v = dV_{out} / dV_{in} = - R G$
- Changing R (0, 1kΩ, 2kΩ):

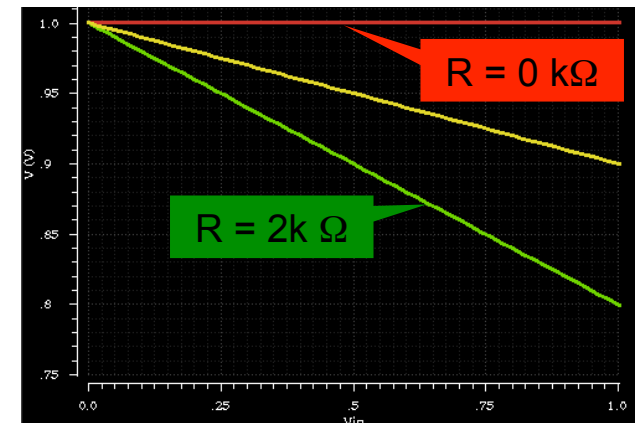




  Exercise 5.3: Idealized Amplifier 2

- In the previous circuit, change V_0 . What happens with the *DC offset* of the output and with the *gain*? Explain!
- So, what is the difference between the following two circuits ?





- PREDICT the gain ($V_{IN} \rightarrow V_{OUT}$) of the following circuit (Thévenin!):
- Verify this by simulation (for instance $R1 = 1 \text{ k}\Omega$, $R2 = 2 \text{ k}\Omega$)
- What happens when you exchange $R1$ and $R2$?

 



Solution 5.3

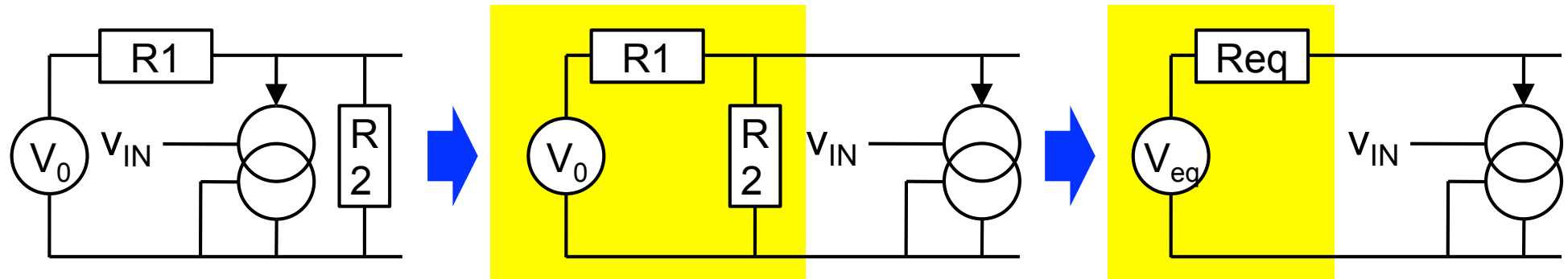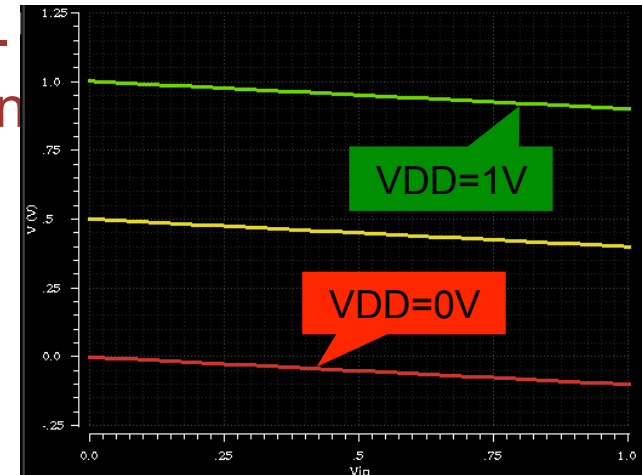- Changing VDD just changes the offset (i.e. shifts the curve up and down)
 - With the ideal source, the circuit also works at VDD=0V.
- The gain of the two circuit is the same. For a gain analysis, we can drop VDD for simplicity!





- $V_0/R_1/R_2$ can be replaced by V_{eq}/R_{eq} . R_{eq} is $R_1 \parallel R_2$. V_{eq} is irrelevant for gain. Gain becomes $G R_{eq}$.
- Gain is $-100\mu A \times 2k\Omega / 3 = -0.066$.
- Swapping R_1/R_2 makes no difference!



  Exercise 5.4: Idealized Amplifier 3

- Load the output with a capacitor (1 pF) to ground (left) and make an *ac* sweep. What is the dc gain?
- Where is the corner frequency? Why?





- Now try the right circuit. Is there a difference? Explain!
- Draw an equivalent circuit without V_0 !



Solution 5.4

 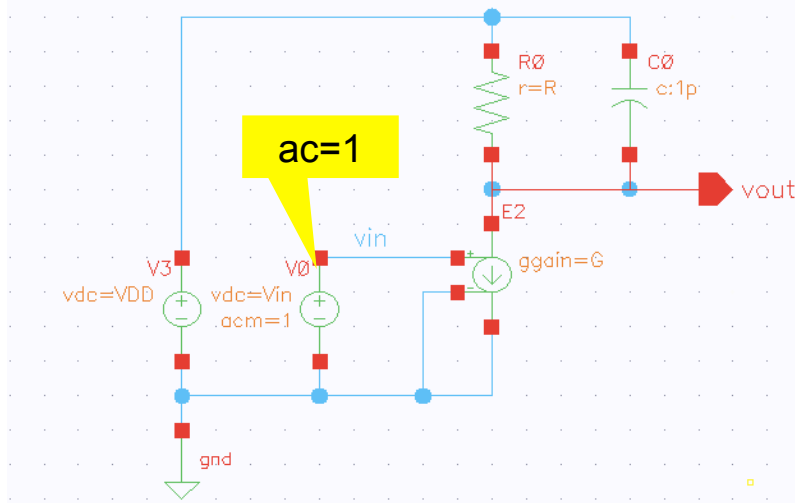- Remember to add an ac component to V_{in} !




- We see a Low Pass behavior
 - DC gain is $100\mu \times 2k = 0.2$
 - Corner is at $\omega = 1/RC = 1/2n = 500M \rightarrow \nu = 500M/6.28 = 79.6 \text{ MHz}$

- Derivation by current sum at v_{out} :

$$G v_{in} + v_{out}/R + v_{out} s C = 0$$


$$\rightarrow v_{out} / v_{in} = - \frac{G R}{1 + C R s}$$

 



 Exercise 5.5 (advanced!): More capacitors

- Consider this circuit with an extra C_1 between V_{IN} and V_{OUT}




- Draw the circuit without V_0 !
- What gain do you expect at *dc* ? Sign?
- What gain do you expect for *very* high frequencies? Sign?
- Calculate the transfer function $H[s]$ and the gain
 - Verify your predictions
- Simulate the circuit




Solution 5.5

- All elements to VDD to to ground:

 

 - Gain at DC (no caps) should be as before $-GR$
- At high frequencies, impedances of C dominate. We have a capacitive divider with gain $+ C_1/(C_1+C_L)$ (positive!)
- Derivation (current sum at v_{out}):



$$\text{Solve} \left[(v_{out} - v_{in}) s C_1 + G v_{in} + \frac{v_{out}}{R} + v_{out} s C_L = 0, v_{out} \right]$$


$$v = -RG \frac{1 - C_1 / G s}{1 + R (C_L + C_1) s} \quad \begin{matrix} v / . s \rightarrow 0 & \text{Limit}[v, s \rightarrow \infty] \\ -GR & \frac{C_1}{C_1 + C_L} \end{matrix}$$



Solution 5.5

$$v = -R G \frac{1 - C_1 / G s}{1 + R (C_L + C_1) s}$$

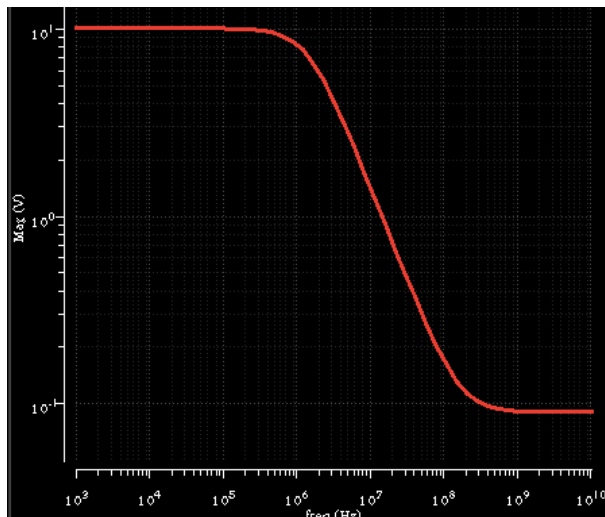- We have a pole at $p=1/R(C_1+C_L)$ and a ZERO at $z=G/C_1$
- Gain changes from negative to positive!
- Bode Plot depends on whether pole or zero is higher frequency



Example for $p > z$:
 $G=100\mu$, $R=100k$, $C_1=0.1p$, $C_L=1p$
 $p = 1/R(C_1+C_L) \sim 1/RC_L = 10MHz$
 $z = G/C_1 = 1GHz$

