



Exercise 10: Source Follower and Differential Amplifier

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



10.1 NMOS Source Follower

- Implement an NMOS Source follower
 - Use an NMOS with $W/L = 1\mu / 0.2\mu$
 - Connect Bulk to Source
 - Use an NMOS mirror with $W/L = 1\mu / 0.5\mu$ as current source
 - Bias the circuit with $10\mu\text{A}$

- Perform a DC and a transient analysis
 - What is the gain?
 - What happens for low input voltages? Why?
 - How does the gain change when you connect the bulk of the SF - NMOS to ground?




10.2 *PMOS* Source Follower

- Now draw a PMOS source follower with the same transistor dimensions & current...



10.3 Differential pair

- Draw a differential NMOS pair

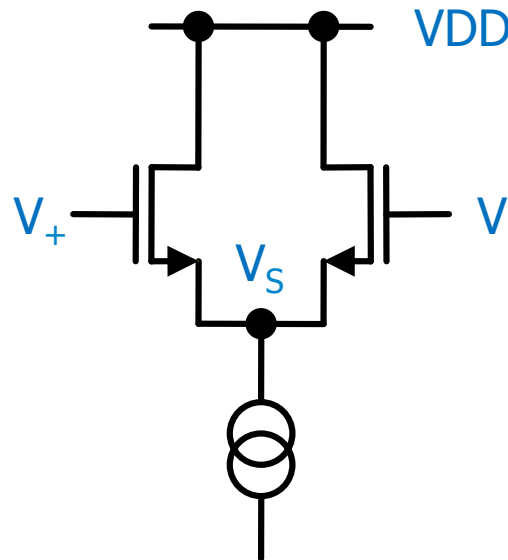


- Set $V_- = 1V$ and vary V_+ from 0 to $V_{DD} = 1.8V$
 - Observe I_+ , I_- and V_S .
 - Explain what you see!



10.4 Differential Amplifier

- Draw a full differential amplifier

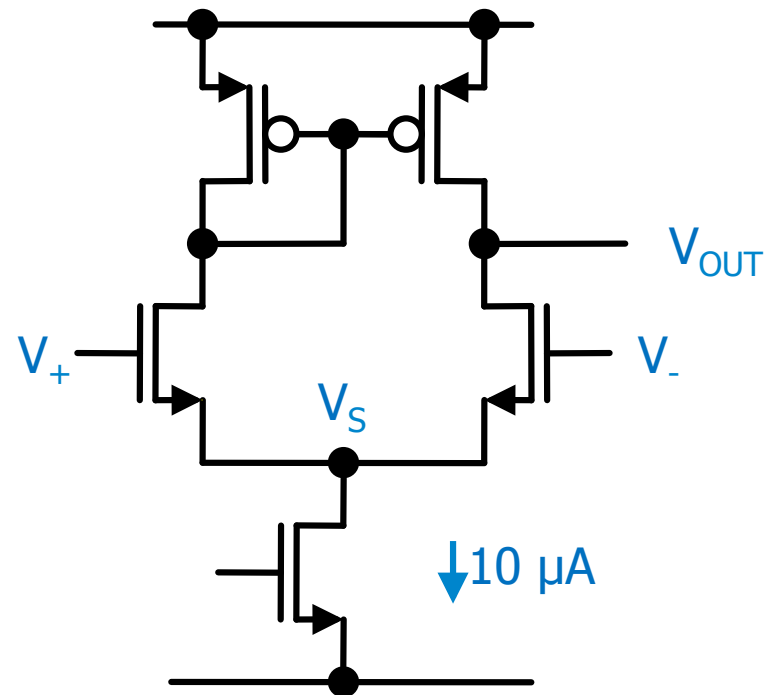

- Start with $V_- = 0.5V$
- What is the gain?
 - Can you guess an analytical approximation for the gain?
- Check the large signal behavior for different V_- .



10.5 *PMOS* Differential Amplifier

- Draw a full differential amplifier with a PMOS input stage
 - You must also change the other MOSs...