




Basic Circuits

Current Mirror, Gain stage, Source Follower, Cascode,
Differential Pair,...



Reminder: Effect of Transistor Sizes


- Very crude classification:

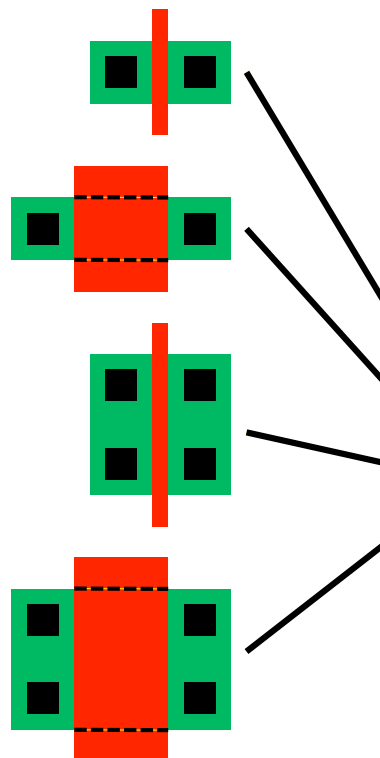

W	L	Current (const. V_{GS})	Output Resistance (const. V_{GS})	Gate Capacitance
small	small	0	low	small
small	large	-	high	high
large	small	+	low	high
large	large	0	high	very high




Reminder: Transistor Characteristics

 




The Three Basic Configurations:

 
- ‘Common **xxx** configuration’ means:
Terminal **xxx** of the MOS is common to input and output



 - common **source** config.
- ‘gain stage’
- inverting **voltage gain**
- *high* input impedance
- *high* output impedance



 - common **drain** config.
- ‘source follower’
- voltage gain ~ 1
- *high* input impedance
- **low output impedance**





- common **gate** config.
- ‘cascode’
- current gain = 1
- **low input impedance**
- *high* output impedance



The Diode-Connect MOS

- Consider a MOS with Drain and Gate connected
- $V_{DS} = V_{GS} \rightarrow V_{DS} = V_{GS} > V_{GS} - V_T = V_{DSat}$

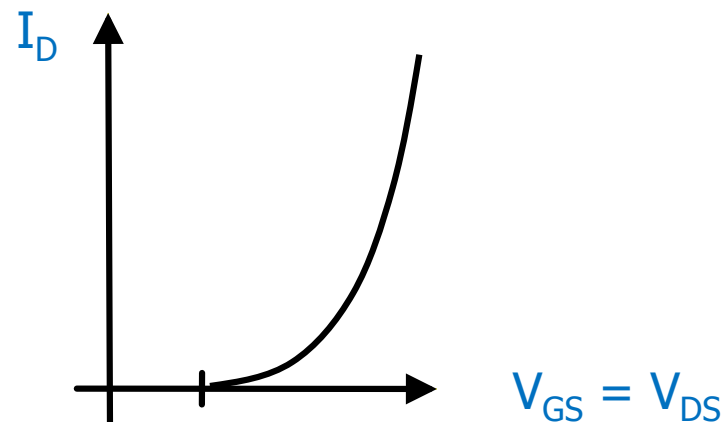 → A diode connected MOS is always in saturation!



$$I_D = K/2 W/L (V_{DS} - V_T)^2 (1 + \lambda V_{DS})$$

(in 'strong inversion')

- Important:

For *any* current I_D , V_{GS} adjust so that this current can flow!



THE CURRENT MIRROR



What You Should Learn

- In this first part, you should learn / understand
 - What 'saturation' is
 - How transistor geometry affects circuit properties
 - How circuit properties can be improved by *transistor geometry*
 - How small signal models can be applied
 - How circuit properties can be improved by *better circuits*

- What a current mirror is
- How several scaled currents can be generated
- What a bias voltage is




Transistors with same V_{GS}

- Consider 2 NMOS with same V_{GS} :

- Assuming saturation:

- $$I_1 = \frac{K}{2} \frac{W_1}{L_1} (V_G - V_T)^2 (1 + \lambda_1 V_{D1})$$
- $$I_2 = \frac{K}{2} \frac{W_2}{L_2} (V_G - V_T)^2 (1 + \lambda_2 V_{D2})$$

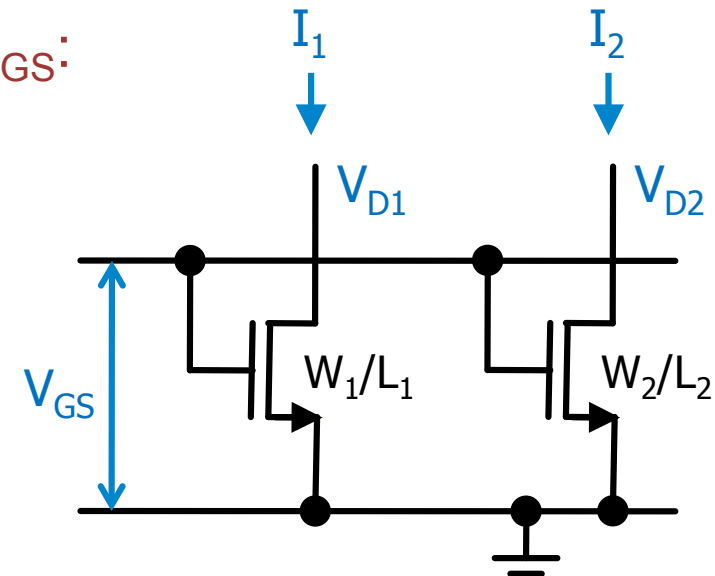- $$\rightarrow \frac{I_2}{I_1} = \frac{W_2/L_2}{W_1/L_1} \frac{1 + \lambda_2 V_{D2}}{1 + \lambda_1 V_{D1}}$$



- The Early effect leads to a ,small‘ deviation


- For $L_1 = L_2$:

- The ratio of input/output current is given by the ratio of the W s
- The Early effects cancel if $V_{D1} = V_{D2}$ (must watch λ)



The Current 'Mirror'

 - First, we assume that M_1 and M_2 are identical
 - $W_1 = W_2, L_1 = L_2$
- Now connect M_1 as a diode
 - V_G adjusts such that I_{in} flows into M_1
- M_2 and M_1 have the same gate voltage $\rightarrow I_{out} = I_{in}$
 - The current is 'mirrored' from the input to the output




- In more detail, Early Effect must be taken into account
 - $I_{out} = I_{in}$ *exactly* only for $V_D = V_G$ (do you understand why?)



Varying the Output Current

 - If $W_2 \neq W_1$ (assuming still $L_1=L_2$), then $I_{out} = W_2/W_1 I_{in}$
- $L_1 \neq L_2$ should be avoided because Early Effects are different
- Additional MOS can be connected to give further outputs




- The gate voltage of the sources is called a '*Bias*' Voltage




Large W vs. Multiple MOS

 - The *ratio* W_2/W_1 is used for current multiplication
- If this implemented by MOSs with different layouts, *edge effects* can lead to unknown ratios.
 - To be more precise, the real W of a device is often $W_{\text{real}} = W_{\text{drawn}} - W_{\text{offset}}$ (W_{offset} can have both signs)



 - It is much safer to use *multiple identical* devices!
- For a non-integer ratio A/B , use B MOS on diode side and A MOS on output side.





Exercise: NMOS Mirror

- Design a NMOS current mirror arrangement which converts an *input current of $10\mu\text{A}$* into two output currents of $10\mu\text{A}$ and $30\mu\text{A}$.
 - Chose $W/L = 1\mu\text{m} / 1\mu\text{m}$
 - Connect the outputs to $V_{DD} = 1.8\text{V}$
- What is the gate voltage?
- Compare it to the threshold voltage of the MOS!
- What is the lowest voltage at the outputs for which you expect the mirror to work? Is it the same for both outputs?
- Verify this with simulation by forcing the outputs to some voltage V_{out} and perform a DC sweep of V_{out} .
- How can you make the mirror still work at lower output voltages? Simulate this!
- For which output voltage is I_{out} 'perfect', i.e. exactly $10/30\mu\text{A}$?




Exercise: PMOS Mirror

- Design a PMOS 1:1 current mirror
- Verify its operation by simulation



The PMOS mirror

 
- Here is how the PMOS mirror looks like:





Output Resistance

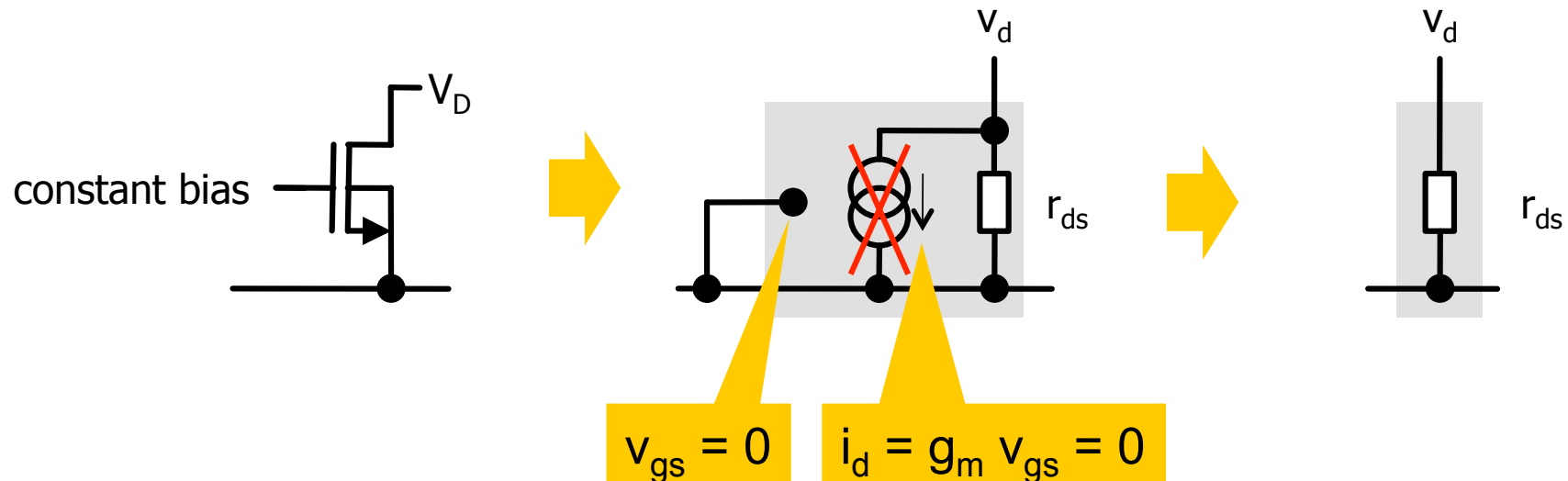- The Output Resistance r_{out} of the Mirror is just that of the (output) MOS
- This is obvious from the small signal model
 - The Gate voltage is *constant*, so there is *no small signal*: $v_{gs} = 0$





- r_{ds} depends on the current and on the geometry (W,L)



Good and Bad Mirrors

  - Normally, the output MOS of the mirror is used as a current source. We therefore want
 - high output resistance r_{ds} → we need small I_D , large L
 - low saturation voltage → we need small I_D , small L , large W



- Therefore: Good mirrors must have large L and W
 - large L to increase output resistance
 - large W to lower saturation voltage




THE CASCODE



Improving the Mirror: The Cascode

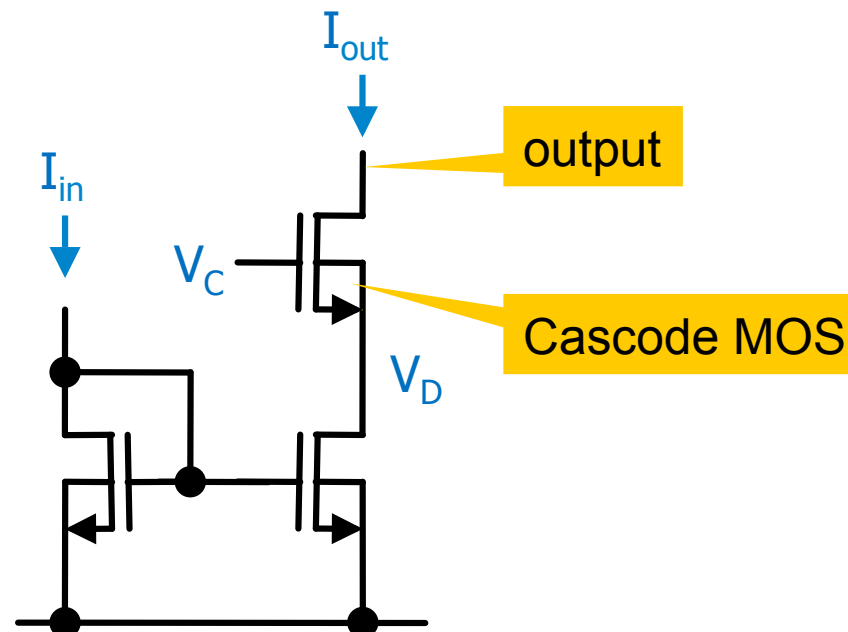
- The output current in a normal mirror changes, because output voltage = drain voltage
- By inserting another MOS *between* output and drain, the drain voltage is kept (more) constant
 - the current changes (less)
 - the output resistance is higher :-)
- The upper MOS is called a **CASCODE**





The Cascoded Current Source in Action

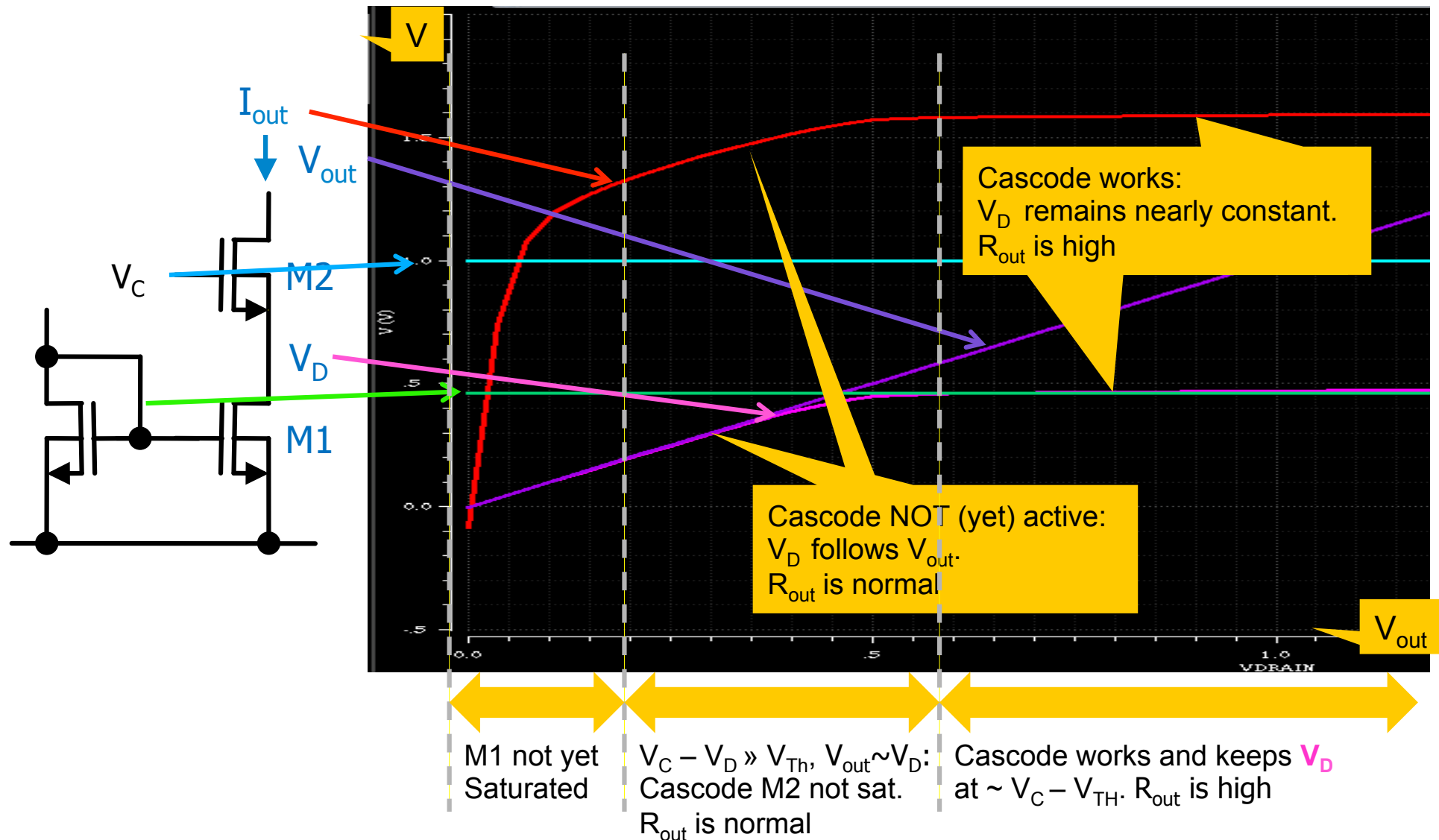
- Simulation for $V_C = 1V$ (not optimal, see later...)





Biasing the Cascode


- The *gate* voltage of the cascode MOS M2, V_C , defines the *drain* voltage V_D of the 'current setting' MOS M1
 - V_D is *roughly one threshold* voltage below V_C
 - More precisely, $V_D = V_C - V_T - \text{Sqrt}(I_D 2/K L/W)$
 - (This holds when Bulk and Source are connected (-), otherwise, the Substrate Effect lowers V_D)
- V_D (and thus V_C) should be chosen
 - *High enough* to keep M1 'just' saturated
 - *As low* as possible so that V_{out} can be low
- The 'total' saturation voltage at the output for optimal V_D / V_C is \sim twice that of M1 (if M1 and M2 have same sizes)

 



Simulation: Varying V_C


- Sweep V_C from 0.2...1.8 V:

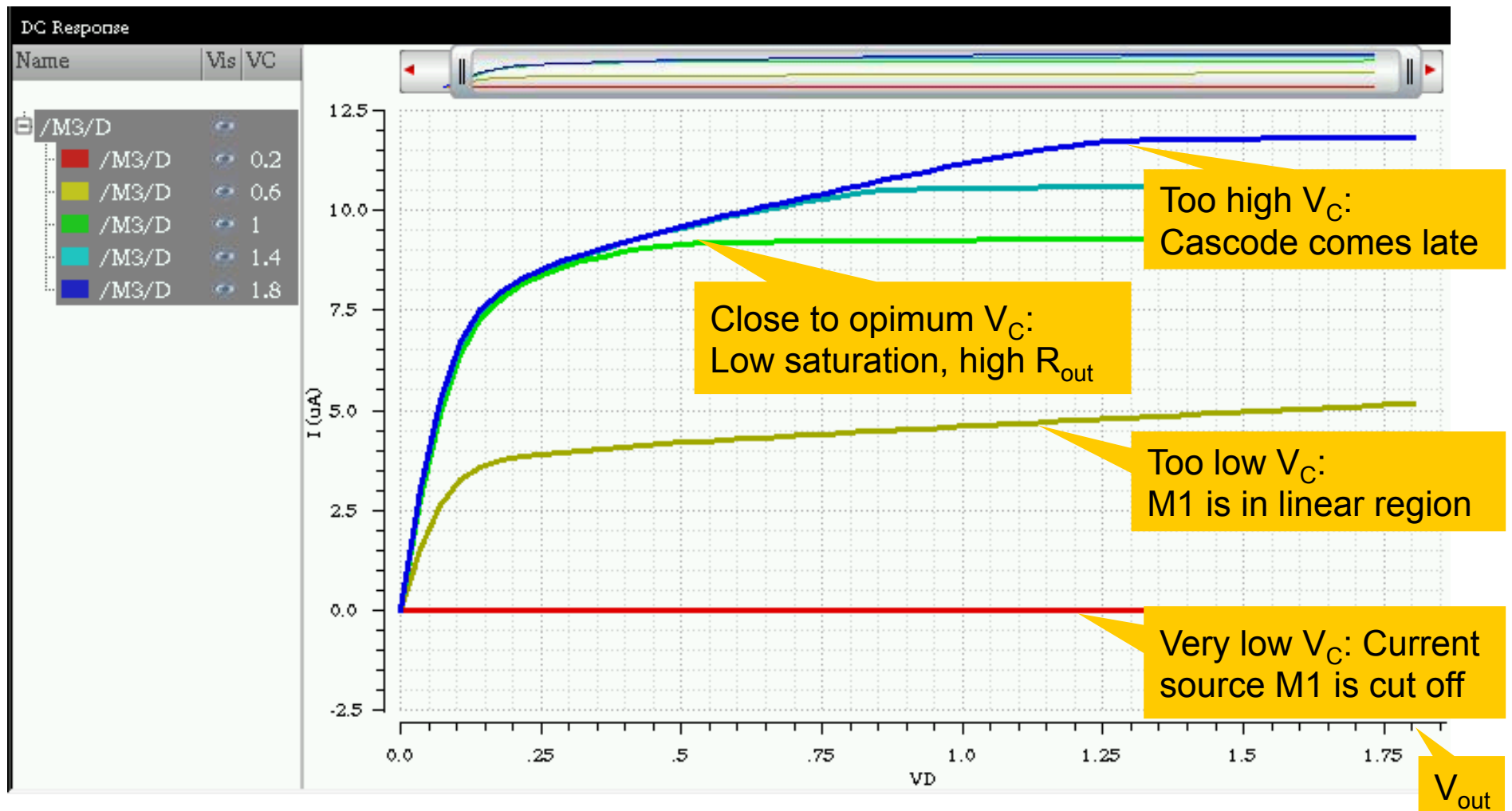



Zoom of 'Optimum' V_C :


- Sweep 0.7...1.0 V

 



R_{out} and *dynamic range* in more detail

 - Look at derivative of output characteristic ($\partial I_{out} / \partial V_{out} = 1/r_{out}$)
 - Small is good
- Again, blue (0.8 V) or red (0.9 V) are best...






Output Resistance of Cascoded MOS

■ Small signal analysis

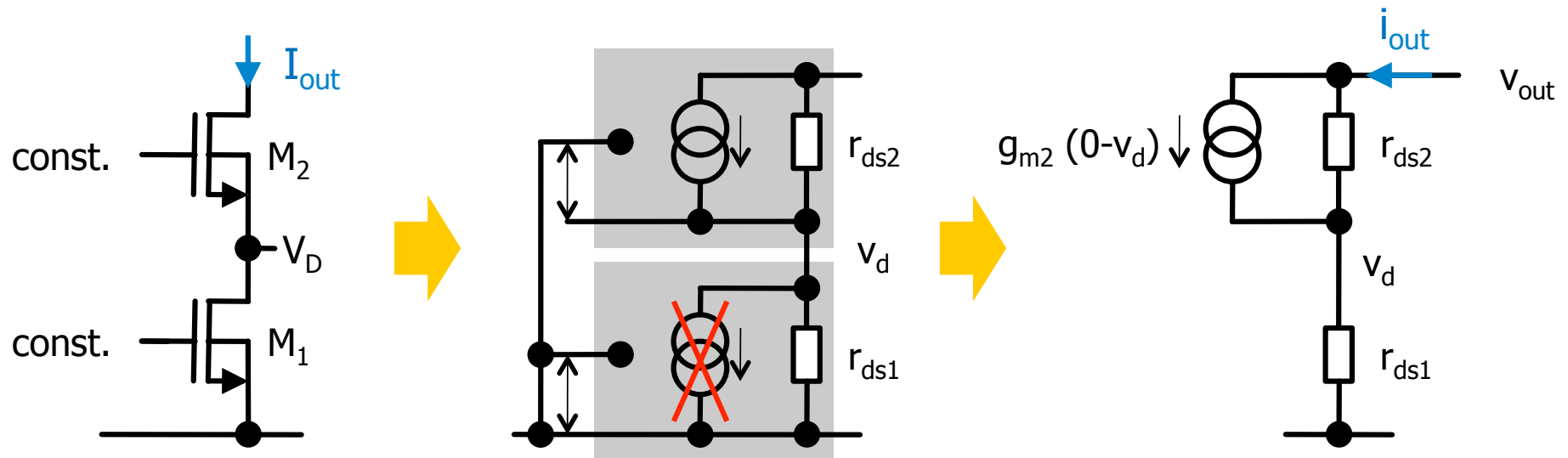- We only need to consider the output part
- Fixed voltages are equivalent to ground
- Current source M1 delivers no current ($V_{GS} = \text{fix}$)



■ Current sums:

$$\bullet \quad i_{\text{out}} = (v_{\text{out}} - v_d)/r_{\text{ds2}} - g_{\text{m2}} v_d = v_d / r_{\text{ds1}} \rightarrow v_d = \dots \rightarrow r_{\text{out}} = v_{\text{out}}/i_{\text{out}}$$

$$\rightarrow r_{\text{out}} = r_{\text{ds1}} + r_{\text{ds2}} + g_{\text{m2}} r_{\text{ds1}} r_{\text{ds2}} \rightarrow r_{\text{out}} \cong r_{\text{ds1}} \times (g_{\text{m2}} r_{\text{ds2}})$$



The Calculation

$$\frac{v_{out} - v_d}{r_{ds2}} - g_{m2}v_d = \frac{v_d}{r_{ds1}} = i_{out}$$

$$\frac{v_{out}}{r_{ds2}} = \frac{v_d}{r_{ds1}} + \frac{v_d}{r_{ds2}} + g_{m2}v_d$$

$$\frac{1}{v_d} = \frac{r_{ds2}}{v_{out}} \left(\frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} + g_{m2} \right)$$

$$r_{out} = \frac{v_{out}}{i_{out}} = \frac{v_{out}r_{ds1}}{v_d} \quad i_{out} = v_d / r_{ds1}$$

$$= v_{out}r_{ds1} \frac{r_{ds2}}{v_{out}} \left(\frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} + g_{m2} \right)$$

$$= r_{ds2} + r_{ds1} + g_{m2}r_{ds1}r_{ds2}$$



Summary: The Cascoded Current Source

- A cascode MOS stabilizes the drain voltage of the current source
- The output resistance increases by a *factor* $g_{m2} r_{ds2}$
 - This is the ‘intrinsic gain’ of M2
 - It is typically >20 (depending on geometry and current)
- The cascode bias voltage should be chosen such that the current source is *just above* the *edge* of saturation
- The overall saturation voltage of the cascoded source is ~ 2 times the ‘unit’ saturation voltage
- For advanced circuits, see the exercises!



Design Goals for Current Sources

- High output resistance
 - large L , cascode, regulation
- Low saturation voltage
 - large W , optimal biasing
- Matching
 - Same Drain voltages (and of course same geometries)
- Speed (sometimes)
 - small devices, high current



Advanced Current Source Circuits

- See Exercises



THE GAIN STAGE (COMMON SOURCE AMPLIFIER)



The Gain Stage


- The current in the MOS is set by the (large signal) $V_{GS} = V_{in}$
- We assume for now that this current is coming from an *ideal* voltage source sourcing I_0
- In the operation point, V_{GS} and I_0 must 'correspond'!

- When V_{in} **raises** (above the op. point)

- I_D increases. It becomes $> I_0$
- Current is pulled out of the load
- V_{out} **drops**

- When V_{in} **drops**

 - I_D decreases. It becomes $< I_0$
- Current is pushed into the load
- V_{out} **increases**




Inverting amplifier



Large Signal Behavior

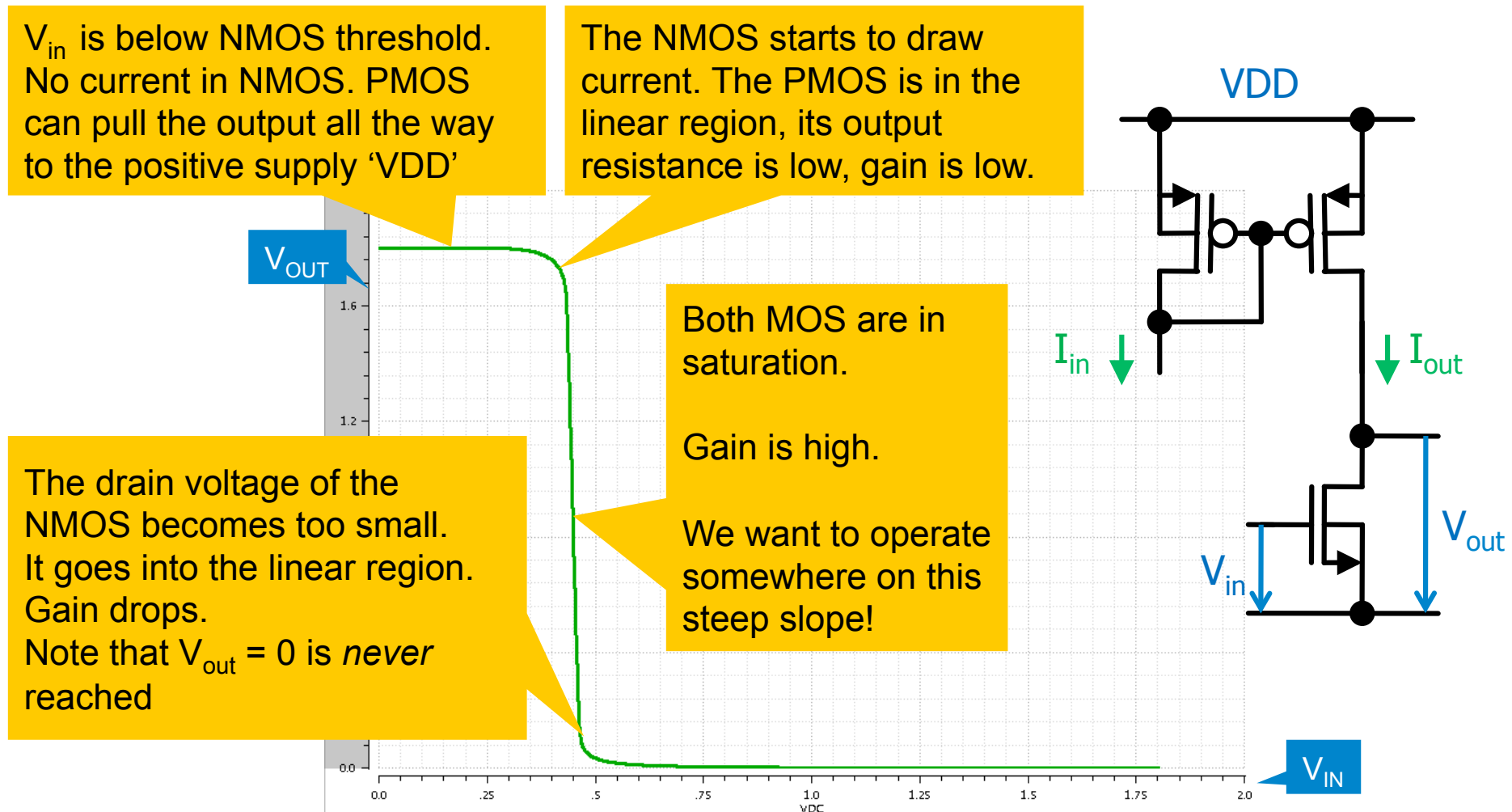
- Use real current source now (PMOS mirror)
- Observe the 4 main operation regimes:





Changing the Bias Current

 More Bias Current ('stronger current source')




- 'Threshold' is 'later'
 - V_{IN} must be higher until I_D reaches $100 \mu A$
- 'Round region' is wider
 - PMOS is longer in linear region because V_{GS} is higher
- Output does not go so low (all the way to GND)
 - NMOS cannot deliver enough (relative to $100 \mu A$) current, it comes into the linear region



Gain of the Gain Stage: Intuitive Way

 - When V_{in} changes by a small amount $\Delta V_{in} = v_{in}$, how much does V_{out} change, i.e. what is v_{out} ?
 - Note difference in Capital and Small letters: $V_{in} \neq v_{in}$




- What happens?
 - v_{in} leads to a change i_D of I_D of $i_D = g_m v_{in}$ (Definition of g_m !)
 - With a resistive load R , this gives a voltage change $v_{out} = R \times i_D$
 - This change is opposite in direction to v_{in}
 - Therefore: $v_{out} = - R \times g_m \times v_{in}$

$$\text{gain } v = v_{out}/v_{in} = - R \times g_m$$



Gain of the Gain Stage: Small Signal Calculation

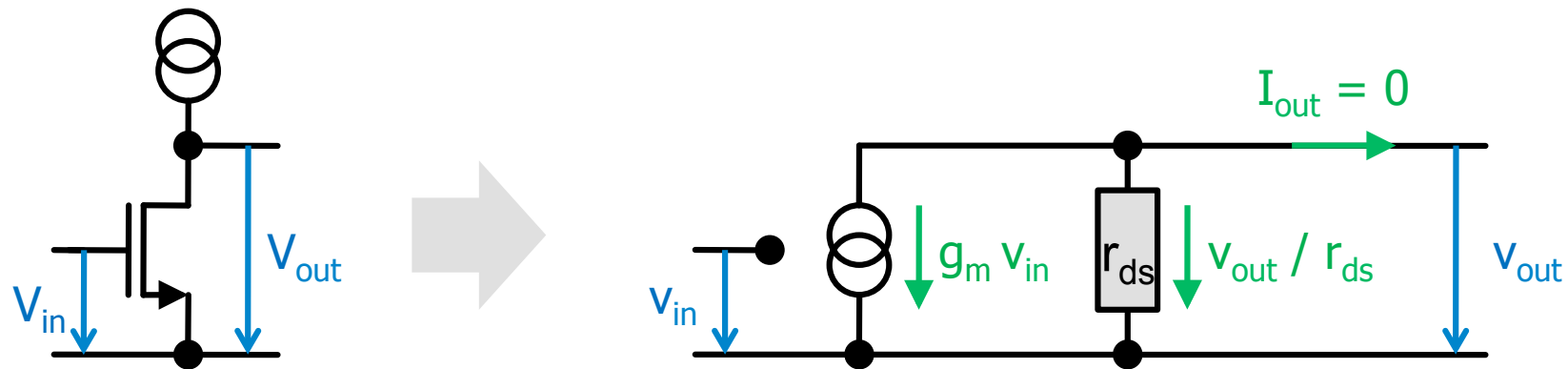- Consider only the MOS
- Replace it by its small signal equivalent:



- Calculation
 - current at output node = 0 (Kirchhoff)
 - therefore: $0 = g_m \times v_{in} + v_{out} / r_{ds}$
 - so that, again

$$v = v_{out} / v_{in} = - g_m \times r_{ds}$$



Numbers

- Typical gains are 10 ... 40
 - they depend on technology, current, transistor size,...

▪ Therefore: $|v| = g_m r_{ds} = g_m / g_{ds} > 10 \gg 1$

or $g_m > 10 / r_{ds} = 10 g_{ds}$




The transconductance g_m of a MOS is usually much larger than the output conductance g_{ds} .

- This can often be used to simplify small signal expressions!



AC Sweep

  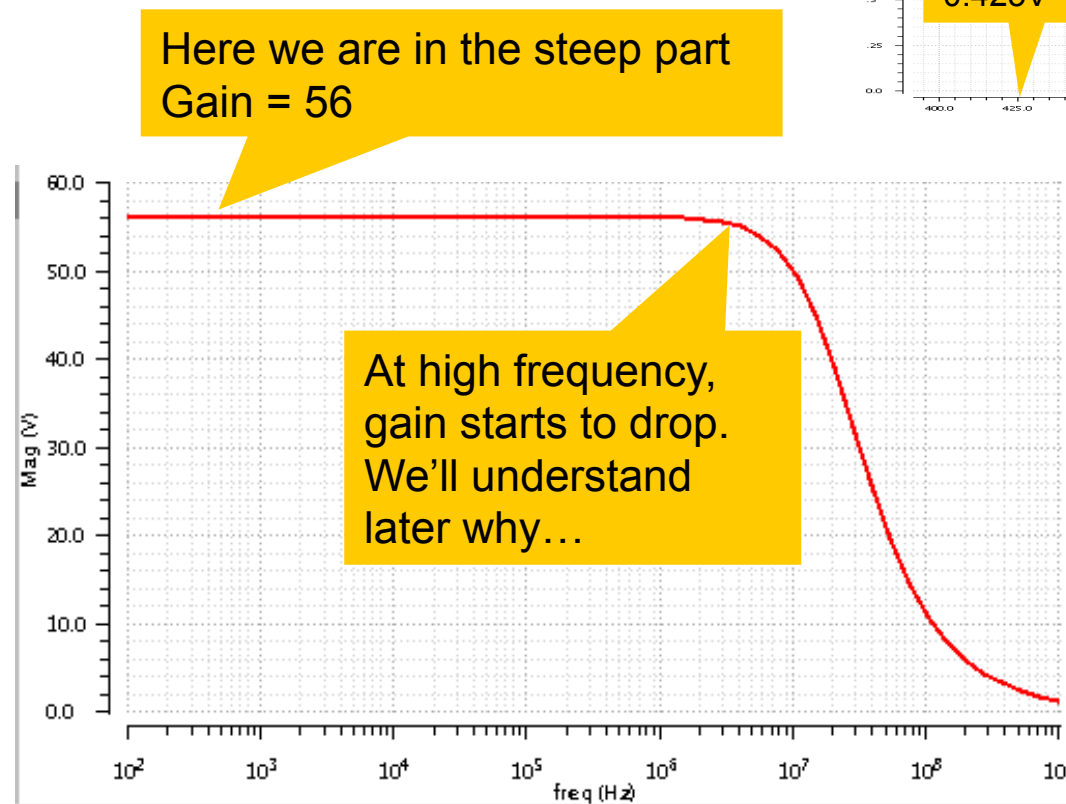
- Chose the DC potential of the input such that we are in the steep part (here: 0.45V):





Change of Operation Point

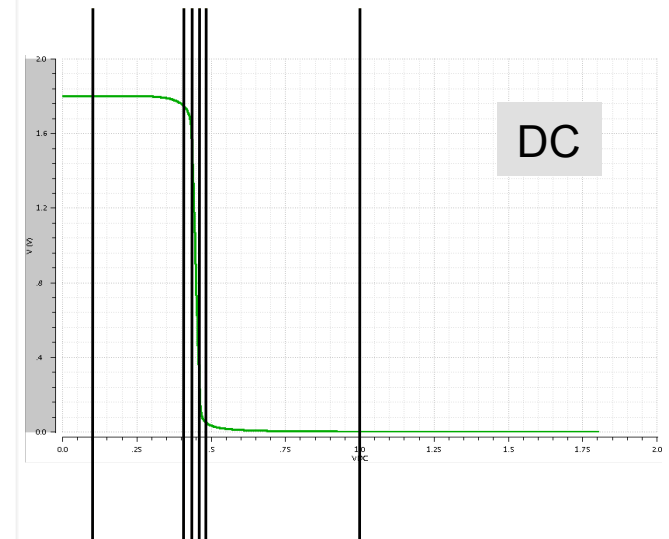
- It the DC potential of V_{IN} is changed, we move to different points of the transfer curve:





Gain vs. V_{IN}

 
- Can be obtained by taking derivative of transfer curve





Gain at Different bias Currents

 
- Position of 'maximal gain' *depends on bias current*
- Max. gain is lower for high current





Biasing the Gain Stage

 - In practice (& in simulation), V_{GS} and I_0 must 'correspond'
- This can be achieved (for instance) by a 'diode' connection of the MOS
- In simulation: To *let signals pass through*, the connection is done with a very large resistor and the input signal is ac coupled with an 'infinite' capacitor.




- In practice, other methods can be used...



Another View on the Bias Problem

 
- The resistor forces $V_{out} = V_{in}$
- The operation point is the crossing between the *diagonal* and the *transfer characteristic*
- This is usually a good point (maybe a bit low...)
- This works 'automatically' for changing bias & geometry





Adding a Capacitive Load – ‘The Speed’

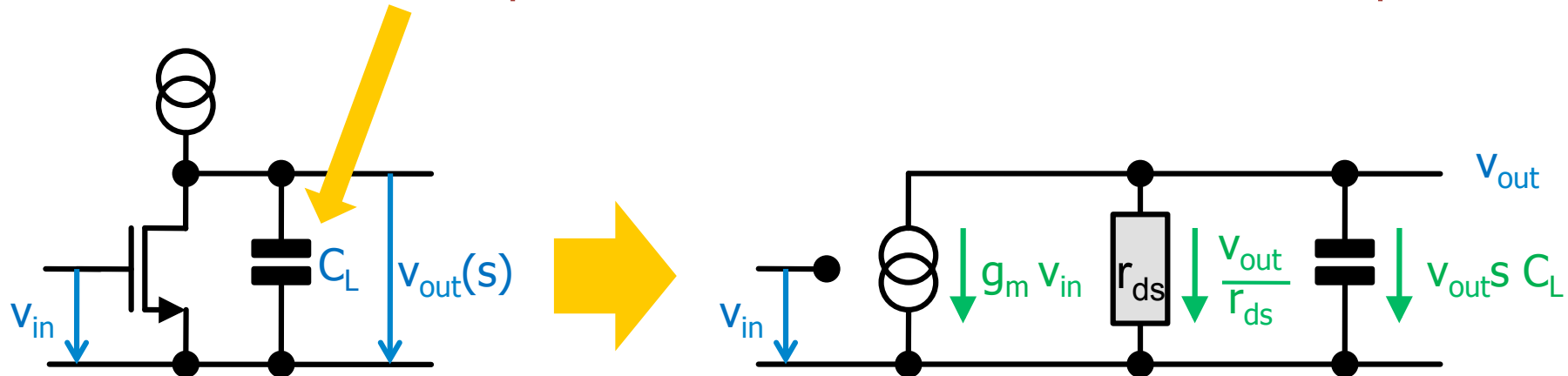- With a capacitive load, we have another current path:



- Current sum at output node = 0:

$$0 = g_m v_{in} + v_{out} / r_{ds} + s C_L v_{out}$$


$$v(s) = - \frac{g_m r_{ds}}{1 + s r_{ds} C_L}$$

DC gain (as before)

Low pass behavior
Corner at $1/(r_{ds} C_L)$



Bode Plot of the Gain Stage

 



Remember: Gain-Bandwidth-Product


$$GBW = \frac{g_m}{C_L}$$

$$v = - \frac{g_m r_{ds}}{1 + s r_{ds} C_L}$$



Bode Plot for two current

 - Increasing I_D
 - increases g_m and thus GBW
 - decreases r_{ds} and thus dc gain





Increasing the gain


- The gain of a single MOS is $v = g_m r_{ds}$.
- $g_m \sim \text{sqrt}[2 K I_D W/L]$ (strong inversion)
- $r_{ds} \sim L / I_D$

	$I_D \rightarrow 2 I_D$ (strong inv.)	$I_D \rightarrow 2 I_D$ (weak inv.)	$I_D \rightarrow 2 I_D$ (vel. sat.)	$W \rightarrow 2 W$ (s.i.)	$L \rightarrow 2 L$ (s.i.)
g_m	$\rightarrow \sqrt{2} g_m$	$\rightarrow 2 g_m$	$\rightarrow g_m$	$\rightarrow \sqrt{2} g_m$	$\rightarrow g_m / \sqrt{2}$
r_{ds}	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds}$	$\rightarrow 2 r_{ds}$
v	$\rightarrow v / \sqrt{2}$	$\rightarrow v$	$\rightarrow v / 2$	$\rightarrow \sqrt{2} v$	$\rightarrow \sqrt{2} v$

- We see:
 - gain is *increased* by *larger* W or L and by *smaller* I_D
 - *gain-bandwidth* only depends on g_m , i.e. mainly on I_D



How about a Resistive Load?

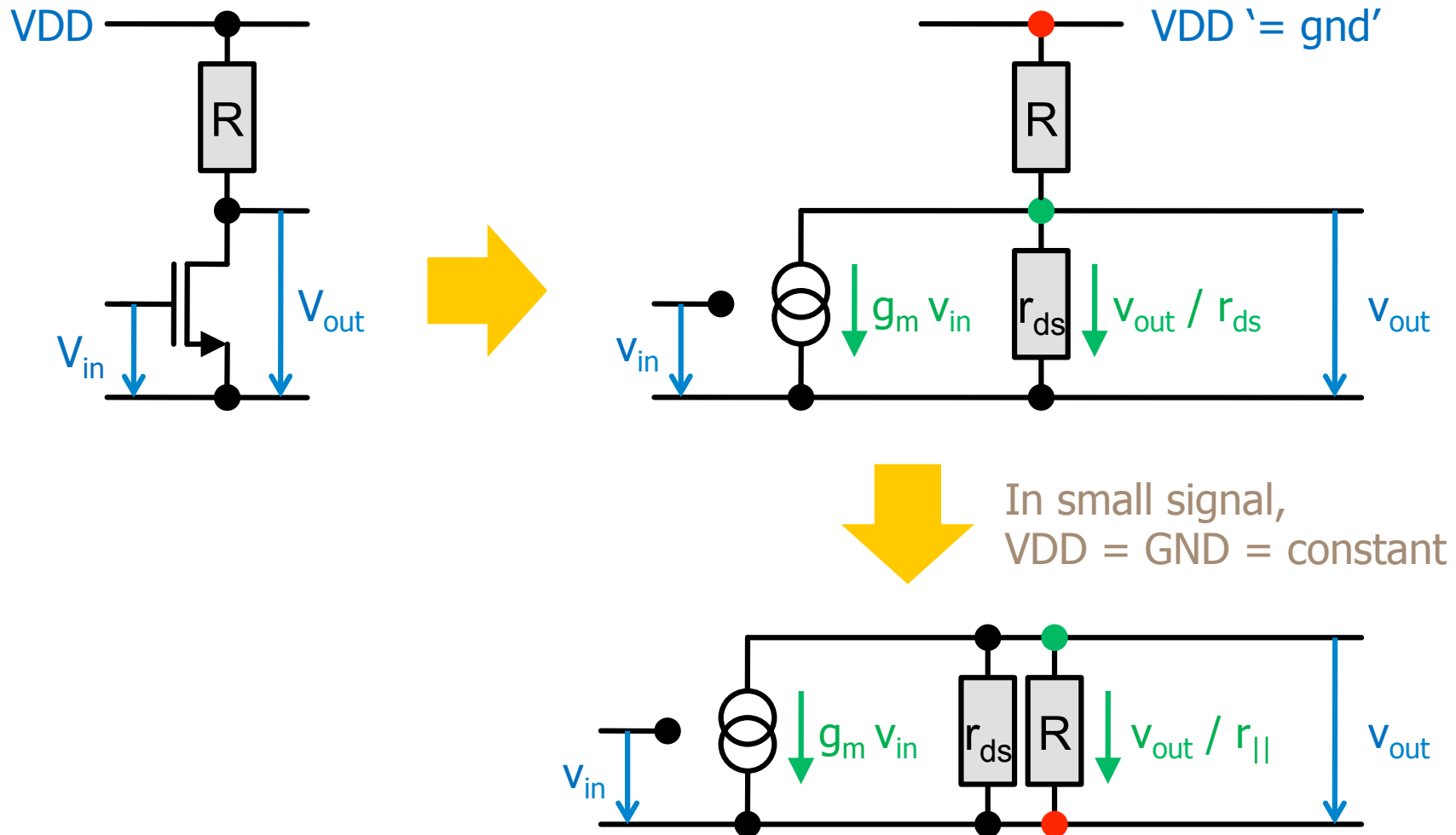


→ R and r_{ds} act in parallel: $v = -g_m \times (r_{ds} \parallel R)$



Non-Ideal (PMOS) current source

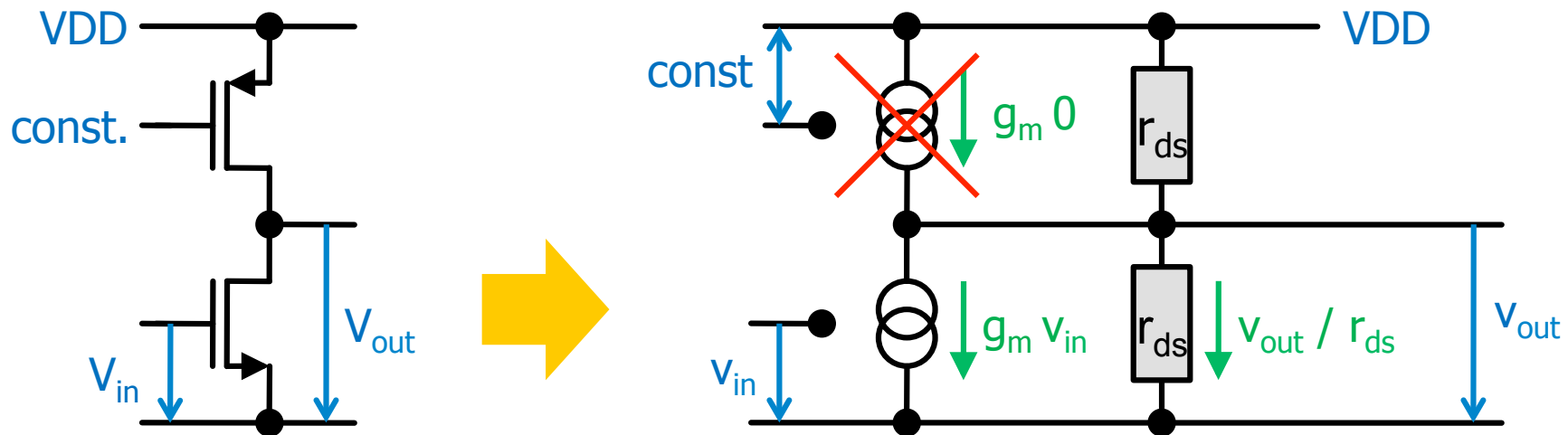- When a PMOS is used as current source, it ALSO has an output resistance.




- The transconductance part of the PMOS is off ($v_{gs} = 0$)
- The PMOS behaves just like a pure resistor (but r_{ds} is usually higher when in saturation)



CMOS Inverter

- Now consider a CMOS inverter:

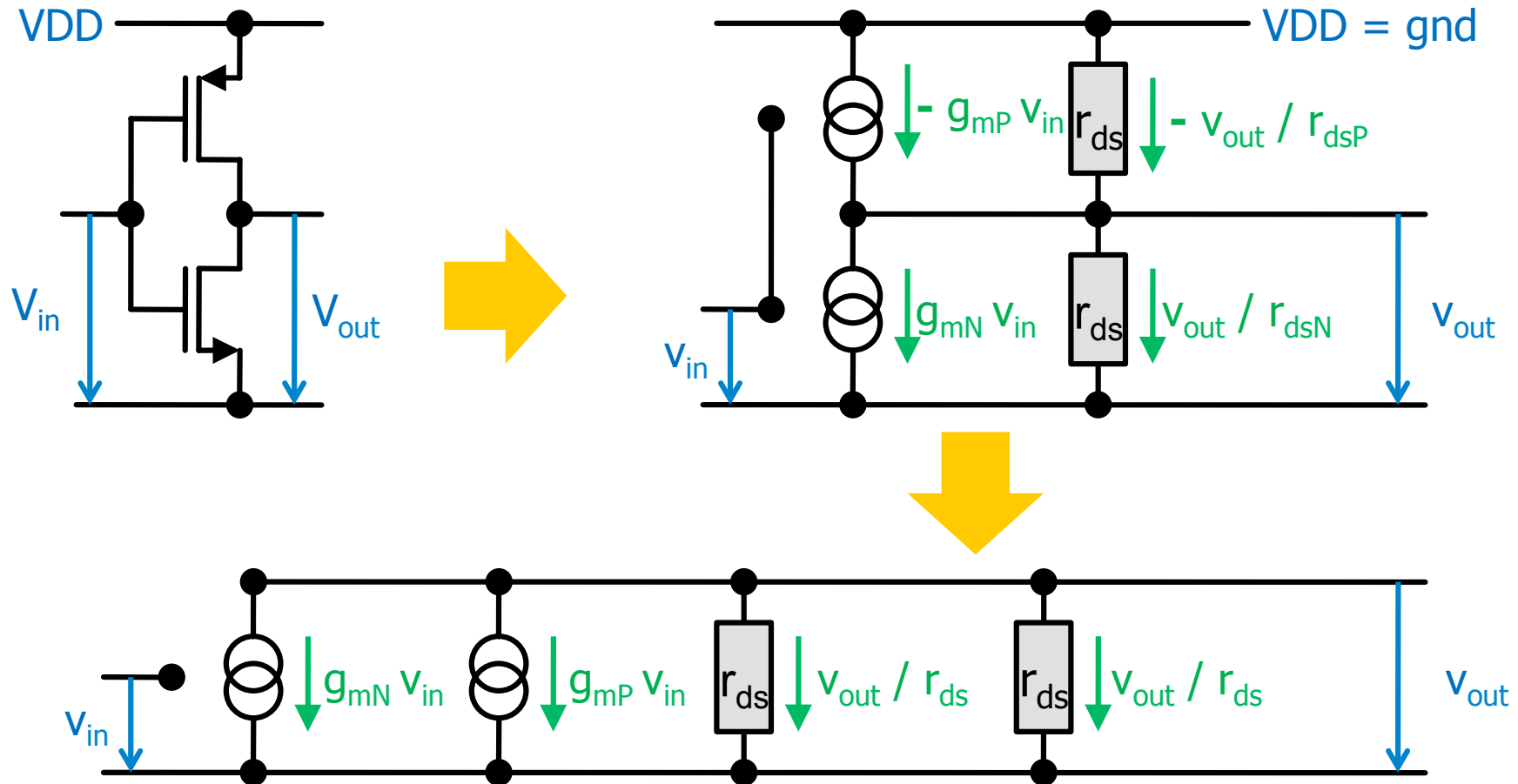


- g_m and r_{ds} of both MOS are in **parallel**

$$v = - (g_{mN} + g_{mP}) \times (r_{dsN} \parallel r_{dsP})$$




Reminder: Transistor Characteristics

 




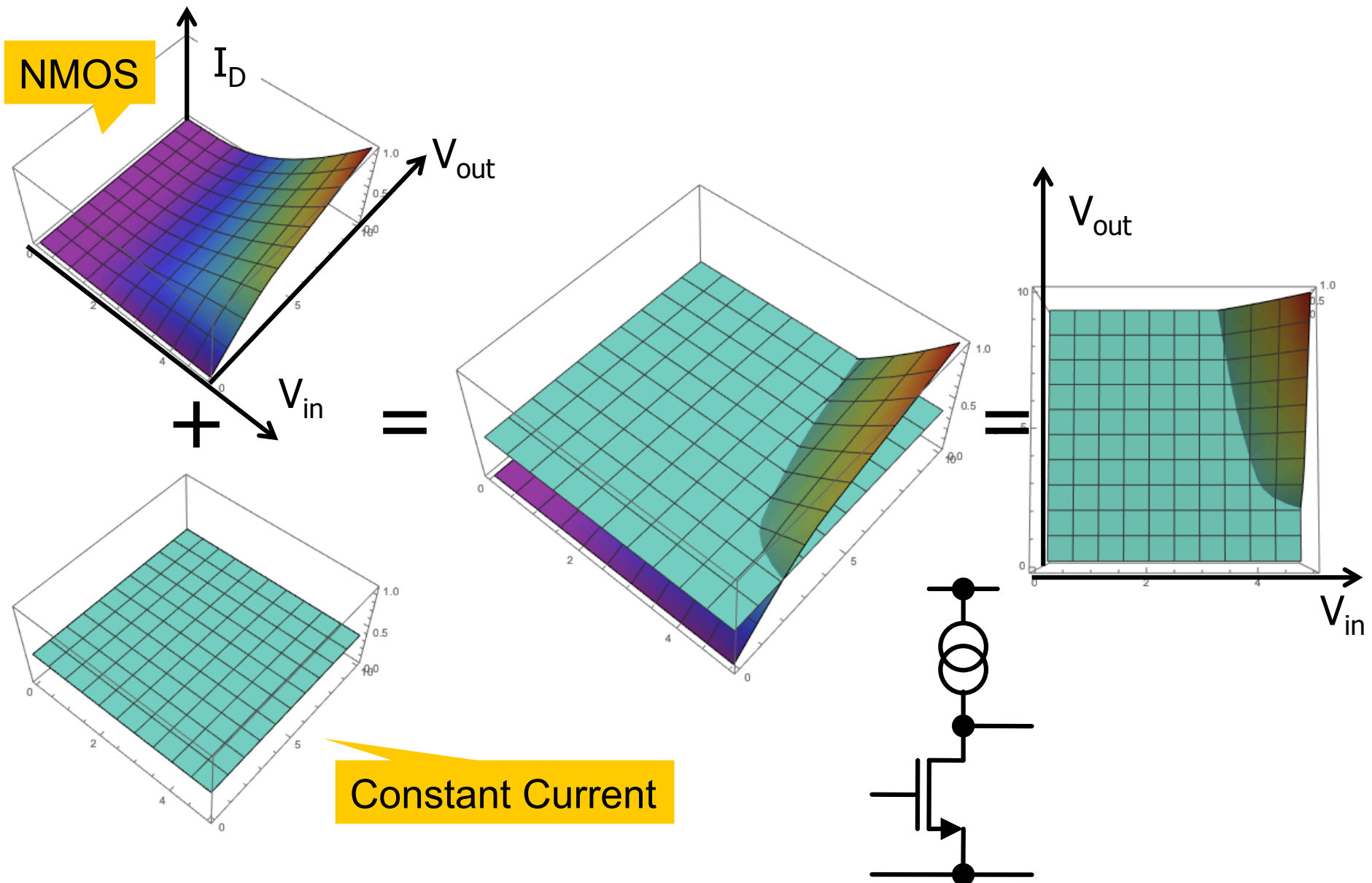Visualization of Transfer Function: I-Load










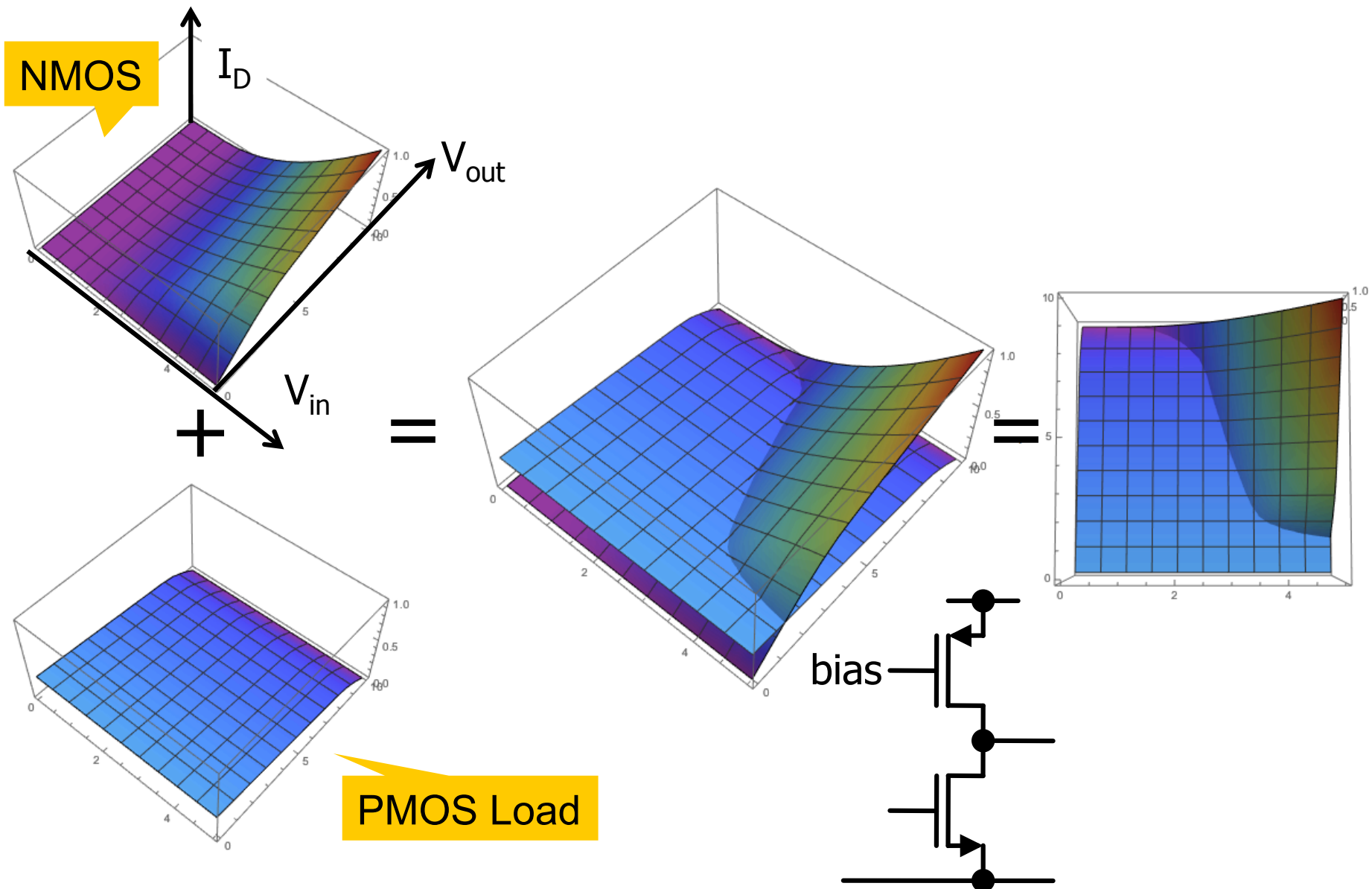Visualization of Transfer Function: PMOS Load







Load = Diode Connected (N)MOS

     






Visualization of Transfer Function: Inverter

NMOS

  



Active PMOS

   



Visualization of Inverter Transfer


■ $I_D(V_{gs}, V_{ds})$

  



How to get very high gain ?

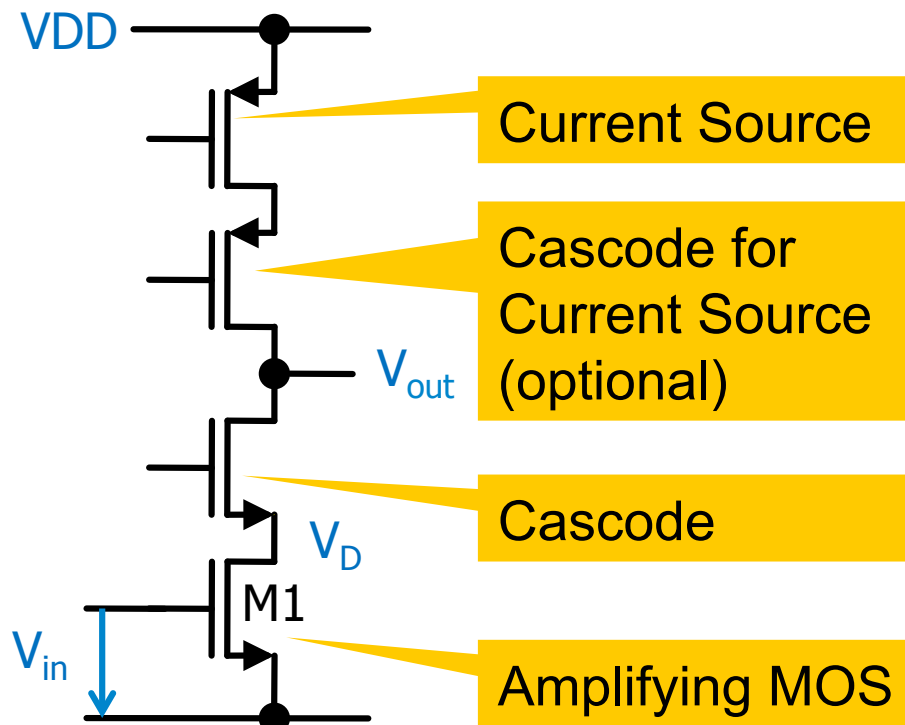- g_m is very much limited by the current
- r_{ds} can be increased by a cascode
- 'Straight' cascode gain stage:



Defines Current

Increase output Resistance of PMOS


Fix V_D so that changes In V_{out} do not lead to current change in M1

Convert input voltage change to current change



Small Signal Analysis

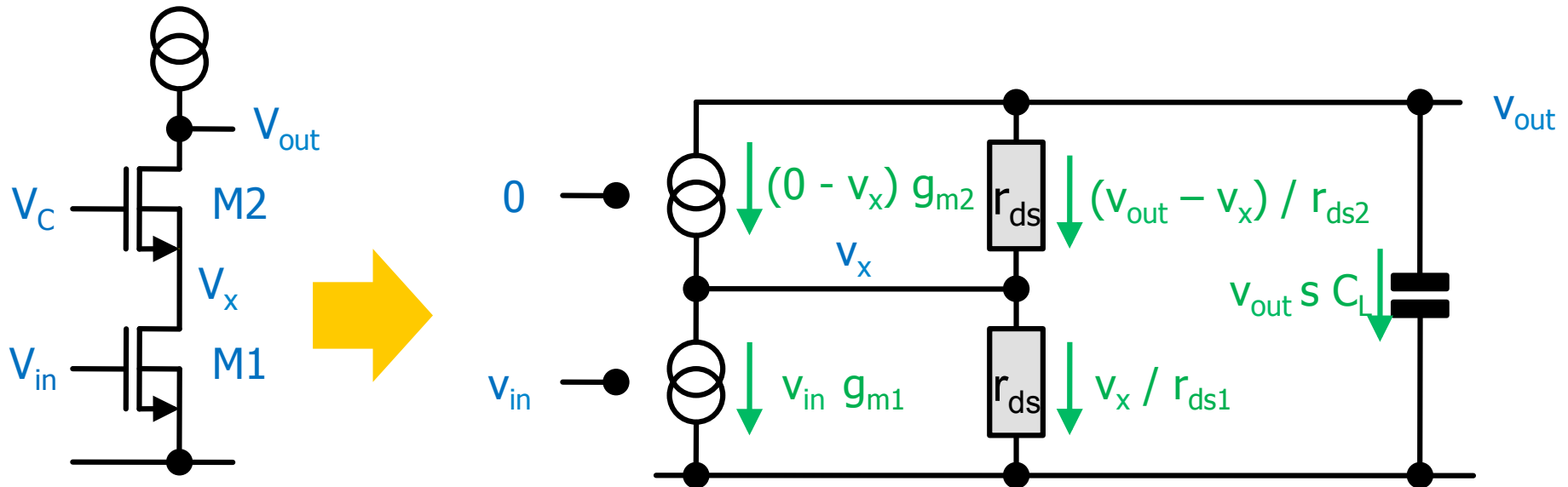- Assume bulks are connected to sources (no substrate effect)
 - Not always true in reality when NMOS are used...



- EQ1 (current sum at node v_{out}):

$$-v_x g_{m2} + (v_{out} - v_x) / r_{ds2} + v_{out} s C_L = 0$$
- EQ2 (current sum at node v_x):

$$-v_x g_{m2} + (v_{out} - v_x) / r_{ds2} = v_{in} g_{m1} + v_x / r_{ds1}$$




Solution

- $H(s) = - \frac{g_{m1} r_{ds1} (1 + g_{m2} r_{ds2})}{1 + C_L (r_{ds1} + r_{ds2} + g_{m2} r_{ds1} r_{ds2}) s}$
- As usually $g_m r_{ds} \gg 1$, the parenthesis can be simplified:
- $H(s) \sim - \frac{g_{m1} r_{ds1} g_{m2} r_{ds2}}{1 + C_L g_{m2} r_{ds1} r_{ds2} s}$ (= single pole low pass)
- The *DC gain* is $|H(0)| = g_{m1} r_{ds1} \times g_{m2} r_{ds2}$
(i.e. *squared* wrt. a simple gain stage!)
- The bandwidth is $BW = (C_L r_{ds1} \times g_{m2} r_{ds2})^{-1}$
(decreased by same factor)
- The unity gain bandwidth is $GBW = BW \times |H(0)| = g_{m1}/C_L$
(**same** as simple stage!)



Comparing Simple / Cascoded Gain Stage

 
- DC gain is increased by the 'gain' $g_m \times r_{ds}$ of the cascode
 - the cascode 'boosts' the output resistance
- The GBW remains unchanged
 - the current generated in M1 must charge C_L . The cascode does not help here...





How to get EVEN higher gain ?

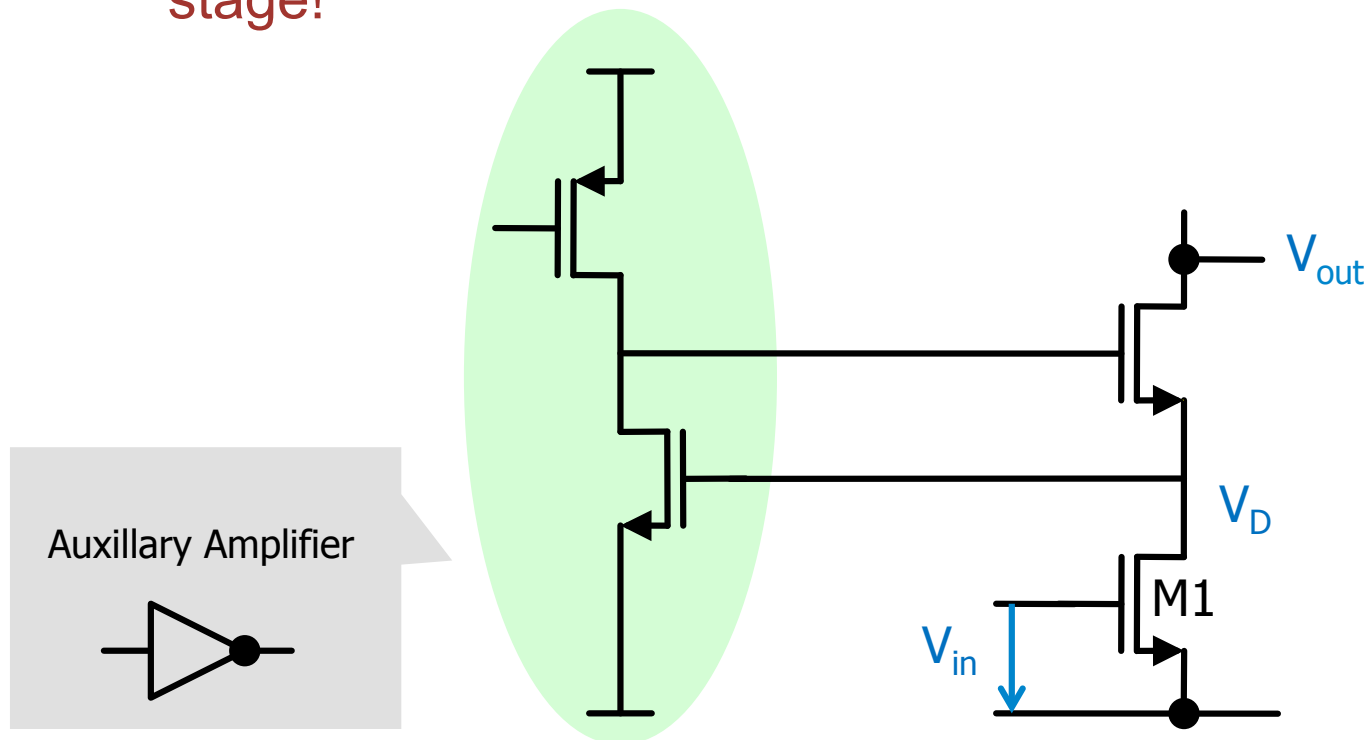
- Just like we have done in the 'regulated' mirror, we can use an amplifier to keep the drain of the amplifying MOS at constant potential.
- For the amplifier, we use (again) a simple gain stage...
- With this method, a gain of 10.000 can be reached in one stage!





C_{GD} : Introducing a 'Zero' (Advanced Topic)

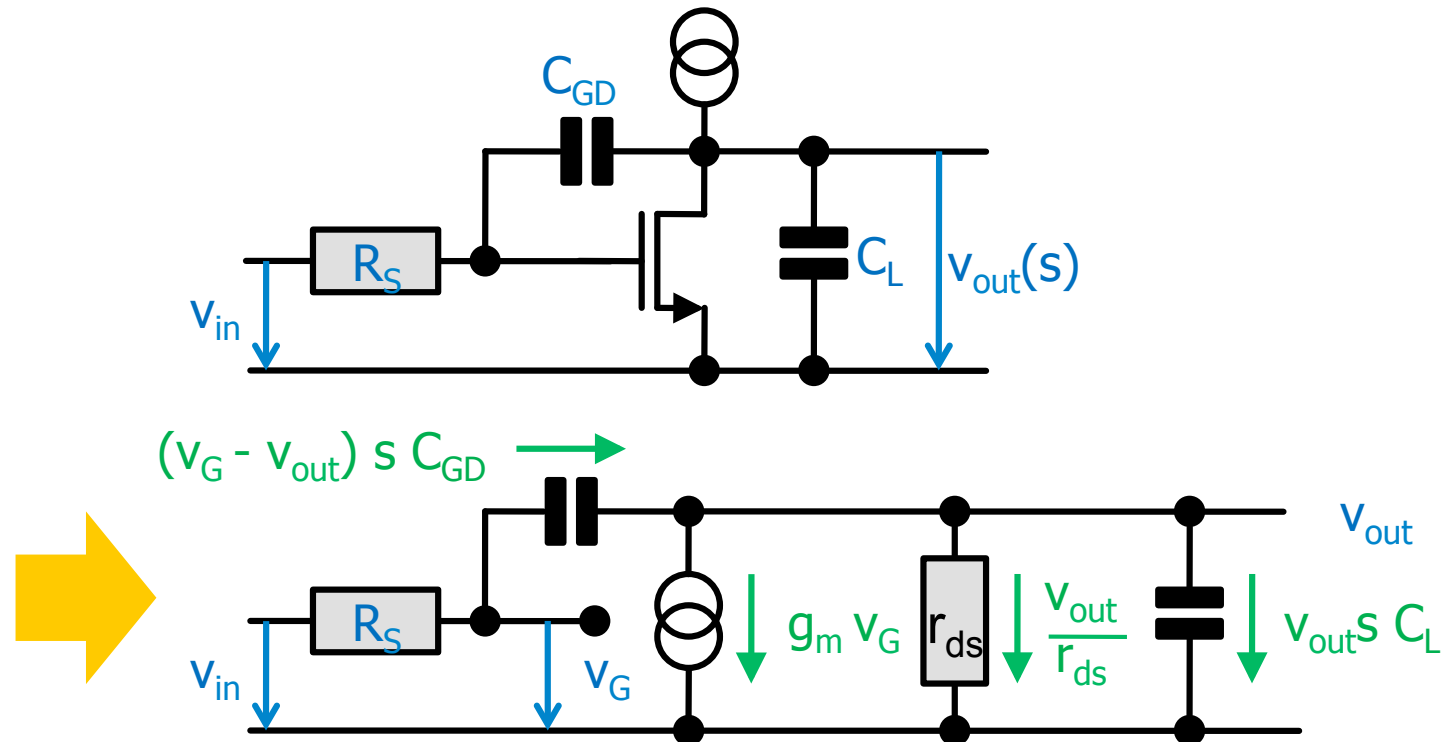- Consider the effect of the gate-drain capacitance C_{GD}
 - Assume a finite driving impedance of the source R_S :




$$H(s) = \frac{-g_m r_{ds} + C_{GD} r_{ds} s}{1 + C_L r_{ds} s + C_{GD} s (r_{ds} + R_S + g_m r_{ds} R_S + C_L r_{ds} R_S s)}$$



New: We get a Zero - What Happens?

 - We have $H(0) = -g_m r_{ds}$ as before.
- For $R_S=0$
 - The input signal propagates directly to the output via C_{GD} .
 - This same phase signal competes with the inverted signal through the MOS.
 - For very large frequencies, C_{GD} 'wins'.
 - We therefore have zero gain at some point
 - At high frequencies, we have a capacitive divider with gain < 1






Miller Effect: C_{GD} is bad

- The input impedance of the circuit at DC ($s=0$) is

$$\frac{1}{C_{GD} (1 + g_m r_{ds}) R_S}$$

 (in addition to C_{GS} , which we have omitted)





- The Gate-Source cap C_{GD} is **AMPLIFIED** by the gain of the stage.
- This surprising property occurs because the right side of C_{GD} sees a large signal of inverted polarity.
- This general effect is called the **MILLER-EFFECT**
- Due to this effect, the small C_{GD} can play an important role.



Check your Understanding:

 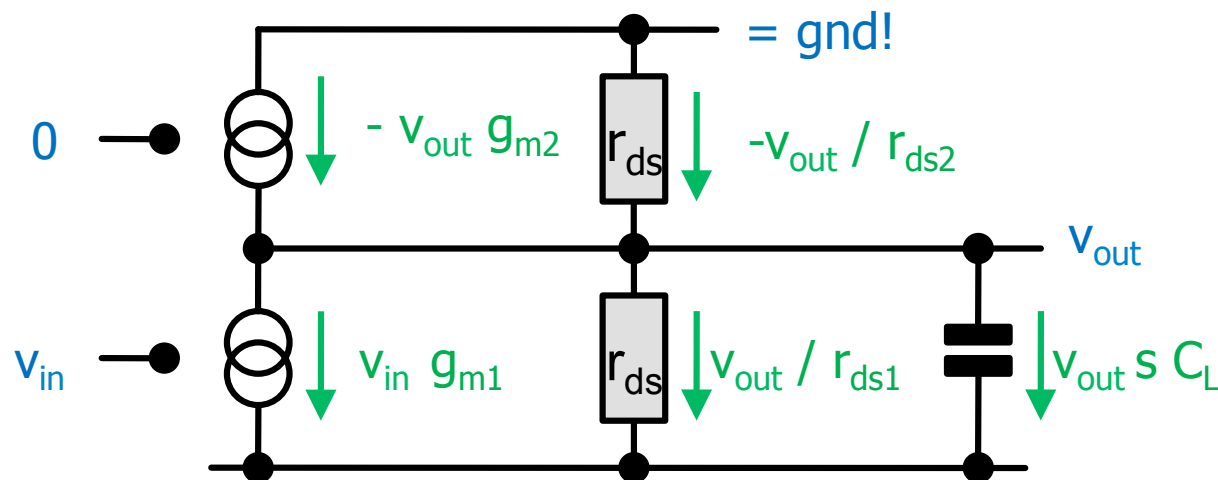- What is $H(s)$ of a gain stage with a (NMOS) diode load:




- $$H(0) = - \frac{g_{m1} r_{ds1} r_{ds2}}{r_{ds1} + r_{ds2} + g_{m2} r_{ds1} r_{ds2}} \sim - \frac{g_{m1}}{g_{m2}}$$

- In strong inversion, this is the square root of the W -ratio
 - For instance: for $W_2 / W_1 = 4$, the gain is ~ 2 .



Increasing gain further

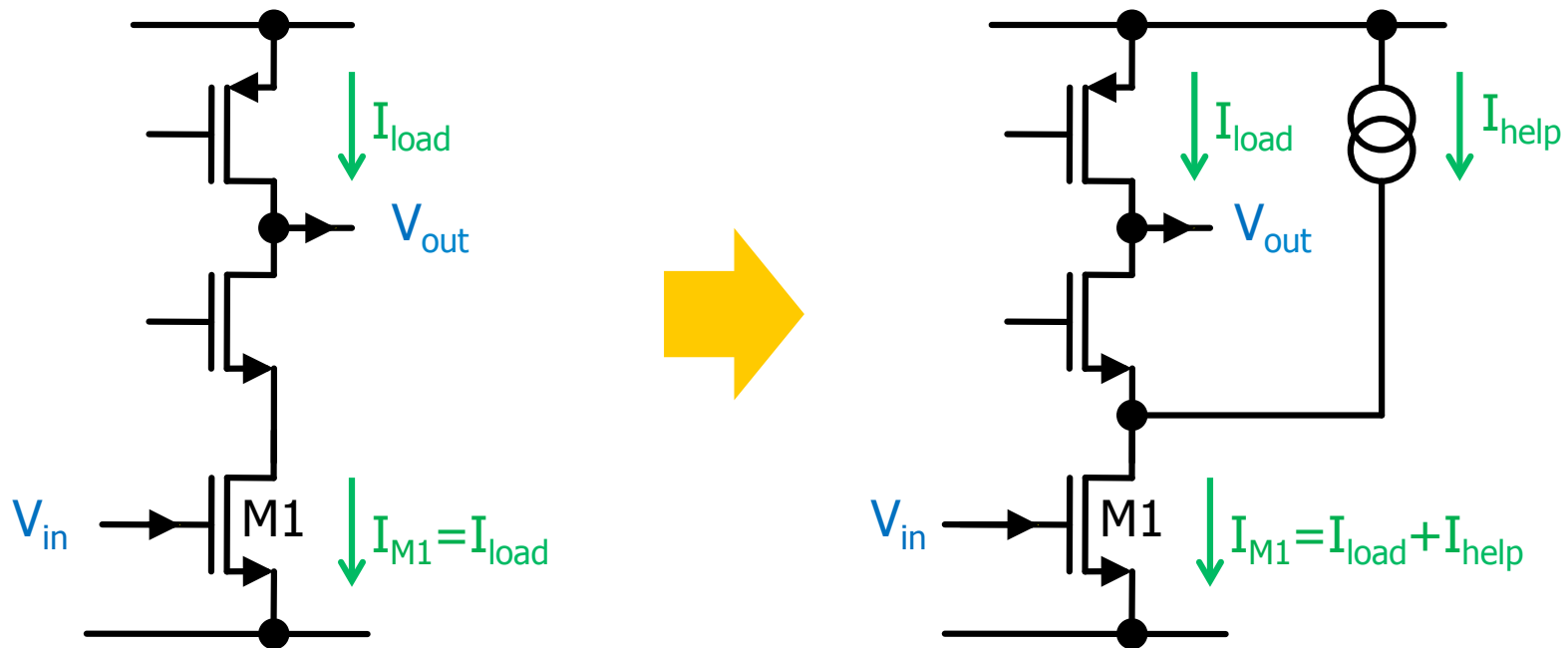
- The gain is limited by the output conductance of the load
 - That is proportional to the current in the load
- Can we *reduce* the current in the *load*, keeping the current in the amplifying MOS M1 unchanged (for g_m)?
- Yes: Add an extra current to M1 at the cascode node:





For Experts: The 'folded' cascode

 - The 'straight' cascode has some drawbacks
 - many MOS are stacked \rightarrow dynamic range suffers
 - DC feedback ($v_{out} = v_{in}$) is marginal as v_{out} cannot go very low
- Alternative: use a PMOS to cascode the input NMOS M1:
 - Quite surprising that this works....



- Current in output branch is smaller than in M1 $\rightarrow r_{out}$ is higher
- Note: It may *look* like this topology has non-inverting gain...




THE CURRENT MIRROR - AGAIN



Active Regulation of the Drain Voltage

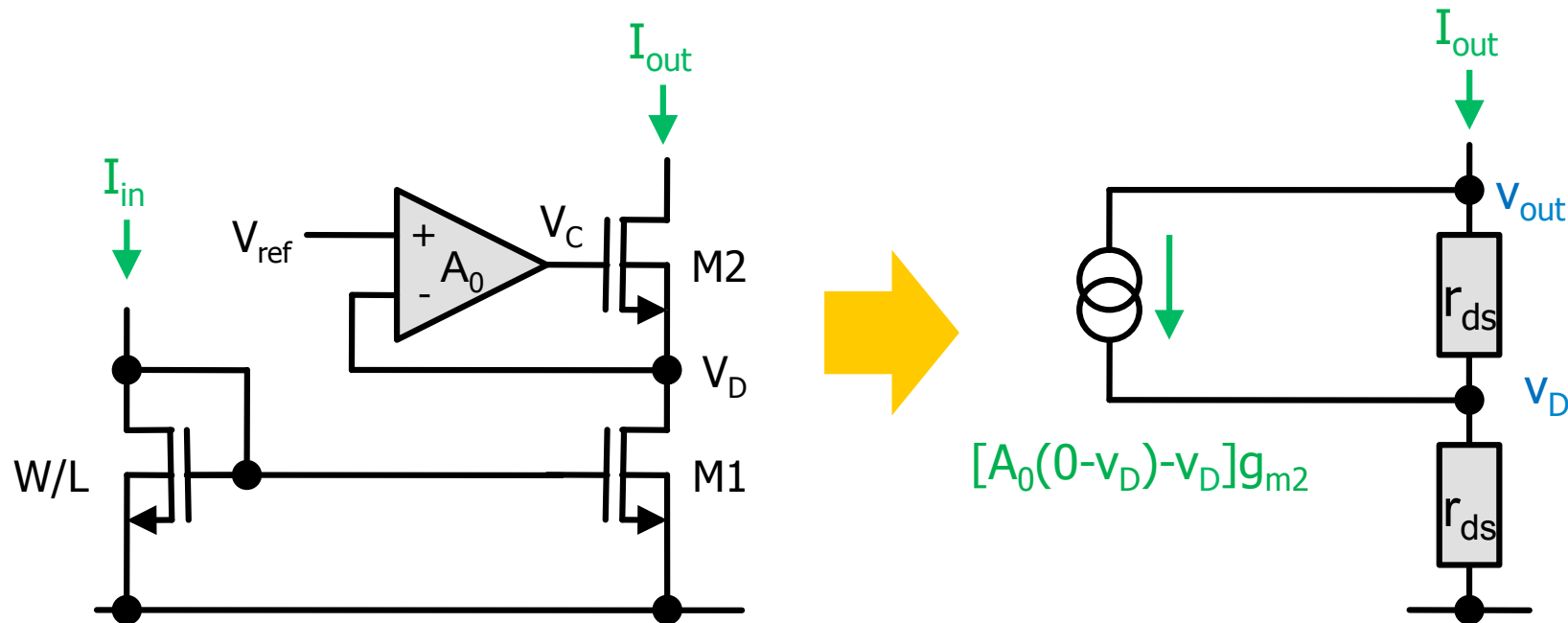- The following circuit uses an amplifier with gain A_0 to keep V_D constant:
 - V_D is compared to a (fixed) reference V_{ref} .
 - $V_C = A_0 (V_{ref} - V_D)$
- For better *matching*, the input must be cascoded as well..




$$r_{out} = r_{ds2} + r_{ds1} (1 + (1 + A_0) g_{m2} r_{ds2})$$



Practical Realization

 - The amplifier can just be a gain stage...
- This gives the 'regulated current mirror':



- Here, $A_0 \sim g_{m3} r_{ds3}$, Therefore $r_{out} \sim r_{ds1} \times g_{m2} r_{ds2} \times g_{m3} r_{ds3}$
- Note:
 - V_{DS} of M1 is $\sim V_{TN}$, which is higher than needed (wasting dyn.). (Using M3 with lower threshold helps)
 - Matching is *not* good, because $V_{DS0} \neq V_{DS1}$




THE SOURCE FOLLOWER



The Source Follower (Common Drain Stage)

- Current source I_0 pulls a constant current through the MOS
- This fixes V_{GS} of M1 (to $V_T + \text{Sqrt}(\dots)$)
- Therefore, $V_{in} - V_{out} = V_{GS} \sim \text{constant}$

 
$$V_{out} = V_{in} - \text{constant} \quad \rightarrow \quad V_{out} = V_{in}$$





Simulation

 - NMOS Source Follower with NMOS current source:






Real Source Follower (Here with substrate effect)

- In reality, must consider
 - r_{ds} of M1 and current source
 - body effect (sometimes)

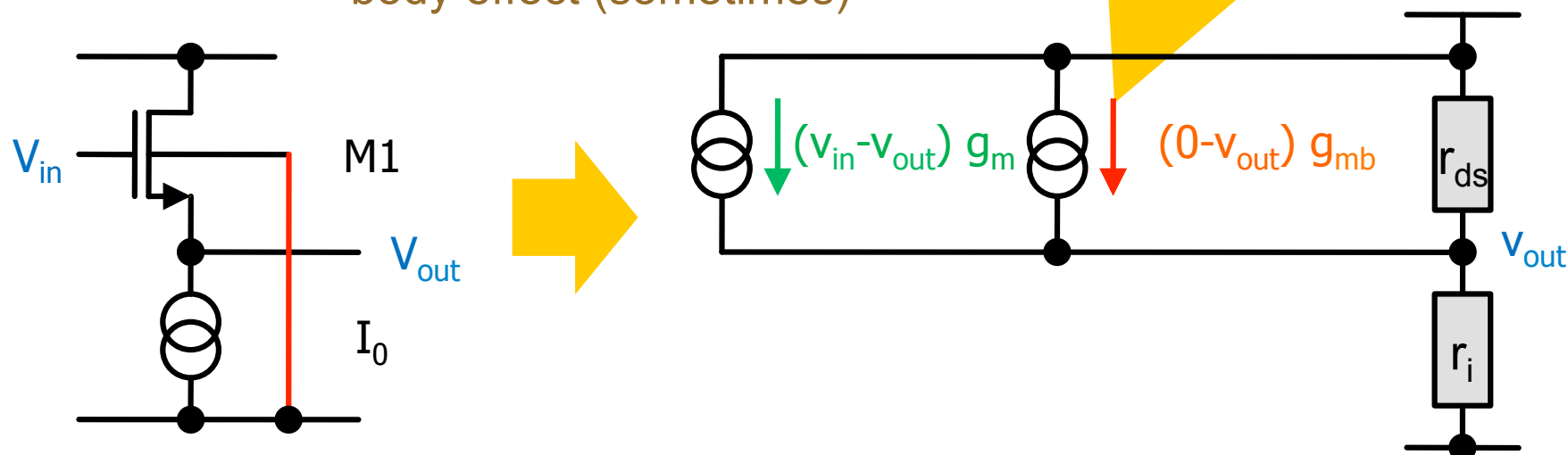body effect (only if body = ground):
 $i = v_{BS} g_{mb}$



$$\text{gain} = \frac{g_m r_{ds} r_i}{r_{ds} + r_i + g_m r_{ds} r_i + g_{mb} r_{ds} r_i} = \frac{g_m}{g_{ds} + g_i + g_m + g_{mb}} \sim \frac{g_m}{g_m + g_{mb}}$$


with $g_{ds} = 1 / r_{ds}$, $g_i = 1/r_i$ and $g_{ds} \ll g_m \dots$

- Gain is < 1 . With $g_{mb} = (n-1) g_m$, gain $\sim 1/n \sim 0.7$



Advanced: Source Follower with finite source imp.

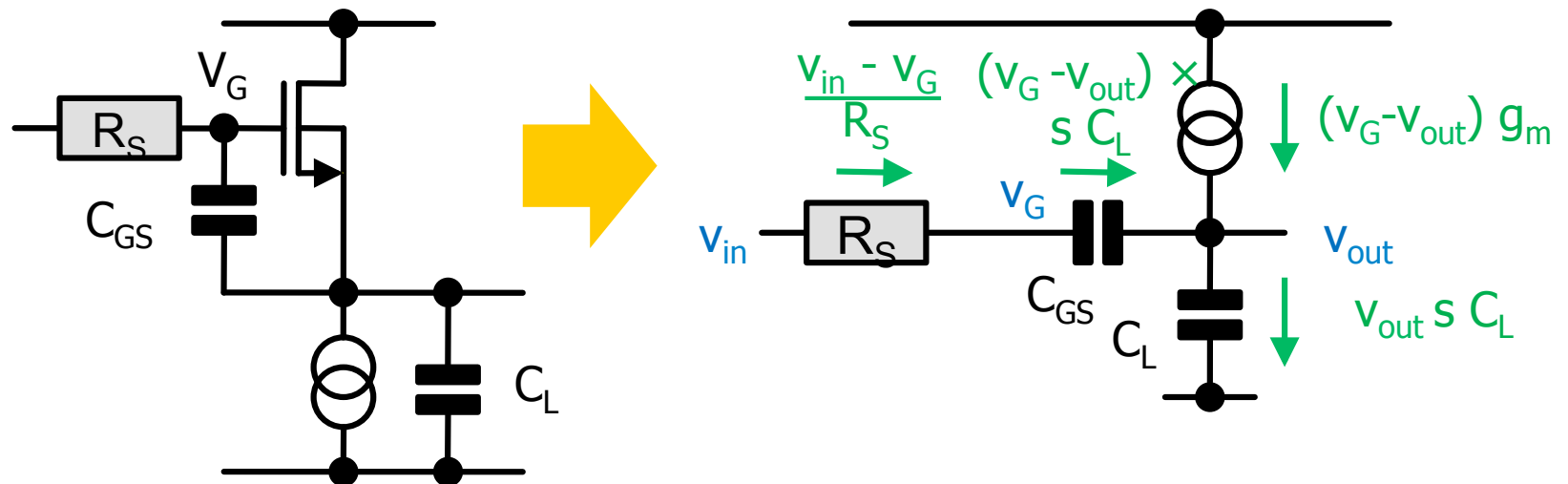- Study in more detail the case when the SF is driven by a 'high impedance' source (with output resistance R_S):
 - consider Gate-Source cap. C_{GS} and output cap. C_L
 - neglect output impedances and g_{mb} for simplicity...





- The transfer function has two poles:
$$\frac{g_m + C_{gs} s}{g_m + s(C_{gs} + C_L + C_{gs} C_L R_S s)}$$
- There is an *Overshoot* as soon as $R_S > \frac{(C_{gs} + C_L)^2}{4 C_{gs} C_L g_m}$



Simulation

  - $W/L = 1\mu/0.18\mu$, $C_L = 100\text{fF}$, $I_{\text{bias}} = 10\mu\text{A}$
- Transient and AC simulation:







THE DIFFERENTIAL PAIR



The (Differential) Pair

  - Very often, the *difference* of voltages must be amplified
- The basic circuit are two MOS with connected sources:




- How does it work?
 - Assume $V_+ > V_-$
 - $\rightarrow V_{GS}$ of the left MOS is larger than V_{GS} of the right MOS
 - $\rightarrow I_+ > I_-$
- $V_+ = V_- \rightarrow I_+ = I_- = I_0 / 2$
- $V_+ \gg V_- \rightarrow I_+ = I_0, I_- = 0$



The Differential Amplifier


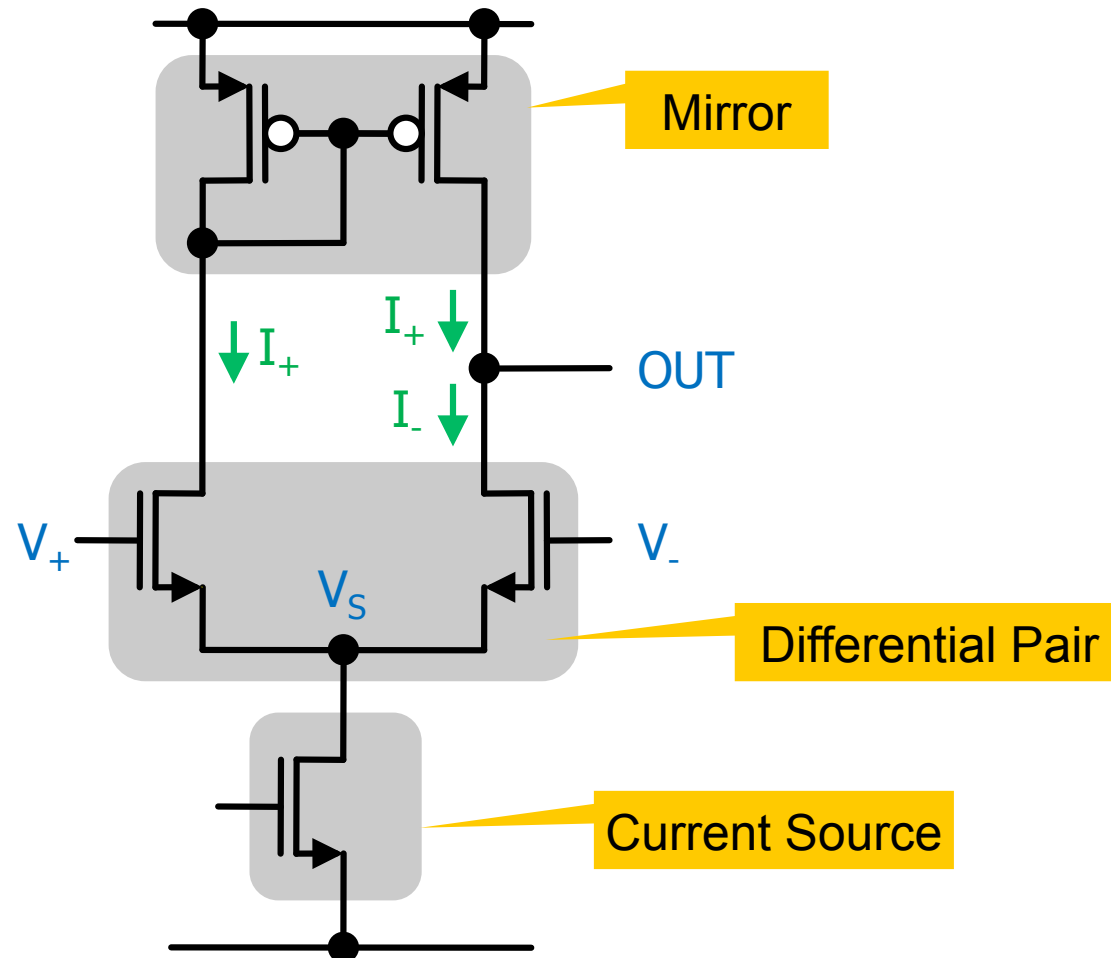
- One current is often mirrored and added to the other:





Output Current of the DiffAmp

  - If the output voltage is *fixed*, the current is just $I_+ - I_-$
- The circuit is a *Transconductor* (it converts $U \rightarrow I$)





This only works if the V_{OUT} is 'good'
? What does this mean ?



Output Voltage of the DiffAmp

  - If the *no current* flows out of the circuit and the output voltage is left free, we have *voltage gain*





Output cannot
go lower than
 $V_S \sim V_+ - V_T$



Simulation


■ $V_N = 1.2V$

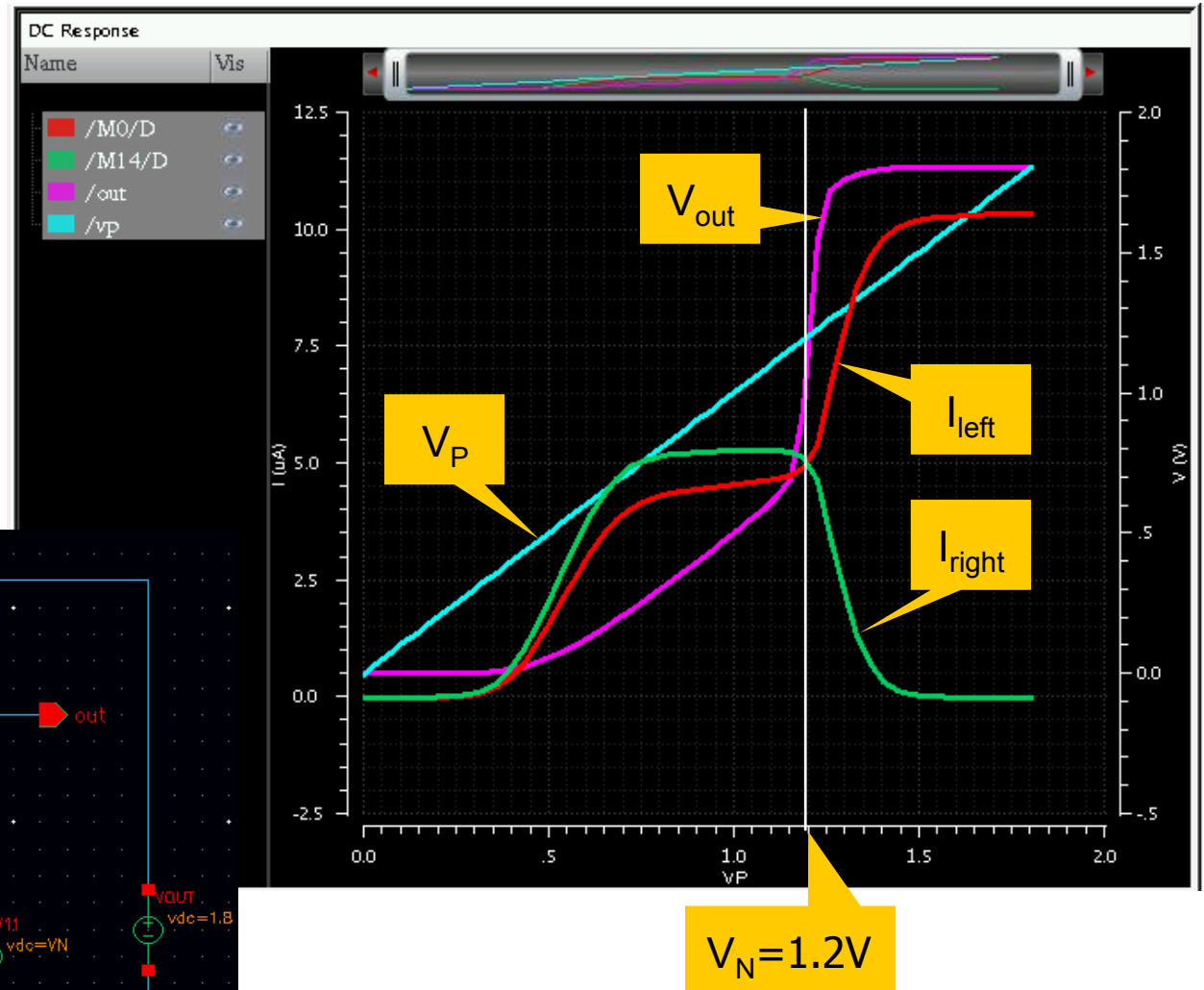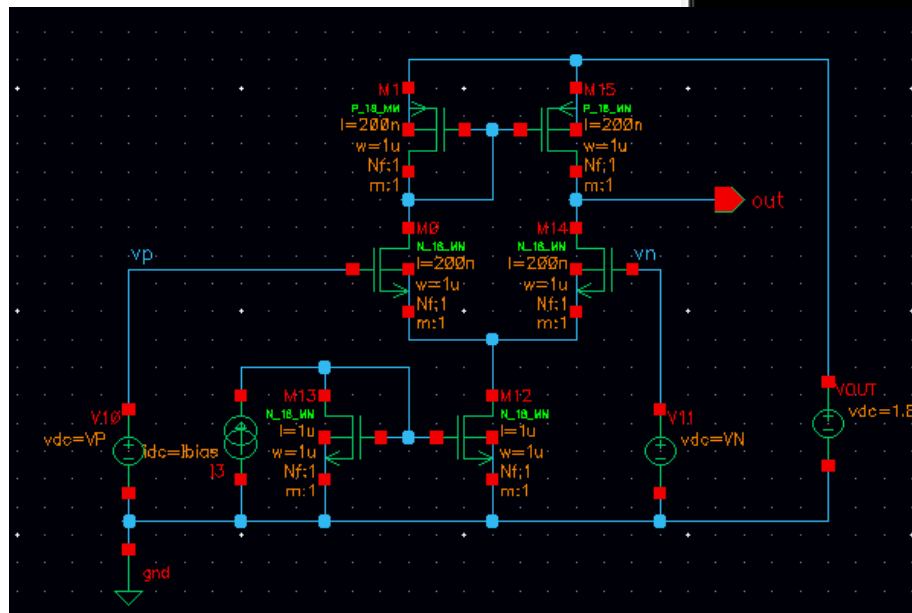



Sweeping V_-

- $V_- = 0.2, 0.4, \dots 1.6 \text{ V}$

 




Comments

- Understanding the large signal behaviour for very different V_p, V_n is important, but in practical circuits, feedback is often applied so that $V_p = V_n$.
- Another important property is the *common mode input range*. This is limited by the V_{GS} of the input pair and the compliance of the tail current source: An *NMOS* differential pair *does not work* any more at *low* (common mode) input voltage.
- If the amplifier is loaded with a resistive load, gain drops. Therefore a source follower is often added.
 - Stability in feedback circuits is then more trick. Compensation methods are needed.



Diff-Amp with Gain Stage

 
- The differential amplifier is often followed by a gain stage
 - This two-stage design has two ,main' poles and may need compensation in feedback circuits





Differential Pair + Current Mirror

 - The problem of limited output voltage swing for high input common mode can be solved by mirroring the currents:





SUMMARY



Summary Circuits

- Most important topologies are
 - Current mirror
 - Gain stage
 - Cascode
 - Source Follower
 - Differential Pair
- Their properties depend on
 - Transistor sizes
 - Currents
 - Bias Points
- Better performance can be achieved by extending the topologies
 - Cascodes
 - Current mirrors
 - ...



Summary Circuits

- Circuits must be brought to the correct operation point
- MOS are mostly operated in saturation
 - To gain dynamic range, operate 'just at the edge of saturation'
- Small signal models give 'quick' insight in the ac behaviour
 - They can be used to understand & optimize circuits
- AC analysis gives more insight in the effect of parameter variations on gain, bandwidth, stability
- Transient Analysis checks the large signal behaviour



Summary Circuits

- (DC) Gain can be modified by tricks
- Gain-Bandwidth is fundamentally limited by g_m and C_{load}



Exam Topics

- Basic components, parallel, serial connection, Thevenin
- Transfer functions, Bode Plot, Phase shift
- Diode characteristic, capacitance
- MOS in linear and saturated operation, ideal strong inversion, g_m , r_{ds} , dependence on geometry & current
- Small signal model
- Current mirror, ratio, output conductance, matching. Also with PMOS!
- Cascode in mirror, benefit, biasing, minimum output voltage
- Gain stage (also with PMOS) with different loads, gain, bandwidth, GBW
- Cascoding of gain stage
- Source Follower (NMOS / PMOS)
- Differential pair