



Exercise 1: Thévenin Equivalent & RC-Circuits

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg





Recommendations

- I strongly recommend to use a mathematical program (Mathematica, Maple, SageMath,..) to solve the exercises
- For transfer functions, inspect each result:
 - What happens for $\omega \rightarrow 0, \infty$?
 - What happens if component values go to 0 or ∞ ?




Exercise 1.0

- Derive the expressions for the series and parallel connection of capacitors using
 - Charge conservation
 - Complex impedance & Kirchhoff's law

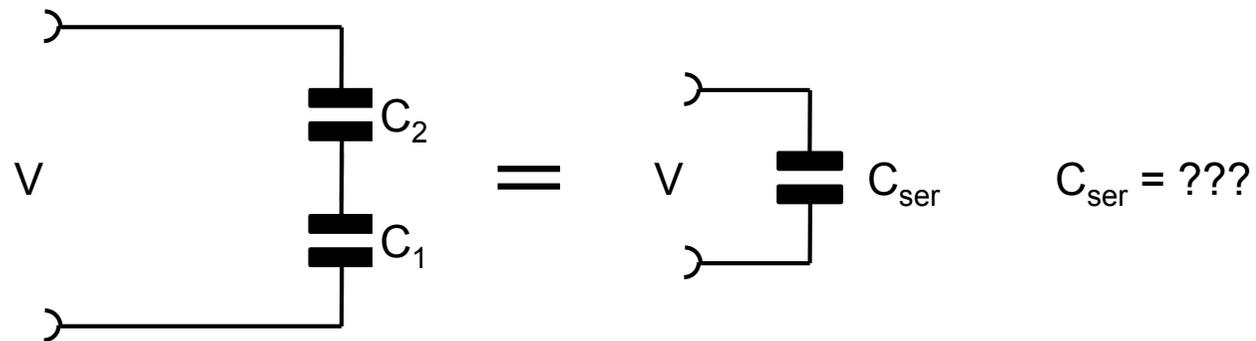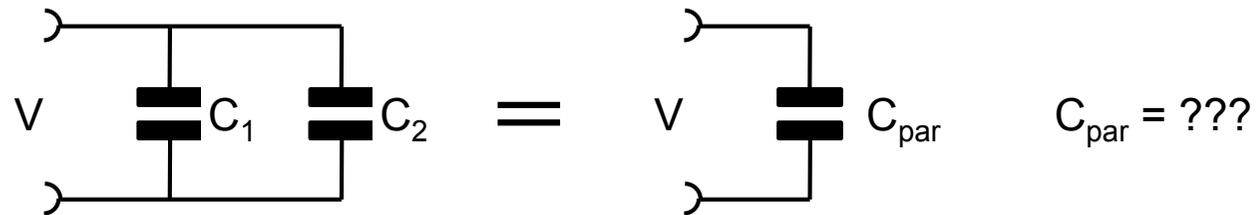



Solution 1.0

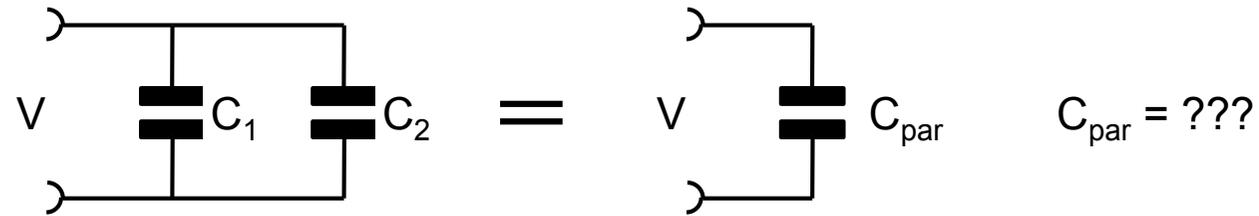

1. Charge conservation:


$$V \times C_1 + V \times C_2 = Q_1 + Q_2 = Q_{\text{par}} = V \times C_{\text{par}} \rightarrow C_1 + C_2 = C_{\text{par}}$$

2. Kirchhoff & complex impedance:

$$V sC_1 + V sC_2 = i_1 + i_2 = i_{\text{par}} = V sC_{\text{par}} \rightarrow C_1 + C_2 = C_{\text{par}}$$



Solution 1.0

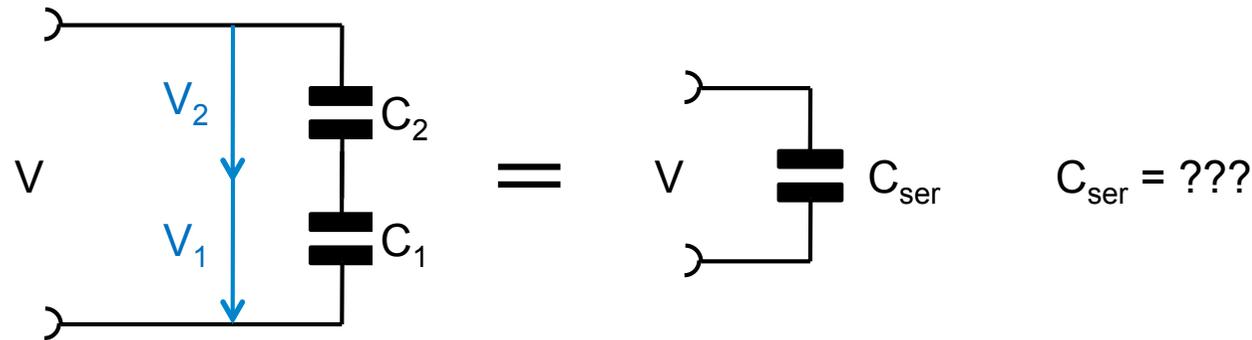

1. Charge conservation:

Note: no charge can 'escape' the middle node, so that $Q_1 = Q_2 = Q_{\text{ser}}$

$$V = V_1 + V_2 = Q_1/C_1 + Q_2/C_2 = Q/C_1 + Q/C_2 = Q/C_{\text{ser}}$$

$$\rightarrow 1/C_1 + 1/C_2 = 1/C_{\text{ser}}$$

2. Kirchhoff & complex impedance:

$$V_1 sC_1 = V_2 sC_2 \quad \text{and} \quad V_1 + V_2 = V \quad \rightarrow \quad V_1 = V C_2 / (C_1 + C_2)$$


$$\rightarrow i_1 = V_1 sC_1 = V s C_1 C_2 / (C_1 + C_2)$$

$$\rightarrow C_{\text{ser}} = i / (Vs) = i_1 / (Vs) = C_1 C_2 / (C_1 + C_2)$$



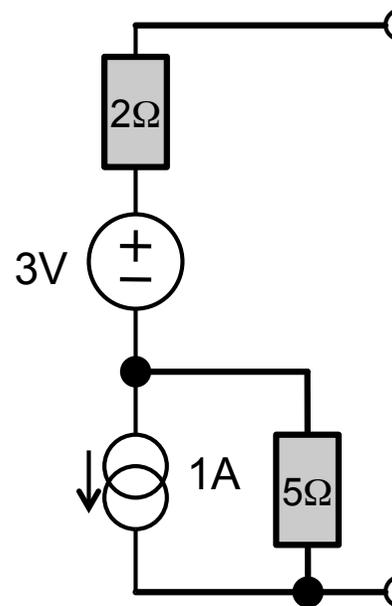Exercise 1.1

- Derive the Thévenin Equivalent for the following circuit:





- Try two different methods:
 - Use the Open/Short method with Kirchhoff's rules
 - Convert the I-source part to a voltage source first...



Solution 1.1 – Kirchhoff

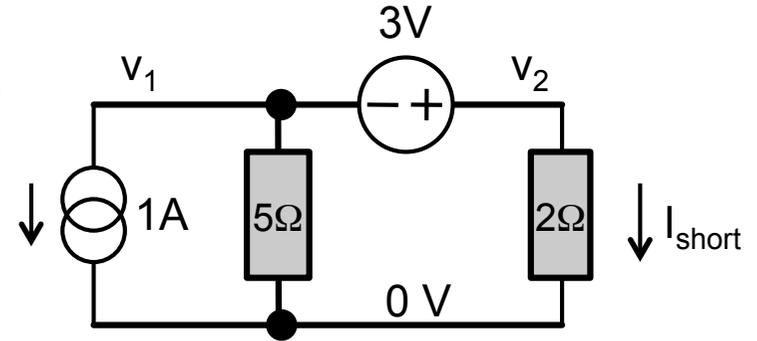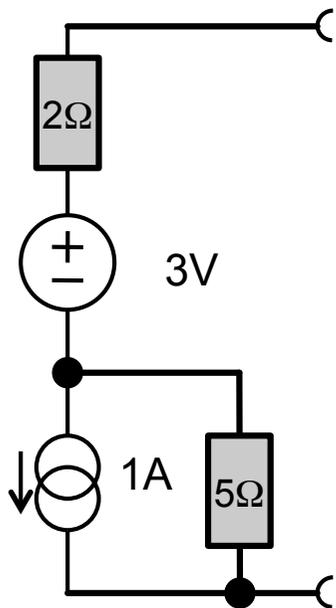
1. Short circuit current:

- EQ1: $1\text{ A} + v_1 / 5\Omega + v_2 / 2\Omega = 0$
- EQ2: $v_2 = v_1 + 3\text{ V}$
- $\rightarrow v_2 = -4 / 7\text{ V}$
- $\rightarrow I_{\text{short}} = -2 / 7\text{ A}$



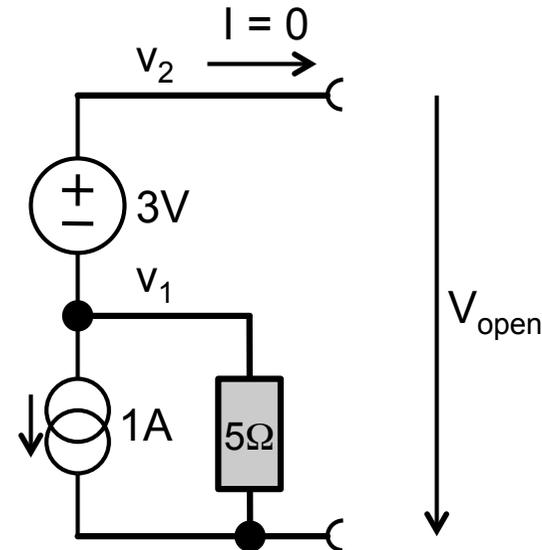2. Open circuit voltage:

- EQ1: $1\text{ A} + v_1 / 5\Omega = 0$
- EQ2: $v_2 = v_1 + 3\text{ V}$
- $\rightarrow v_1 = -5\text{ V}$
- $\rightarrow v_2 = V_{\text{open}} = -2\text{ V}$




- Source: $V_0 = V_{\text{open}} = -2\text{ V}$, $R_V = V_0 / I_{\text{short}} = 7\Omega$




Solution 1.1 – Thévenin Transformations

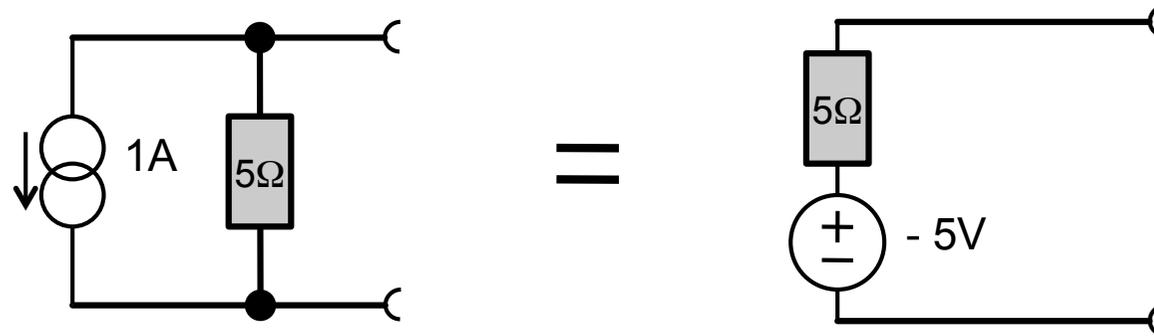1. Convert the current source to a voltage source:




2. Use this in the circuit:

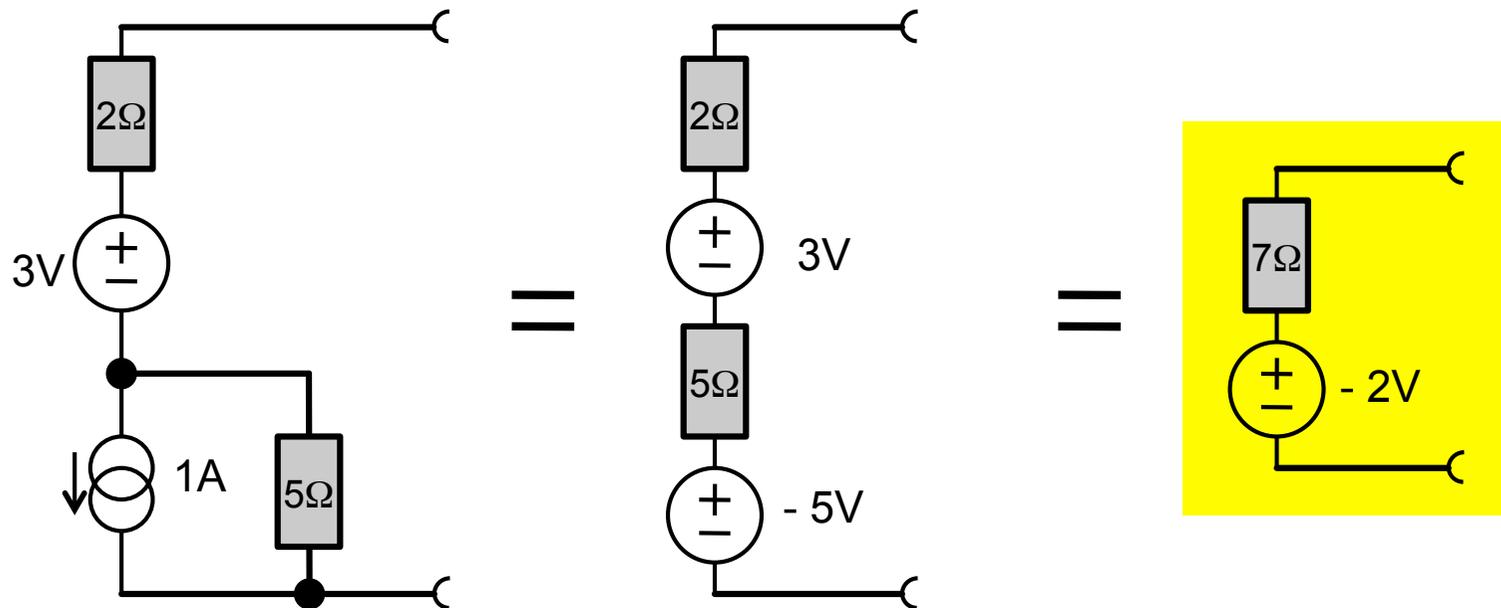



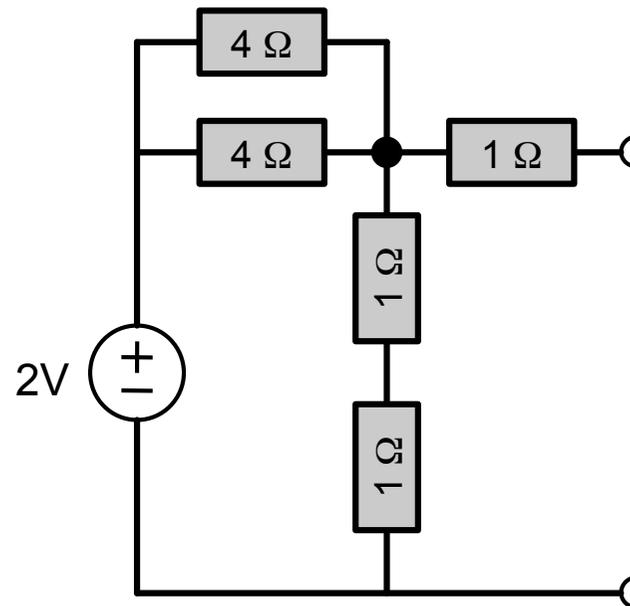Exercise 1.2

- What is the Thévenin Equivalent of the following circuit?




- Use two methods to find the result:
 - parallel / series connection of resistors and your knowledge about the voltage divider
 - short/open method



Solution 1.2


- Parallel-Series Connection, Voltage Divider:

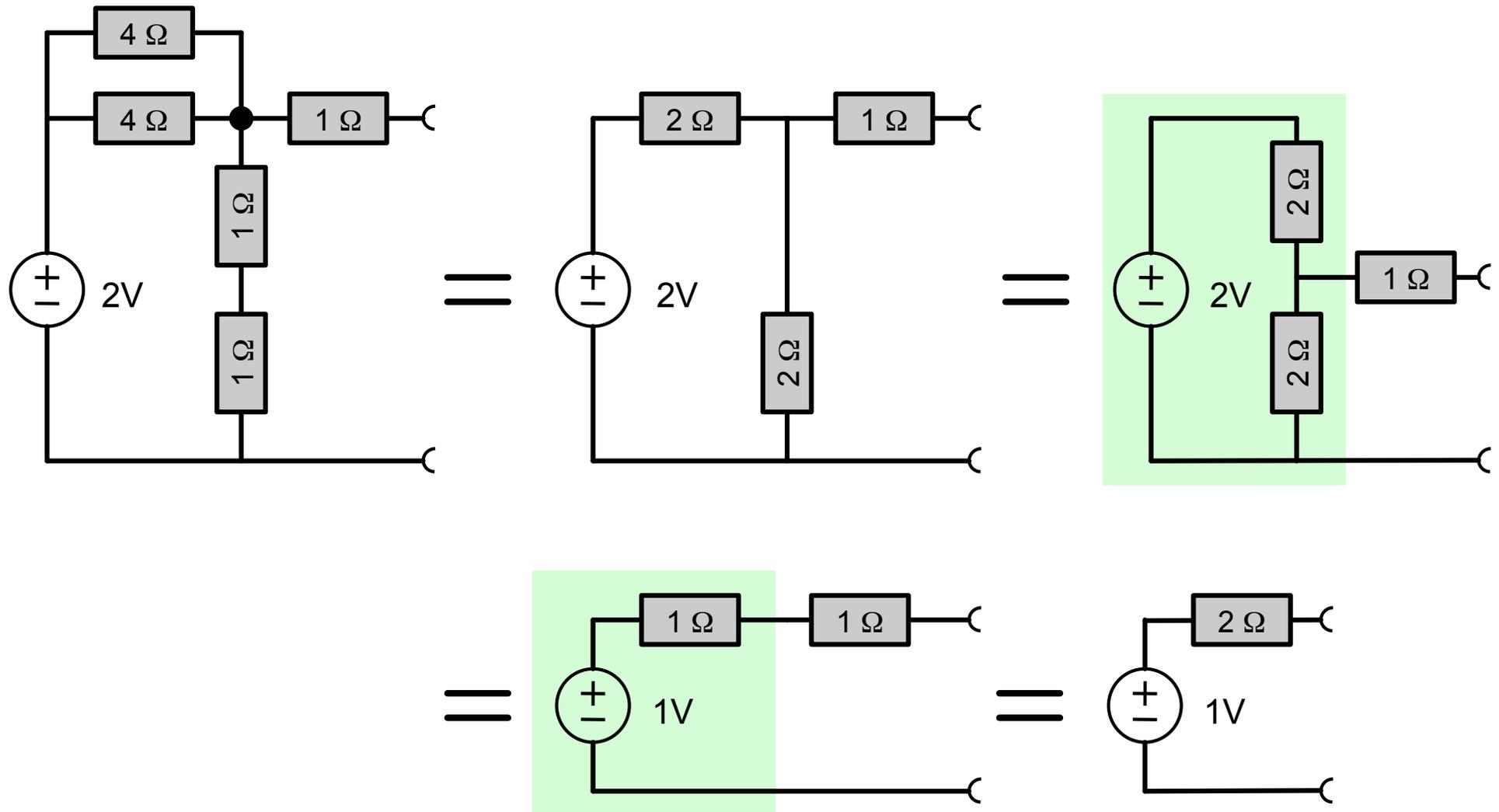




Solution 1.2

▪ Open: $V_{open} = 1V$

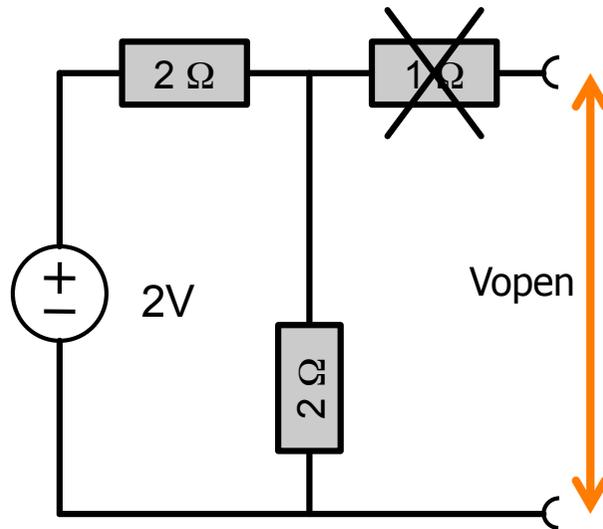

Short:

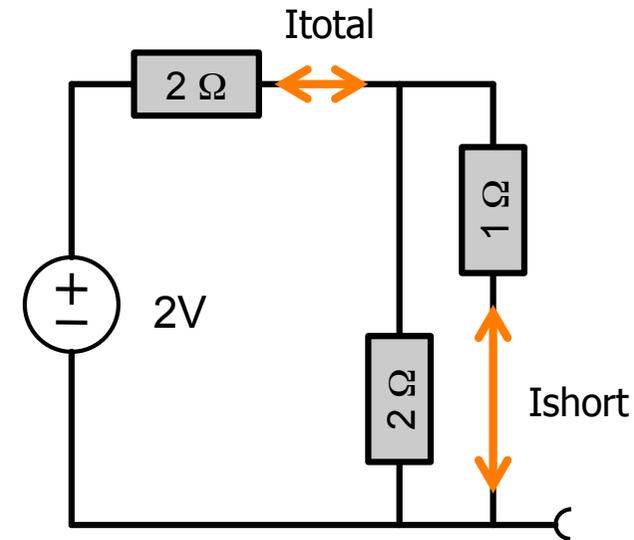

$$R_{total} = 2\Omega + 2/3\Omega = 8/3 \Omega$$

$$I_{total} = 2V / R_{total} = 3/4 A$$


$$I_{short} = 2/3 I_{total} = 1/2 A$$

$$\begin{aligned} Z_{in} &= V_{open} / I_{short} \\ &= 1V / 1/2 A \\ &= 2 \Omega \end{aligned}$$



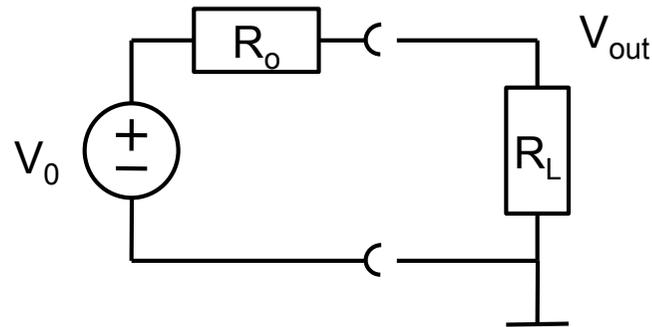Exercise 1.3

- A voltage source with voltage V_0 and output resistance R_0 is loaded by a resistor R_L :



- What is the output voltage V_{out} ?
- Which current flows in R_L ?
- What power is dissipated in R_L ?
 - Check that nothing is dissipated for $R_L=0$ and $R_L \rightarrow \infty$
- For which value of R_L is the dissipation maximized?
 - What is the dissipation?



Solution 1.3

```
In[29]:= Vout = V0  $\frac{RL}{R0 + RL}$  ;
```

```
In[30]:= Iout =  $\frac{Vout}{RL}$ 
```

```
Out[30]=  $\frac{V0}{R0 + RL}$ 
```

```
In[31]:= Pout = Vout Iout
```

```
Out[31]=  $\frac{RL V0^2}{(R0 + RL)^2}$ 
```

```
In[38]:= Table[Limit[Pout, RL → x], {x, {0, ∞}}]
```

```
Out[38]= {0, 0}
```

```
In[39]:= Solve[D[Pout, RL] == 0, RL] // First
```

```
Out[39]= {RL → R0}
```


```
In[40]:= Pout /. %
```

```
Out[40]=  $\frac{V0^2}{4 R0}$ 
```



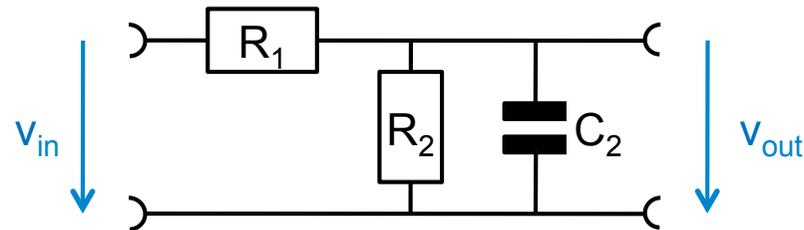Exercise 1.4

- Derive the Transfer Function of this circuit:



- Use 3 different approaches:
 - Treat the circuit directly (using Kirchhoff's rule)
 - Consider it as a voltage divider of two Impedances. Use R_1 for Z_1 and the parallel connection of R_2 and C_2 for Z_2
 - Replace the (resistive) voltage divider by its Thévenin equivalent and then add the capacitor
- Make a Bode Plot
 - Describe the difference to the normal Low Pass Filter



Solution 1.4

Direct Treatment:

$$\text{EQ} = \frac{V_{in} - V_{out}}{R_1} == V_{out} s C_2 + \frac{V_{out}}{R_2};$$

`Solve[EQ, Vout] // First`

$$\left\{ V_{out} \rightarrow \frac{R_2 V_{in}}{R_1 + R_2 + C_2 R_1 R_2 s} \right\}$$

$$\text{Hdirect} = \frac{V_{out}}{V_{in}} /. \%$$

$$\frac{R_2}{R_1 + R_2 + C_2 R_1 R_2 s}$$

Voltage Divider:

$$\text{Hdiv} = \frac{Z_2}{Z_1 + Z_2} /. \left\{ Z_1 \rightarrow R_1, Z_2 \rightarrow \left(\frac{1}{R_2} + s C_2 \right)^{-1} \right\} // \text{Simplify}$$


$$\frac{R_2}{R_1 + R_2 + C_2 R_1 R_2 s}$$

`Hdirect == Hdiv`

`True`



Solution 1.4

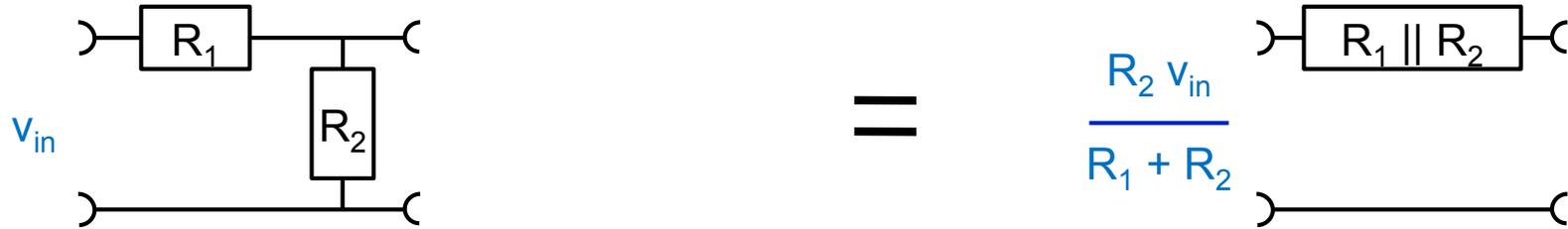

$$H_{thenevin} = \frac{g}{1 + s R R C_2} / \cdot \left\{ g \rightarrow \frac{R_2}{R_1 + R_2}, RR \rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} \right\} // \text{Simplify}$$


$$\frac{R_2}{R_1 + R_2 + C_2 R_1 R_2 s}$$

Simple Low Pass



Solution 1.4


- Compared to the 'simple' Low-Pass:
 - The signal is attenuated by $R_1/(R_1+R_2)$
 - The time constant is lowered (i.e. the corner frequency is raised)
- Plot for $R_1 = R_2 = C_2 = 1$: $HLP = \sqrt{\frac{1}{1 + i \omega RC} \text{Conjugate}\left[\frac{1}{1 + i \omega RC}\right]} \cdot \{RC \rightarrow 1\}$

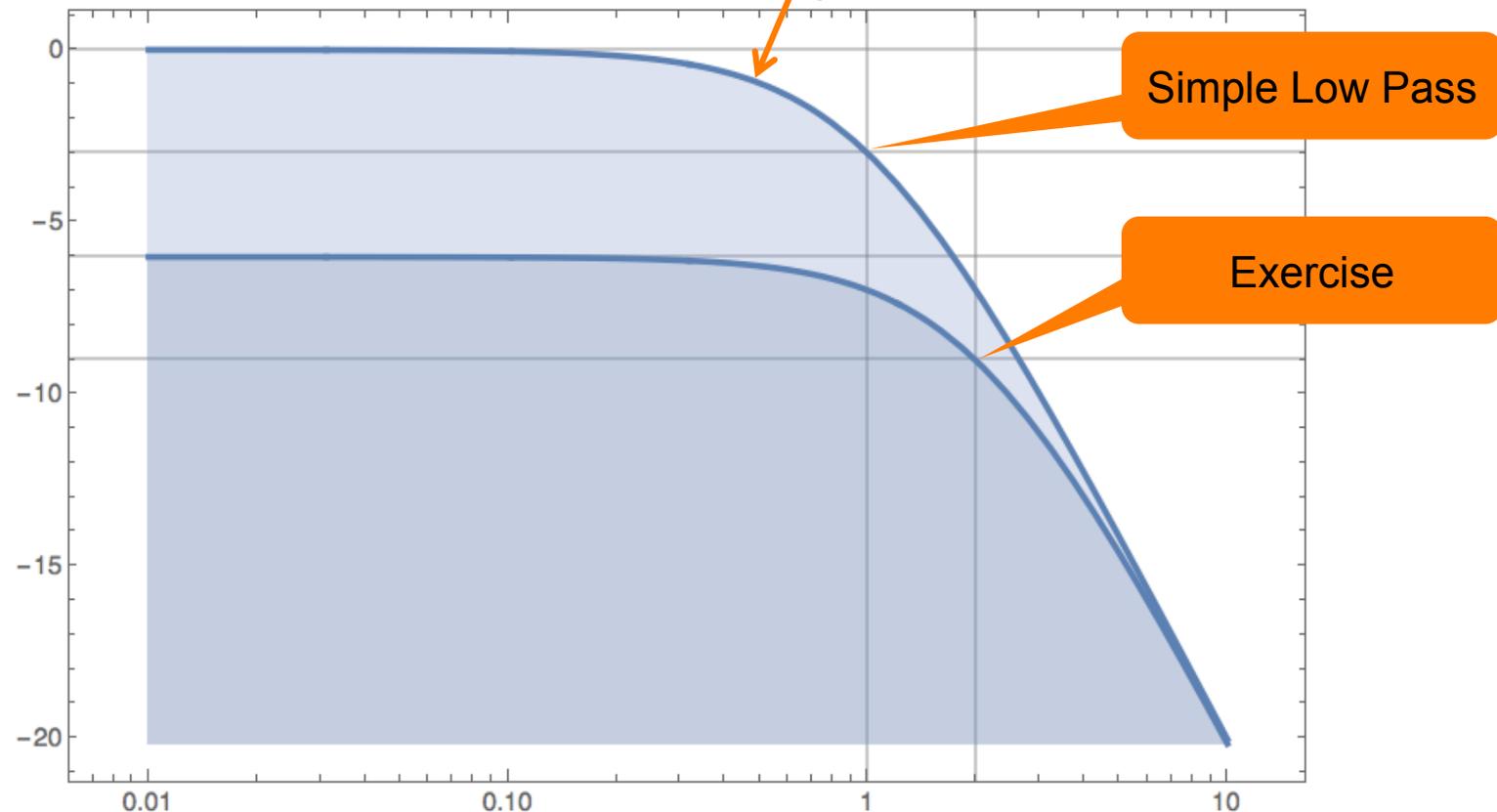



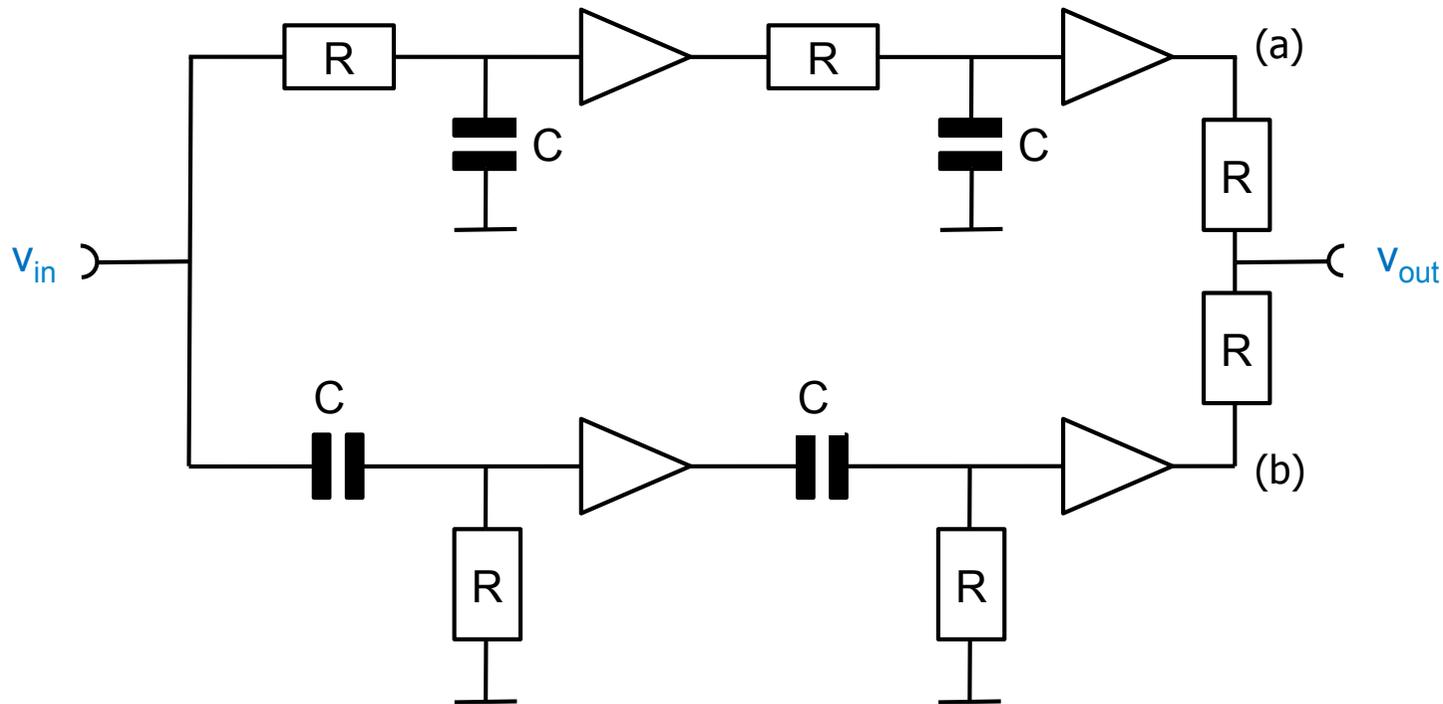Exercise 1.5: Notch Filter

- Consider the following circuit made of cascaded High- and Low Pass stages:
 - The resistors at the output just add the signals at (a) and (b)



- What is the output signal at the corner frequency?
 - Explain this by comparing amplitudes *and phases* at (a) and (b)



Solution 1.5

$$\$Assumptions = \omega > 0 \ \&\& \ RC > 0; \ HLP = \frac{1}{1 + i \omega RC}; \ HHP = \frac{i \omega RC}{1 + i \omega RC};$$

$$v_{out} = V_b + \frac{1}{2} (V_a - V_b) \ // \ Simplify \ (* \ Output \ is \ average \ of \ V_a \ and \ V_b \ *)$$

$$\frac{V_a + V_b}{2}$$


$$H = \frac{HLP \ HLP + HHP \ HHP}{2} \ // \ Simplify$$

$$\frac{-1 + RC^2 \omega^2}{2 (-i + RC \omega)^2}$$

$$HMAG = H \ Conjugate[H] \ /. \ RC \rightarrow 1 \ // \ FullSimplify$$

$$\frac{(-1 + \omega^2)^2}{4 (1 + \omega^2)^2}$$
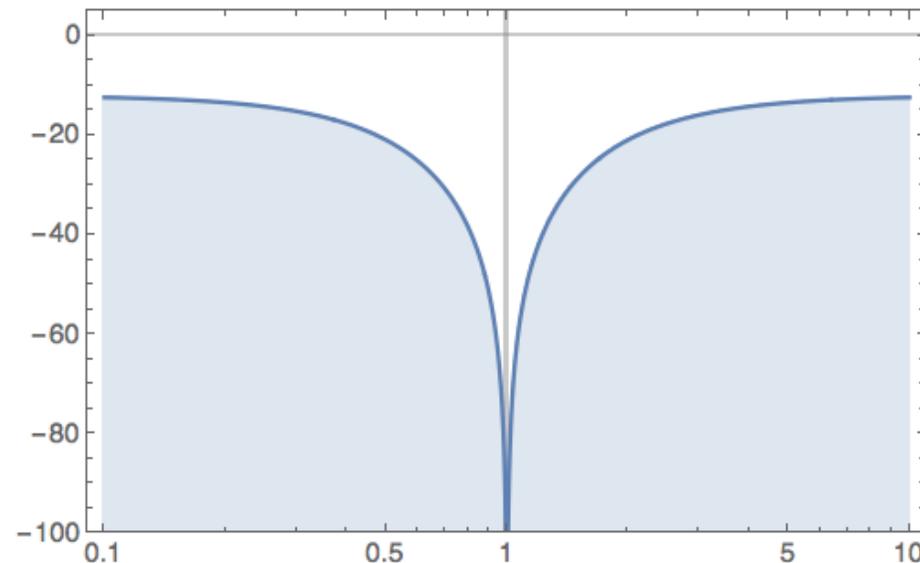
```
LogLinearPlot[dB[HMAG], {ω, 0.1, 10}
, GridLines -> {{1}, {0}}, PlotRange -> {-100, 5}, Filling -> -100]
```




- At the corner frequency, the signal is fully stopped!
- This is because **the phases** of the two signals are $\pm 90^\circ$, i.e. the signals are complementary
 - (A bit tricky to verify in Mathematic due to jump in ArcTan[.]..)



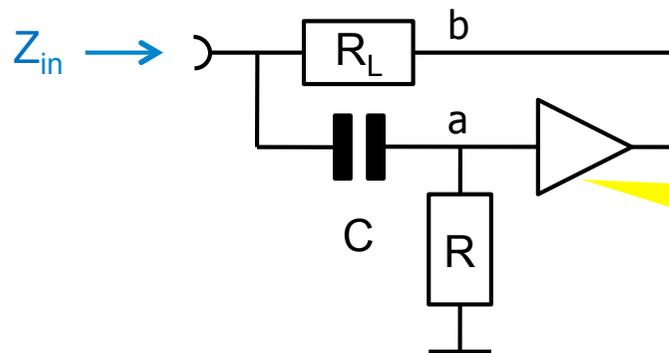Exercise 1.6: Gyrator (difficult)

- A 'Gyrator' can mimic inductive behaviour, while using only resistors, capacitors and amplifiers
- Consider the following circuit:



the triangle is a voltage amplifier with gain=1 ('follower'). It forces node b to the potential of node a

- **Calculate** the input impedance $Z_{in} = U_{in}/I_{in}$ of the circuit
 - (Use Kirchhoff's law at the input node and node a)
- For frequencies $< 1/C R_L$, the denominator can be neglected.
- Compare the result to an inductor in series with R_L
- Simulate.
 - Note that R should be larger than R_L (what happens for $R=R_L$?)
 - Plot i_{in} .
 - Add another capacitor in series to produce a resonant circuit.



Solution 1.6

Mathematica:

```
EQin = iin == (vin - va) s C + (vin - vb) / RL /. vb -> va;
```

```
EQa = (vin - va) s C == va / R;
```

```
Eliminate[{EQin, EQa}, va] // Simplify
```

```
iin (RL + C R RL s) == vin + C R L s vin
```

```
sol = Solve[%, iin] // First
```

```
{iin -> (vin + C R L s vin) / (RL (1 + C R s))}
```

```
Zgyrator[s_] = (vin / iin) /. sol // Simplify
```

```
(RL + C R RL s) / (1 + C R L s)
```

