



Exercise: (More) Filters


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



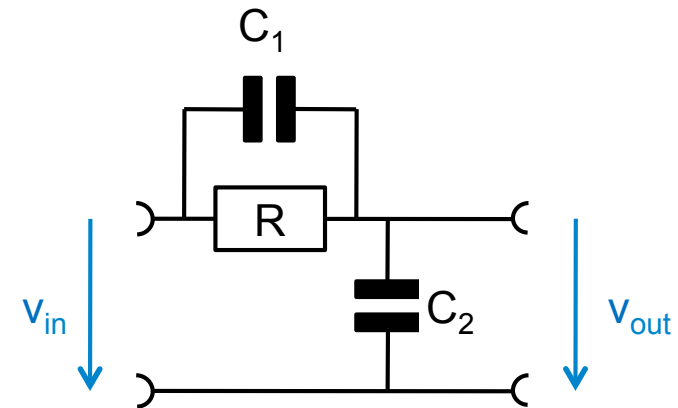Exercise 1

- Analyze the following circuit (simulation & calculation!):




- What is the transfer function ?
- At which frequencies are the ‘pole’ in the denominator and the ‘zero’ in the nominator ?
- What are gain and phase for $s \rightarrow 0$ and for $s \rightarrow \infty$? Why?
- What happens for $C_1 \rightarrow 0$, for $R \rightarrow 0$, for $R \rightarrow \infty$? Reasonable?
- Simulate the circuit for $C_1 = C_2 = 10\text{pF}$ and $R = 10\text{ k}\Omega$. Plot gain and phase!
- Chose values so that the circuit attenuates to 1/10 at high frequencies.
- For fun: At which frequency is phase shift maximal?



Solution 1

■ Two possibilities:

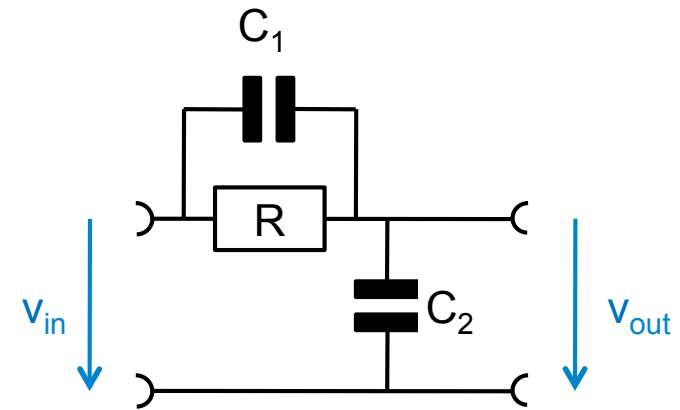
1. Treat circuit as voltage divider with $C_1 // R$ and C_2
2. Use Kirchhoff's law @ node v_{out}



■ Voltage divider:

- For any Z_1, Z_2 , we have $v = v_{out}/v_{in} = Z_2 / (Z_1 + Z_2)$
- With $1/Z_1 = 1/R + s C_1$ and $1/Z_2 = s C_2$:
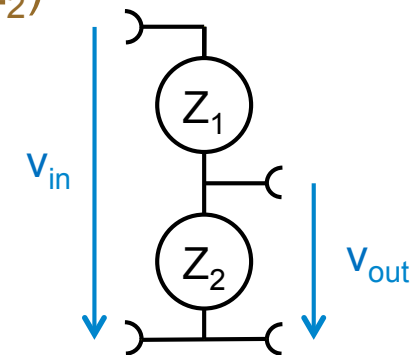
$$v = \frac{1 + C_1 R s}{1 + (C_1 + C_2) R s}$$



■ Kirchhoff:

- Solve $(v_{in} - v_{out})/R + (v_{in} - v_{out}) s C_1 = v_{out} s C_2$ for v_{out}



Solution 1

■ Limits

$$v = \frac{1 + C_1 R s}{1 + (C_1 + C_2) R s}$$

- $s \rightarrow 0$: caps are gone. v is just 1. No phase shift.
- $s \rightarrow \infty$: R can be neglected. frequency dependencies cancel. This is just a capacitive voltage divider. No phase shift

■ Phase shift:

```
gain = Sqrt[(HH /. s -> i ω) (HH /. s -> -i ω)] // FullSimplify
```

$$\sqrt{\frac{1 + C_1^2 R^2 \omega^2}{1 + (C_1 + C_2)^2 R^2 \omega^2}}$$

```
phase = - 180 / π ArcTan[Im[ComplexExpand[HH /. s -> i ω]] / Re[ComplexExpand[HH /. s -> i ω]]] // FullSimplify
```

$$\frac{180 \text{ ArcTan}\left[\frac{C_2 R \omega}{1 + C_1 (C_1 + C_2) R^2 \omega^2}\right]}{\pi}$$


```
PhaseDeriv = D[phase, ω] // FullSimplify
```

$$\frac{180 C_2 R (1 - C_1 (C_1 + C_2) R^2 \omega^2)}{\pi + (2 C_1^2 + 2 C_1 C_2 + C_2^2) \pi R^2 \omega^2 + C_1^2 (C_1 + C_2)^2 \pi R^4 \omega^4}$$

```
ωmax = ω /. Solve[PhaseDeriv == 0, ω] // Last // FullSimplify
```

$$\frac{1}{\sqrt{C_1 (C_1 + C_2) R^2}}$$


```
LogLinearPlot[phase /. PARAM, {ω, 1 × 103, 1 × 109}]
```

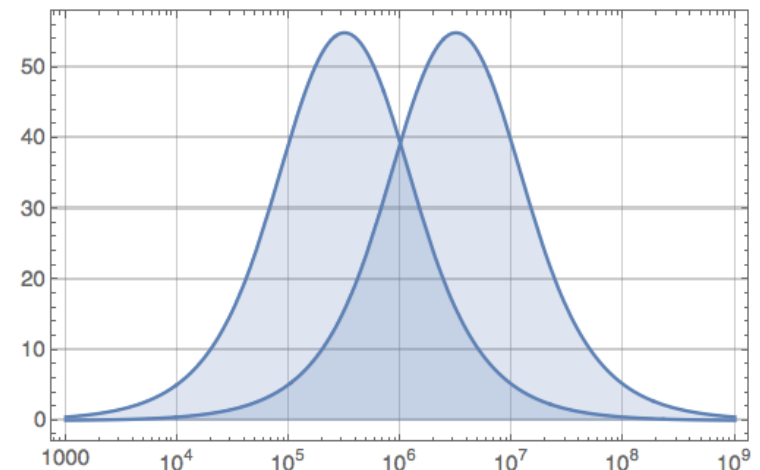



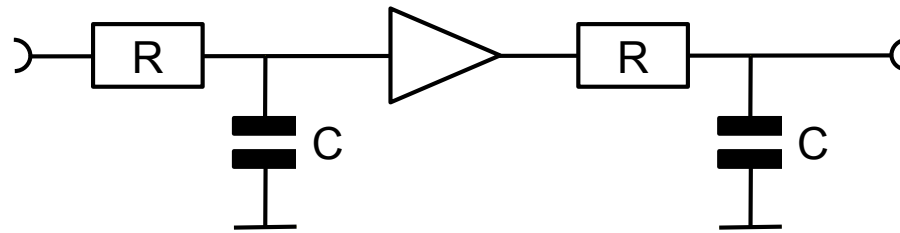Exercise 2: Cascaded Stages

- Consider the following two stage circuit (again):



- The triangle is a (voltage) buffer with infinite input impedance (it does not load the first low-pass) and zero output impedance. From the analogLib, use vcvs (voltage controlled voltage source)
- What transfer function do you expect ?
- Simulate the circuit !
- Simulate in parallel** a version **without** buffer. Where are differences ?
- Use a much larger R and correspondingly smaller C in the second low pass.
- Now **calculate** the exact transfer function **without** buffer



Solution 2

Transfer Function with buffers

$$HH1 [s_] = \left(\frac{1}{1 + s R C} \right)^2; (* \text{ with buffers: square of } s$$

$$\text{gain1}[\omega_] = \text{Sqrt}[HH1[i \omega] HH1[-i \omega]] // \text{FullSimplify}$$

$$\frac{1}{1 + C^2 R^2 \omega^2}$$

Without Buffers:

$$EQ1 = \frac{v_{in} - v_1}{R_1} == v_1 s C_1 + \frac{v_1 - v_{out}}{R_2}; (* \text{ node } v_1 *)$$

$$EQ2 = \frac{v_1 - v_{out}}{R_2} == v_{out} s C_2; (* \text{ output node } *)$$

$$\text{Eliminate}\{\{EQ1, EQ2\}, v_1\} // \text{Simplify}$$

$$v_{in} == (1 + C_2 (R_1 + R_2) s + C_1 R_1 s (1 + C_2 R_2 s)) v_{out}$$

$$HH2 [s_] = \frac{v_{out}}{v_{in}} /. \text{Solve}\{\%, v_{out}\} // \text{First}$$


$$\frac{1}{1 + C_1 R_1 s + C_2 R_1 s + C_2 R_2 s + C_1 C_2 R_1 R_2 s^2}$$




Solution 2

■ Bode Plot for different RC combinations in second stage:

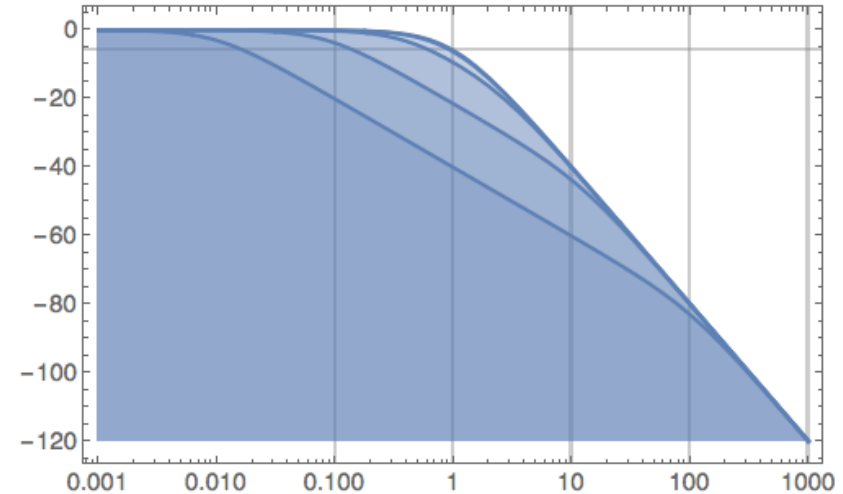- We note two poles.
- They coincide, when the second low pass does not load the first




■ Plot the poles as a function of f where $R_2 = R_1 f$, $C_2 = C_1 / f$, so that $R_2 C_2 = R_1 C_1$:

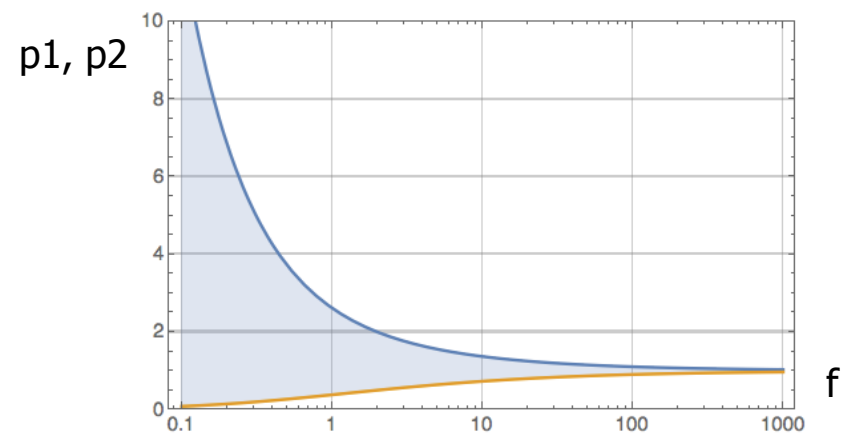



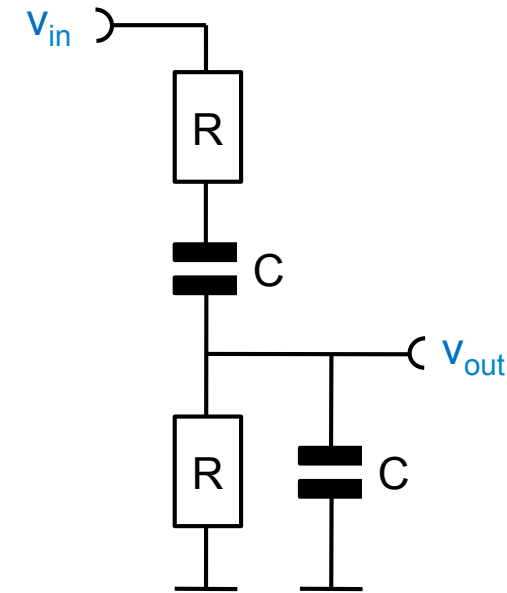Exercise 3: Wien Bridge / Oscillator

- Consider this circuit:
- What is the transfer function?
- What is the magnitude at the center frequency?
- What is the Phase at the center frequency?
- Simulate the circuit for $R=1k$ $C=1n$



- You can use this 'Wien Bridge' to make an oscillator:
 - Amplify v_{out} by *exactly* 3 (vcvs !) and feed the signal back to v_{in} .
 - Set an initial condition of 1V (parameter!) for the lower C and start a transient simulation.
 - How does this work?
 - What happens if the gain is not exactly 3 ?

Temp rise from ambient	<input type="text"/>
Initial condition	<input type="text" value="1"/>
Temperature coefficient 1	<input type="text"/>




Itermezzo: Wien Oszillator

- Wien bridge: Max Wien (1891)
- An Oscillator using a *light bulb* to stabilize gain (leading to with very low distortion) is patented 1939 by William Hewlett and David Packard (Stanford University)
- Founders of Hewlett – Packard (HP)
- Their first product: HP 200A 'Audio Oscillator'






Schematic Diagram (HP 200 B)

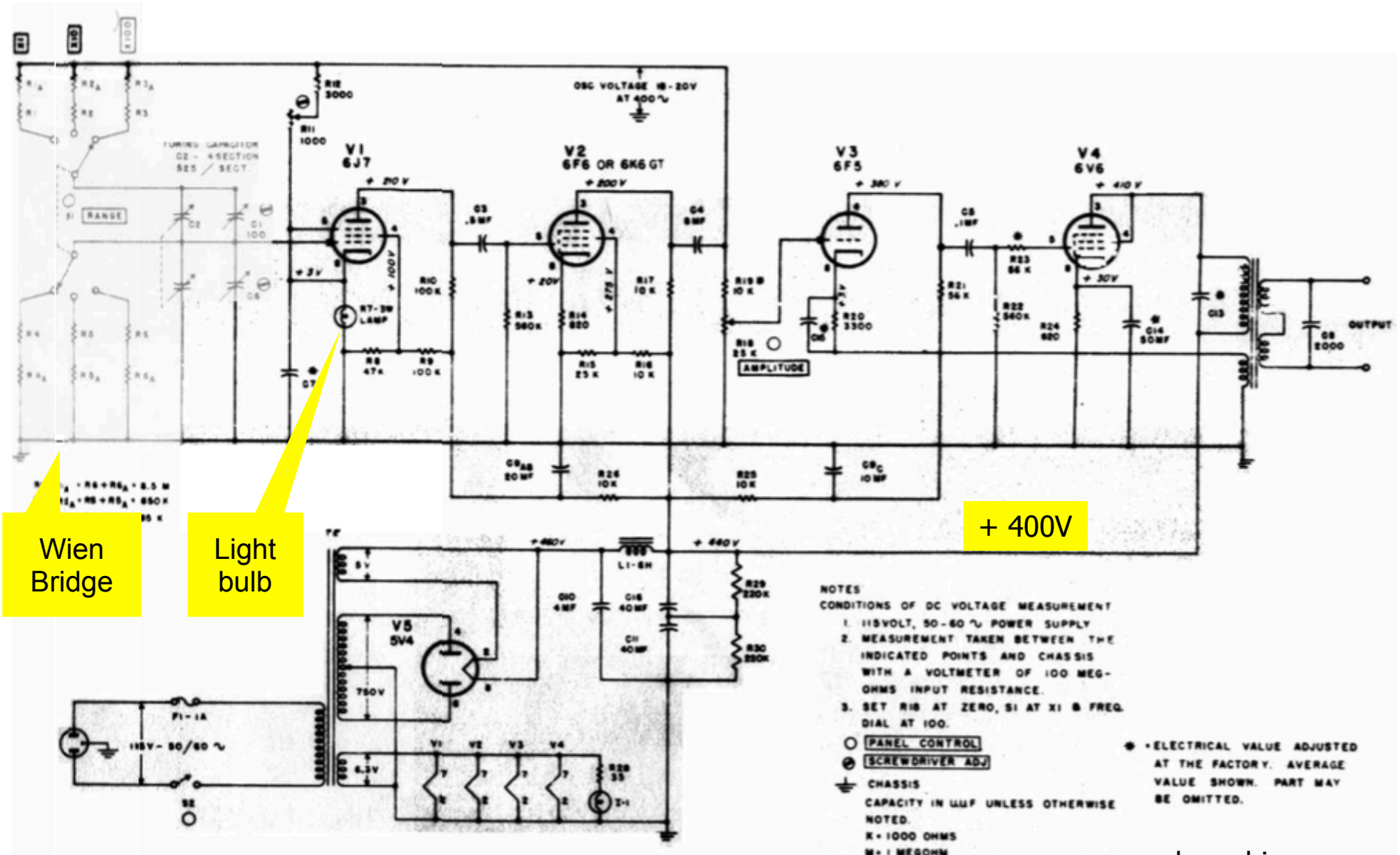

hparchive.com



Inside..

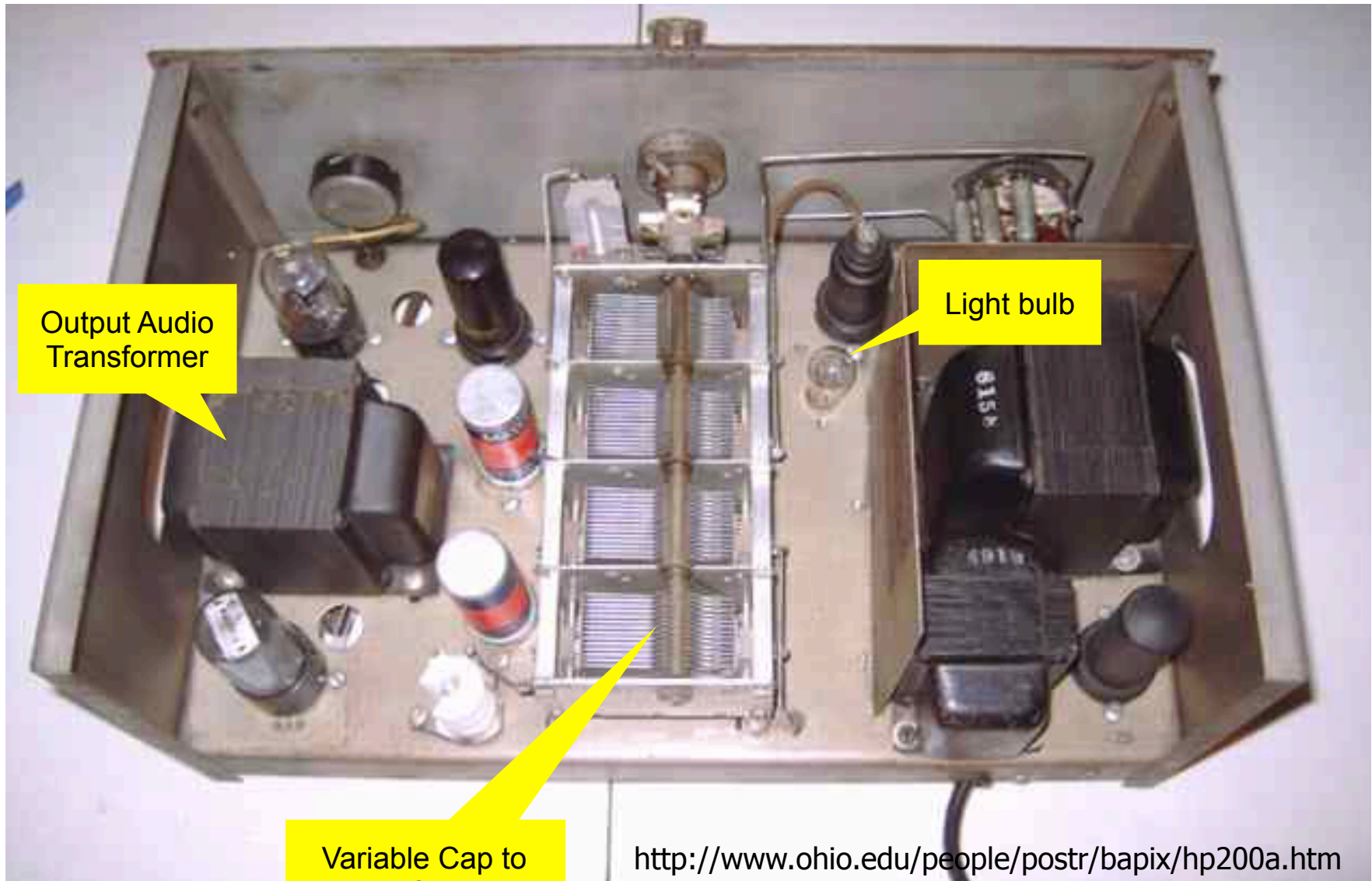


<http://www.ohio.edu/people/postr/bapix/hp200a.htm>




Discrete circuit versions

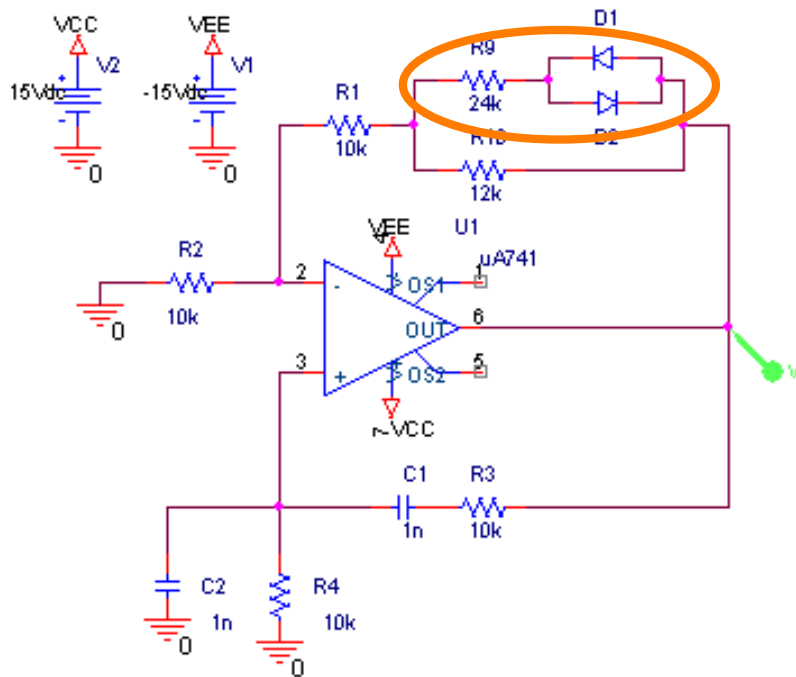
- The problem is to stabilize the gain to exactly 3
- This is achieved by a regulation loop which monitors the output amplitude by some means



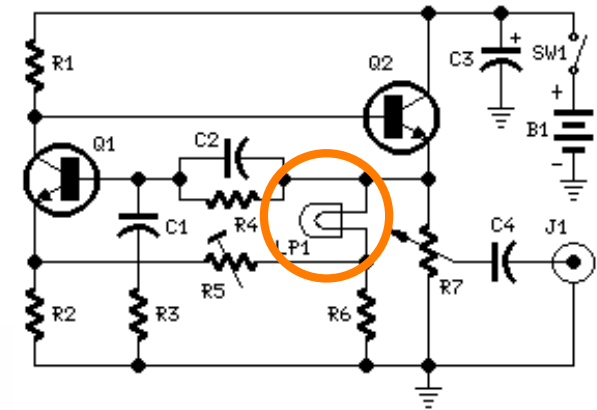www.calvin.edu/~pribeiro/courses/engr332/Handouts



<http://www.redcircuits.com//Page13.htm>

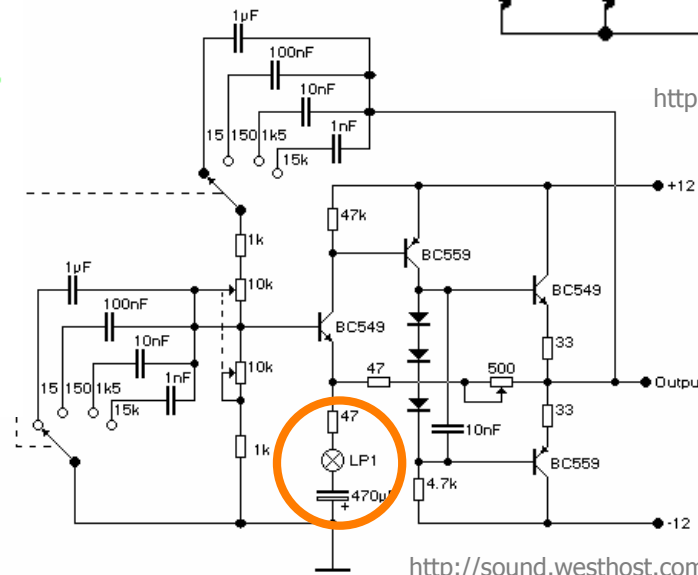


<http://sound.westhost.com/project22.htm>



Solution 3

- $H[s] = \frac{C R s}{1 + 3 C R s + C^2 R^2 s^2}$
- Centre frequency is at $\omega_0 = 1/RC$.
 - Gain there is 1/3. Phase is 0
 - Note that H becomes real valued at $s=i \omega_0$
- Oscillator:

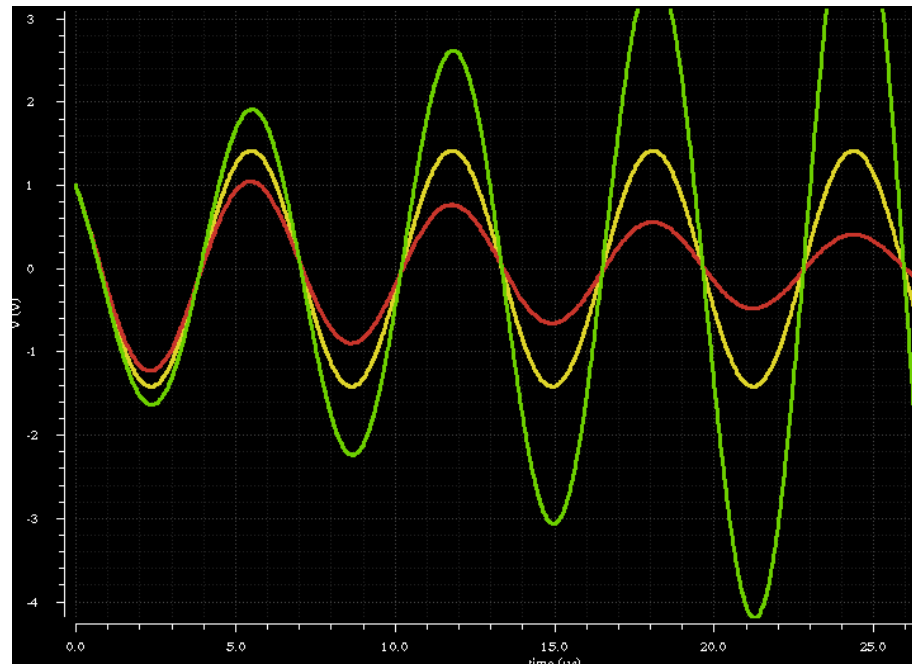



Exercise 5: Low Pass & High Pass

- Plot (on a paper) the Bode diagram for a low pass filter
 - **Calculate** the amplitude at the corner frequency $\omega_C = 1/(RC)$
 - **Calculate** the phase for $\omega = 0$, $\omega = \omega_C$, $\omega \rightarrow \infty$

- Simulate this circuit (using an ac sweep)
 - Do not forget to set the 'ac magnitude' to 1
 - Change the vertical scale to 'log'
 - Plot gain in dB and phase:
Results → Direct Plot → Gain and Phase → Select output and the Input
 - Check the numerical value of the corner frequency

- Add a high pass and plot the two outputs simultaneously