



# Exercise: Current Mirrors


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg


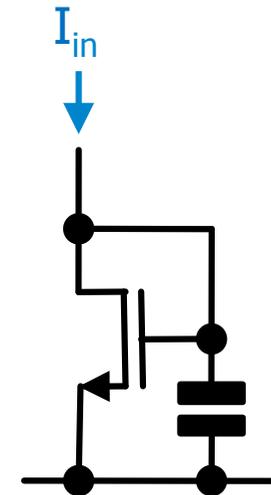
# Exercise 1: Dynamic Regulation


- Draw a diode connected NMOS
  - Connect a large ,extra' capacitance to the gate (some pF) with an *initial condition* of 0 V
    - Use a transistor 'n\_18\_mm' from the UMC library 'UMC\_018\_CMOS'. Connect bulk and source.
    - Set the initial condition ('IC') in the properties of the capacitor
  - Send a small current  $I_{in}$  (nA- $\mu$ A) into the ,diode'
  - Perform a transient simulation
- 
- Observe the Input = Gate = Drain Voltage
  - Use different initial conditions (0...1.8V, Parametric sweep!)
  - Understand how the equilibrium point is reached!
  - Vary  $I_{in}$ !




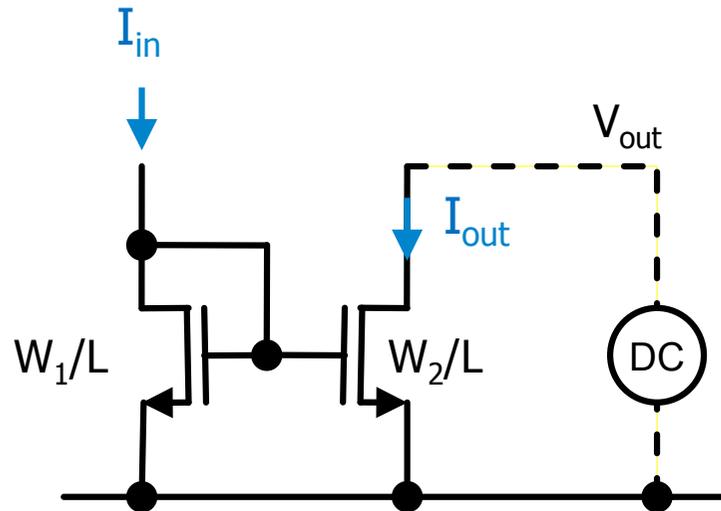
## Exercise 2: A First Mirror

- Draw the following *current mirror*, with  $W_1 = W_2 = 1\mu\text{m}$ . Use for instance  $L = 0.5\mu\text{m}$  and  $I_{\text{in}} = 10\mu\text{A}$




- Sweep the output voltage  $V_{\text{out}}$  and observe the current  $I_{\text{out}}$ .
  - When is  $I_{\text{out}} = I_{\text{in}}$  exactly? Why?
  - Try another input current!
  - Change  $W_2$ !
- For fixed  $I_{\text{in}}$ ,  $W_1, W_2$ , vary  $L$  (same in both MOS).
  - Explain what you see!


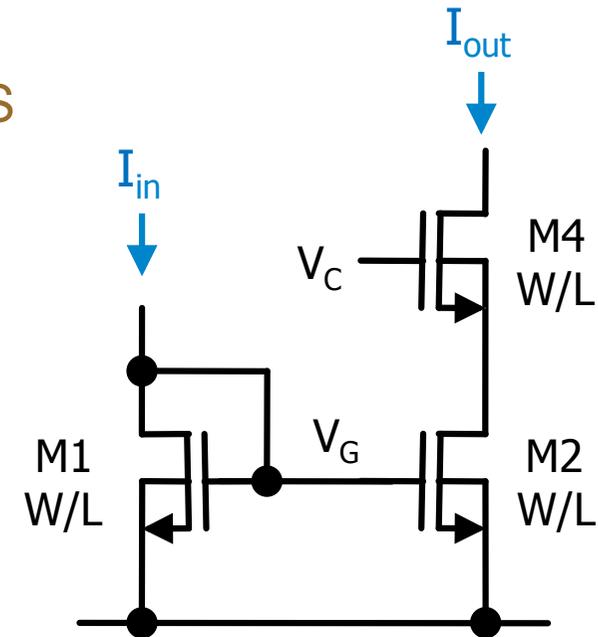
## Exercise 3: A Better Mirror


- The output current varies with  $V_{out}$  (i.e. the output resistance is not infinite) due to the Early Effect in M2.
- Try the following circuit:
  - Connect bulk and source in all MOS
  - Start with  $V_C = 1.2V$
  - Use  $I_{in} = 1\mu A$
- Sweep  $V_{out}$ 
  - How is the output resistance now? (You may simulate the 'simple' mirror of the previous exercise in parallel for comparison)
- Calculate the small signal output resistance!
  - You only need to consider M2 and M4 (because  $V_G$  is constant)
- Vary  $V_C$  (from 0V to 1.8V) and see what happens
  - What is the 'ideal'  $V_C$  ?




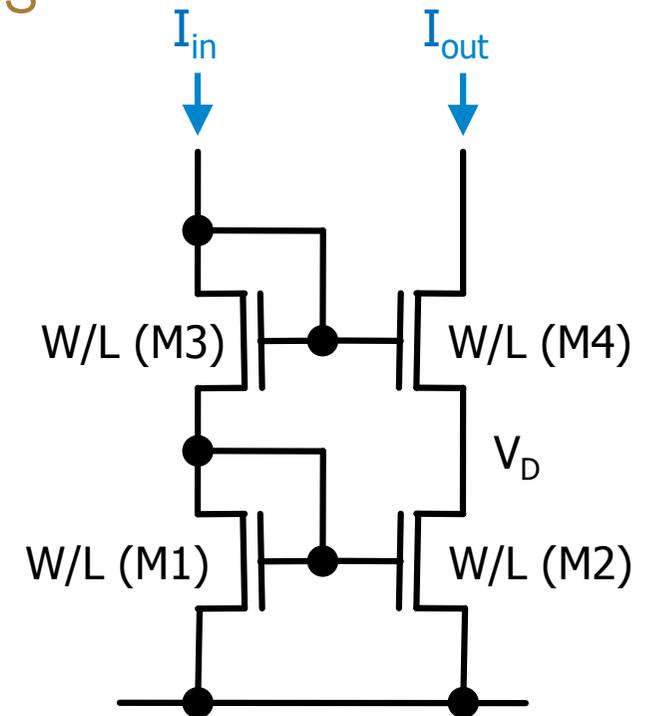
## Exercise 4: A Mirror with Better Matching

- Unfortunately, the previous circuit does NOT reproduce  $I_{in}$  exactly. Why?
- Try this circuit (which does not need  $V_C$  and more):
  - Connect bulk and source in each MOS
  - It is called the ‚stacked mirror‘
- Sweep  $V_{out}$ 
  - Do currents match?
  - What is  $r_{out}$  ?
  - Where is the saturation ?




- What is the drain voltage  $V_D$  of M2? Is that optimal?


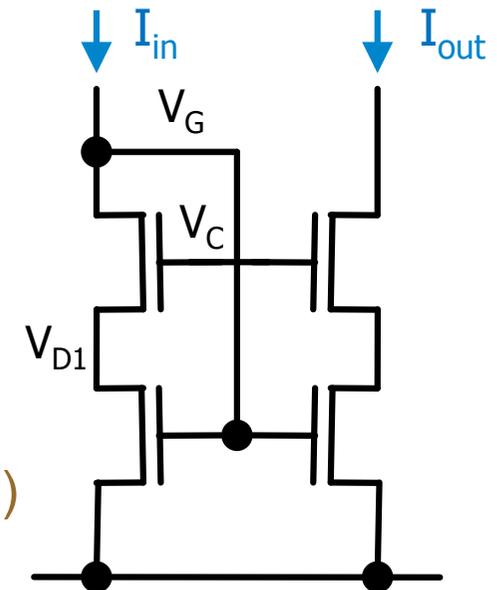
## Exercise 5: The Low Voltage Mirror


- In the stacked mirror of the previous exercise, the drain voltage  $V_D$  of the current source M2 is fixed by the diode connection of M1.
- This is simple, but provides a *too high* voltage (by  $\sim V_T$  !)
- The following circuit connects the diode differently:
  - Understand that the gate voltage  $V_G$  still stabilizes to the 'correct' level!
  - We now need to find  $V_C$
  - Sweep  $V_C$  from 0.4 to 1.4V in steps of 0.2V
  - What is a good choice?
  - Why do very low voltages fail (check  $V_G$  !)
  - What happens at high voltages? Why? (this is tricky to understand... Look at  $V_{D1}$ ...)
  - Note that the 'best'  $V_C$  depends in  $I_{in}$




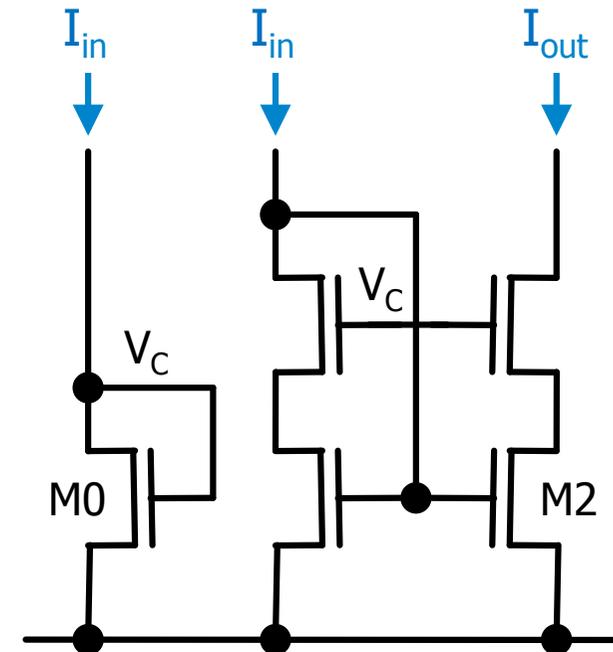
## Exercise 6: The Low Voltage Mirror

- The required optimal cascode voltage  $V_C$  can be generated *automatically* by a diode connected MOS M0 with different geometry than the others:  
 $(W/L)_0 = k (W/L)_{\text{others}}$
- We assume that we have a second input current  $I_{in}$  available (both  $I_{in}$ s are equal)



- Calculate  $k$  so that M2 is just saturated.
  - Use the *large signal* model in strong inversion with no Early effect
- Simulate the circuit



## Exercise 7: An *Even* Better Mirror

- The key trick is obviously to keep the drain voltage of M2 very constant irrespective of the output voltage.
- This can be done with an active circuit (with an amplifier):
  - Amp amplifies the difference of the two input voltages by  $A_0$
  - Where is the positive/negative input for table operation?
  - Simulate the circuit. Use a voltage controlled voltage source vcvs from the analogLib for Amp with  $A_0=1000$

- *Calculate* the output resistance!

- This topology is called the *Regulated Mirror*

