



Exercise: Gain Stage


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



 1. Basic Gain Stage

- Implement a NMOS gain stage.
 - Use a NMOS with $W/L = 1\mu/0.2\mu$
 - Use a PMOS of same dimension as a current source
 - Bias the PMOS with a *mirror* to $10\mu\text{A}$
 - Operate at $V_{DD} = 1.8\text{ V}$



- Sweep V_{in} and observe V_{out}
 - What is the largest gain (derivative!) ?
 - Change
 - the bias current
 - W of the input transistor
 - L of the PMOS
- and observe what happens. Explain!



2. Comparing Gain to Theory

- In the previous circuit, fix an operation point in the high gain region (i.e. pick a V_{in} and note the corresponding V_{out})
- Determine the gain by calculating the derivative of the transfer function
- Compare this to an AC sweep at the operation point

- Now extract
 - g_m of the NMOS (at the operation point!)
 - r_{ds} of NMOS and PMOS (at the operation point!)
- Calculate the gain. Does it match?



3. Bandwidth

- Load the gain stage with a capacitor (1 pF)
- Observe the bandwidth

- Modify the load capacitor
 - Is bandwidth inversely proportional to C_L ?

- Modify I_D
 - Make a Parametric Sweep with 2-3 values (1 μ A, 10 μ A, 100 μ A)
 - Do you find what you expect?



3.b Effect of Load Dimension

- Use a simple gain stage with an NMOS and a PMOS (mirror) load
- Introduce a self-bias (automatic setting of the operation point, see lecture slides) to $V_{in} = V_{out}$ with
 - a large (1 G Ω) resistor between input and output and
 - a large (1 F) capacitor to ac couple the input signal
- Check with an AC sweep that the circuit works
 - A DC sweep will NOT work with this same circuit! (why?)
- At constant bias, change L of the load (and the mirror) and see how the (dc) gain varies
- Repeat this for a longer input NMOS



4 Cascoded Gain stage

- Set up a cascoded gain stage
 - Use $W/L = 5\mu / 0.2\mu$ for all 4 MOS
 - Use $I_{\text{bias}} = 10 \mu\text{A}$
 - Use a stacked mirror on the PMOS side
 - Use a 'safe' cascode voltage for the NMOS
 - Make a DC sweep

- Use the self bias presented in the lecture to set a good operation point
 - First check with the DC sweep that $v_{\text{out}} = v_{\text{in}}$ is a good operation point

- What is the gain?




5. Transfer Function of the Cascoded Gain Stage

- *Calculate* the transfer function of the cascoded gain stage
 - Assume an ideal load (current source)
 - Consider a load capacitor C_L

- What are
 - the DC gain?
 - the unity gain bandwidth?

- Compare to the case with no cascode

 - Use the simulation from Exercise 4 to verify your finding





6. The Inverter

- The PMOS 'load' in the gain stage supplies a more or less constant current
- In the CMOS Inverter shown, the PMOS is switched with the input signal, it acts as the NMOS
- Simulate the DC transfer function $V_{out}(V_{in})$
 - For instance $L_N = L_N = 0.2\mu$, $W_N = 1\mu$, $W_P = 2\mu$
 - What is different from the normal gain stage ?
 - What is the maximum gain ?
- Use a small signal analysis to find the gain

