




# FOR FUN: HIGHER ORDER FILTERS

(Mathematica file: CCS\_HigherOrderFilters.nb)



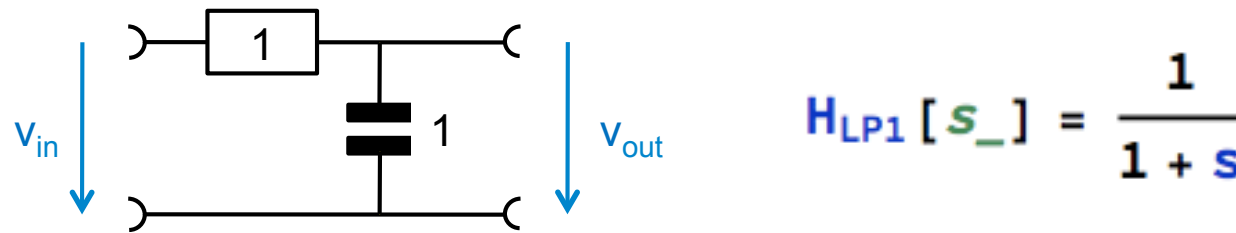
## Reminder: One Low Pass

- (For simplicity, we use fixed values for R and C, often 1  $\Omega$ /F)



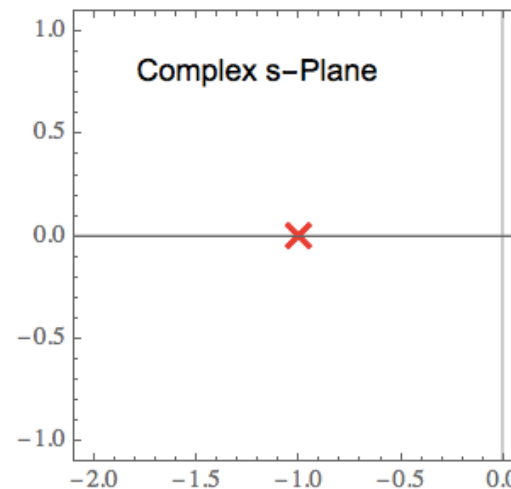- Mathematically,  $H_{LP1}[s]$  has a **POLE** at  $s = -1$ .
- This can be illustrated in the COMPLEX s-Plane:




- This particular pole is **real**, i.e. it lies on the real axis



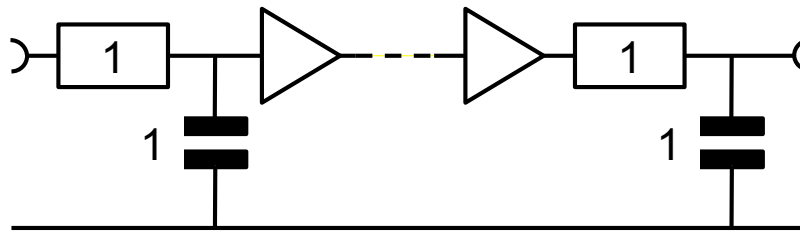
# Reminder: Cascaded Low Pass Stages

- If we cascade  $N$  stages *with buffers*, we get



$$H_{LPN}[s] = \frac{1}{(1 + s)^N}$$

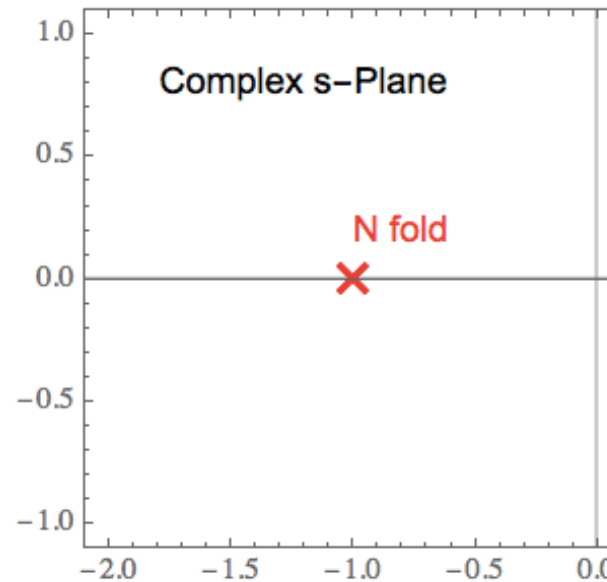
- $H_{LPN}[s]$  has a ***N-fold*** POLE at the same location  $s = -1$ .





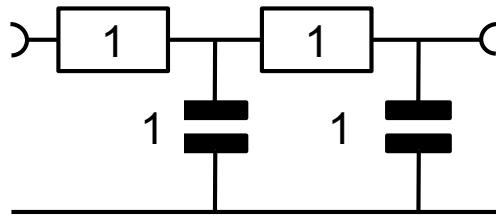
# Two Unbuffered Low Pass Stages

- If we cascade two stages *without buffer*, we get



$$H_{LPCasc}[s] = \frac{1}{1 + 3s + s^2}$$

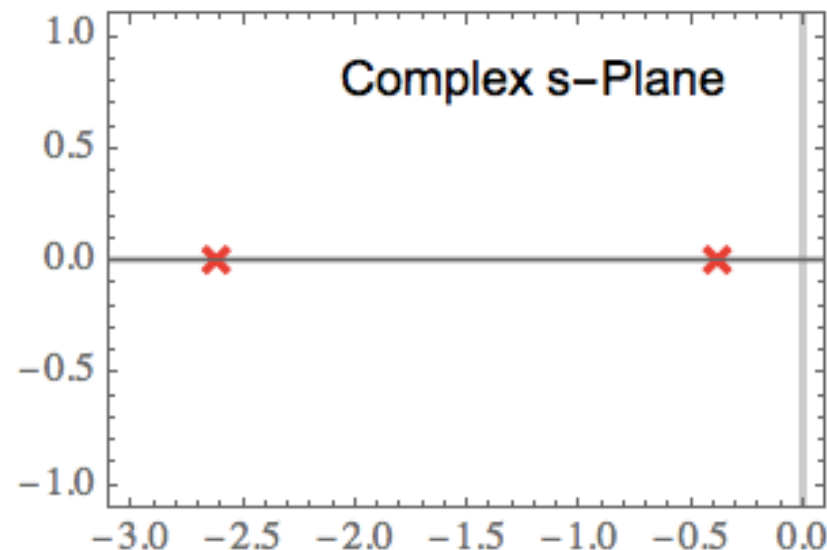- We now have *two different* (still real) poles:




(Their locations depend on R/C of the second stage)



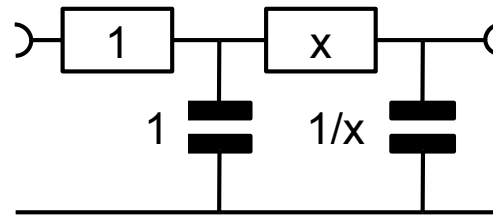
## (Pole Location for Previous Case)

- If we modify R,C of the second stage, keeping  $RC = 1$ , we get



$$H[s] = \frac{x}{s + x + 2sx + s^2 x}$$

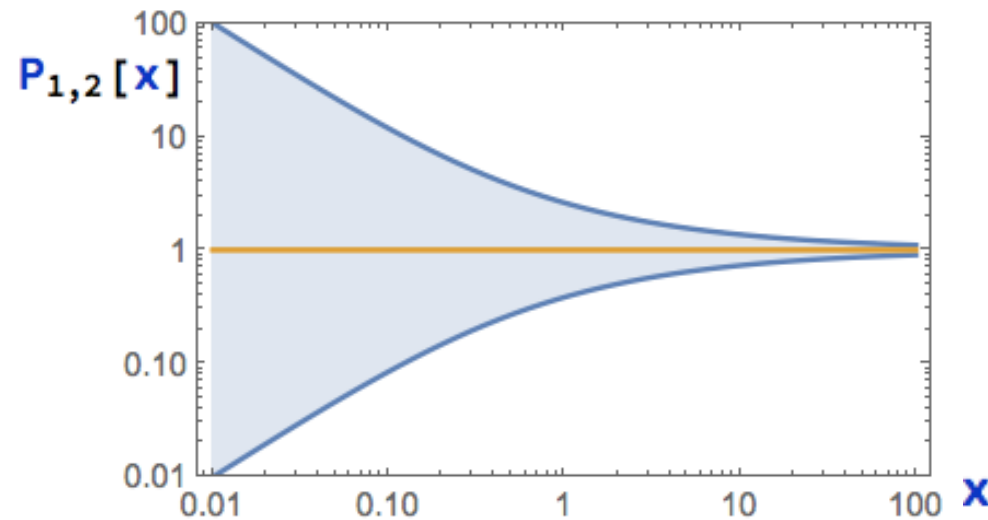- The poles are at  $p_{1,2}[x] = \frac{-1 - 2x \pm \sqrt{1 + 4x}}{2x}$




(when  $x$  is large, the 2<sup>nd</sup> LP does not load the 1<sup>st</sup>)


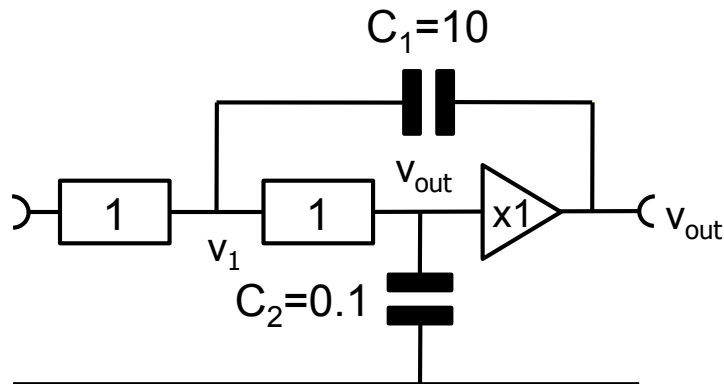
# An Active Filter

- Now consider the following filter ('Sallen and Key')





$$EQ1 = \frac{v_{in} - v_1}{1} = \frac{v_1 - v_{out}}{1} + (v_1 - v_{out}) s 10;$$

$$EQ2 = \frac{v_1 - v_{out}}{1} = v_{out} s \frac{1}{10};$$

$$H[s] = \frac{5}{5 + s + 5 s^2}$$

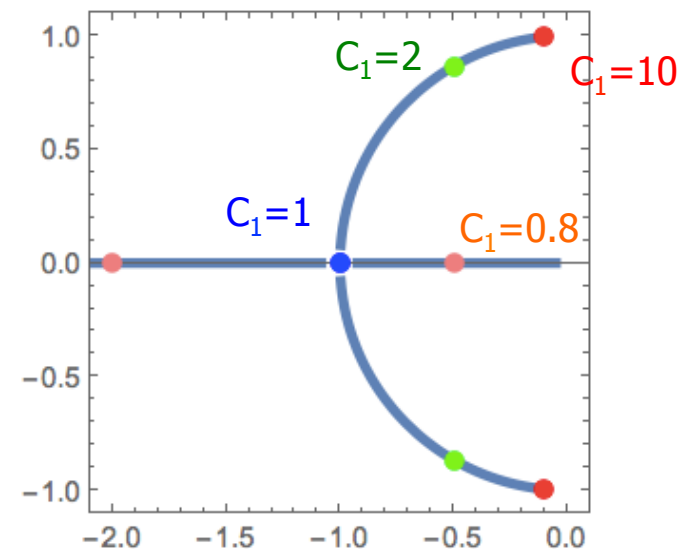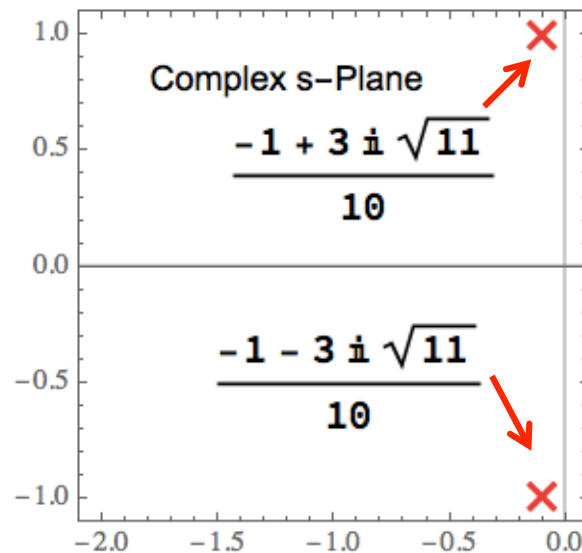
- This transfer function has two **COMPLEX** (conjugate) poles:




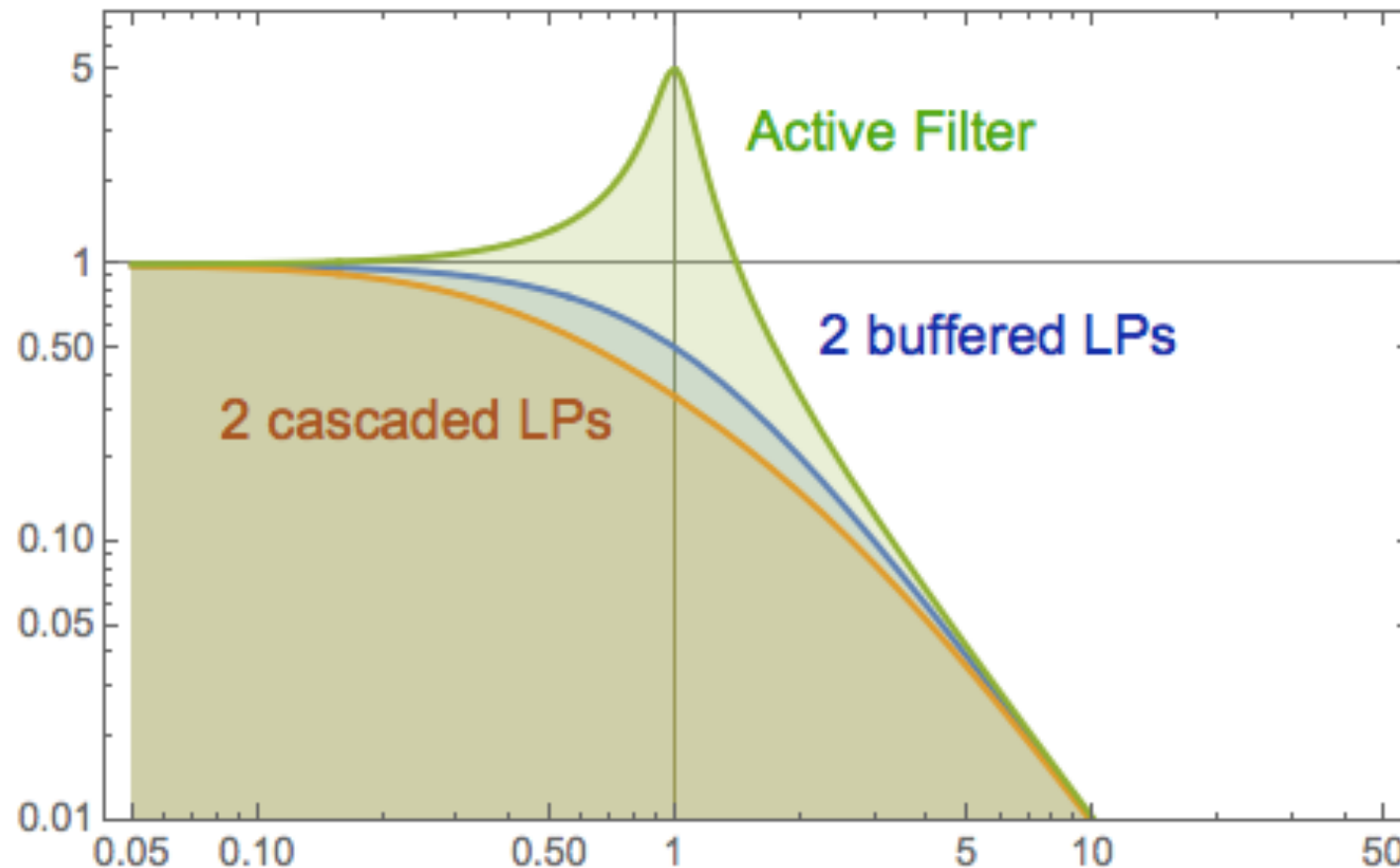
# Bode Plots of 2nd Order Filters

- The active filter has an overshoot (for the values chosen)
- This is typical for complex conjugate poles






# MAKING STEEP FILTERS




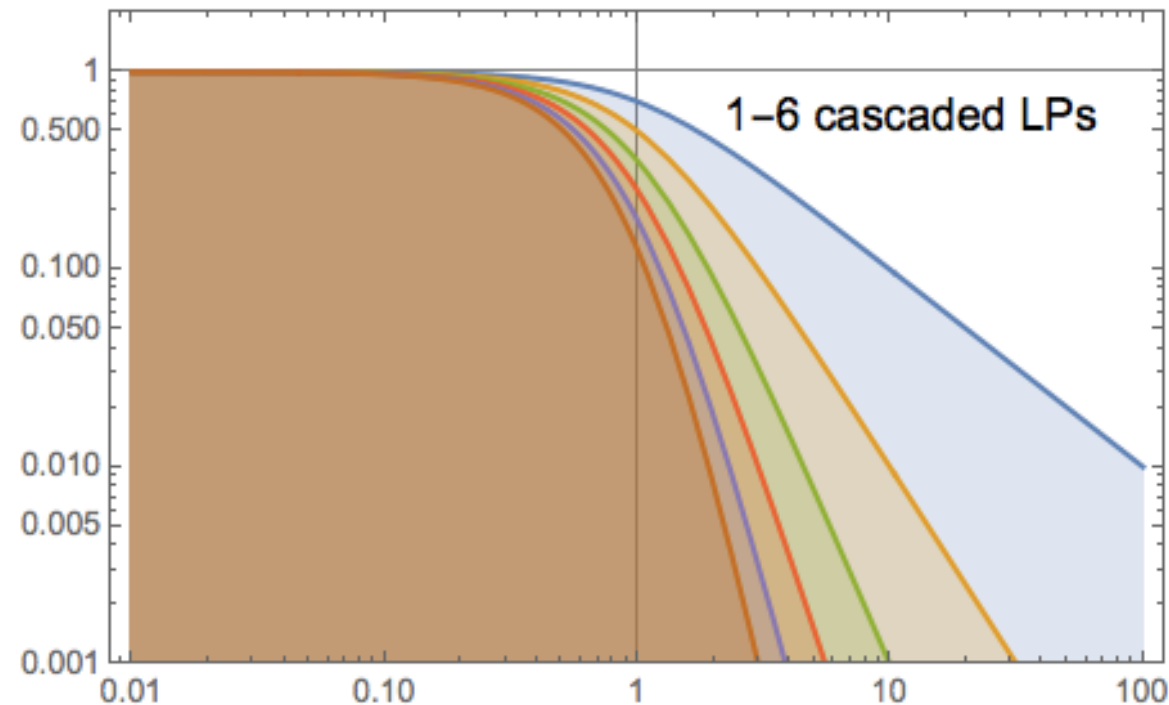
# A Steep Low Pass Filter

- We want to design a higher ( $N^{\text{th}}$ ) order low-pass filter which drops suddenly from **pass band** to **stop band**.
- We know that we roll off with slope  $-N$  at the end (for  $s \rightarrow \infty$ ).




- Simple cascaded LPs attenuate by  $2^{-N/2}$  at the corner
- Can this be improved ?



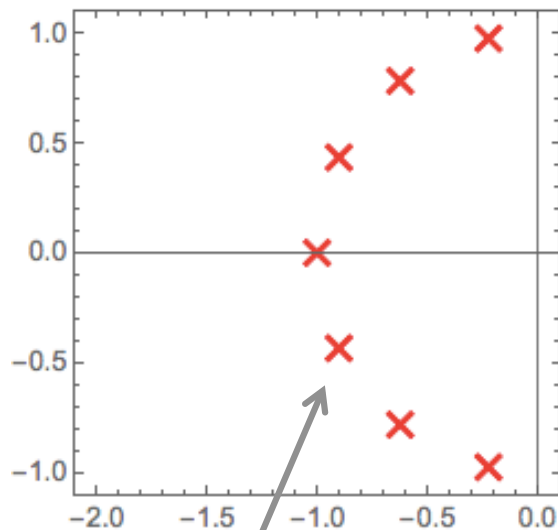
# Choosing the Poles

- The Idea: Use complex poles and adjust them 'somehow'
- 'Butterworth' arranges poles on circle. Here: 7<sup>th</sup> order.



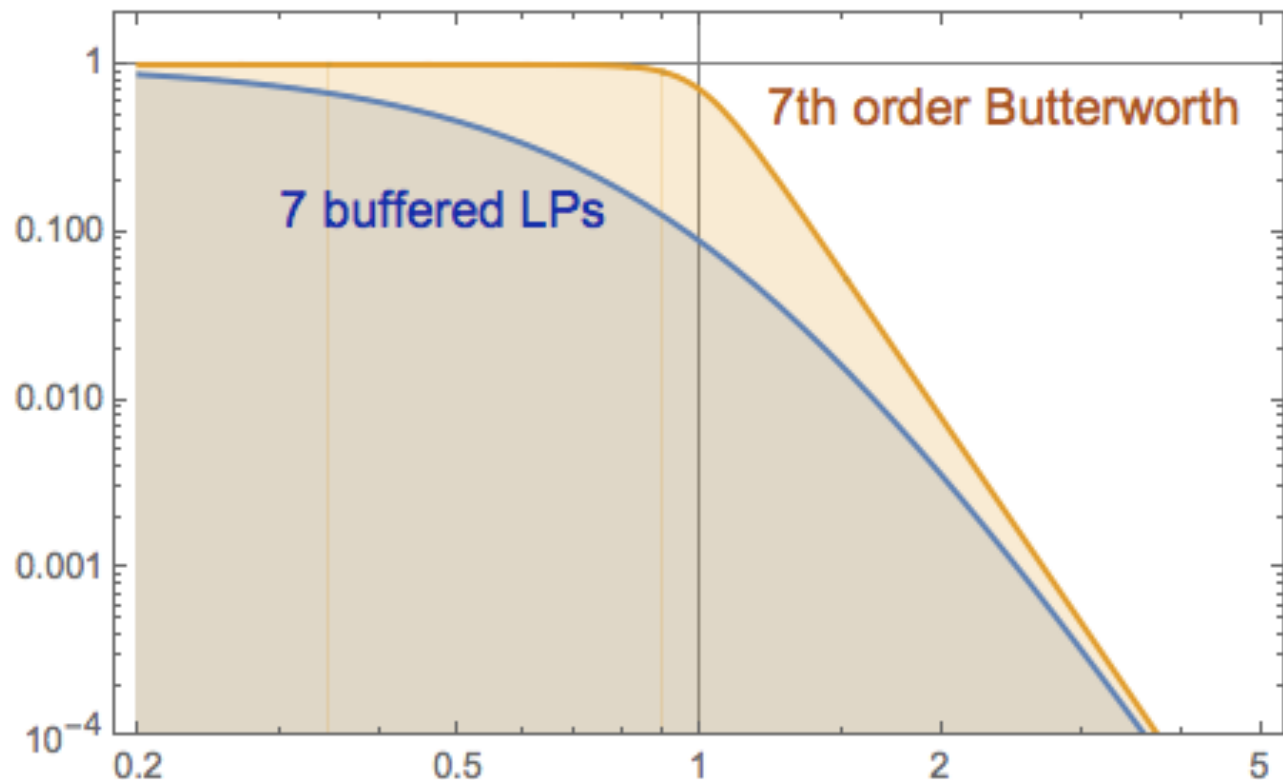It can be shown (easily)  
that poles on a circle have  
same corner frequencies.





- Wow! Butterworth attenuation at the corner is only -3dB !


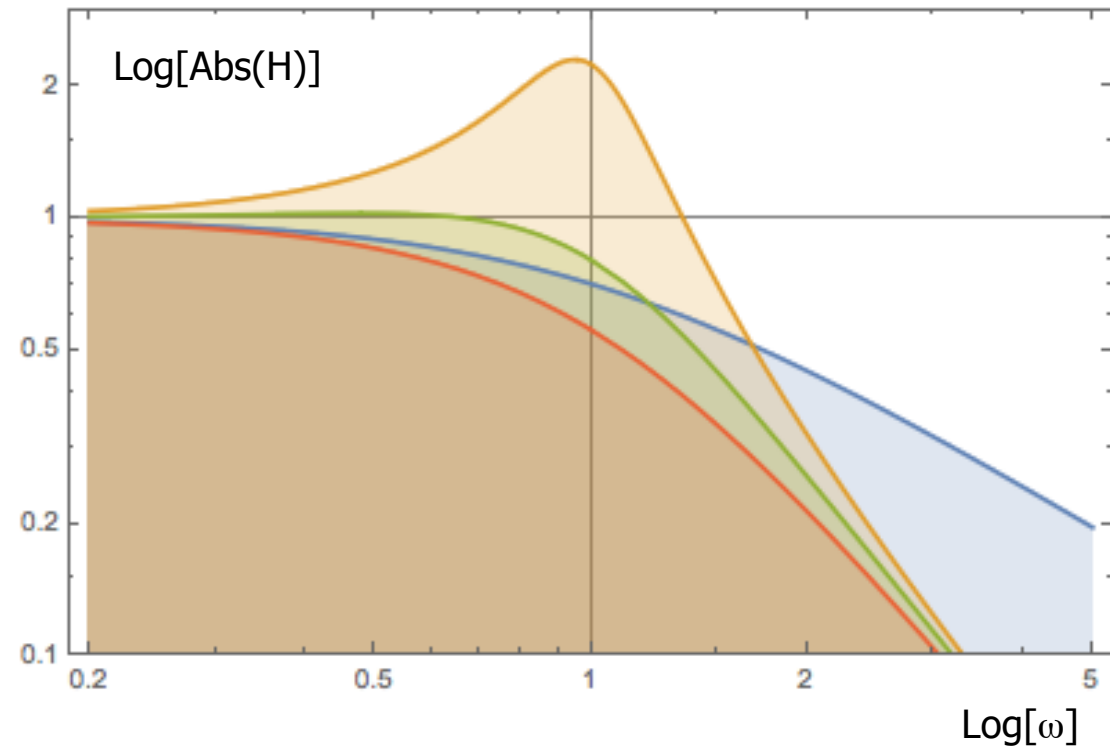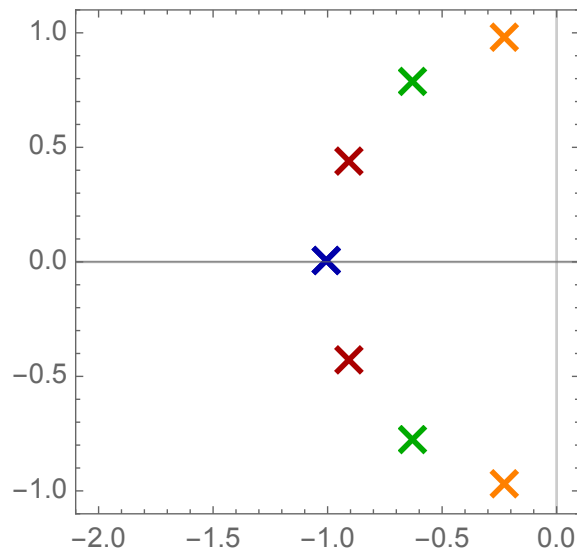
# (Decomposing the Butterworth Filter)


- For  $N=7$ :
  - One real pole (1<sup>st</sup> order, blue)
  - 3 conjugate poles (2<sup>nd</sup> order)




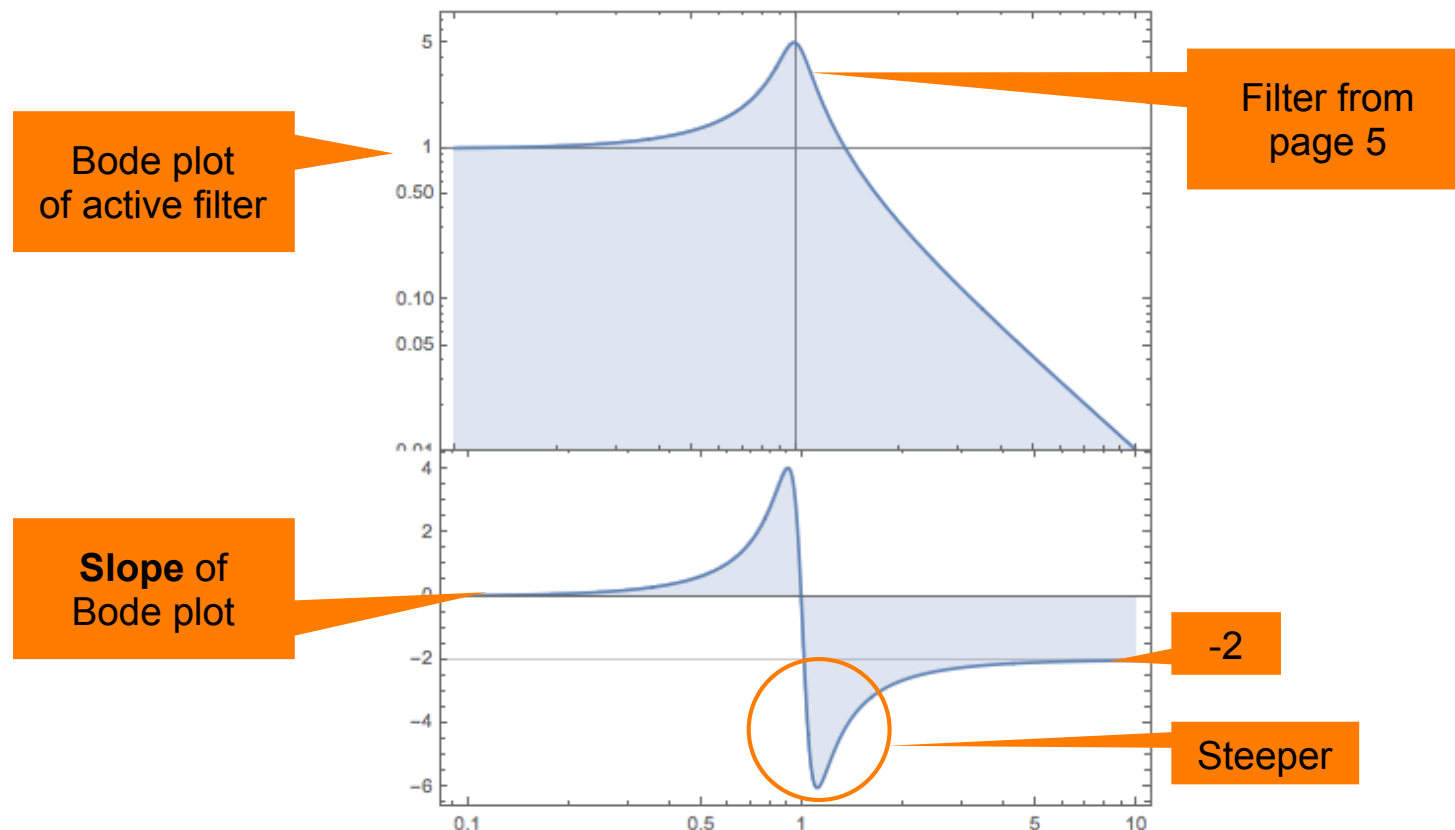
# Even Steeper?

- Remember: For *large* frequencies, we will *always* roll off with  $s^{-N}$  (the order of the filter, i.e. the number of caps)
- But: The 'peaking' for complex poles provides steeper response *close to the bandwidth*:






# Placing the Poles...



- There are obviously MANY possibilities to place the poles...
- Desired filter properties are for instance
  - Flatness/ripple of the response in the pass band
  - Steepness of the drop
  - Ripple in the stop band
  - Response to step signals (overshoots)
  - Phase behavior
- Four main types have evolved:
  - Butterworth: Flat pass band
  - Bessel: No phase shift, no overshoot
  - Chebyshev: Steeper rolloff, but ripple in pass band
  - Elliptic: Even steeper rolloff, but ripple in pass and stop band


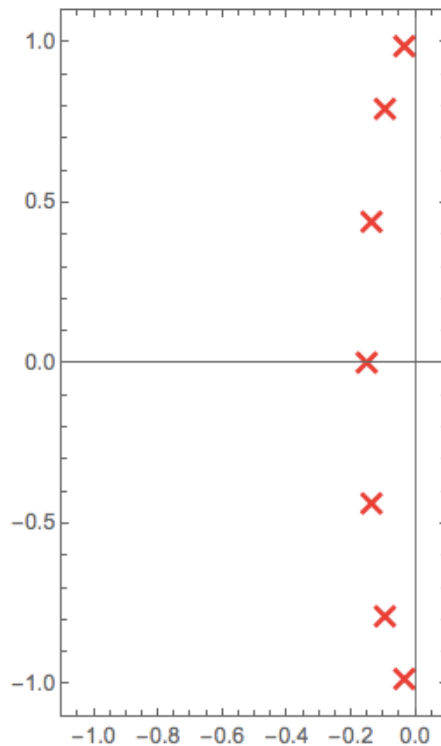
# The Chebyshev Filter (7<sup>th</sup> order)



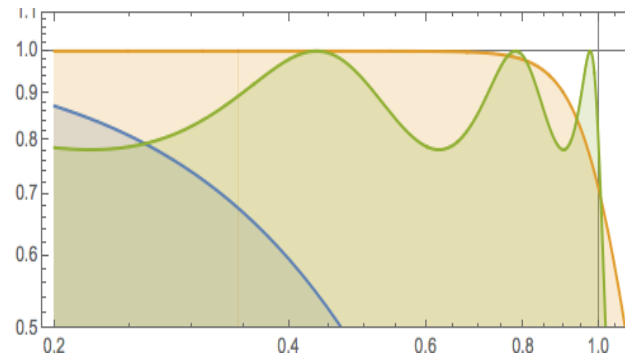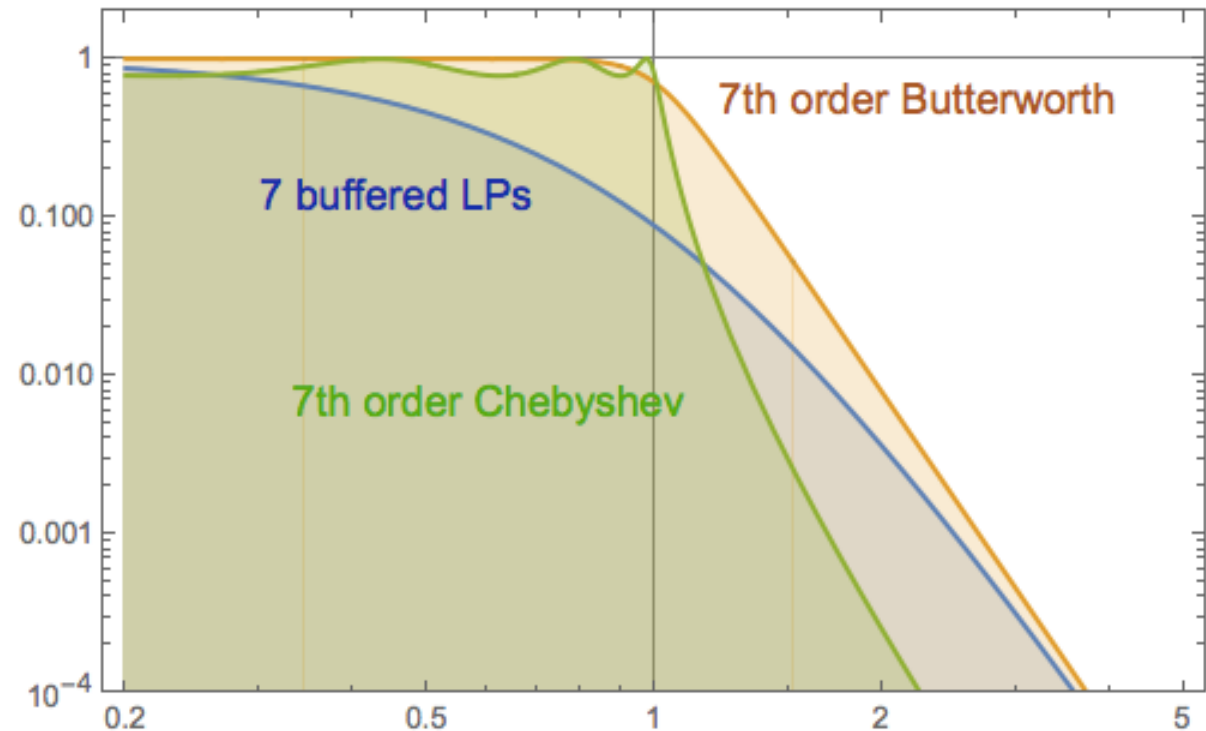Pole location for a 7<sup>th</sup> order Chebyshev filter (there are others, depending on the desired pass band ripple)



Zoom of pass band showing ripple of Chebyshev and flat response of Butterworth