



# Exercise: The MOS Transistor


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg


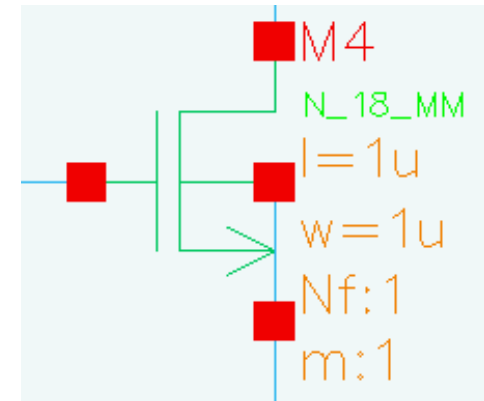
# Exercise 1: NMOS in Linear Region

- Use an *NMOS* transistor of type N\_18\_MM from library UMC\_18\_CMOS with  $W=L=1\mu\text{m}$
- Connect
  - source and bulk to ground
  - the gate to 2 V
- Sweep  $V_{DS}$  from -0.1V to 0.1 V and observe the current
- Extract the resistivity of the channel
- Double *W* or *L* and simulate & extract again.
  - Are the results as expected ? Compare  $W=L=1\mu$  and  $W=L=2\mu$ !
- Now sweep the *gate* voltage from 0.6 V to 2 V. Explain!
- Now sweep the *drain* voltage from 0V to 1V. Verify the saturation point for a few gate voltages.
- What happens if you sweep the drain voltage from -1V on?





## Exercise 2: Transfer Charact. & Transconductance

- For an NMOS of  $W=L=1\mu\text{m}$  with  $V_{BS} = 0$ , keep the drain at 1.8 V and sweep the gate voltage from 0 to 1.8 V. This is the *transfer characteristic* of the MOS.
  - Observe the drain current
  - Plot the square root of the current. Do you find a straight line as expected?
  - Plot the current in log scale. Can you see the sub-threshold region?
  - What is the transconductance at  $V_{GS} = 1\text{V}$  (make a derivative!)?
- Make a parametric sweep changing  $W$  from  $0.24\mu\text{m}$  to  $2\mu\text{m}$ 
  - Is the current proportional to  $W$ ?
- Repeat this for a  $L$ -sweep (start with 180nm)
- Plot the transfer curve for two different values of  $V_{BS}$ , for instance 0 V and -2 V



## Exercise 3: Output Characteristic, Saturation

- Now plot the output characteristic, i.e.  $I_D$  as a function of  $V_{DS}$  for a fixed  $V_{GS}$  (for instance  $V_{GS} = 1.0 \text{ V}$ )
  - Can you see the linear region and the saturated region?
- Extract the output resistance for instance for  $V_{GS}=1.8\text{V}$  and  $V_{DS}=1.8\text{V}$  (derivative!).
- Plot the output characteristic for  $V_{GS} = 0..1.8\text{V}$  in  $0.2\text{V}$  steps
  - Observe how the current changes
  - Observe how the saturation voltage changes
  - Observe how the output resistance changes (Early voltage ?)
- Now use two NMOS with different  $W$  (for instance  $0.5\mu\text{m}$  and  $2\mu\text{m}$ ).
  - Search for gate voltages so that the currents for a given  $V_{DS}$  (for instance for  $1.8 \text{ V}$ ) are similar.
  - Compare the output characteristics & saturation voltages



## Exercise 4: PMOS

- Simulate transfer and output characteristic for a PMOS
  - Note that the source of the transistor is now ,on top‘
  - Gate and drain must be negative with respect to source
  
- Simulate in parallel a NMOS of the same size.
  - Plot the drain current of NMOS and PMOS simultaneously.
  - How big is the difference?