



Exercise: Transfer Functions, Filters

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg




Recommendations

- I strongly recommend to use a mathematical program (Mathematica, Maple, SageMath,..) to solve the exercises
- For transfer functions, inspect each result:
 - What happens for $\omega \rightarrow 0, \infty$?
 - What happens if component values go to 0 or ∞ ?



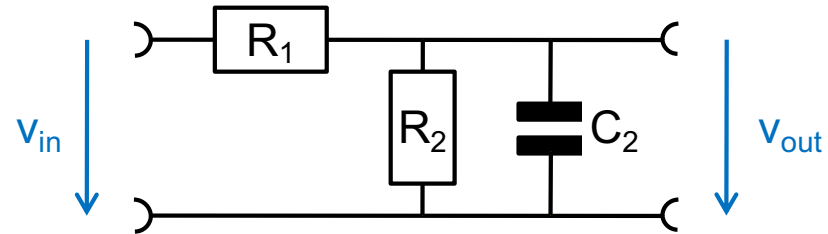Exercise 1

- Derive the Transfer Function of this circuit:




- Use 3 different approaches:
 - Treat the circuit directly (using Kirchhoff's rule)
 - Consider it as a voltage divider of two Impedances. Use R_1 for Z_1 and the parallel connection of R_2 and C_2 for Z_2
 - Replace the (resistive) voltage divider (R_1, R_2) by its Thévenin equivalent and then add the capacitor
- Make a Bode Plot
 - Observe the difference to the normal Low Pass Filter



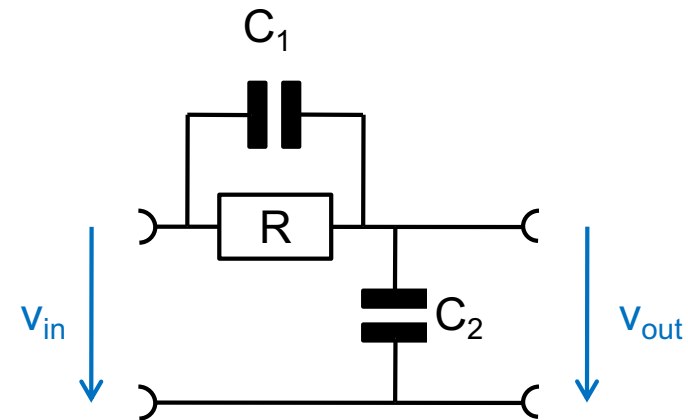Exercise 2

- Analyze the following circuit (simulation & calculation!):




- What is the transfer function ?
- At which frequencies are the 'pole' in the denominator and the 'zero' in the nominator ?
- What are gain and phase for $s \rightarrow 0$ and for $s \rightarrow \infty$? Why?
- What happens for $C_1 \rightarrow 0$, for $R \rightarrow 0$, for $R \rightarrow \infty$? Reasonable?
- Simulate the circuit for $C_1 = C_2 = 10\text{pF}$ and $R = 10\text{ k}\Omega$. Plot gain and phase!
- Chose values so that the circuit attenuates to $1/10$ at high frequencies.
- For fun: At which frequency is phase shift maximal?



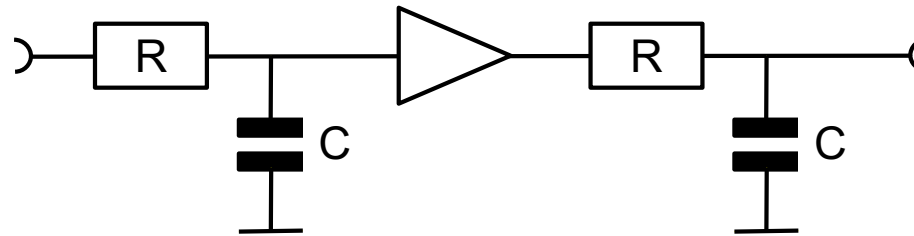Exercise 3: Cascaded Stages

- Consider the following two stage circuit (again):




- The triangle is a (voltage) buffer with infinite input impedance (it does not load the first low-pass) and zero output impedance. For simulation use a vcvs (voltage controlled voltage source) from analogLib with gain 1
- What transfer function do you expect ?
- Simulate the circuit !
- Simulate** a version **without** buffer in the same schematic
- Where are differences ?
- Use a much larger R and correspondingly smaller C in the second low pass.
- Now **calculate** the exact transfer function **without** buffer



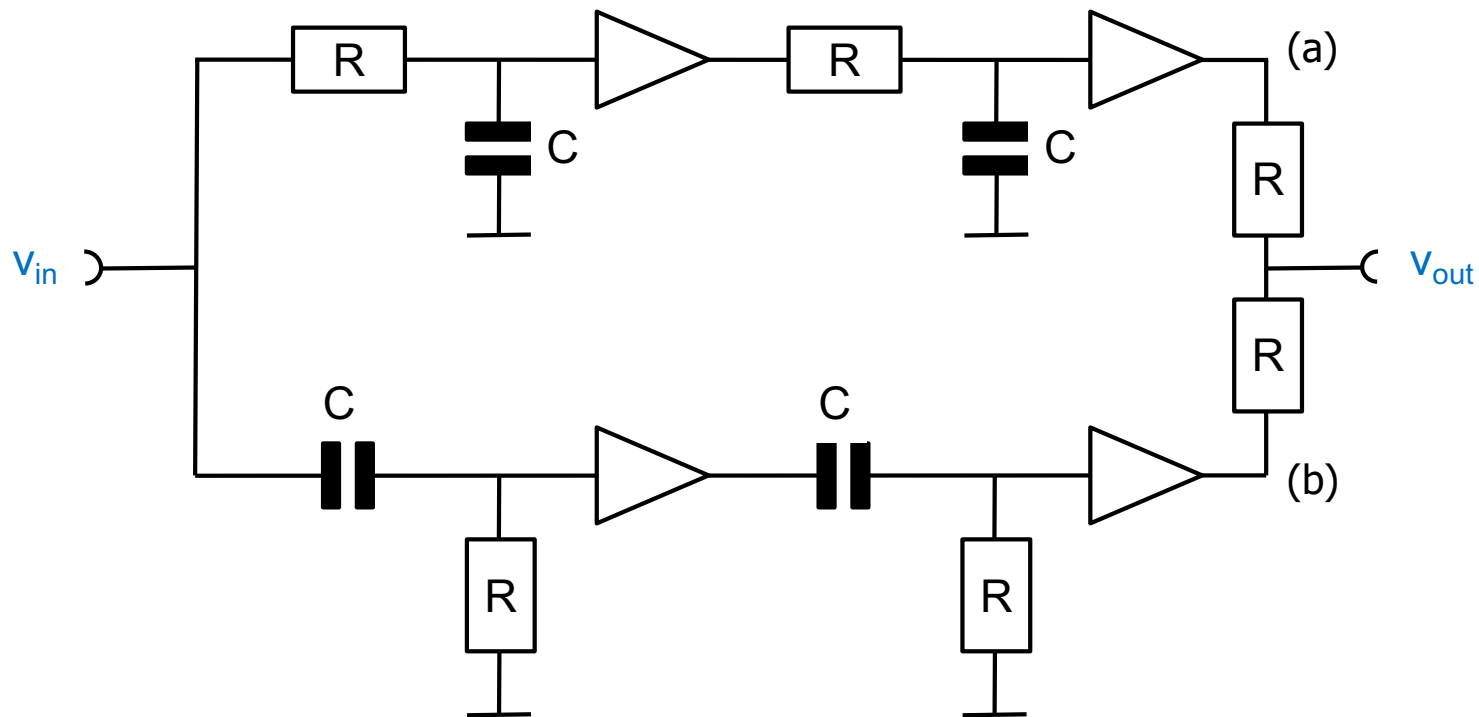Exercise 4: Notch Filter

- Consider the following circuit made of cascaded High- and Low Pass stages:
 - The resistors at the output just add the signals at (a) and (b)




- What is the output signal at the corner frequency?
 - Explain this by comparing amplitudes *and phases* at (a) and (b)



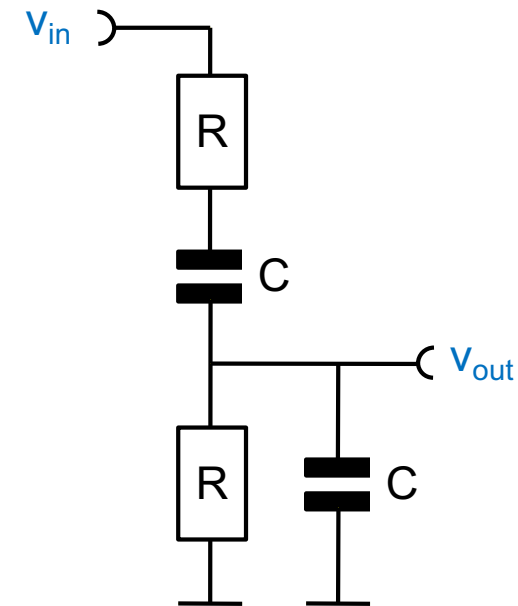Exercise 5: Wien Bridge / Oscillator

- Consider this circuit:
- What is the transfer function?
- What is the magnitude at the center frequency?
- What is the Phase at the center frequency?
- Simulate the circuit for $R=1k$ $C=1n$




- You can use this ‘Wien Bridge’ to make an oscillator:
 - Amplify v_{out} by *exactly* 3 (vcvs !) and feed the signal back to v_{in} .
 - Set an initial condition of 1V (parameter!) for the lower C and start a transient simulation.
 - How does this work?
 - What happens if the gain is not exactly 3 ?





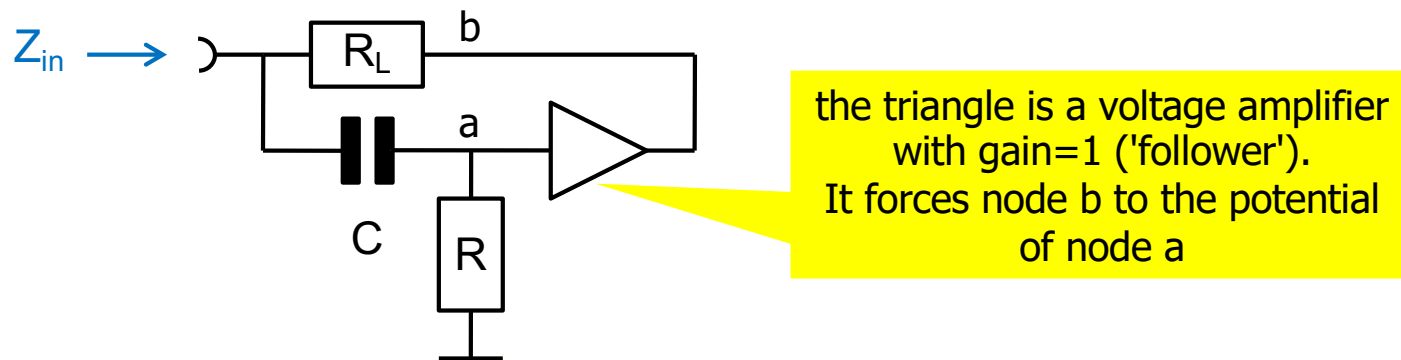Exercise 6: Gyrator (difficult)

- A 'Gyrator' can mimic inductive behaviour, while using only resistors, capacitors and amplifiers
- Consider the following circuit:



- **Calculate** the input impedance $Z_{in} = U_{in}/I_{in}$ of the circuit
 - (Use Kirchhoff's law at the input node and node a)
- For frequencies $< 1/C R_L$, the denominator can be neglected.
- Compare the result to an inductor in series with R_L
- Simulate.
 - Note that R should be larger than R_L (what happens for $R=R_L$?)
 - Plot i_{in} .
 - Add another capacitor in series to produce a resonant circuit.