



Exercise: Making a Steep Filter


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



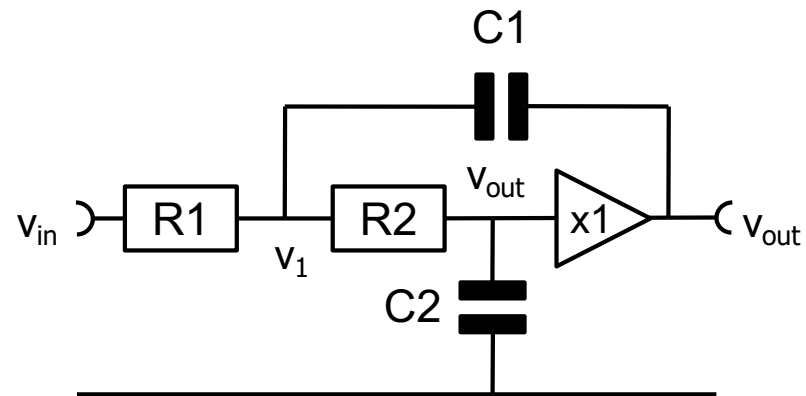Exercise

- Just for fun, we want to design a steep Butterworth Low Pass filter
 - Let the corner frequency be 1 MHz
 - Let's chose order $N=6$
 - Implement it using 'Sallen and Key' stages with $k=1$



- After you have derived component parameters for the 3 filter stages, simulate the result.



Hints

- The poles of a Butterworth filter are placed on the left half circle with equal angles (see slide ‘choosing the poles’ in the lecture), i.e. with $d\phi = \pi/N$ and $r = \omega$.
- Each complex-conjugate pair of poles is handled by one 2nd order ‘Sallen and Key’ filter. So we need $N/2$ stages.
- Each filter (with dc gain 1) has a general transfer function of $1/(1+s/p_a)(1+s/p_b) = 1/(1+as+bs^2)$ where p_a and p_b are the two complex conjugate poles.



Steps

■ Step1:

- Given a pole pair, we want to know the transfer function
- Write $p_a = r (\sin(\phi)+i \cos(\phi))$, $p_b = \dots$
- From p_a and p_b , calculate a , b

■ Step2:

- Our filter has 4 parameters (R_1, R_2, C_1, C_2), but its behaviour is described by 2 (e.g. corner, peaking), there are several ways to implement it. For example:
- Set $R_1=R_2=R$ and $C_2 = 1\text{nF}$. This leaves us with 2 parameters
- Derive the transfer function of a filter stage

■ Step3:

- For a given (r, ϕ) and thus (a, b) , derive R and C_1 by equating the coefficients of s and s^2 .

■ Step 4:

- Derive (r, ϕ) for each pole-pair of the Butterworth and get R and C_1 for that filter stage.



Step 1

`$Assumptions = r > 0 && φ ∈ Reals; (* needed for Conjugate[] *)`

Assume we have a complex conjugate pole pair (p_a, p_b) with radius r and angles $\pm \phi$:

`In[8]:= p_a = r (Cos[φ] + i Sin[φ]); p_b = Conjugate[p_a] // Simplify; {p_a, p_b}`

`Out[8]= {r (Cos[φ] + i Sin[φ]), r (Cos[φ] - i Sin[φ])}`

`Den = (1 + $\frac{s}{p_a}$) (1 + $\frac{s}{p_b}$) // Simplify (* This is the denominator of the TF *)`

`Out[11]= $\frac{r^2 + s^2 + 2 r s \text{Cos}[\phi]}{r^2}$`

s

s²

`In[13]:= {a, b} = Table[SeriesCoefficient[Den, {s, 0, k}], {k, 1, 2}]`


`Out[13]= $\left\{ \frac{2 \text{Cos}[\phi]}{r}, \frac{1}{r^2} \right\}$`

This function finds a Taylor coefficient of function 'Den'. It assumes variable s, expands at 0 and looks for degree k



Step 2a

General Derivation of H[s]:

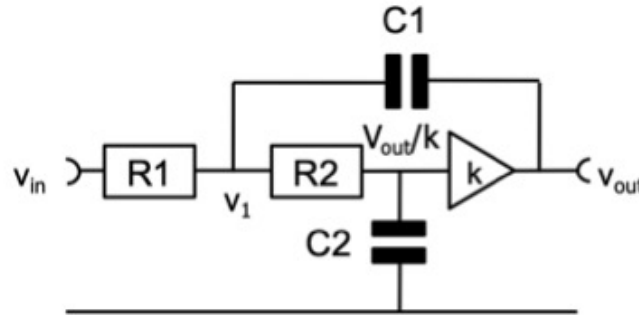

$$\text{In[39]:= EQ1} = \frac{v_{in} - v_1}{R1} == \frac{v_1 - v_2}{R2} + (v_1 - v_{out}) s C1;$$

$$\text{EQ2} = \frac{v_1 - v_2}{R2} == v_2 s C2;$$

$$\text{EQ3} = v_{out} == k v_2;$$

`In[42]:= Eliminate[{EQ1, EQ2, EQ3}, {v1, v2}] // Simplify`

`Out[42]= k v_in == (1 + C2 (R1 + R2) s + C1 R1 s (1 - k + C2 R2 s)) v_out`

`In[43]:= Solve[%, v_out] // First`

$$\text{Out[43]= } \left\{ v_{out} \rightarrow - \frac{k v_{in}}{-1 - C1 R1 s - C2 R1 s + C1 k R1 s - C2 R2 s - C1 C2 R1 R2 s^2} \right\}$$

`In[44]:= H[s_] = v_out/v_in /. % /. k -> 1 // Simplify`

$$\text{Out[44]= } \frac{1}{1 + C2 s (R1 + R2 + C1 R1 R2 s)}$$



Step 2b and 3

- Now fix $R1=R2=RR$, $C2 = 1nF$ and $C1=CC$
 - For some reason using $C1$ etc. in Mathematica causes trouble.. I have not yet found out why. So I use RR and CC

```
In[127]:= Coef = Table[SeriesCoefficient[ $\frac{1}{H[s] /. \{R1 \rightarrow RR, R2 \rightarrow RR, c2 \rightarrow 10^{-9}, c1 \rightarrow CC\}}$ , {s, 0, kk}], {kk, 1, 2}]
```

```
Out[127]= { $\frac{RR}{500\,000\,000}$ ,  $\frac{CC\,RR^2}{1\,000\,000\,000}$ }
```

```
In[128]:= {EQA, EQB} = {Coef[[1]] == a, Coef[[2]] == b} // Simplify
```

```
Out[128]= {r RR == 1\,000\,000\,000 Cos[\phi], CC r^2 RR^2 == 1\,000\,000\,000}
```

```
In[166]:= Solve[{EQA, EQB}, {RR, CC}] // First
```

```
Out[166]= {RR ->  $\frac{1\,000\,000\,000\,Cos[\phi]}{r}$ , CC ->  $\frac{Sec[\phi]^2}{1\,000\,000\,000}$ }
```

```
In[167]:= {Rsol, Csol} = {RR, CC} /. %
```

```
Out[167]= { $\frac{1\,000\,000\,000\,Cos[\phi]}{r}$ ,  $\frac{Sec[\phi]^2}{1\,000\,000\,000}$ }
```

Fix components in $H[s]$, take denominator, find coefficients of s and s^2

Equate these coefficients with a and b
This gives 2 equations EQA and EQB

Solve the 2 equations for RR, CC
(R and $CC1$ in the exercise)

For later: Assign the result to $Rsol$ and $Csol$




Step 4

This is the angle for one of the two partners of a pair.

```
In[77]:= ORDER = 6;
```
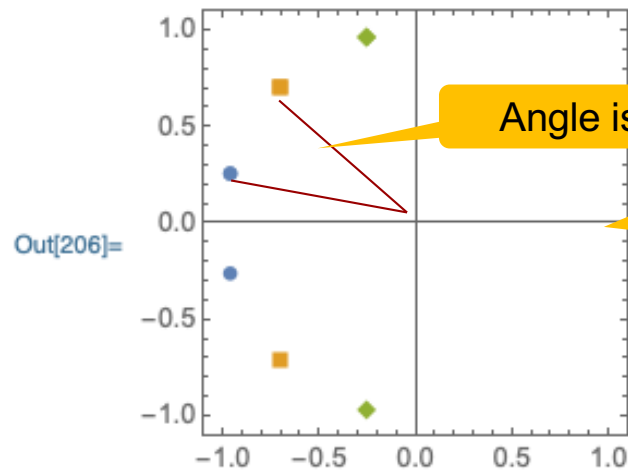
```
In[206]:= ComplexListPlot[Table[-{pa, pb} /. {r → 1, φ → (2 k - 1)  $\frac{\pi}{2 \text{ ORDER}}$ }, {k, 1,  $\frac{\text{ORDER}}{2}}$ ],  
PlotRange → {{-1.1, 1.1}, {-1.1, 1.1}},  
AspectRatio → 1, Frame → True, ImageSize → Small, PlotMarkers → Automatic]
```



Angle is π/ORDER

Illustrate again where the poles are (for $r=1$)

Finally we get Rsol and Csol for the 3 stages!


```
In[207]:= Table[{Rsol,  $\frac{\text{Cisol}}{nF}$ } /. {r →  $2 \pi 10^6$ , φ → (2 k - 1)  $\frac{\pi}{2 \text{ ORDER}}$ }, {k, 1,  $\frac{\text{ORDER}}{2}}$ ] // N
```

```
Out[207]:= {{153.732, 1.0718}, {112.54, 2.}, {41.1923, 14.9282}}
```




Simulation

■ Schematic:

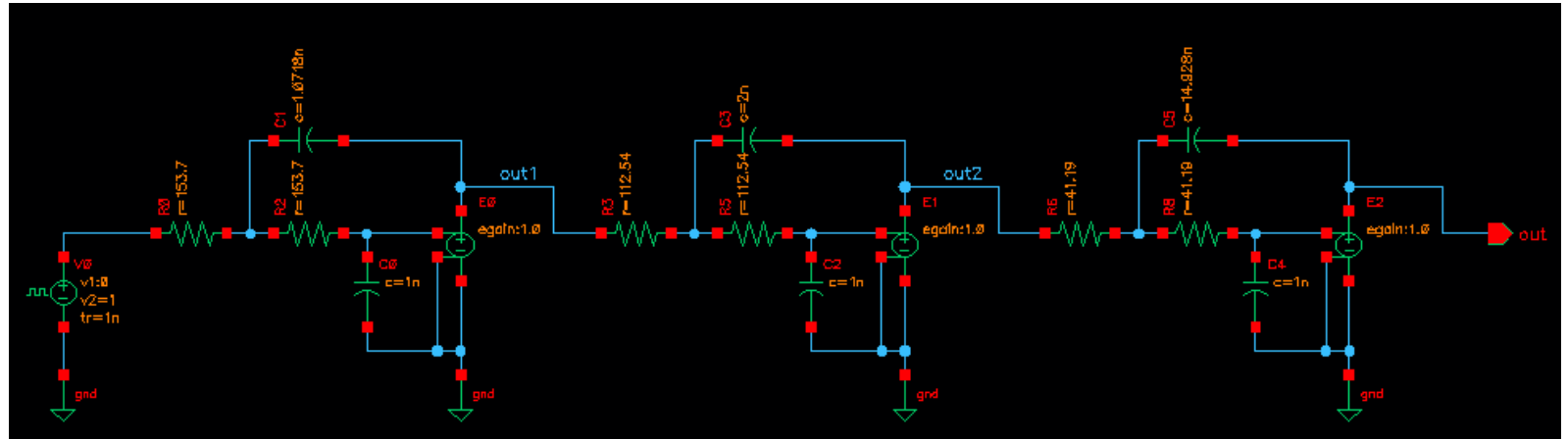

■ AC Sweep:

