



Exercise: Current Mirrors


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Exercise 1: Dynamic Regulation


- Draw a diode connected NMOS
 - Connect a large ,extra' capacitance to the gate (say, 1 pF) with an *initial condition* of 0 V
 - Use a 'simple' MOS model
 - Set the initial condition ('IC') in the properties of the capacitor
 - Send a small current I_{in} (1 μ A) into the ,diode'
 - Perform a transient simulation
 - Estimate / Calculate a reasonable max. time!
 - Observe the Input = Gate = Drain Voltage
-
- Use different initial conditions (0...1.8V, Parametric sweep!)
 - Understand how the equilibrium point is reached!
 - Vary I_{in} !

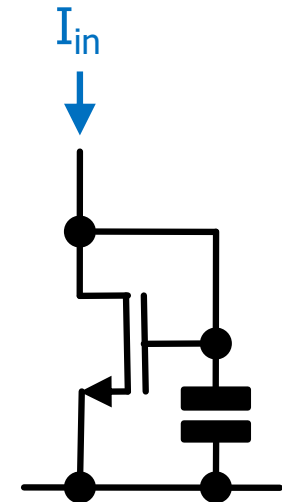



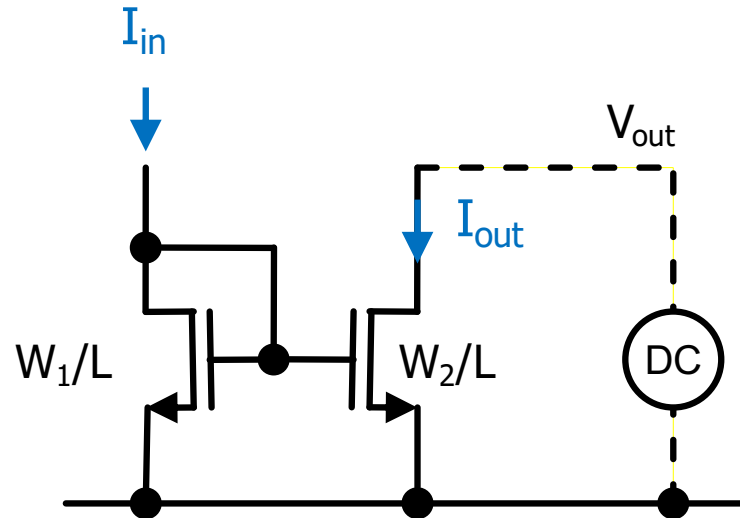Exercise 2: A First Mirror

- Draw the following *current mirror*, with $W_1 = W_2 = 1\mu\text{m}$.
Use for instance $L = 0.5\mu\text{m}$ and $I_{\text{in}} = 10\mu\text{A}$



- Sweep the output voltage V_{out} and observe the current I_{out} .
 - When is $I_{\text{out}} = I_{\text{in}}$ *exactly*? Why?
 - Try another input current!
 - Change W_2 !
- For fixed I_{in} , W_1, W_2 , vary L (same in both MOS).
 - Explain what you see!



Exercise 3: A Better Mirror


- The output current varies with V_{out} (i.e. the output resistance is not infinite) due to the Early Effect in M2.

- Try the following circuit:

- Connect bulk and source in all MOS
- Start with $V_C = 1.2V$
- Use $I_{in} = 1\mu A$

- Sweep V_{out}

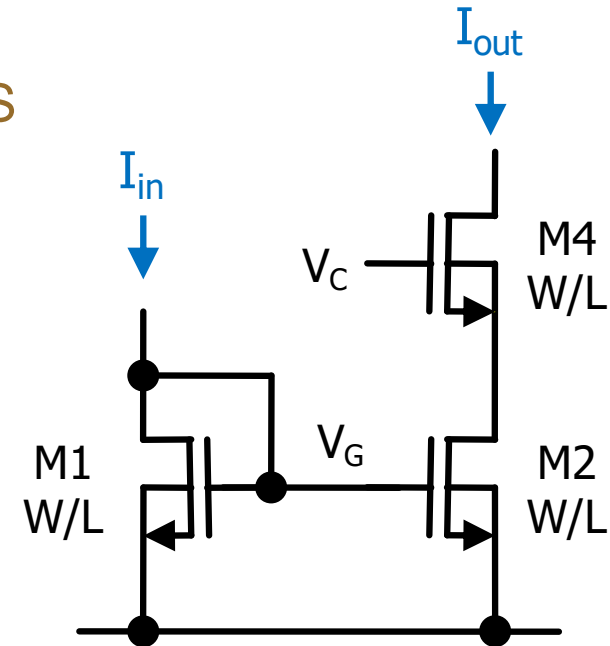- How is the output resistance now?
(You may simulate the 'simple' mirror of the previous exercise in parallel for comparison)



- *Calculate* the small signal output resistance!

- You only need to consider M2 and M4 (because V_G is constant)


- Vary V_C (from 0V to 1.8V) and see what happens

- What is the 'ideal' V_C ?



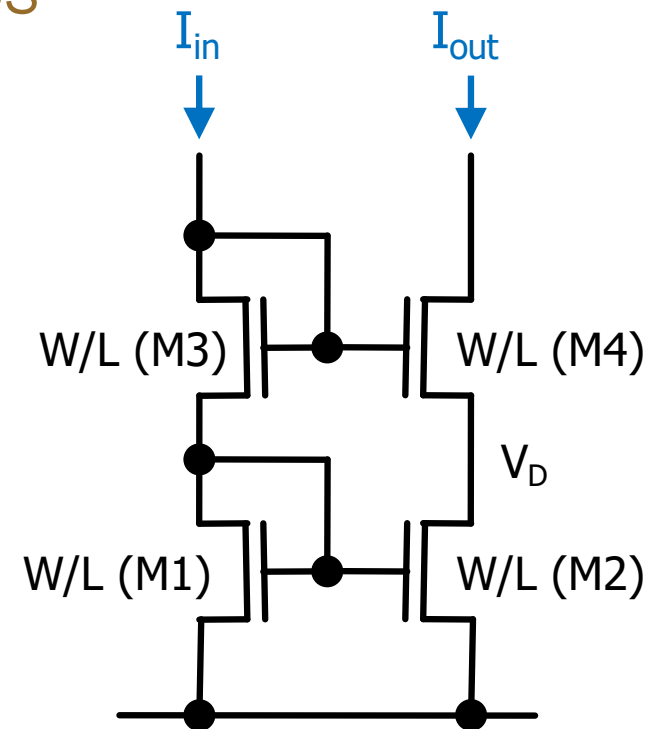Exercise 4: A Mirror with Better Matching

- Unfortunately, the previous circuit does NOT reproduce I_{in} exactly. Why?
- Try this circuit (which does not need V_C and more):
 - Connect bulk and source in each MOS
 - It is called the ,stacked mirror‘
- Sweep V_{out}
 - Do currents match?
 - What is r_{out} ?
 - Where is the saturation ?




- What is the drain voltage V_D of M2? Is that optimal?



Exercise 5: The Low Voltage Mirror


- In the stacked mirror of the previous exercise, the drain voltage V_D of the current source M2 is fixed by the diode connection of M1.
- This is simple, but provides a *too high* voltage (by $\sim V_T$!)
- The following circuit connects the diode differently:
 - Understand that the gate voltage V_G still stabilizes to the 'correct' level!
 - We now need to find V_C
 - Sweep V_C from 0.4 to 1.4V in steps of 0.2V
 - What is a good choice?
 - Why do very low voltages fail (check V_G !)
 - What happens at high voltages? Why? (this is tricky to understand... Look at V_{D1} ...)
 - Note that the 'best' V_C depends in I_{in}

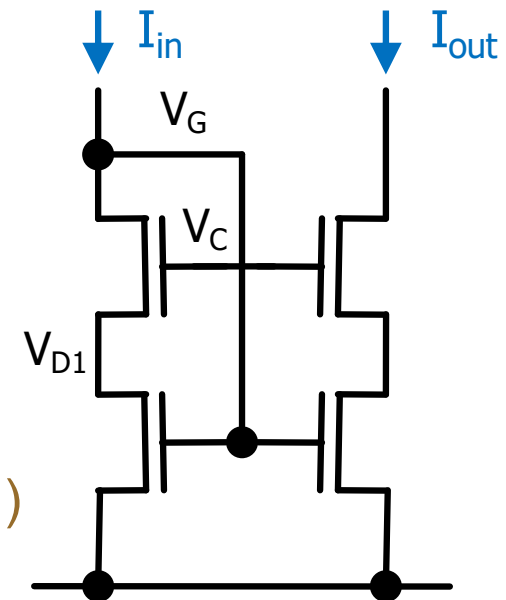



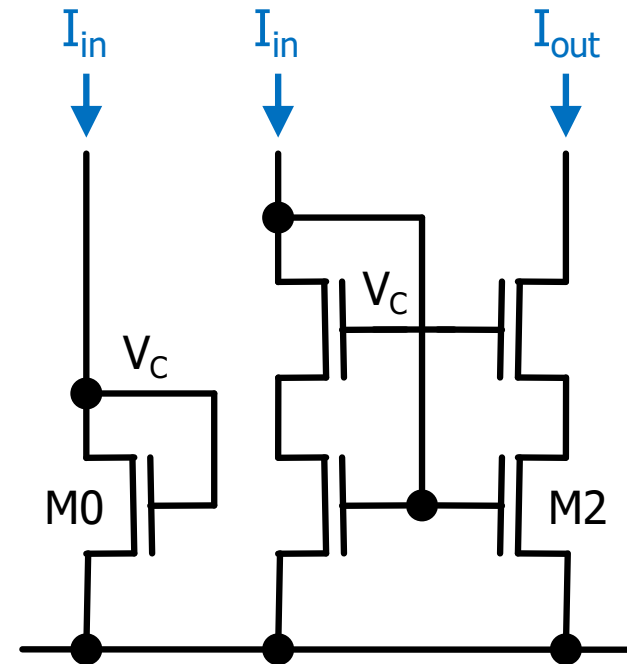Exercise 6: The Low Voltage Mirror

- The required optimal cascode voltage V_C can be generated *automatically* by a diode connected MOS M0 with different geometry than the others:
 $(W/L)_0 = k (W/L)_{\text{others}}$
- We assume that we have a second input current I_{in} available (both I_{in} s are equal)



- Calculate k so that M2 is just saturated.
 - Use the *large signal* model in strong inversion with no Early effect
- Simulate the circuit



Exercise 7: An *Even Better* Mirror

- The key trick is obviously to keep the drain voltage of M2 very constant irrespective of the output voltage.
- This can be done with an active circuit (with an amplifier):
 - Amp amplifies the difference of the two input voltages by A_0
 - Where is the positive/negative input for stable operation?
 - Simulate the circuit. Use a voltage controlled voltage source vcvs from the analogLib for Amp with $A_0=1000$

- *Calculate* the output resistance!

- This topology is called the *Regulated Mirror*

