



Exercise: Current Mirrors


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Exercise 1: Dynamic Regulation


- Draw a diode connected NMOS
 - Connect a large ,extra' capacitance to the gate (say, 1 pF) with an *initial condition* of 0 V
 - Use a 'simple' MOS model
 - Set the initial condition ('IC') in the properties of the capacitor
 - Send a small current I_{in} (1 μ A) into the ,diode'
 - Perform a transient simulation
 - Estimate / Calculate a reasonable max. time!
 - Observe the Input = Gate = Drain Voltage
-
- Use different initial conditions (0...1.8V, Parametric sweep!)
 - Understand how the equilibrium point is reached!
 - Vary I_{in} !

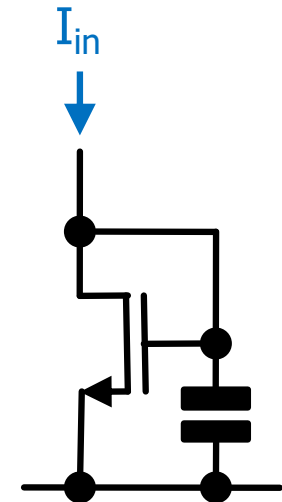



Solution 1


- The ramping slope us $dU/dt = I/C = 1\mu/1p=1M$ (V/s), or $1V / \mu s \rightarrow$ simulate $1 \mu s$

 



Solution 1


- When I_{in} is changed, the gate settles to another voltage:

 



 Exercise 2: A First Mirror


- Draw the following *current mirror*, with $W_1 = W_2 = 1\mu\text{m}$. Use for instance $L = 0.5\mu\text{m}$ and $I_{\text{in}} = 10\mu\text{A}$



- Sweep the output voltage V_{out} and observe the current I_{out} .
 - When is $I_{\text{out}} = I_{\text{in}}$ *exactly*? Why?
 - Try another input current!
 - Change W_2 !
- For fixed I_{in} , W_1, W_2 , vary L (same in both MOS).
 - Explain what you see!



Solution 2

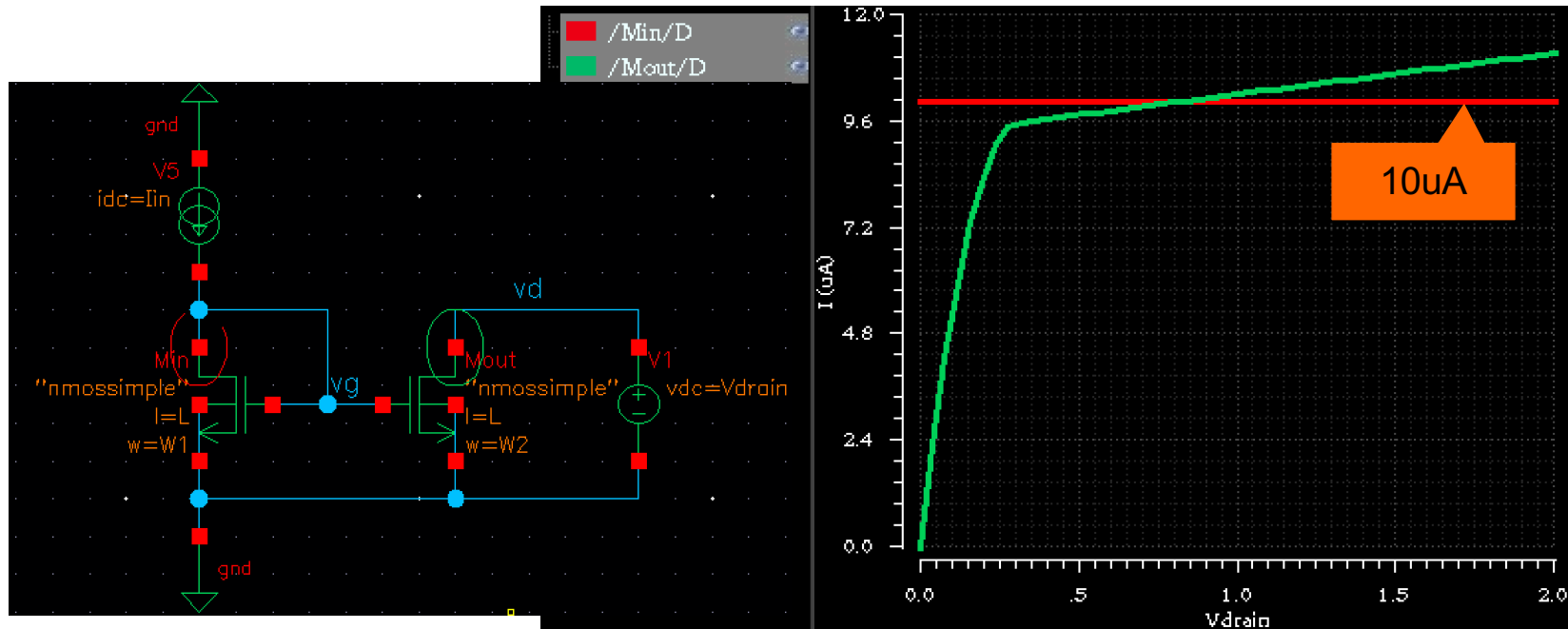


- Currents are equal when Drain voltages are equal, i.e. when $V_{out} = V_g$ (this depends on I_{in})
- When $W2$ is increased, current scales up



Solution 2

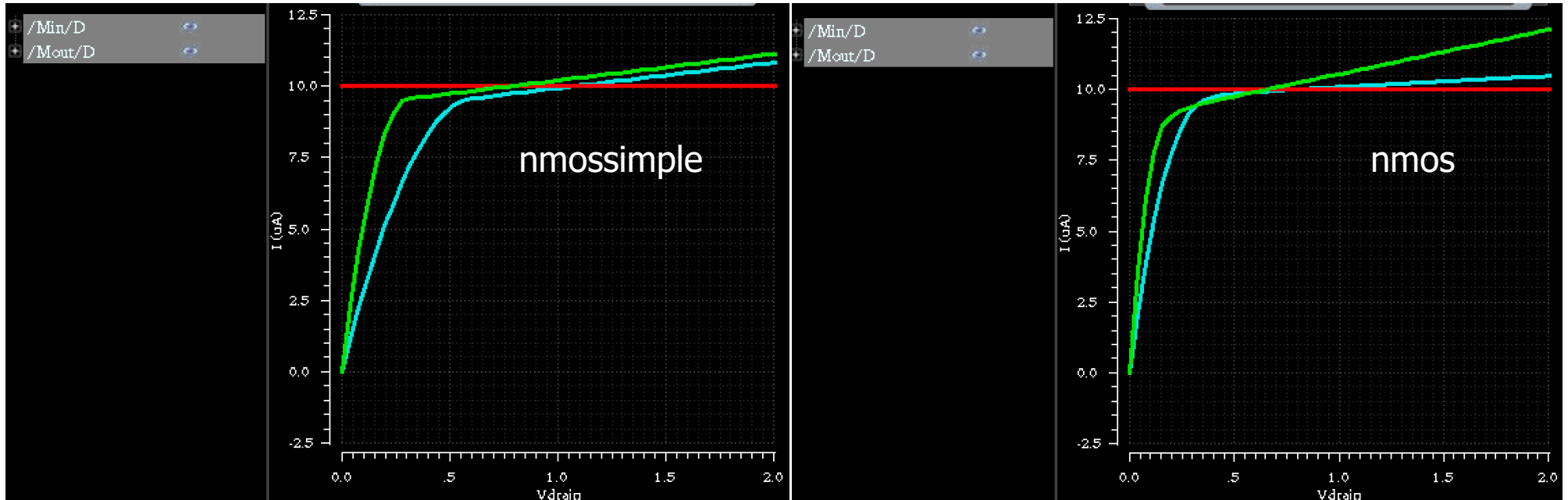- When varying L with `nmossimple`, we get (left):




- The saturation point changes, as expected, but not the slope: The simple model does not take L into account!
- Using model 'nmos', we see the increase in output resistance with longer L (right)



Exercise 3: A Better Mirror


- The output current varies with V_{out} (i.e. the output resistance is not infinite) due to the Early Effect in M2.
- Try the following circuit:
 - Connect bulk and source in all MOS
 - Start with $V_C = 1.2V$
 - Use $I_{in} = 1\mu A$
- Sweep V_{out}
 - How is the output resistance now?
(You may simulate the 'simple' mirror of the previous exercise in parallel for comparison)
- *Calculate* the small signal output resistance!
 - You only need to consider M2 and M4 (because V_G is constant)
- Vary V_C (from 0V to 1.8V) and see what happens
 - What is the 'ideal' V_C ?

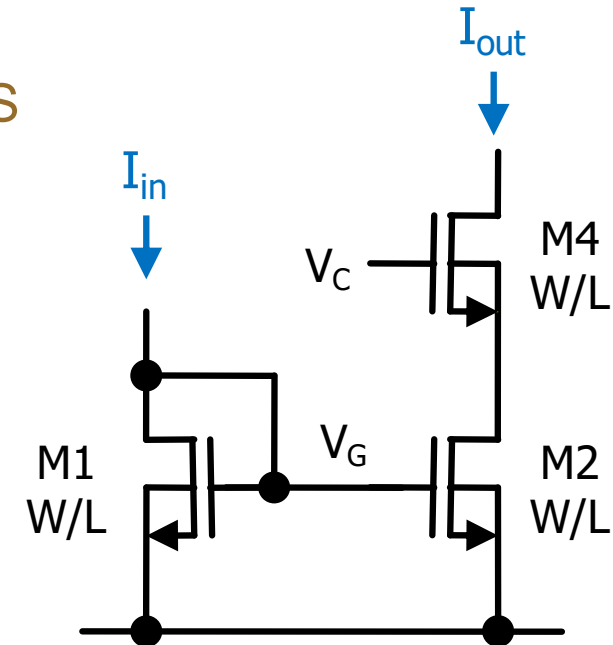



Solution 3: Output Resistance of Cascode Mirror

 - Small signal analysis (for simulation, see lecture slides)
 - We only need to consider the output part
 - Fixed voltages are equivalent to ground
 - Current source of M1 delivers no current ($V_{GS} = \text{fix}$)



- Current sum at middle node:


$$\bullet \quad i_{\text{out}} = (v_{\text{out}} - v_d)/r_{\text{ds}2} - g_{\text{m}2} v_d = v_d / r_{\text{ds}1}$$

$$\rightarrow r_{\text{out}} = r_{\text{ds}1} + r_{\text{ds}2} + g_{\text{m}2} r_{\text{ds}1} r_{\text{ds}2} \rightarrow r_{\text{out}} \cong r_{\text{ds}1} \times (g_{\text{m}2} r_{\text{ds}2})$$



Solution 3: Simulation

- nmos model, All W/L = 1u/0.3u

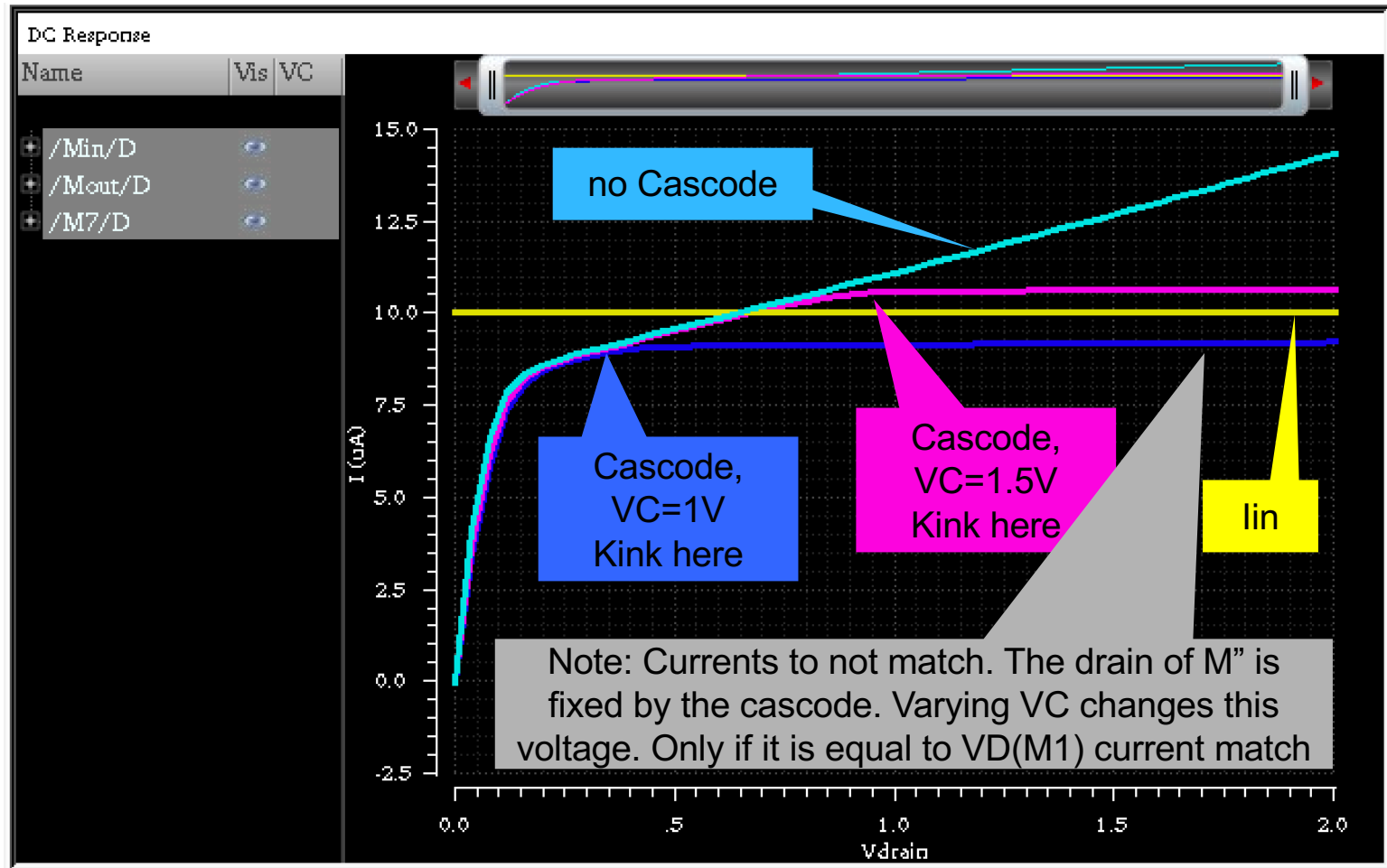


- VC is 'ideal' if the onset of cascode action (the kink) is just above the saturation voltage of M2



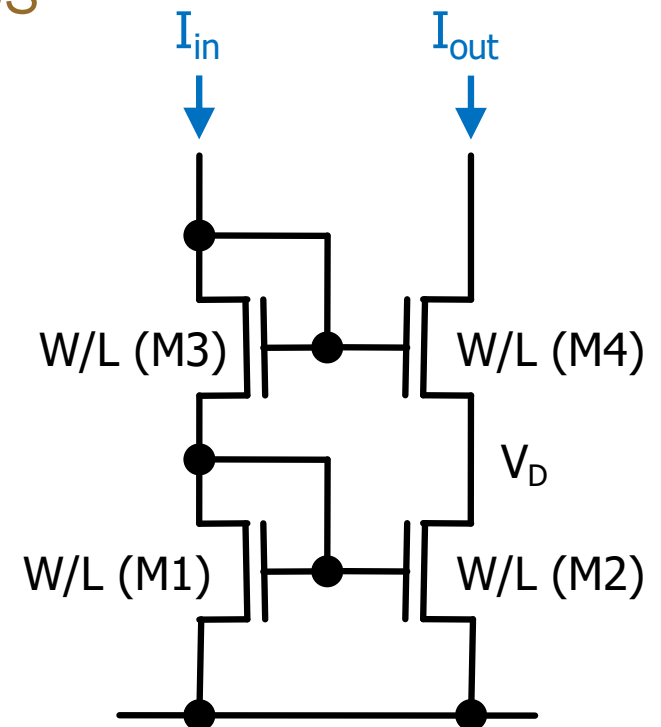Exercise 4: A Mirror with Better Matching

- Unfortunately, the previous circuit does NOT reproduce I_{in} exactly. Why?
- Try this circuit (which does not need V_C and more):
 - Connect bulk and source in each MOS
 - It is called the ,stacked mirror‘
- Sweep V_{out}
 - Do currents match?
 - What is r_{out} ?
 - Where is the saturation ?





- What is the drain voltage V_D of M2? Is that optimal?




Solution 4

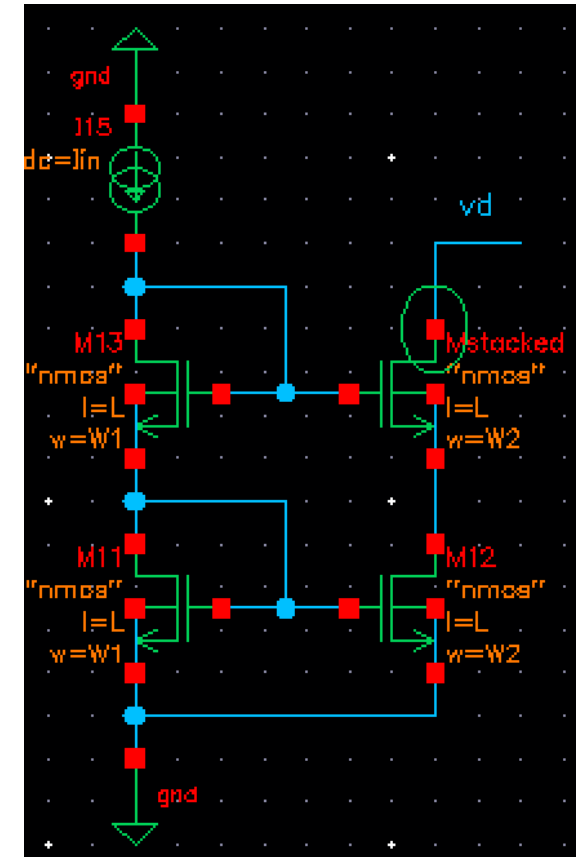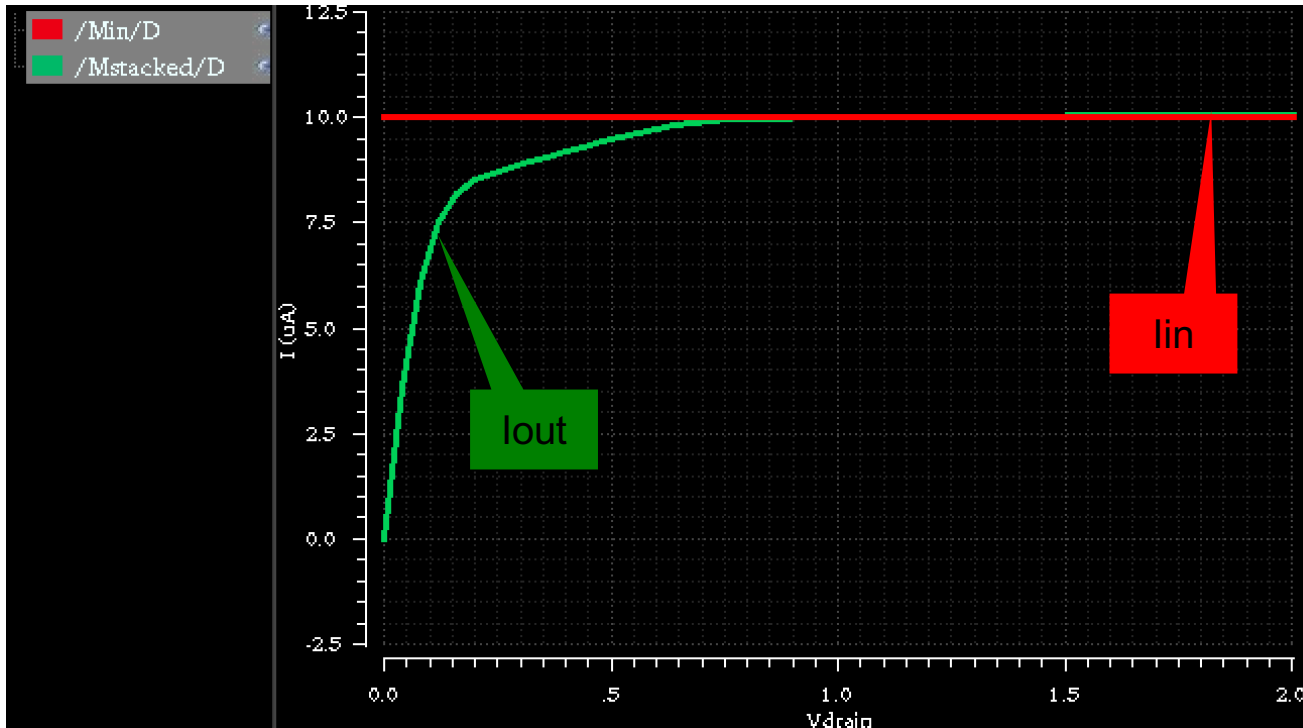- Very nice current match, but 'kink' at too high voltage



10.1uA = 10 + 1%


9.9uA = 10 - 1%

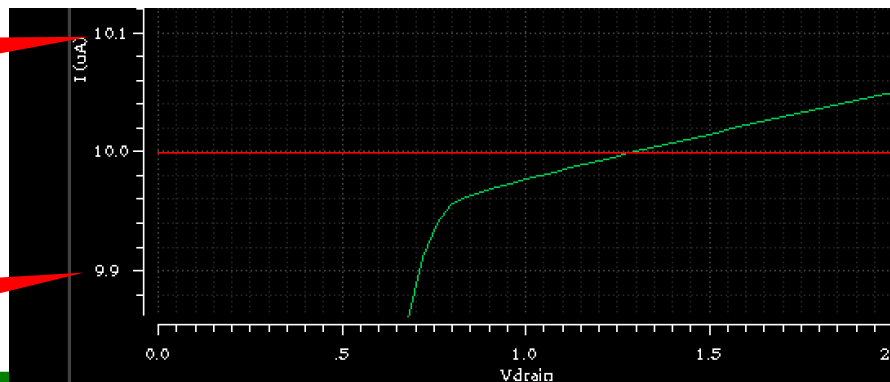






Exercise 5: The Low Voltage Mirror

- In the stacked mirror of the previous exercise, the drain voltage V_D of the current source M2 is fixed by the diode connection of M1.
- This is simple, but provides a *too high* voltage (by $\sim V_T$!)
- The following circuit connects the diode differently:
 - Understand that the gate voltage V_G still stabilizes to the 'correct' level!
 - We now need to find V_C
 - Sweep V_C from 0.4 to 1.4V in steps of 0.2V
 - What is a good choice?
 - Why do very low voltages fail (check V_G !)
 - What happens at high voltages? Why? (this is tricky to understand... Look at V_{D1} ...)
 - Note that the 'best' V_C depends in I_{in}

 



Solution 5: Results

 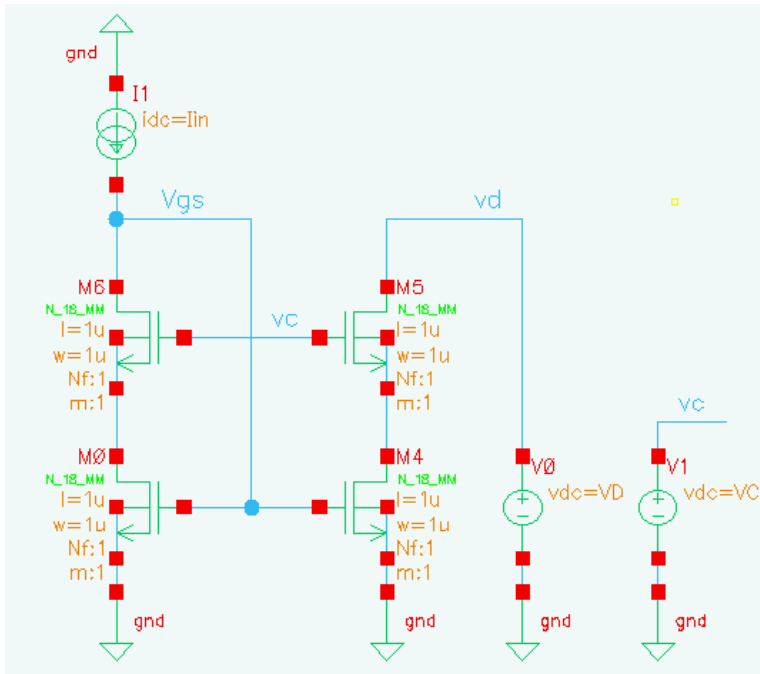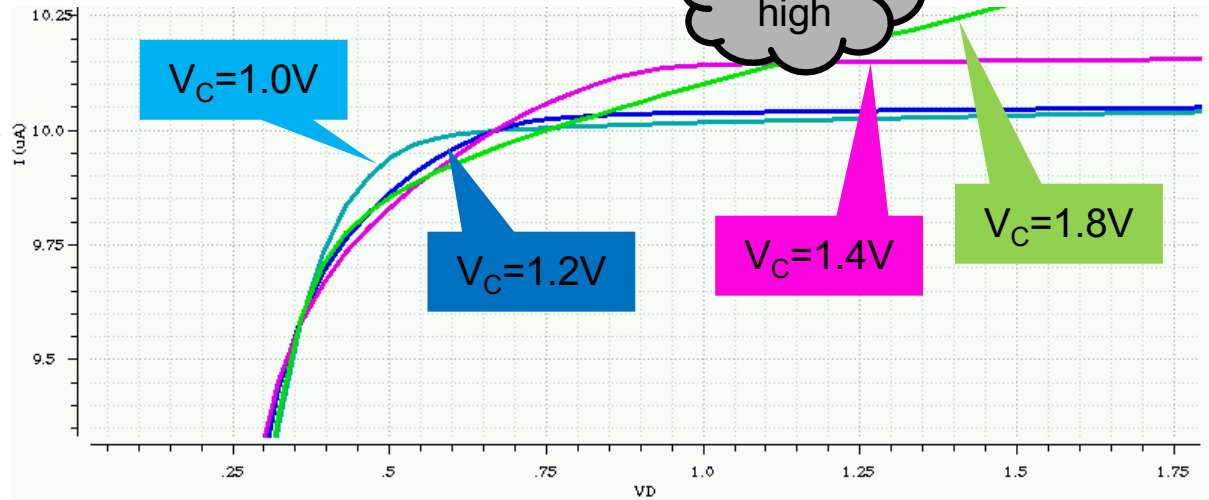




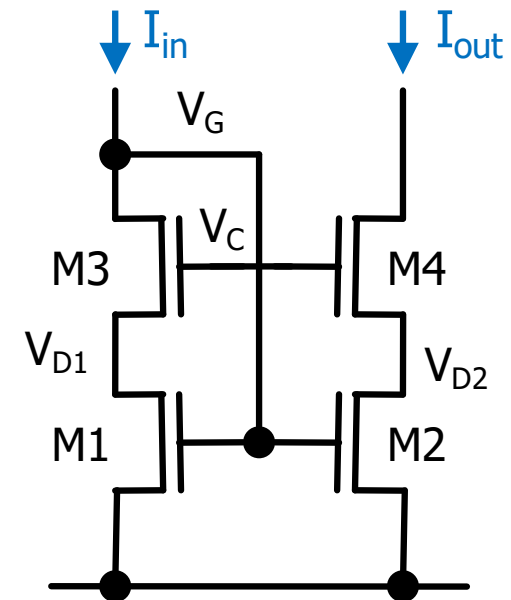Exercise 5: Explanations (for experts)

- Low V_C :
 - V_{D1} is very low
 - M1 is in linear region
 - current is low
 - V_G must be very (too) high to conduct requested current

- High V_C :
 - V_C pulls V_{D1} up
 - V_G is fixed, therefore V_{DS} of **M3** is small, M3 is in linear region
 - $V_{D1} \sim V_G$
 - Cascode M4 also in linear mode, does not work properly




- Optimal V_C :
 - M1 should *just* be saturated. This is then also optimal for M2



 Exercise 6: The Low Voltage Mirror

- The required optimal cascode voltage V_C can be generated *automatically* by a diode connected MOS M0 with different geometry than the others:
 $(W/L)_0 = k (W/L)_{\text{others}}$
- We assume that we have a second input current I_{in} available (both I_{in} s are equal)




- Calculate k so that M2 is just saturated.
 - Use the *large signal* model in strong inversion with no Early effect
- Simulate the circuit



Solution 6

- We use $I_D = \beta (V_{GS} - V_T)^2$
- Gate voltage of M1:
 $I_{in} = \beta (V_G - V_T)^2$
 $V_G = V_T + \sqrt{I_{in} / \beta}$
- Saturation voltage of M1/M2:
 $V_{DSat1} = V_{GS1} - V_T = \sqrt{I_{in} / \beta}$
- Voltage V_C (current in M3):
 $I_{in} = \beta (V_C - V_{DSat1} - V_T)^2$
 $= \beta (V_C - V_T - \sqrt{I_{in} / \beta})^2$
- $\sqrt{I_{in} / \beta} = V_C - V_T - \sqrt{I_{in} / \beta}$
- Geometry of M0:
 $I_{in} = \beta_0 (V_C - V_T)^2 = \beta_0 (\sqrt{I_{in} / \beta} + \sqrt{I_{in} / \beta})^2 = \beta_0 4 I_{in} / \beta$

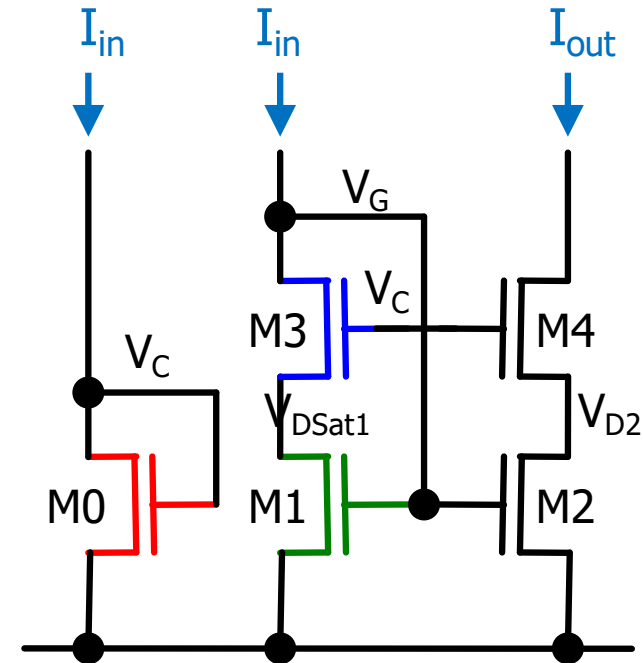

$$\beta_0 = \beta / 4$$






Exercise 7: An *Even Better* Mirror

- The key trick is obviously to keep the drain voltage of M2 very constant irrespective of the output voltage.
- This can be done with an active circuit (with an amplifier):
 - Amp amplifies the difference of the two input voltages by A_0
 - Where is the positive/negative input for stable operation?
 - Simulate the circuit. Use a voltage controlled voltage source vcvs from the analogLib for Amp with $A_0=1000$

- *Calculate* the output resistance!


- This topology is called the *Regulated Mirror*

 



Solution 7: Theory

 
- Same result as stacked mirror, but with g_m increased by factor A_0





Exercise 8 (Advanced): Implementing the Regulated Mirror




- The amplifier in Ex. 7 can be implemented by a gain stage
- Simulate such a circuit!
- You can use a Spice current source in the regulation amplifier to start with...
- Explain why V_D is not optimal. Can you use a transistor with low threshold?
- You could also cascode in the gain stage...

 



Solution 7: Practical implementation

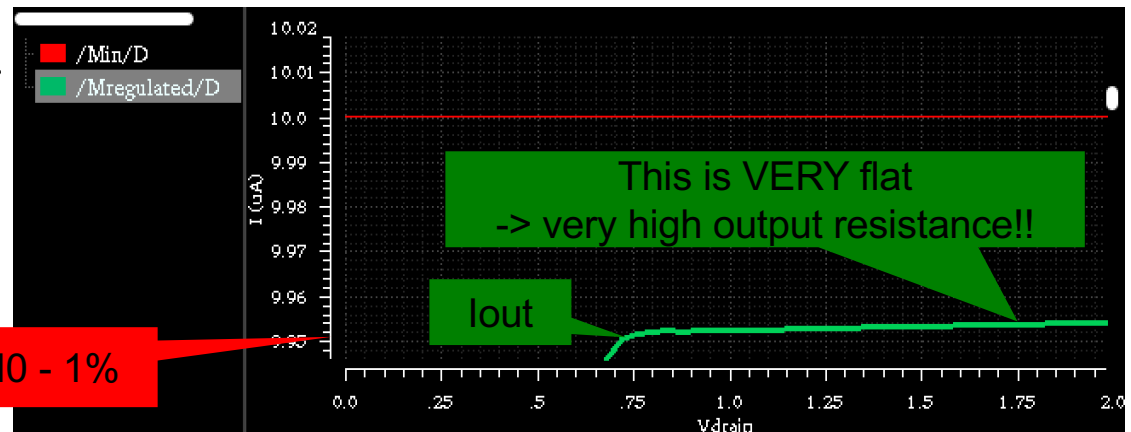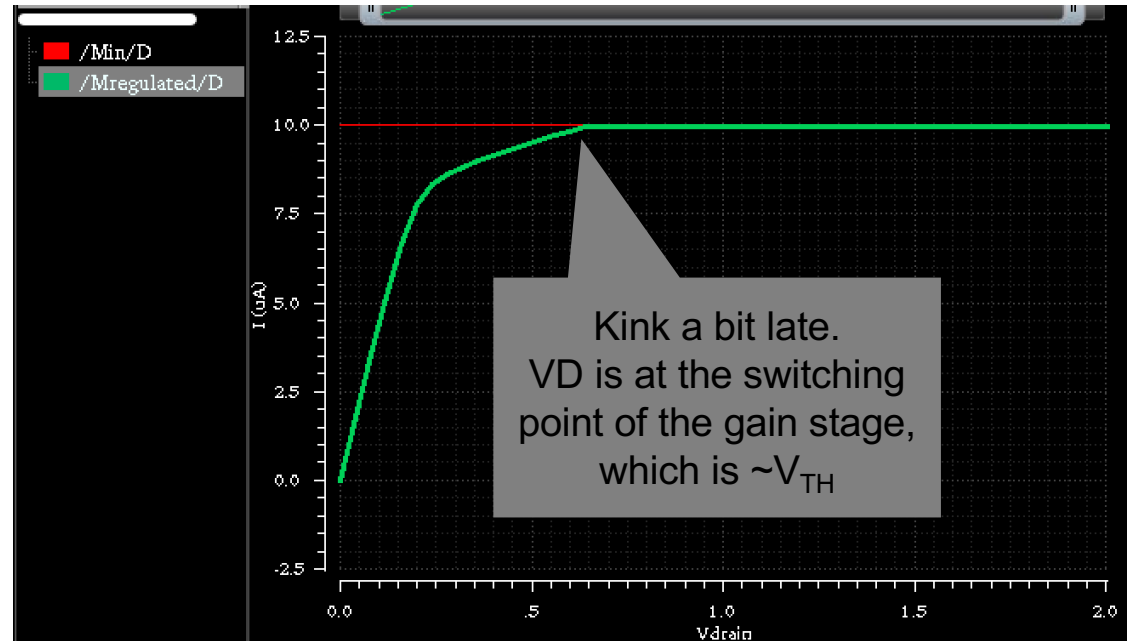 - The amplifier in Ex. 7 can be implemented by a gain stage:



9.95uA = 10 - 1%