



Exercise: Resistors, Capacitors, Thévenin

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation Uni Heidelberg

CCS Exercise: Thévenin Equivalent

© P. Fischer, ZITI, Uni Heidelberg Page 1

RUPRECHT-KARLS-UNIVERSITÄT HEIDELBERG

Exercise 1: Electric Car

- An electric car has a battery of $E_{Bat} = 50$ kWh and operates at a voltage of V_{Bat} . Assume $V_{Bat} = 100$ V for a start.
- It is charged from an ideal voltage source (of V_{Bat}) through a pair of $L_{Cable} = 2 \times 3 \text{ m}$ long copper cables of massive cylindrical shape with $D_{cable} = 1 \text{ cm}$ diameter.
- The resistivity of copper is $\rho_{Cu} = 1.68 \times 10^{-8} \Omega m$.
- How much current would you need to load an empty battery fully in 15 Minutes (if the battery would support that..)?
- How much voltage drop does this current produce in the cable? So what fraction of energy is lost in the cable?
- What power (in Watt) is dissipated in the cable?
- How does this change for V_{Bat} = 500 V?





- Derive the expressions for the series and parallel connection of capacitors
- Use charge conservation (at node x)









Derive the Thévenin Equivalent for the following circuit:



- Try two different methods:
 - Use the Open/Short method with Kirchhoff's rules
 - Convert the I-source part to a voltage source first...





What is the Thévenin Equivalent of the following circuit?



- Use two methods to find the result:
 - parallel / series connection of resistors and your knowledge about the voltage divider
 - short/open method





What is the 'gain' (attenuation) of the following voltage divider (all resistors have 1 Ohm):



- Try 3 different methods:
 - Your knowledge of parallel / serial connection of resistors
 - Kirchhoff's law
 - Use your knowledge about the Thévenin equivalent of a voltage divider

RUPRECHT-KARLS-UNIVERSITÄT HEIDELBERG



 A voltage source with voltage V₀ and output resistance R₀ is loaded by a resistor R_L:



- What is the output voltage V_{out}?
- Which current flows in R_L?
- What power (P = U I) is dissipated in R_L?
 - Check that noting is dissipated for $R_L {=} 0$ and $R_L {\rightarrow} {\sim}$
- For which value of R_L is the dissipation maximized?
 - What is the dissipation?

RUPRECHT-KARLS-UNIVERSITÄT HEIDELBERG



 We consider charging of a capacitor C though a resistor R to a voltage U₀.



- Show that $U(t) = U_0 U_0 e^{-\frac{t}{RC}}$ satisfies the differential equation
- Simplify U(t) for small times t<<RC.</p>
- What is the initial slope ?
- Derive this slope directly (assuming U(0) = 0).

Exercise 8: R-2R DAC

RUPRECHT-KARLS-UNIVERSITÄT

HEIDELBERG

- Digital-Analog-Converters (DACs) convert a digital (normally binary coded) value into a voltage (or current) which is a normally proportional to the digital value.
- A simple circuit is the R-2R DAC:



- The input voltages at the lower side of the 2R resistors is either 0V or some V_{REF} , depending of the binary bit (Q_0 is the Least Significant Bit, LSB).
- Show that the output voltage of a R-2R DAC with an arbitrary number N of bits is proportional to Q!
 - Hint: Replace the circuit by Thévenin equivalents at the red lines from left to right.