



Exercise: Thévenin, Resistors, Capacitors



Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg




Exercise 1

- Derive the expressions for the series and parallel connection of capacitors
- Use charge conservation (at node x)

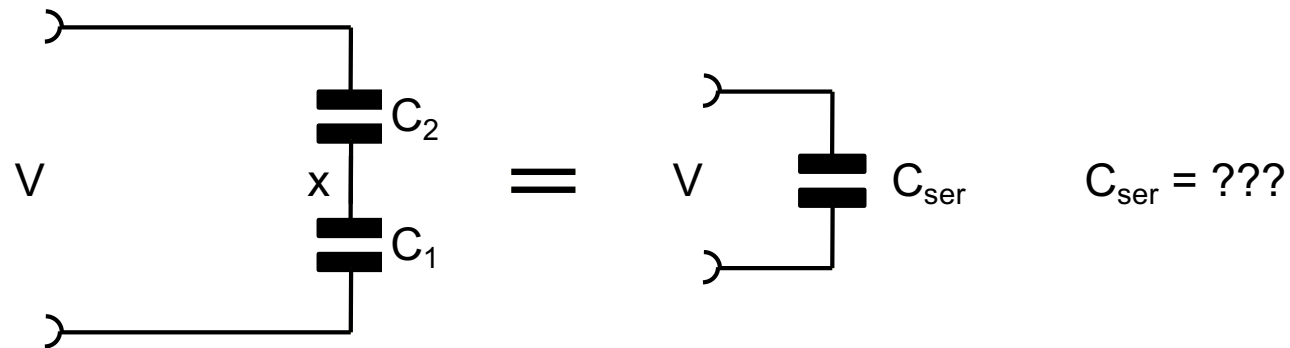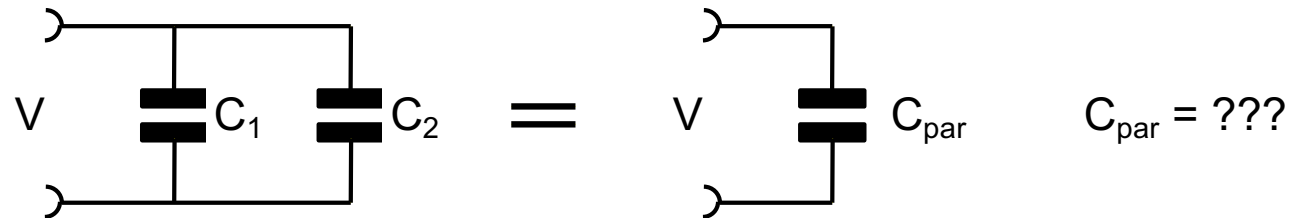



Solution 1

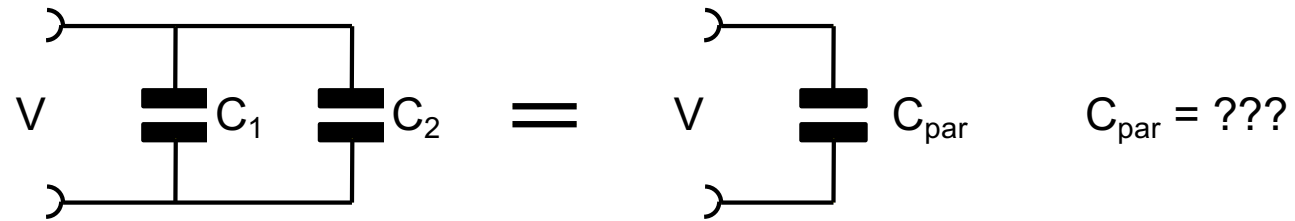

1. Charge conservation:


$$V \times C_1 + V \times C_2 = Q_1 + Q_2 = Q_{\text{par}} = V \times C_{\text{par}} \rightarrow C_1 + C_2 = C_{\text{par}}$$

2. Kirchhoff & complex impedance:

$$V sC_1 + V sC_2 = i_1 + i_2 = i_{\text{par}} = V sC_{\text{par}} \rightarrow C_1 + C_2 = C_{\text{par}}$$



Solution 1

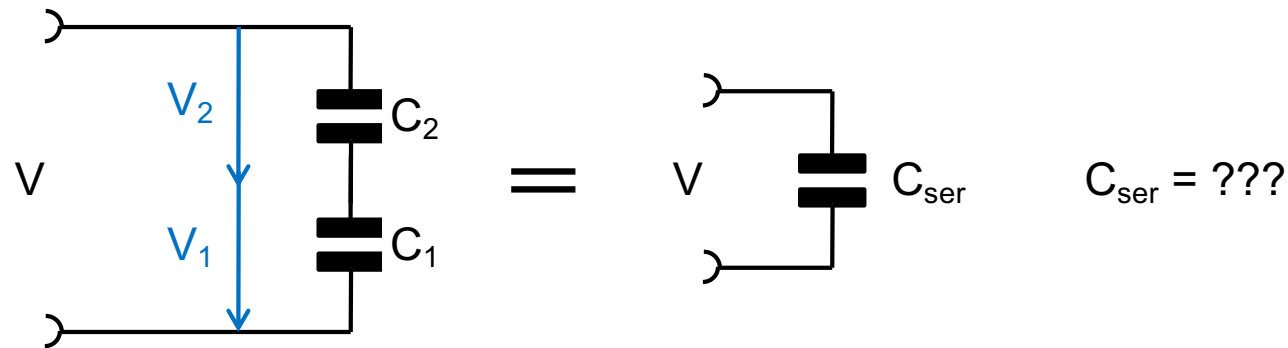

1. Charge conservation:

Note: no charge can 'escape' the middle node, so that $Q_1 = Q_2 = Q_{\text{ser}}$

$$V = V_1 + V_2 = Q_1/C_1 + Q_2/C_2 = Q/C_1 + Q/C_2 = Q/C_{\text{ser}}$$

$$\rightarrow 1/C_1 + 1/C_2 = 1/C_{\text{ser}}$$

2. Kirchhoff & complex impedance:

$$V_1 sC_1 = V_2 sC_2 \quad \text{and} \quad V_1 + V_2 = V \quad \rightarrow \quad V_1 = V C_2 / (C_1 + C_2)$$


$$\rightarrow i_1 = V_1 sC_1 = V s C_1 C_2 / (C_1 + C_2)$$

$$\rightarrow C_{\text{ser}} = i / (Vs) = i_1 / (Vs) = C_1 C_2 / (C_1 + C_2)$$



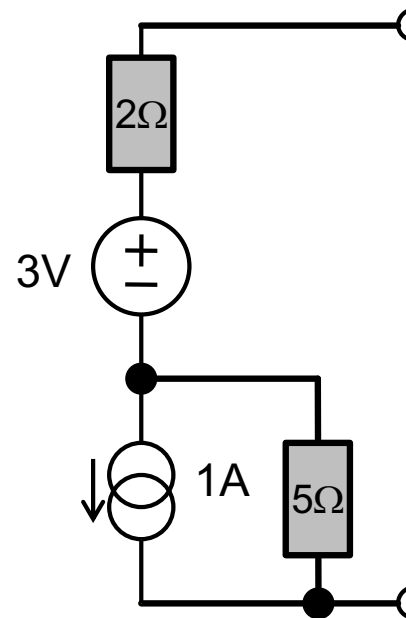Exercise 2

- Derive the Thévenin Equivalent for the following circuit:





- Try two different methods:
 - Use the Open/Short method with Kirchhoff's rules
 - Convert the I-source part to a voltage source first...



Solution 2 – Kirchhoff

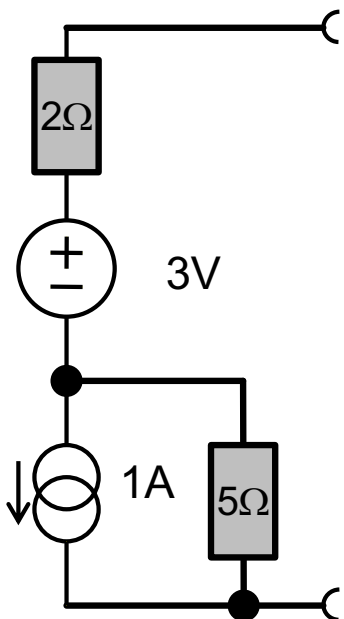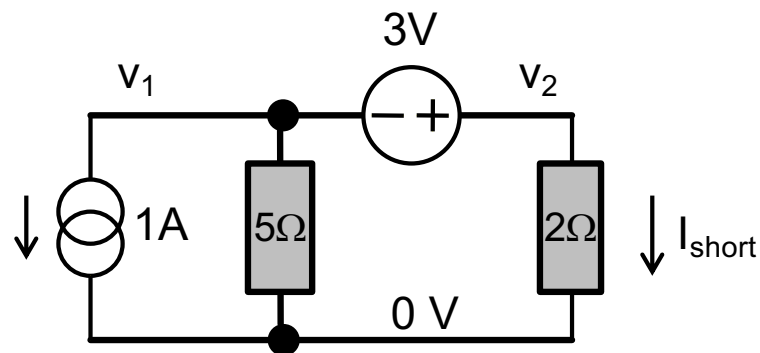
1. Short circuit current:

- EQ1: $1 \text{ A} + v_1 / 5\Omega + v_2 / 2\Omega = 0$
- EQ2: $v_2 = v_1 + 3\text{V}$
- $\rightarrow v_2 = -4 / 7 \text{ V}$
- $\rightarrow I_{\text{short}} = -2 / 7 \text{ A}$



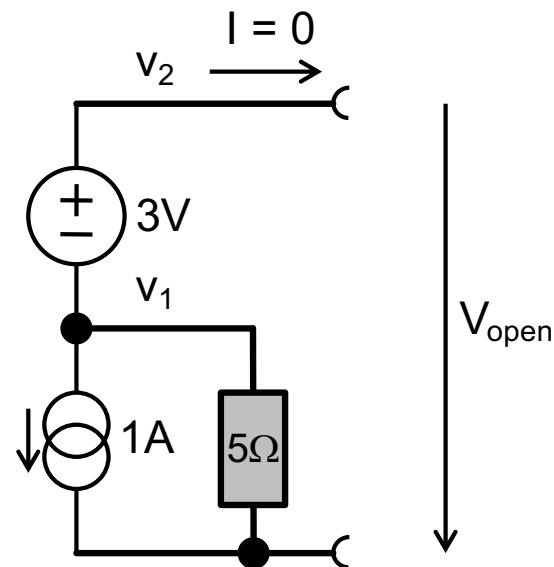1. Open circuit voltage:

- EQ1: $1 \text{ A} + v_1 / 5\Omega = 0$
- EQ2: $v_2 = v_1 + 3\text{V}$
- $\rightarrow v_1 = -5 \text{ V}$
- $\rightarrow v_2 = V_{\text{open}} = -2 \text{ V}$




- Source: $V_0 = V_{\text{open}} = -2 \text{ V}, R_V = V_0 / I_{\text{short}} = 7 \Omega$




Solution 2 – Thévenin Transformations

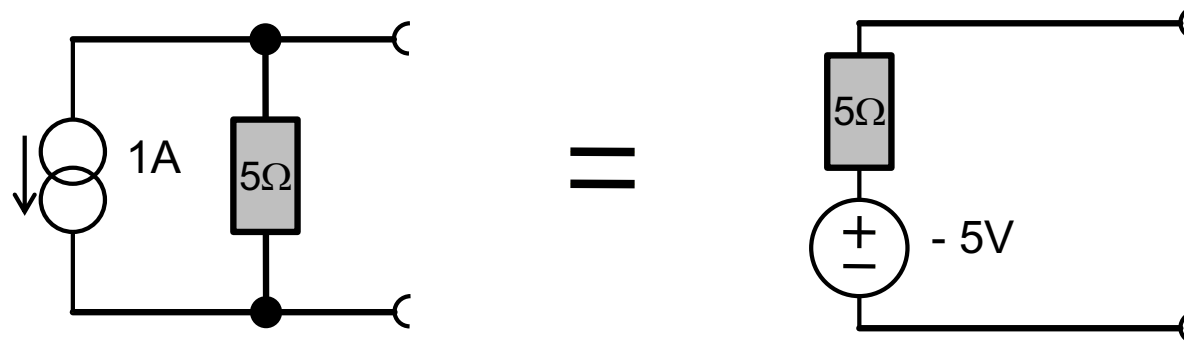1. Convert the current source to a voltage source:




2. Use this in the circuit:

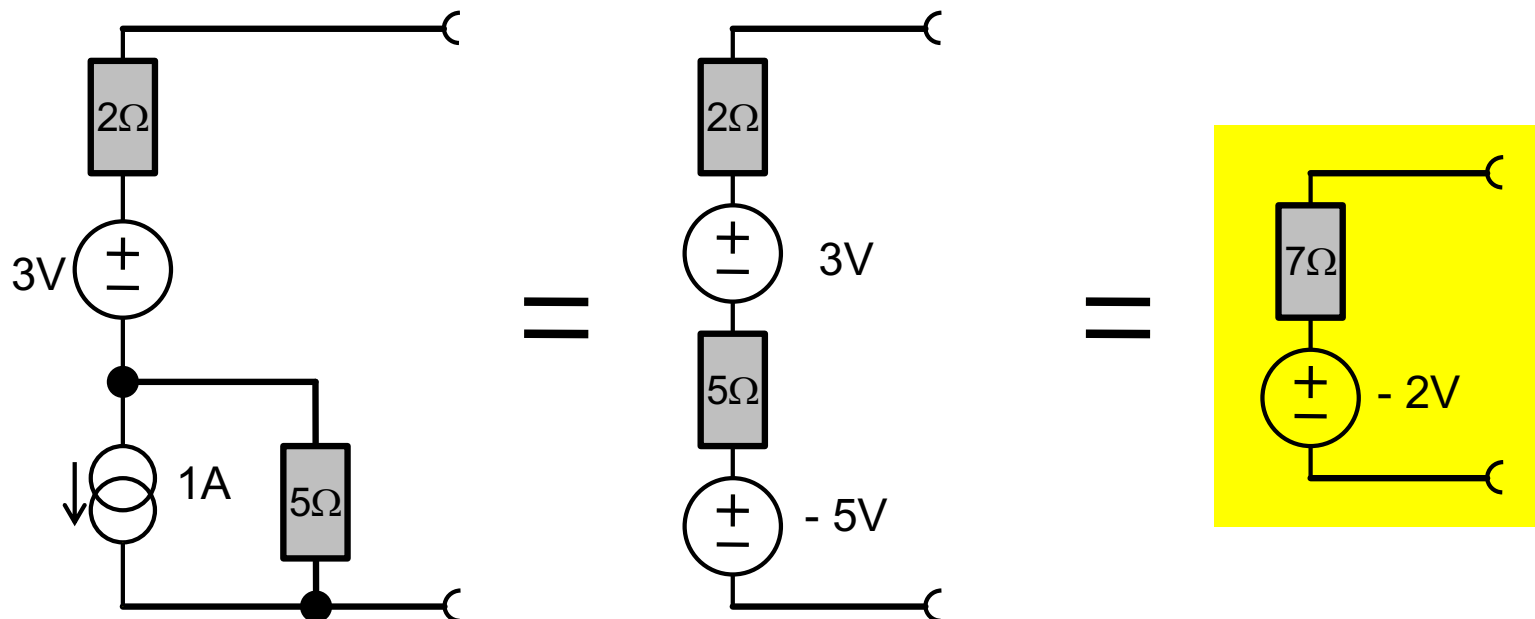



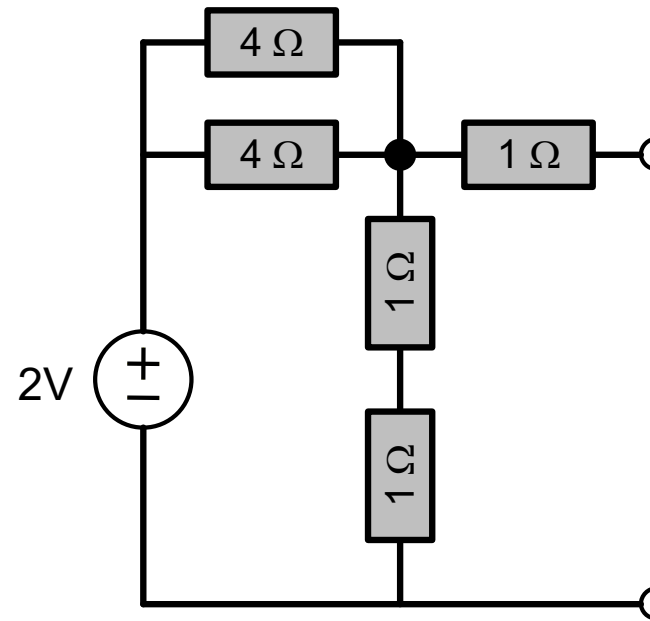Exercise 3

- What is the Thévenin Equivalent of the following circuit?




- Use two methods to find the result:
 - parallel / series connection of resistors and your knowledge about the voltage divider
 - short/open method



Solution 3


- Parallel-Series Connection, Voltage Divider:

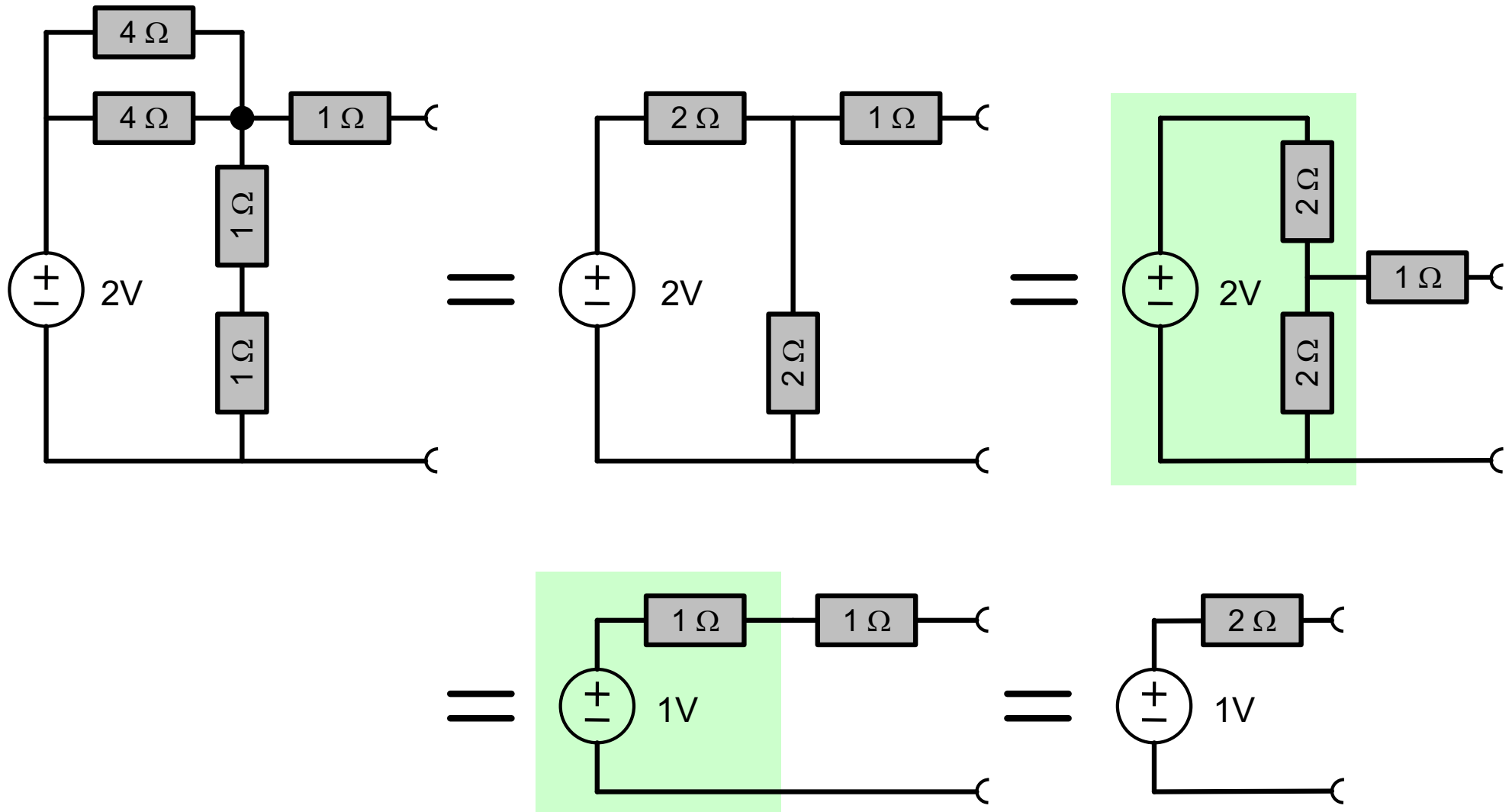




Solution 3

- Open: $V_{open} = 1V$

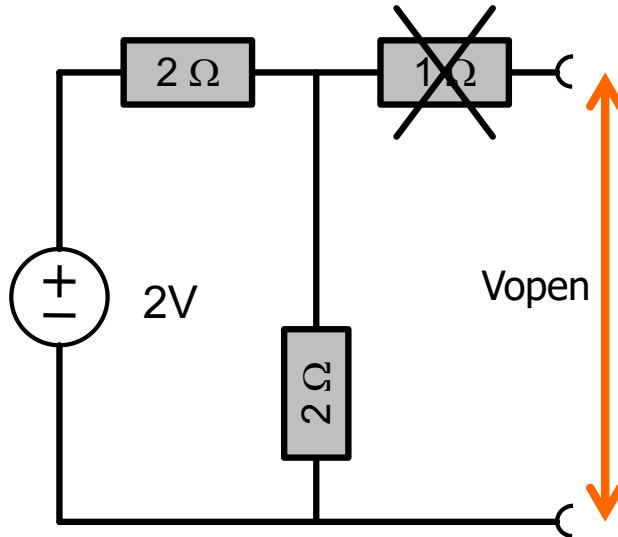

- Short:

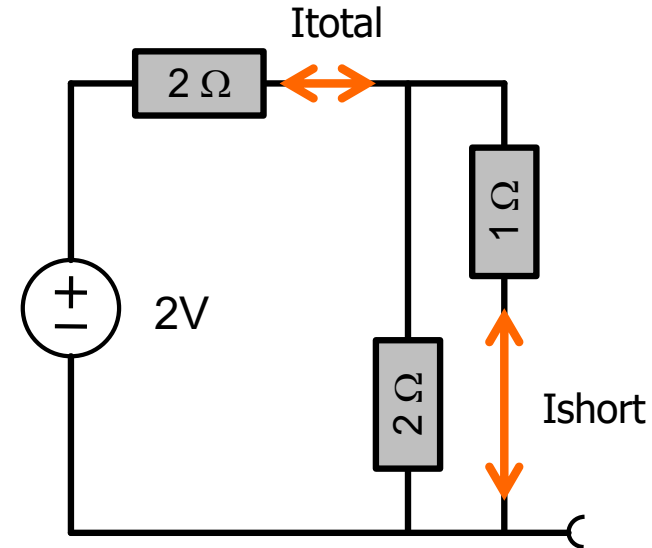

$$R_{total} = 2\Omega + 2/3\Omega = 8/3\Omega$$

$$I_{total} = 2V / R_{total} = 3/4 A$$


$$I_{short} = 2/3 I_{total} = 1/2 A$$

$$\begin{aligned} Z_{in} &= V_{open} / I_{short} \\ &= 1V / 1/2 A \\ &= 2\Omega \end{aligned}$$



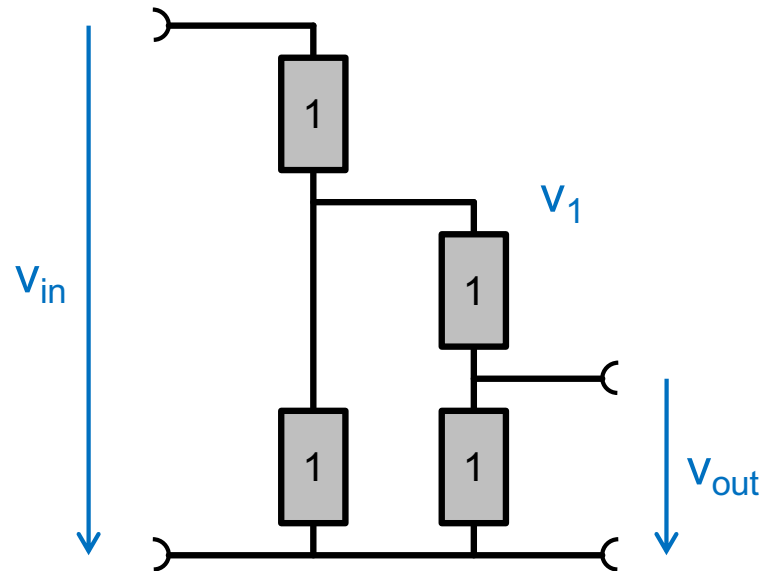Exercise 4

- What is the 'gain' (attenuation) of the following voltage divider (all resistors have 1 Ohm):



- Try 3 different methods:
 - Your knowledge of parallel / serial connection of resistors
 - Kirchhoff's law
 - Use your knowledge about the Thévenin equivalent of a voltage divider



Solution 4

1. 'By hand':

- The lower part is a *parallel* connection of 1Ω and 2Ω .
This gives $(1/1\Omega + 1/2\Omega)^{-1} = 2/3 \Omega$.
- So we have at node v_1 a voltage divider with 1Ω and $2/3 \Omega$.
The voltage at v_1 is $(2/3) / (1+2/3) v_{in} = 2/5 v_{in}$
- The voltage at v_{out} is half of v_1 , so $v_{out} = 1/5 v_{in}$

2. Kirchhoff

- We have current equations at nodes v_1 and v_{out} :

$$\text{EQv1} = \frac{v_{in} - v1}{1} == \frac{v1}{1} + \frac{v1 - vout}{1};$$

$$\text{EQvout} = \frac{v1 - vout}{1} == \frac{vout}{1};$$

`Eliminate[EQv1 && EQvout, v1]`

`5 vout == vin`

`First@Solve[%, vout]`


$$\left\{ vout \rightarrow \frac{vin}{5} \right\}$$



Solution 4

3. Thévenin:


- The first divider (left of the dotted red line) can be replaced by its Thévenin equivalent of a voltage source with $v_{in}/2$ and an outputs resistance of $1/2 \Omega$.
- This creates a divider of $1/2.5$ of a voltage $v_{in}/2$, so that we get $v_{in}/5$.

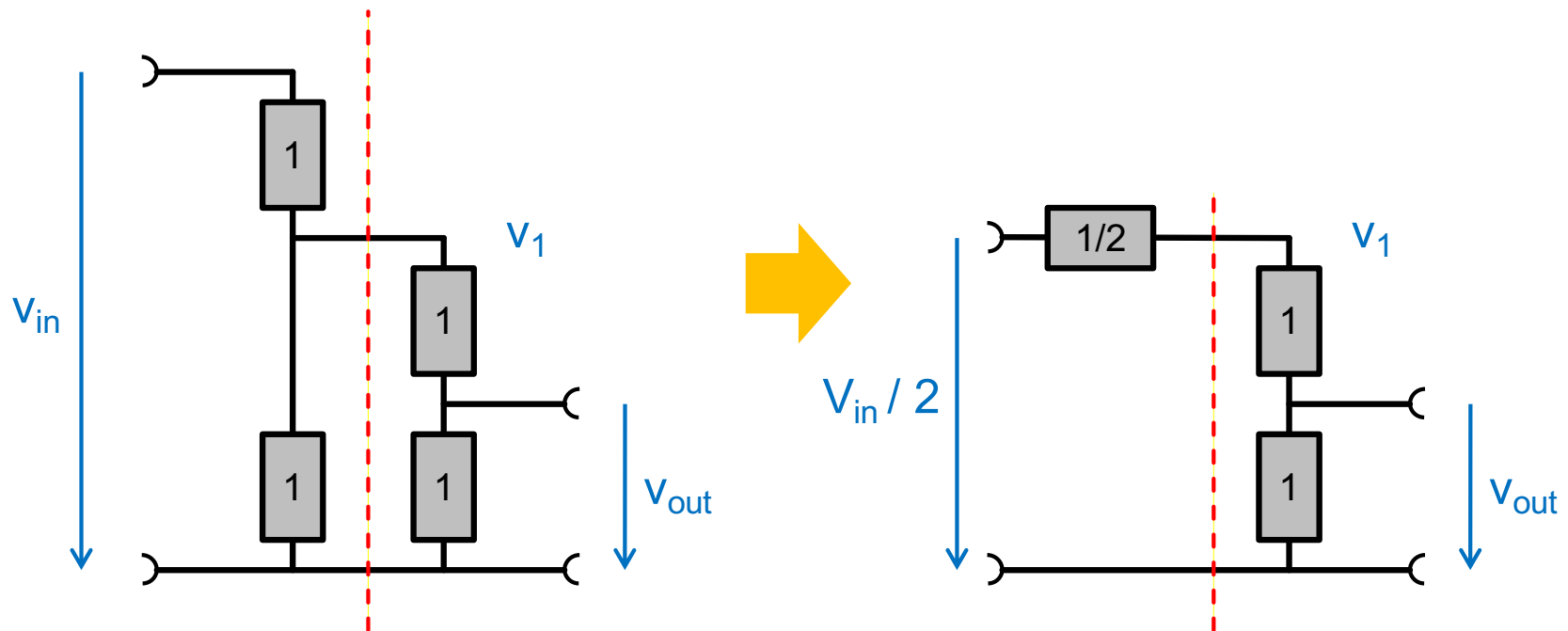



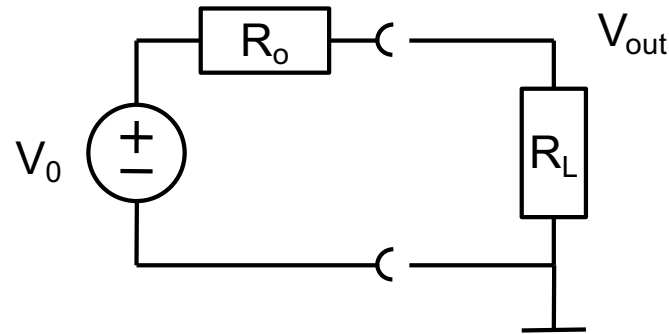Exercise 5

- A voltage source with voltage V_0 and output resistance R_0 is loaded by a resistor R_L :



- What is the output voltage V_{out} ?
- Which current flows in R_L ?
- What power ($P = U I$) is dissipated in R_L ?
 - Check that nothing is dissipated for $R_L=0$ and $R_L \rightarrow \infty$
- For which value of R_L is the dissipation maximized?
 - What is the dissipation?



Solution 5

In[29]:= **Vout** = $V_0 \frac{R_L}{R_0 + R_L}$;

In[30]:= **Iout** = $\frac{V_{out}}{R_L}$

Out[30]= $\frac{V_0}{R_0 + R_L}$

In[31]:= **Pout** = **Vout** **Iout**

Out[31]= $\frac{R_L V_0^2}{(R_0 + R_L)^2}$

In[38]:= **Table**[**Limit**[**Pout**, **RL** → **x**], {**x**, {**0**, **∞**}}

Out[38]= {**0**, **0**}

In[39]:= **Solve**[**D**[**Pout**, **RL**] == **0**, **RL**] // **First**

Out[39]= {**RL** → **R0**}


In[40]:= **Pout** /. %

Out[40]= $\frac{V_0^2}{4 R_0}$



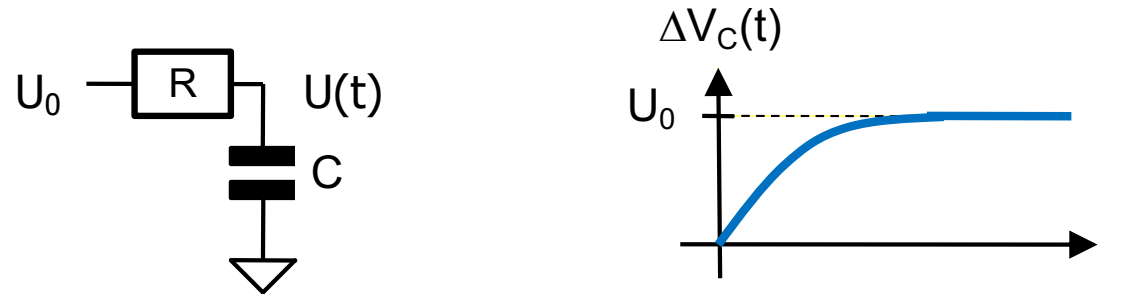Exercise 6

- We consider charging of a capacitor C through a resistor R to a voltage U_0 .



- Show that $U(t) = U_0 - U_0 e^{-\frac{t}{RC}}$ satisfies the differential equation
- Simplify $U(t)$ for small times $t \ll RC$.
- What is the initial slope ?
- Derive this slope directly (assuming $U(0) = 0$).




Solution 6

- For a capacitor, we have $dU/dt = I/C$.
And we have $I = (U_0 - U)/R$
So the DGL is $U'(t) = (U_0 - U)/RC$
- The proposed solution $U(t) = U_0 - U_0 \text{Exp}(-t/RC)$ gives
The left hand side: $U'(t) = U_0/RC \text{Exp}(-t/RC)$
And the right side: $U_0 \text{Exp}(-t/RC) / RC$, i.e. the same.
- For small x , the $\text{Exp}(x)$ is $\sim 1+x$, therefore
 $U(t) \sim U_0 - U_0 (1-t/RC) = t U_0/RC$
- The slope is derivative of this, i.e U_0/RC
- This is a charging I/C with an initial current U_0/R



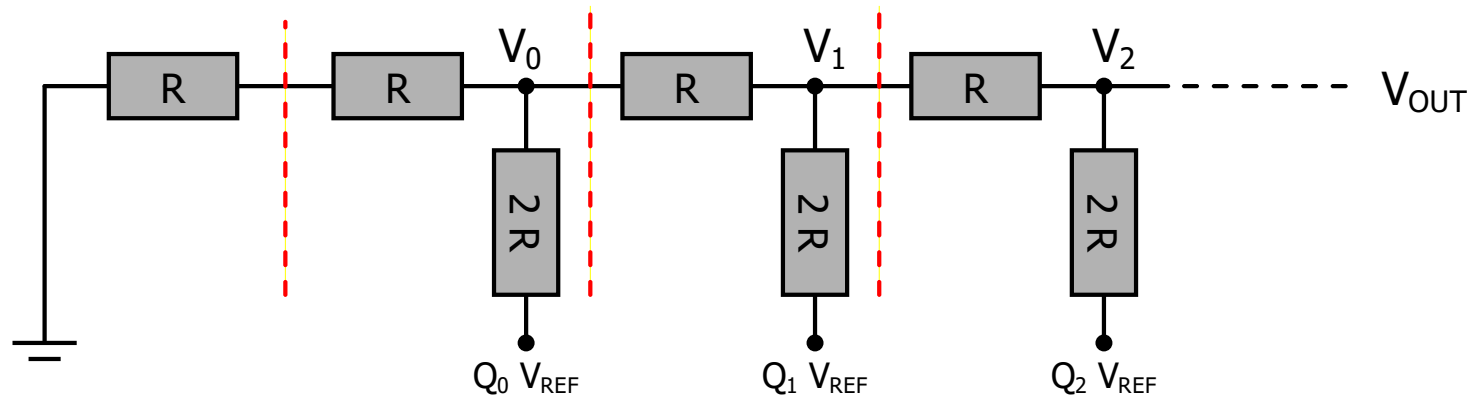Exercise 7 (new): R-2R DAC

- Digital-Analog-Converters (DACs) convert a digital (normally binary coded) value into a voltage (or current) which is normally proportional to the digital value.
- A simple circuit is the R-2R DAC:




- The input voltages at the lower side of the $2R$ resistors is either $0V$ or some V_{REF} , depending of the binary bit (Q_0 is the Least Significant Bit, LSB).
- Show that the output voltage of a R-2R DAC with an arbitrary number N of bits is proportional to Q !
 - Hint: Replace the circuit by Thévenin equivalents at the red lines from left to right.



Solution 7

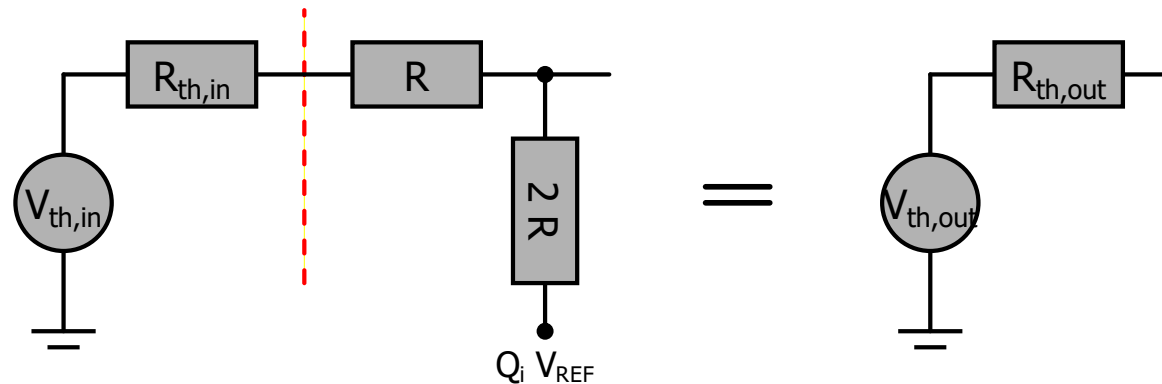- Assume the left (driving) side of a 'red line' is given by $V_{th,in}$ and $R_{th,in}$:



- The output resistance is $R_{th,out} = (R_{th,in} + R) \parallel 2R$.
For $R_{th,in} = R$, we get again $R_{th,out} = 2R \parallel 2R = R$!
Therefore $R_{th} = R$ in all stages.
- Therefore, $R_{th,in}$ and the serial R add up to $2R$ and we *always* have a 1:1 divider!: $V_{th,out}$ *is the average of* $V_{th,in}$ *and* $Q V_{REF}$
- With $V_{th,in}$ of the 0-th stage being 0, we get

$$V_0 = \text{Average}(0, Q_0 V_{REF}) = Q_0 / 2 \times V_{REF}$$

$$V_1 = \text{Average}(Q_0 / 2 \times V_{REF} / 2, Q_1 V_{REF}) = (Q_1 / 2 + Q_0 / 4) V_{REF}$$

$$V_2 = \dots = (Q_2 / 2 + Q_1 / 4 + Q_0 / 8) V_{REF}$$
 and so on. This is the desired linear relationship.