



Exercise: Making a Steep Filter


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



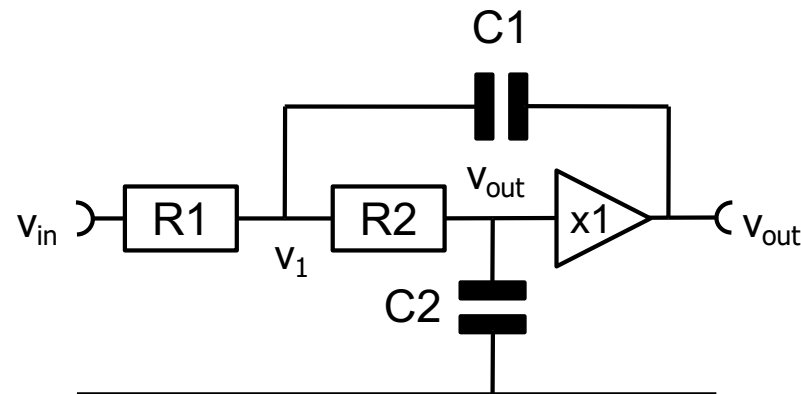Exercise

- Just for fun, we want to design a steep Butterworth Low Pass filter
 - Let the corner frequency be 1 MHz
 - Let's chose order $N=6$
 - Implement it using 'Sallen and Key' stages with $k=1$



- After you have derived component parameters for the 3 filter stages, simulate the result.



Hints

- The poles of a Butterworth filter are placed on the left half circle with equal angles (see slide 'choosing the poles' in the lecture), i.e. with $d\phi = \pi/N$ and $r = \omega$.
- Each complex-conjugate pair of poles is handled by one 2nd order 'Sallen and Key' filter. So we need $N/2$ stages.
- Each filter (with dc gain 1) has a general transfer function of $1/(1+s/p_a)(1+s/p_b) = 1/(1+as+bs^2)$ where p_a and p_b are the two complex conjugate poles.



Steps

■ Step1:

- Given a pole pair, we want to know the transfer function
- Write $p_a = r (\sin(\phi) + i \cos(\phi))$, $p_b = \dots$
- From p_a and p_b , calculate a , b

■ Step2:

- Our filter has 4 parameters (R_1, R_2, C_1, C_2), but its behaviour is described by 2 (e.g. corner, peaking), there are several ways to implement it. For example:
- Set $R_1 = R_2 = R$ and $C_2 = 1nF$. This leaves us with 2 parameters
- Derive the transfer function of a filter stage

■ Step3:

- For a given (r, ϕ) and thus (a, b) , derive R and C_1 by equating the coefficients of s and s^2 .

■ Step 4:

- Derive (r, ϕ) for each pole-pair of the Butterworth and get R and C_1 for that filter stage.