



Exercise: Time Domain

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Exercise 1

- A filter is made up of a
 - low-pass
 - an ideal unity gain buffer
 - a high-pass with same corner frequency as the low-pass
- What is the time response of this filter to a unit step ?
- Calculate and Simulate!




Solution 1

```
In[14]:= f[t_] = InverseLaplaceTransform[1/s - 1/(1 + s/tau) - s/(tau*(1 + s/tau)), s, t]
```

```
Out[14]= E^-t tau t tau
```
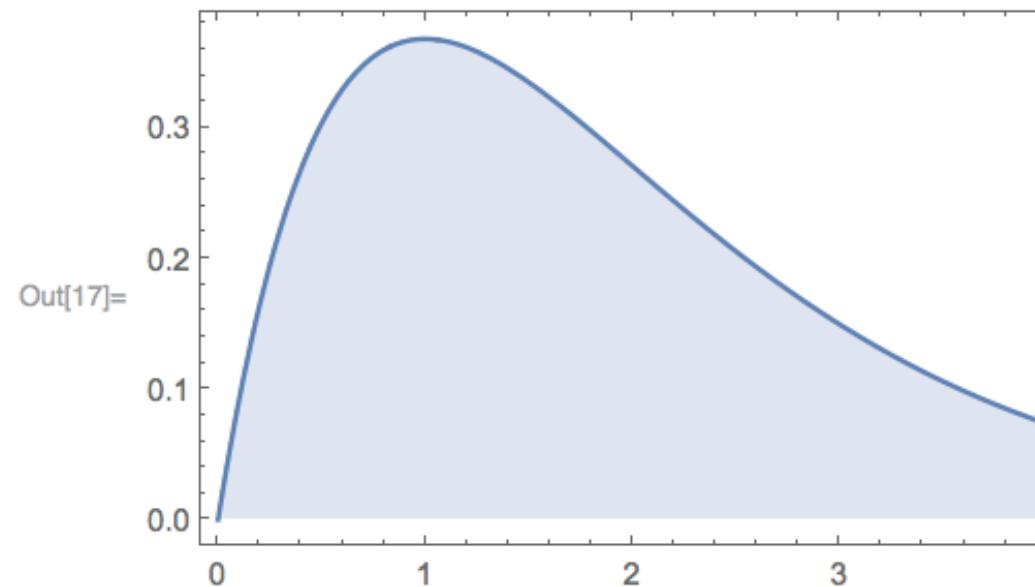
```
In[17]:= Plot[f[t] /. tau -> 1, {t, 0, 4}]
```




```
In[19]:= Solve[f'[t] == 0, t] // First
```

```
Out[19]= {t -> 1/tau}
```



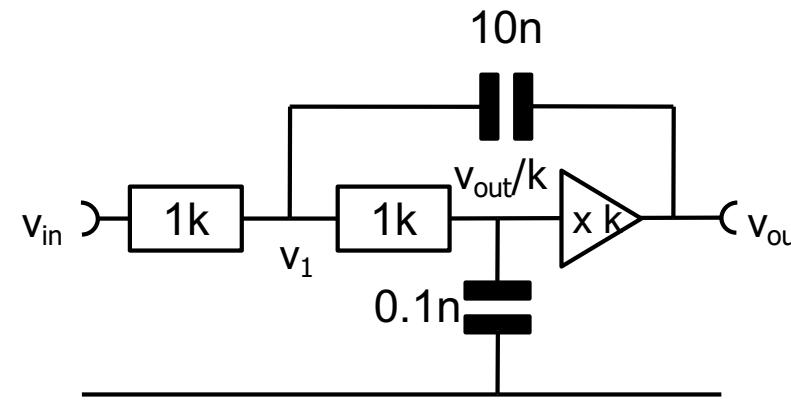Exercise 2

- Derive $H[s]$ for the following active filter (use Mathematica!)
 - The (ideal) voltage amplifier has gain k



- For which k do you get a divergence ?
- What is the step response for $k=1$?
- Simulate the circuit and compare quantitatively.



Solution 2

■ $H[s]$

Absolute frequencies
do not matter. I use
 $R=1$ and $C=10$

$$\text{In[221]:= } \text{EQ1} = \frac{v_{in} - v_1}{1} == \frac{v_1 - \frac{v_{out}}{k}}{1} + (v_1 - v_{out}) s 10;$$

$$\text{EQ2} = \frac{v_1 - \frac{v_{out}}{k}}{1} == \frac{v_{out}}{k} s \frac{1}{10};$$

`In[224]:= $Assumptions = k > 0 && s > 0 && w > 0;`

▼ `In[225]:= Eliminate[{EQ1, EQ2}, v1] // Simplify`

$$\text{Out[225]= } (5 + 51 s + 5 s^2) v_{out} = 5 k (v_{in} + 10 s v_{out})$$

▼ `In[226]:= Solve[%, vout] // First`

$$\text{Out[226]= } \left\{ v_{out} \rightarrow -\frac{5 k v_{in}}{-5 - 51 s + 50 k s - 5 s^2} \right\}$$

▼ `In[227]:= H_active[s_, k_] = vout / . % // Simplify`

$$\text{Out[227]= } \frac{5 k}{5 + (51 - 50 k) s + 5 s^2}$$

▼ `In[228]:= H_active[s, 1]`


$$\text{Out[228]= } \frac{5}{5 + s + 5 s^2}$$



Solution 2

- The filter produces a high output amplitude peaking at $\omega=1$ (for R,C, chosen).
- The peaking depends on k. Plot 3 values of k:

```
LogLogPlot[{Abs@Hactive[i ω, {0.9, 1, 1.02}]}, {ω, 0.1, 10},  
Frame → True, PlotRange → {Full, {0.01, 50}}, Filling → Axis,  
GridLinesStyle → Directive[Gray, Thin], GridLines → {{1}, {1}}]
```

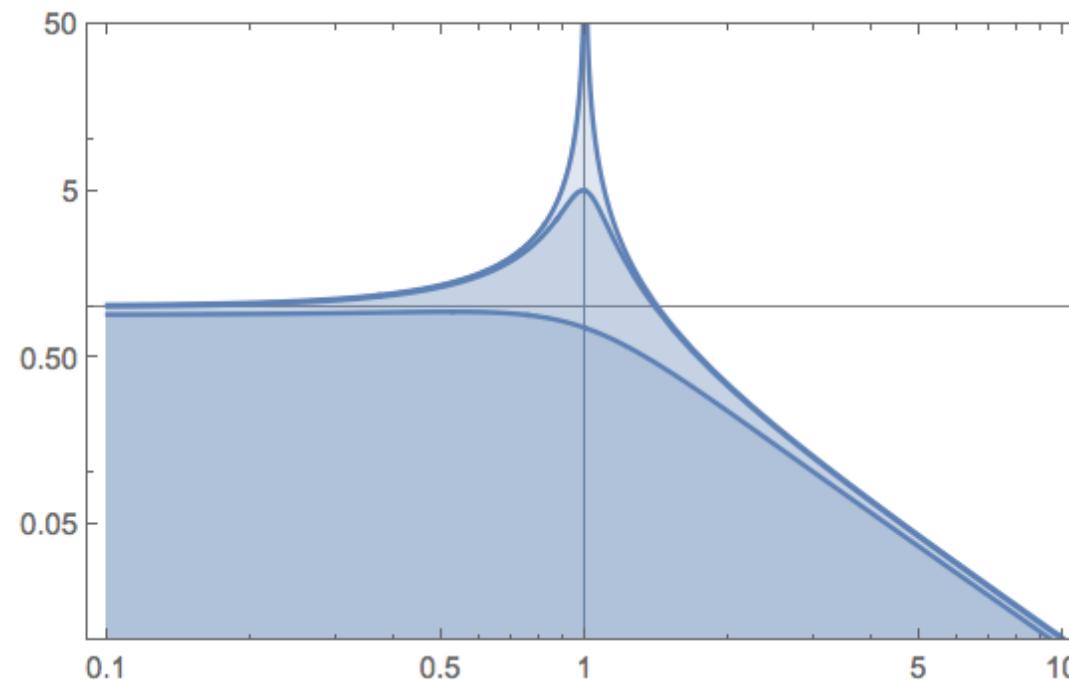



Solution 2

■ Divergence:

- The value at the peak is $H[i \omega]$ for $\omega=1$:

```
In[249]:= gpeak = Abs@Hactive[i, k]
```

$$\text{Out}[249]= 5 \operatorname{Abs}\left[\frac{k}{51 - 50 k}\right]$$

```
In[253]:= Solve[51 - 50 k == 0, k] // N
```

$$\text{Out}[253]= \{ \{k \rightarrow 1.02\} \}$$




Solution 2

▪ Step Response

```
In[322]:= Step1 = InverseLaplaceTransform[ Hactive[s, 1] / s, s, t] // Simplify
```

$$\text{Out}[322]= 1 - e^{-t/10} \cos\left[\frac{3\sqrt{11}t}{10}\right] - \frac{e^{-t/10} \sin\left[\frac{3\sqrt{11}t}{10}\right]}{3\sqrt{11}}$$
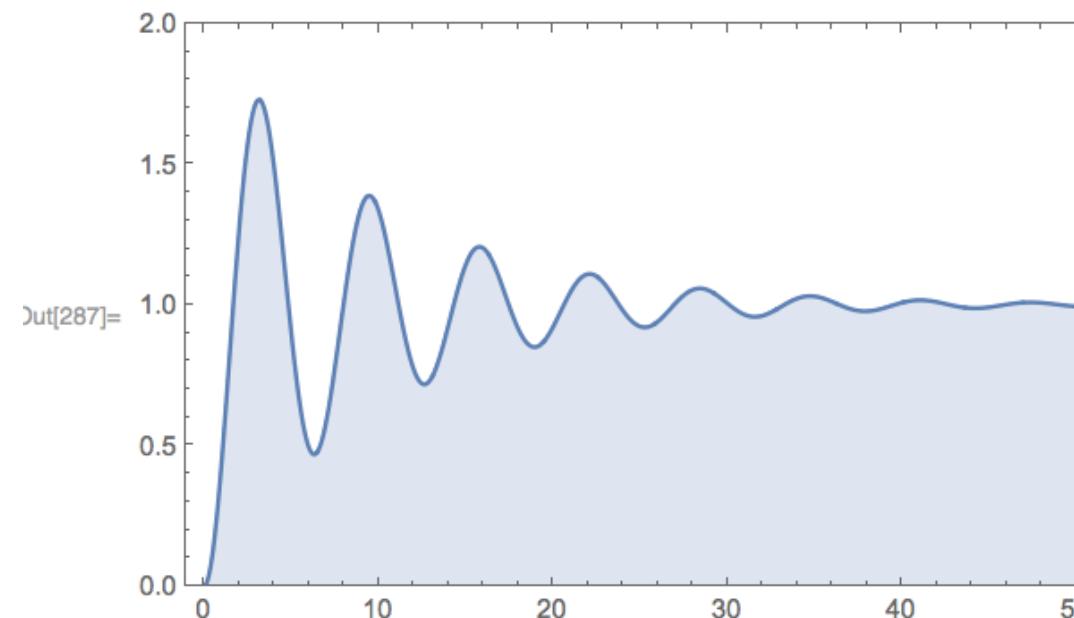
```
In[287]:= Plot[Step1, {t, 0, 50}, PlotRange -> {0, 2}, Frame -> True, Filling -> Axis]
```





Simulation:

