



# Exercise: Gain Stage


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg



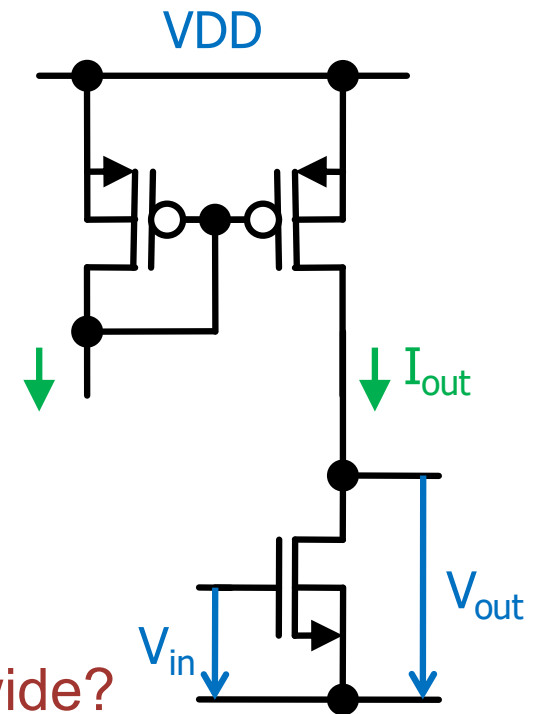
# 1. Basic Gain Stage

- Implement a NMOS gain stage.
  - Use real transistor models ('nmos', 'pmos')
  - Use a NMOS with  $W/L = 1\mu/0.5\mu$
  - Use a PMOS of  $W/L = 1\mu/1\mu$
  - Bias the PMOS with a *mirror* to  $10\mu\text{A}$
  - Operate at  $V_{DD} = 1.8\text{ V}$
- Sweep  $V_{in}$  and observe  $V_{out}$
- What is the largest gain (derivative!) ?
- Why is the 'upper' part of the curves so wide?
- Change
  - the bias current
  - $W, L$  of the input transistor
 and observe what happens. Explain!  
 Why can't you increase gain more with  $W, L$  changes?
- Can you operate at  $100\mu\text{A}$ ?





# Solution 1

 


- $W_N=1\mu$ ,  $L_N=0.5\mu$  -> gain  $\sim -37$
- $W_N=2\mu$  -> gain  $\sim -42$
- $L_N=2\mu$  -> gain  $\sim -31$ ! This is because  $r_{ds}$  of the PMOS limits!  
With an ideal current source, gains are  $(65/115)$  for  $(0.5/2)\mu$


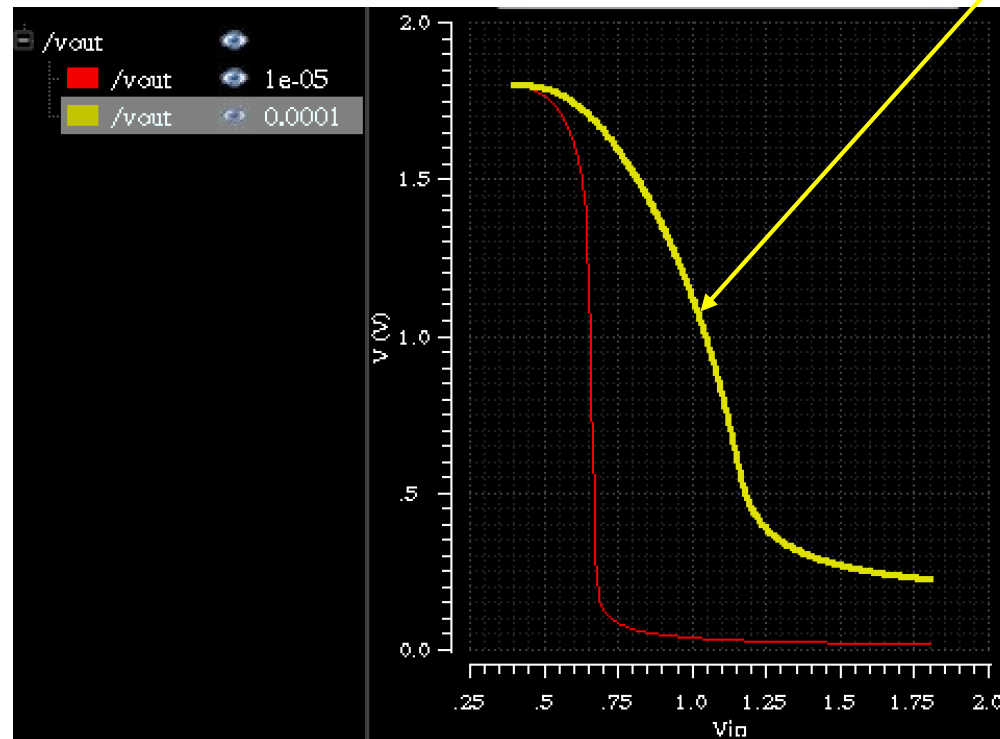
# Solution 1

- At 100 $\mu$ A, the PMOS is nearly always in the linear region.
- The circuit has too small gain



- In order to operate at 100 $\mu$ A, the PMOS must be made shorter and/or wider.





## 2. Operation point

- Use the trick explained in the lecture to set the operation point
  - Use for instance  $C=1\mu\text{F}$ ,  $R=100\text{M}\Omega$
- Make an AC sweep


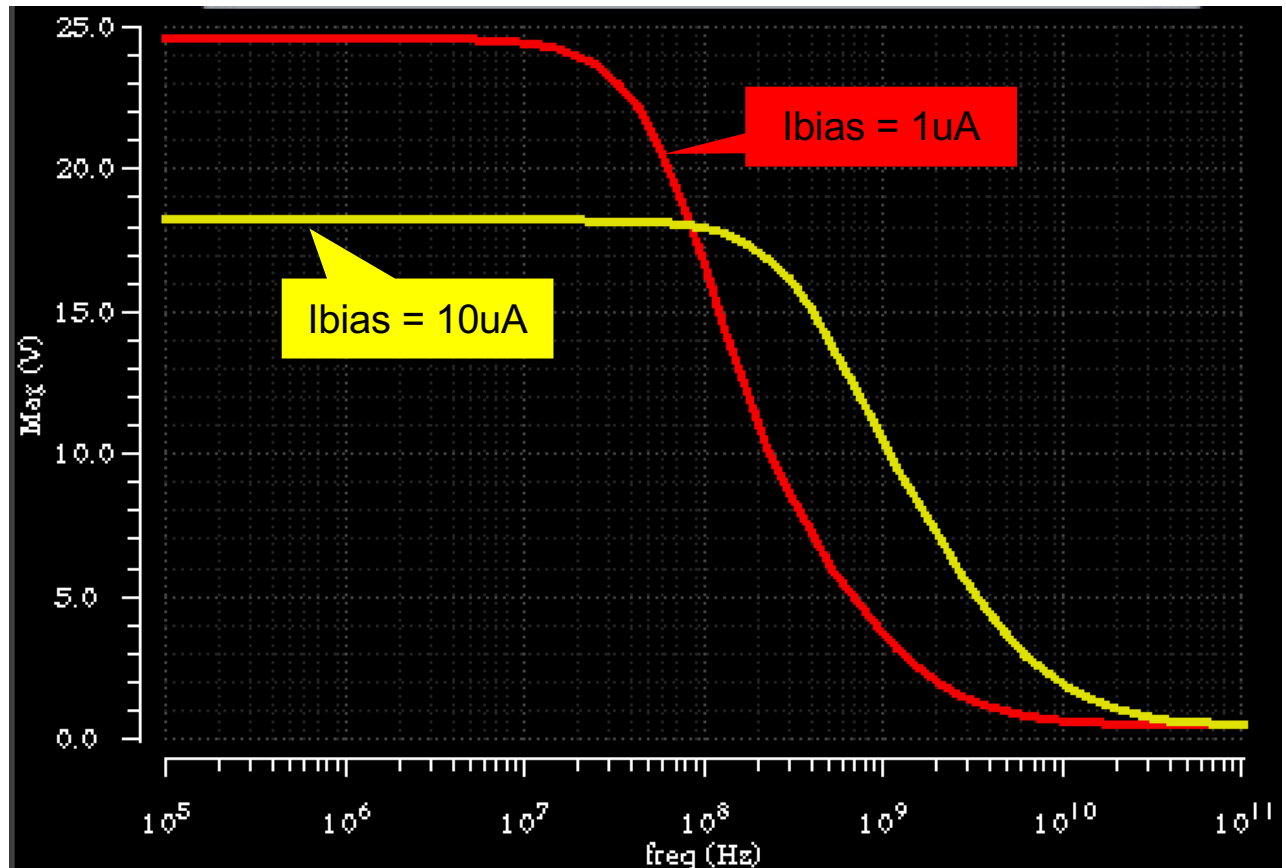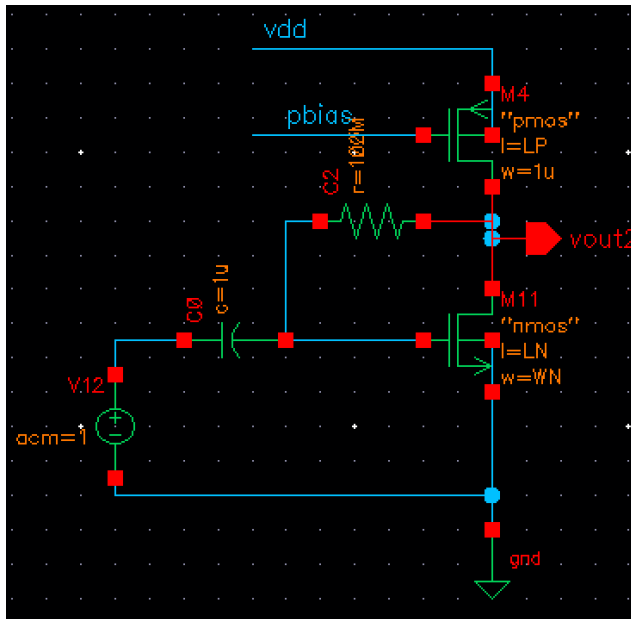
# Solution 2

- Comparing for instance two currents:
- Higher current → less gain, but higher bandwidth






## 3. Bandwidth

- Load the gain stage with a capacitor (1 pF)
- Observe the bandwidth
  - best use the 'automatic' operation point
  
- Modify the load capacitor
  - Is bandwidth inversely proportional to  $C_L$ ?
  
- Modify  $I_D$ 
  - Make a Parametric Sweep with 2-3 values (0.1  $\mu$ A, 1  $\mu$ A, 10  $\mu$ A)
  - Do you find what you expect?


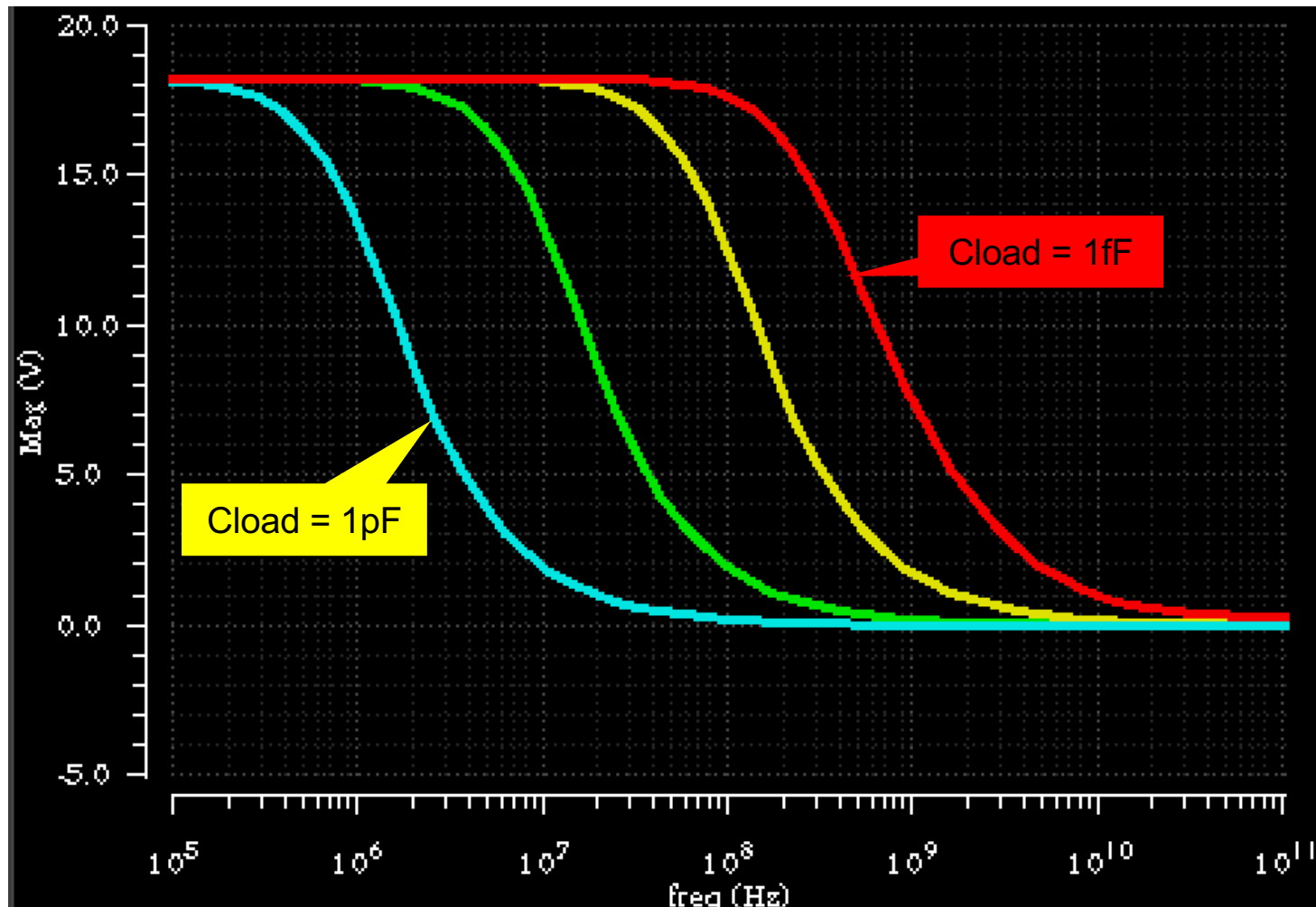
## Solution 3

- Higher Load cap  $\rightarrow$  less bandwidth. Proportional.
- For load cap  $\rightarrow$  0fF, bandwidth is limited by caps in MOS








## 4. PMOS Amplifier

- Design a PMOS gain stage (with a NMOS current mirror load)


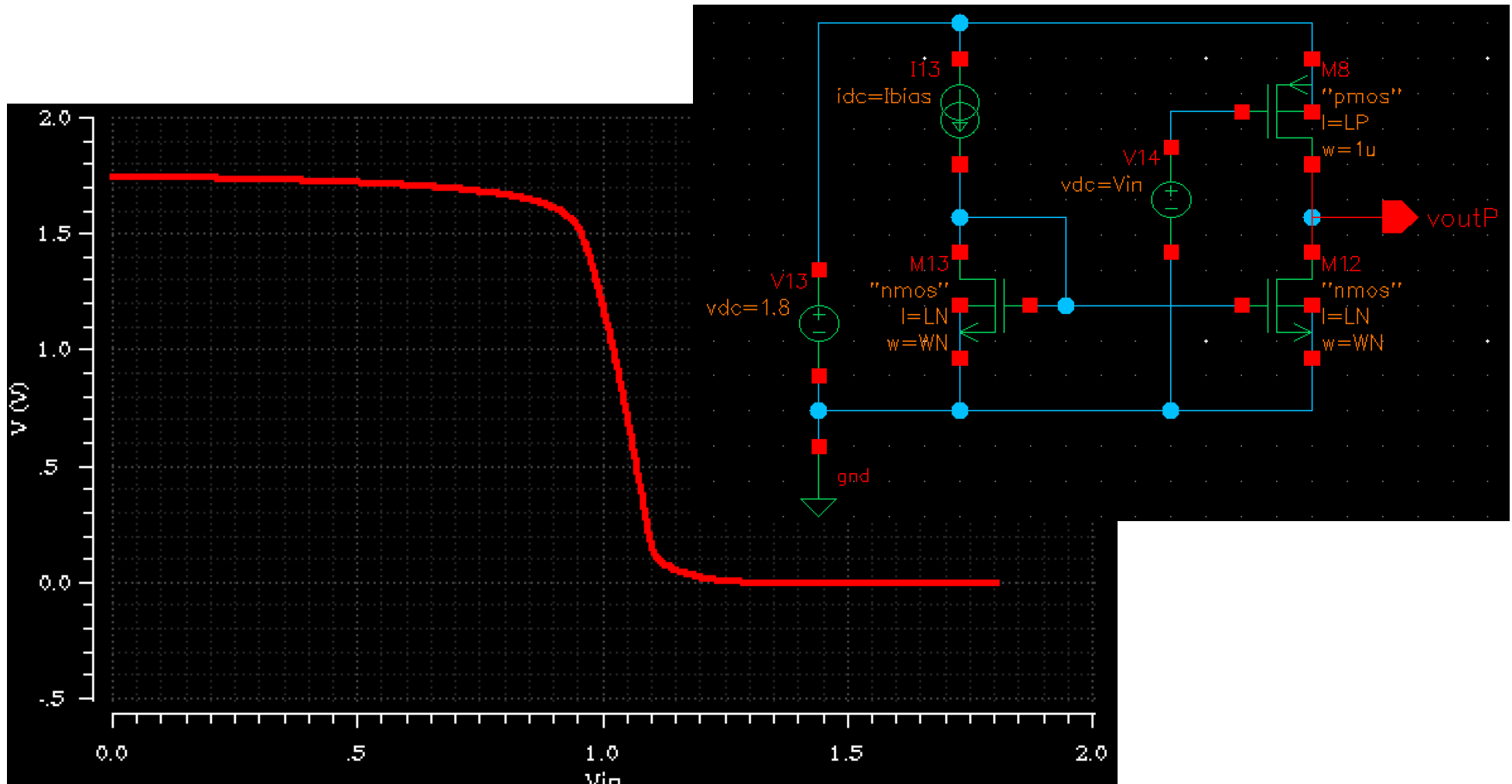
# Solution 4:

- Note: In this case, Ground is reached 'exactly' (when the gain PMOS is off) and VDD is only approached.






## 5. Cascoded Gain stage

- Set up a cascoded gain stage with NMOS input
  - Use  $W/L = 5\mu / 0.4\mu$  for all 4 MOS
  - Use  $I_{\text{bias}} = 10 \mu\text{A}$
  - Use bias voltage  $V_{\text{CN}}$  for the NMOS cascode,  $V_{\text{CP}}$  for the PMOS
  - Chose 'safe'  $V_{\text{CN}}$ ,  $V_{\text{CP}}$  so that the underlying MOS are saturated
  
- Simulate
  - Make a DC sweep. What is the gain ?
  - Try different  $V_{\text{CN}} / V_{\text{CP}}$  voltages. Observe and explain!
  - Use a stacked mirror generating  $V_{\text{CP}}$ . Is that ideal?
  
- Make an AC sweep with a load of  $C_{\text{load}} = 100\text{fF}$ 
  - Check that  $v_{\text{out}} = v_{\text{in}}$  is a good operation point for AC analysis
  - Determine the gain with an AC sweep. Is it the same as above?
  - Simulate a non-cascoded gain stage in parallel an compare



# Solution 5: Cascoded NMOS gain stage

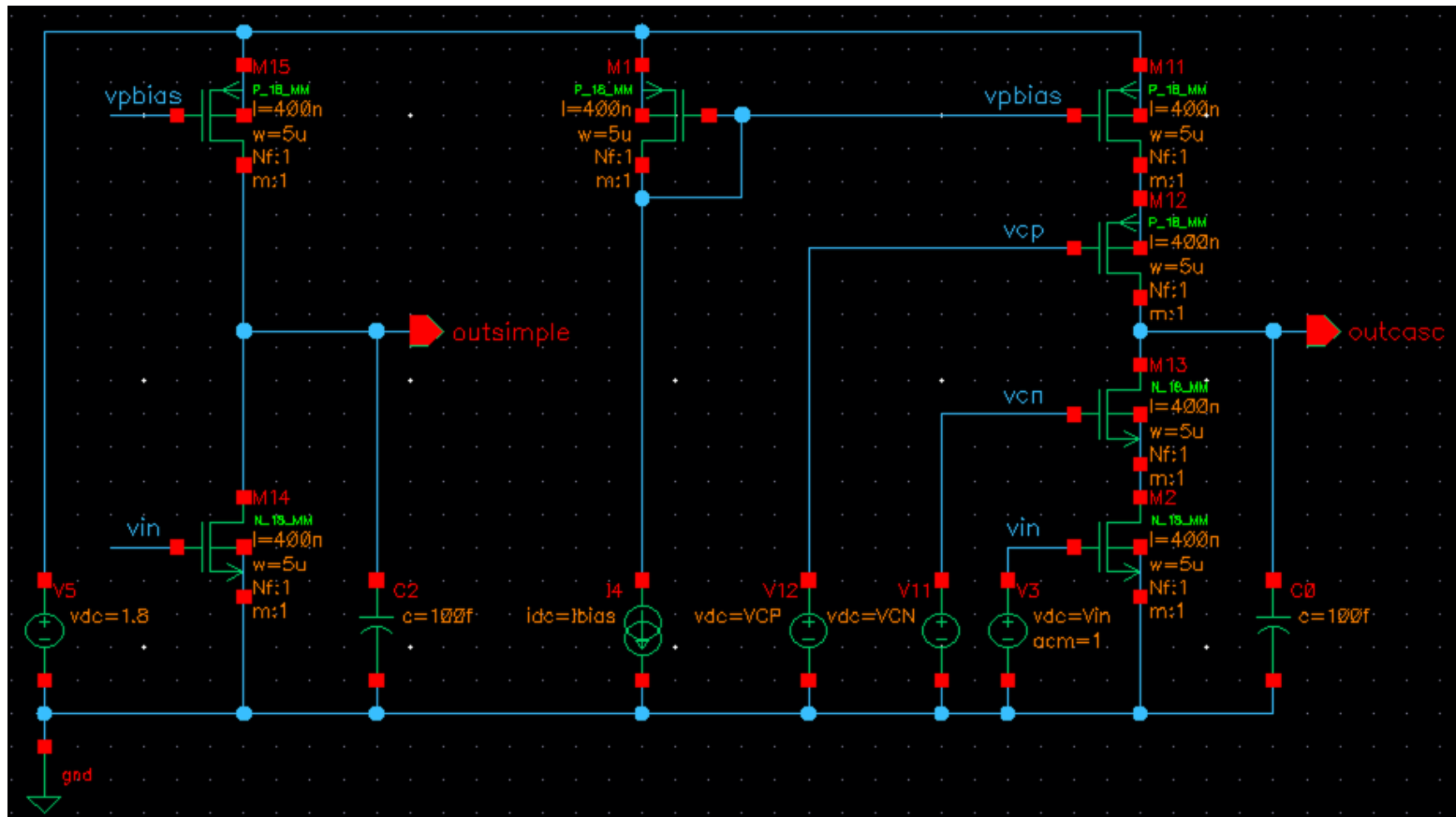


- VCN must be high enough so that the input NMOS (M2) is saturated:  $V_{CN} = V_{th,N}$  (of the cascode) +  $V_{dsat}$  (of M2) +  $V_{dsat}$  of the cascode  $> \sim 0.9V \rightarrow$  start with 1V
- Similarly VCP must be  $> \sim 0.9V$  below VDD  $\rightarrow$  start with 0.8V


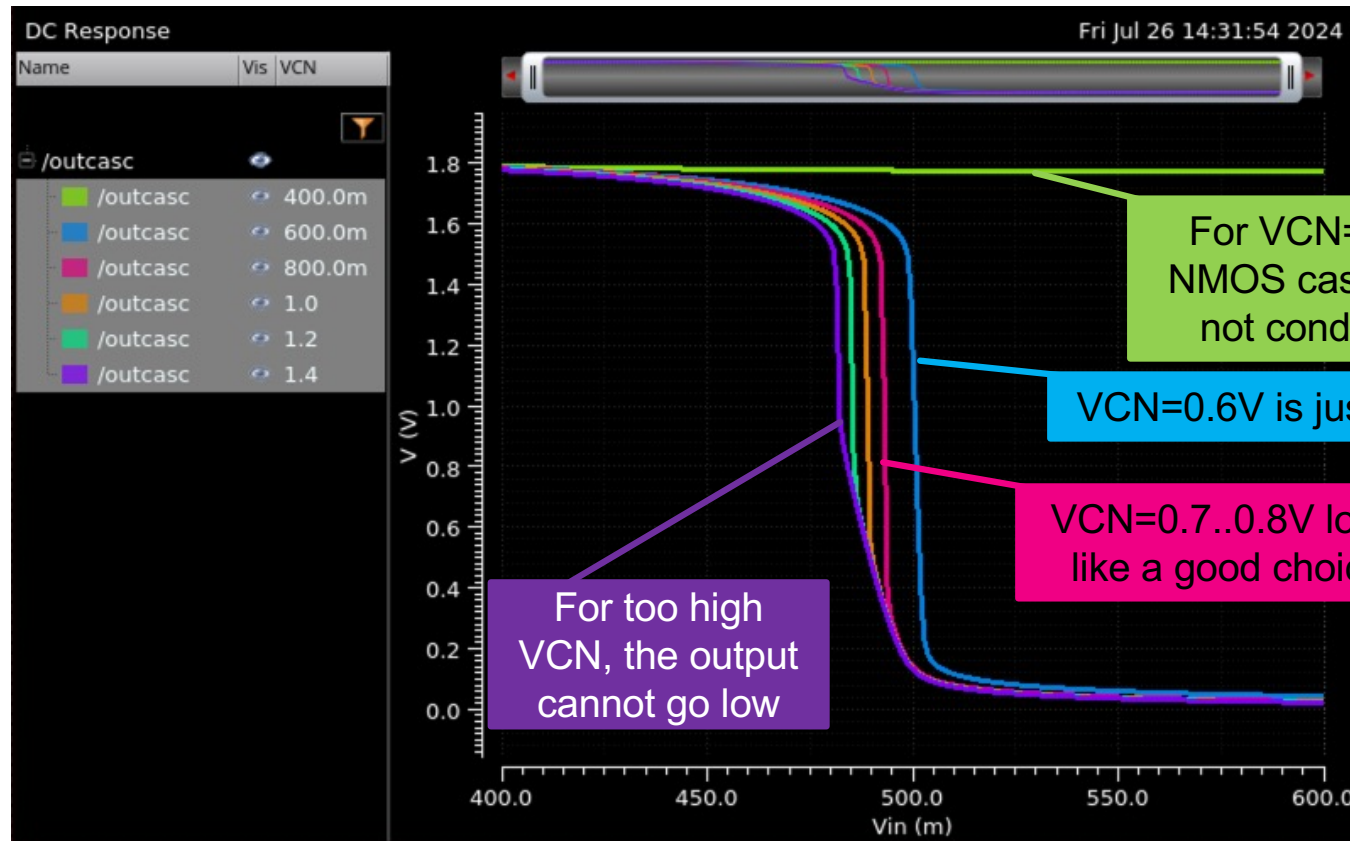
# Solution 5: Cascoded NMOS gain stage

- The switching point is just above the NMOS threshold.
- Trying different VCN (for VCP = 0.8V):




- Note that more headroom is needed for higher currents because  $V_{dsat}$  increases!





# Solution 5: Cascoded NMOS gain stage

- Trying different VCP (for VCN = 0.8V):

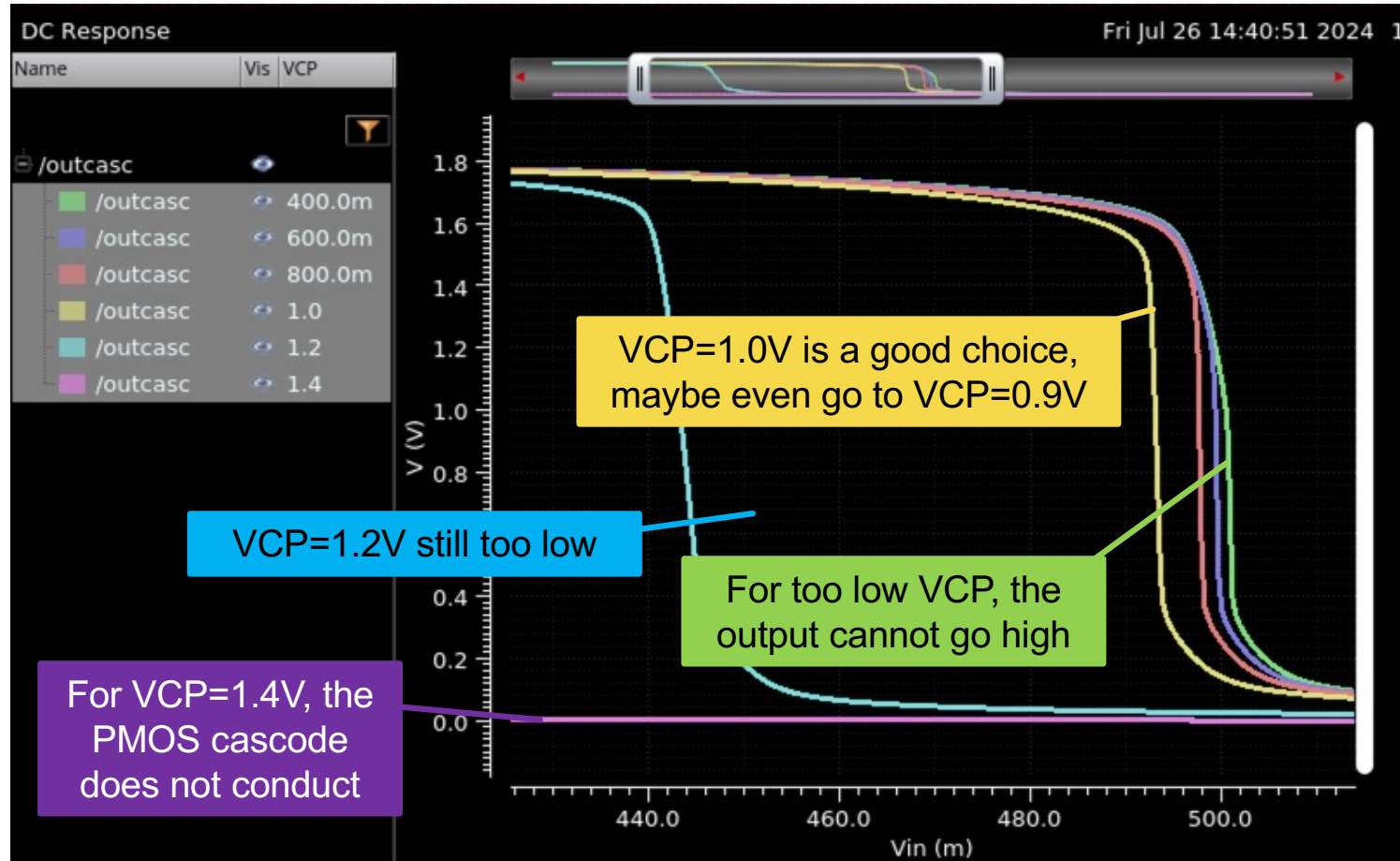



# Solution 5: Stacked PMOS mirror ?

 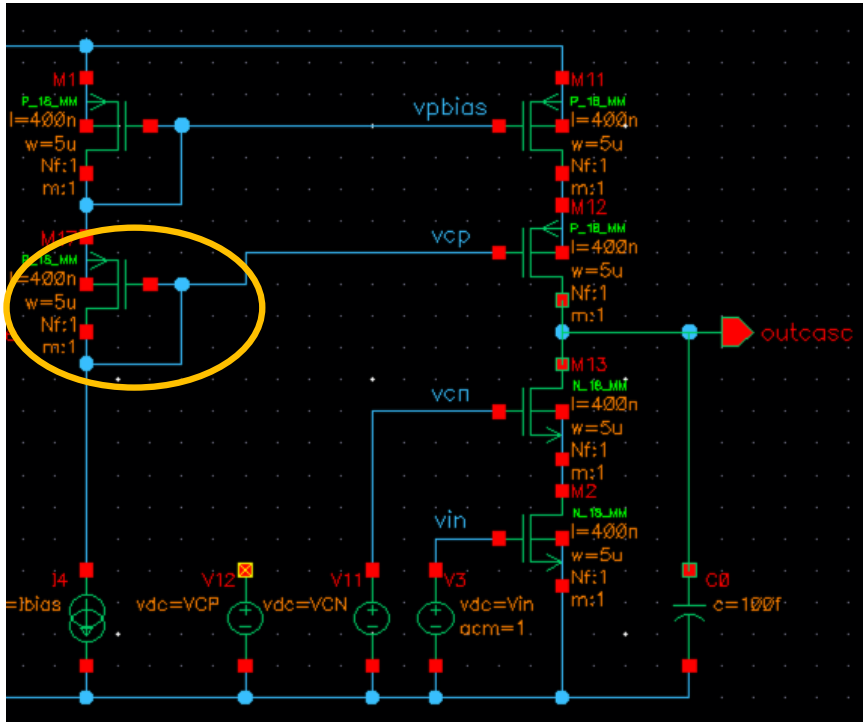


- With stacked PMOS mirror, VCP is only 0.5V
- This is too low. The output cannot go high.  
→ The stacked mirror is wasting too much dynamic range!


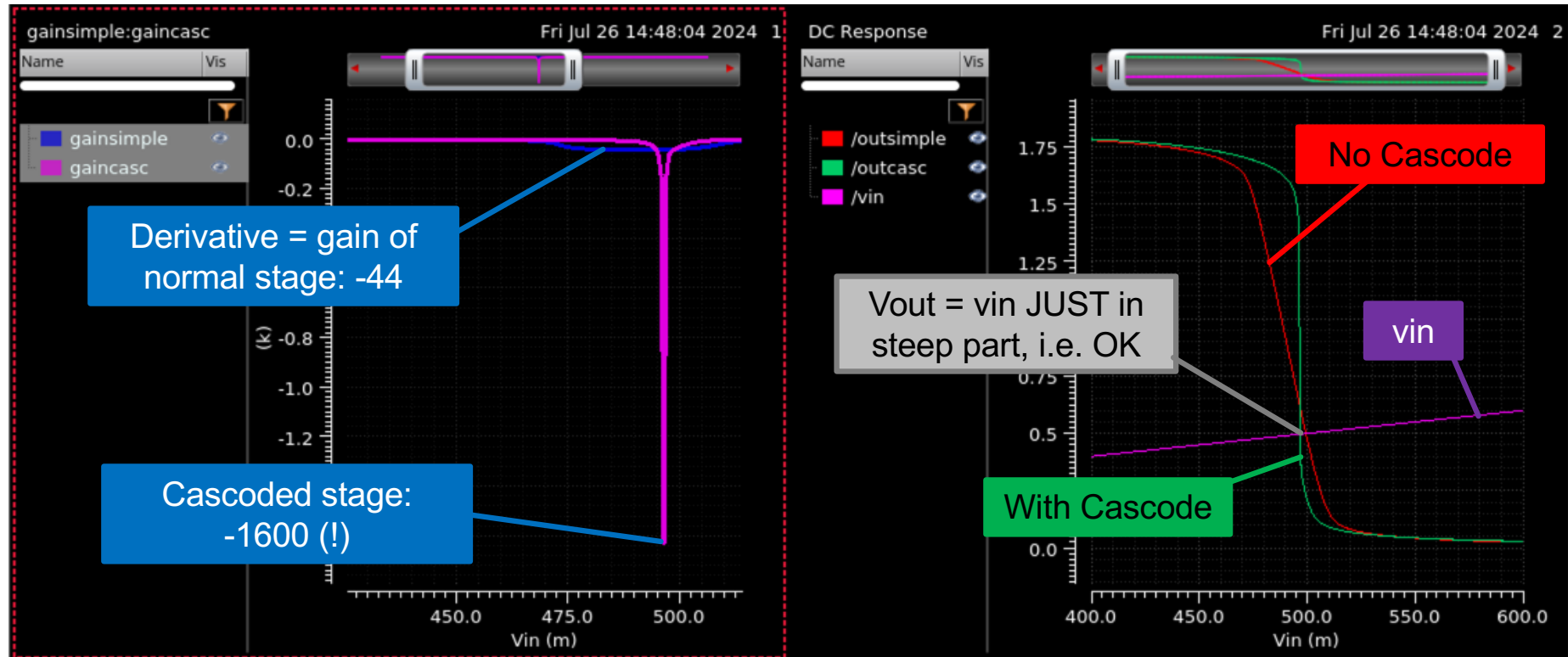
# Solution 5: DC Gain

- For  $V_{CN}=0.8V$  and  $V_{CP}=0.9V$ :




- DC feedback, i.e.  $v_{out} = v_{in}$  is just ok for the cascoded stage, because we are still in the steep high-gain part (see right side)






# Solution 5: AC gain

- Using DC feedback as in lecture:

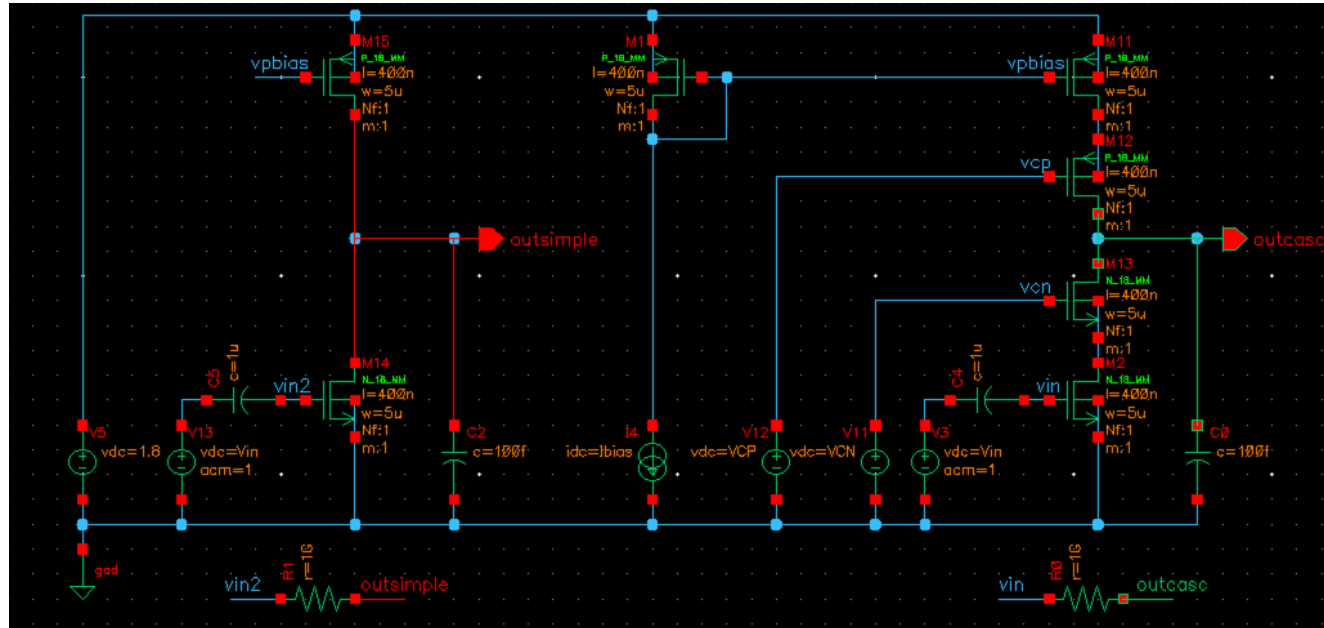

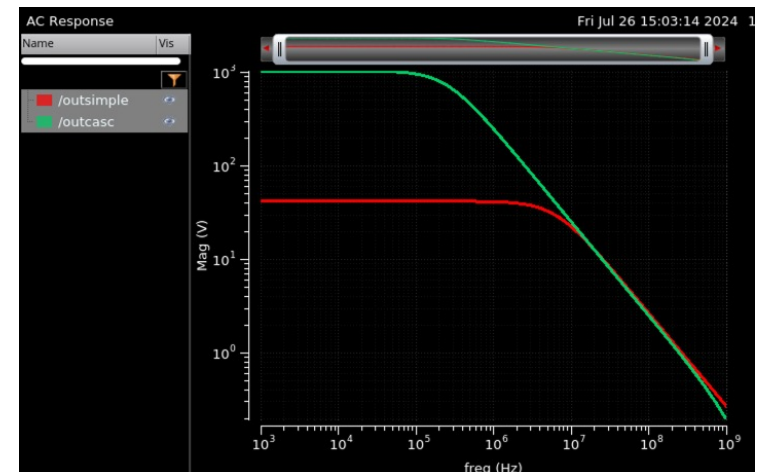
- AC gain is 42 and 1040 (using UMC transistor models)
- Close to DC. Difference is due to operation point.
- GBW is the same!




 
## 6. The Inverter

- The PMOS 'load' in the gain stage supplies a more or less constant current
- In the CMOS Inverter shown, the PMOS is switched with the input signal, it acts as the NMOS
- Simulate the DC transfer function  $V_{out}(V_{in})$ 
  - For instance  $L_N = L_P = 0.5\mu$ ,  $W_N = 1\mu$ ,  $W_P = 2\mu$
  - What is different from the normal gain stage ?
  - What is the maximum gain ?
- Use a small signal analysis to find the gain





## Solution 6: Inverter

- For gain derivation, see lecture slides.
- The output now reaches gnd and vdd fully
- The current is not constant, it depends on  $V_{in}$ . This is bad!

