



# Exercise: Source Follower and Differential Amplifier

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg



# 1. NMOS Source Follower

- Implement an NMOS Source follower
  - Use an NMOS with  $W/L = 1\mu / 0.2\mu$
  - Connect Bulk to Source
  - Use an NMOS mirror with  $W/L = 1\mu / 0.5\mu$  as current source
  - Bias the circuit with  $10\mu A$
  
- Perform a DC and a transient analysis
  - What is the gain?
  - What happens for low input voltages? Why?
  - How does the gain change when you connect the bulk of the SF - NMOS to ground?



## 2. *PMOS* Source Follower

- Now draw a ***PMOS*** source follower with the same transistor dimensions & current...
- Which input voltages are now problematic?




### 3. (Optional: SF Instability)

- Repeat the situation from the lecture slides:
  - SF driven by a (large) source impedance
  - Added load capacitance
  - Added capacitance between input and output (an exaggerated  $C_{GS}$ )
- Observe the overshoot in the transient response for a step input or the increased gain in an AC sweep.



## 4. Differential pair

- Draw a differential NMOS pair

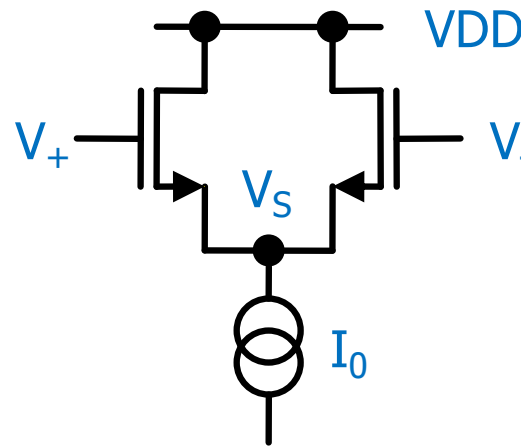


- Set  $V_- = 1\text{ V}$  and vary  $V_+$  from 0 to  $V_{DD} = 2\text{ V}$ 
  - Observe  $I_+$ ,  $I_-$  and the 'tail' voltage  $V_S$ .
  - Explain what you see!
- Change the bias current  $I_0$  or the transistor dimensions.
  - Observe how the switching region changes (i.e. which voltage difference is needed to switch fully). Do you understand?


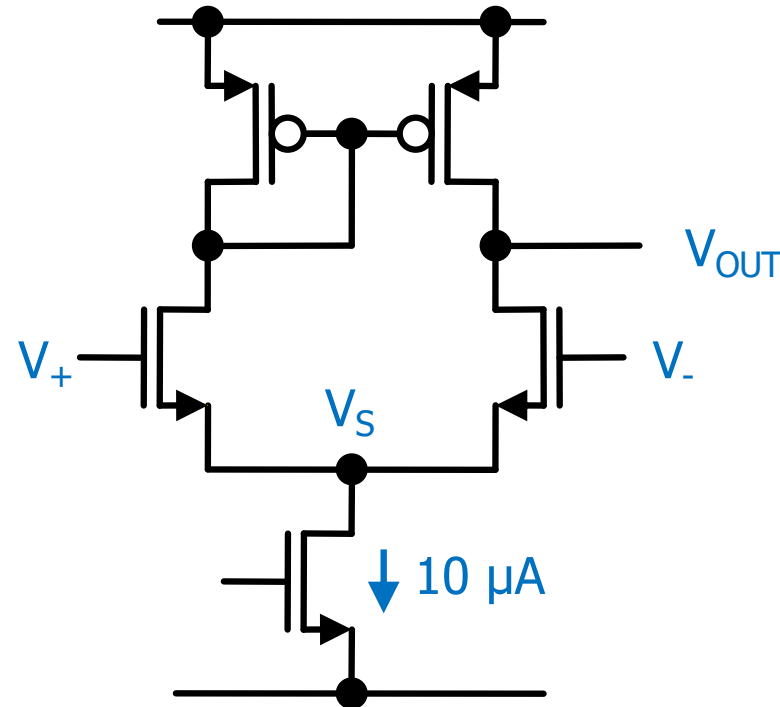
## 5. Differential Amplifier

- Draw a full differential amplifier. Start with all  $W/L = 1\mu/0.5\mu$



- Start with  $V_- = 0.5V$
- What is the gain at the switching point?
  - Use a DC sweep. Also try an AC sweep with appropriate bias.
- Check the large signal behavior for different  $V_-$ .



## 6. *PMOS* Differential Amplifier

- This exercise is only useful if you have problems to switch from NMOS to PMOS circuits...
- Draw a full differential amplifier with a PMOS input stage
  - You must also change the other MOSs...



## 7. Mirrored Amplifier

- Implement the mirrored amplifier from page 23 of the lecture slides.
- Sweep  $V_+$  for various constant  $V_-$ . Observe the output. What is the difference to the normal differential amplifier?
- When used as transconductor (driving in a constant output voltage), what output voltages are possible?