



# Current Mirrors


Our first 'useful' circuit

(you will understand later THAT this is REALLY useful)


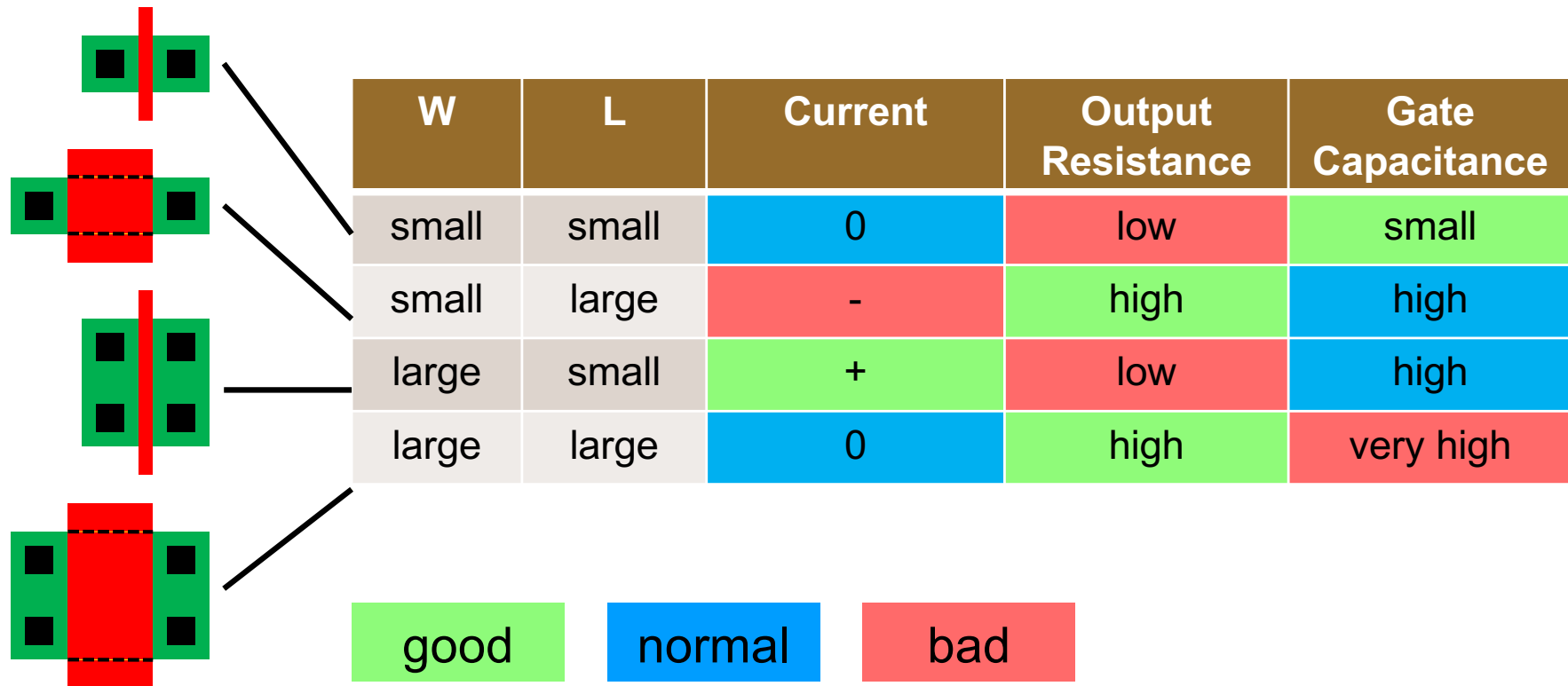
# Reminder: Effect of Transistor Sizes


- Very crude classification (at constant  $V_{GS}$ ):



- There is no 'perfect' size – all depends on what we need!



# Reminder: Transistor Characteristics

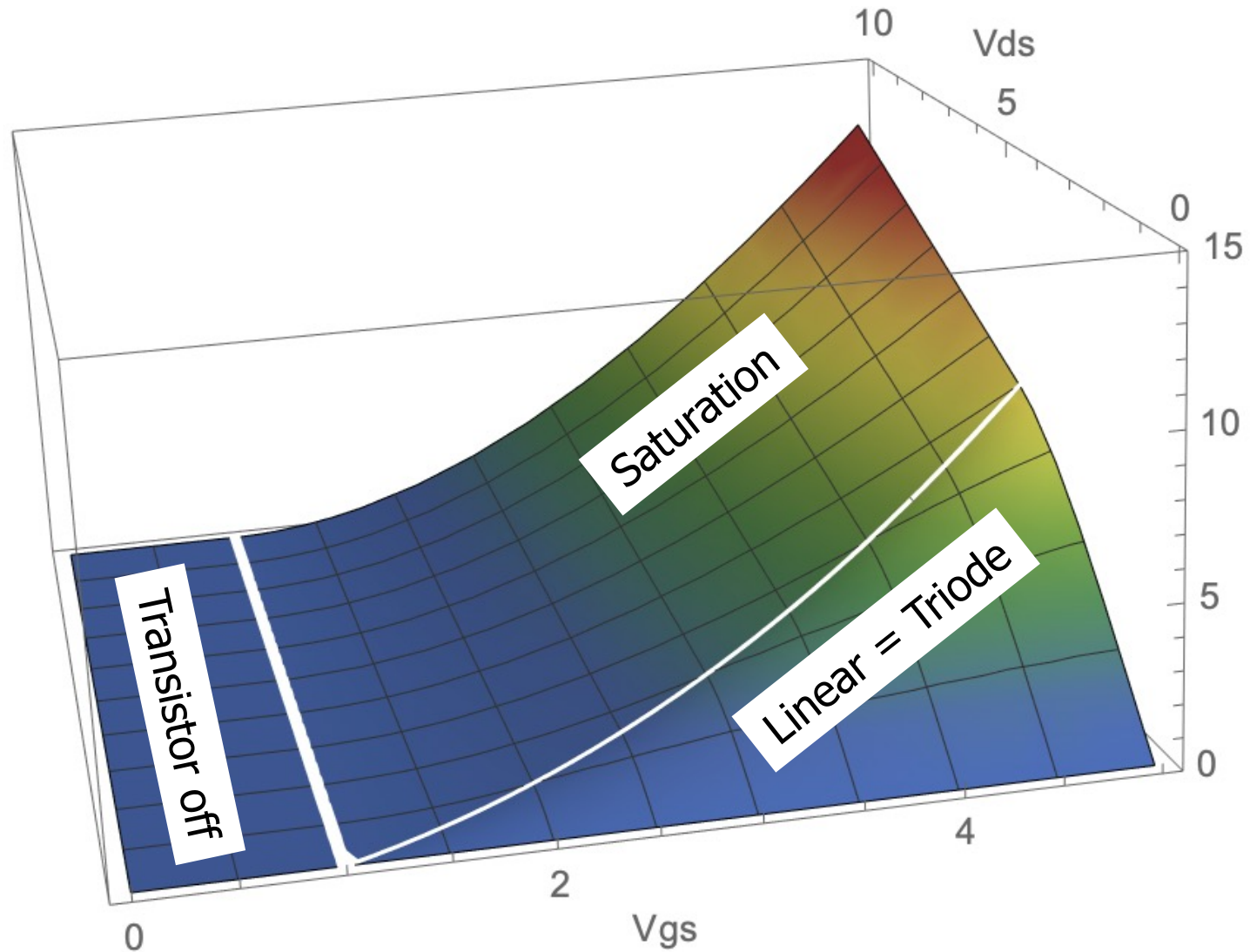




# Reminder: Threshold and Saturation Voltage

$$I_D = \frac{K}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \beta (V_{GS} - V_T)^2$$

$$V_{D,Sat} = V_{GS} - V_T = \sqrt{\frac{I_D}{\beta}}$$

$$V_{GS} = V_T + V_{D,Sat}$$

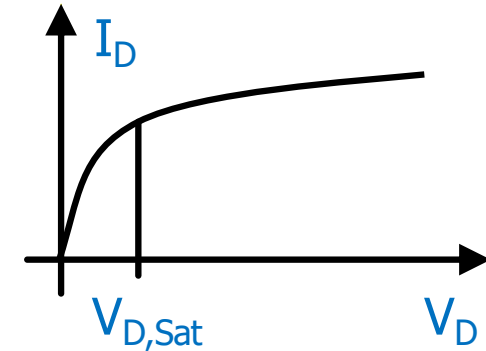

$$K \approx 100 \mu A/V^2, W \approx 1 \mu m, L \approx 0.2 \mu m \rightarrow \beta \approx 250 \mu A/V^2$$

$$\text{For } I_D = 10 \mu A \rightarrow V_{D,Sat} \approx 0.2 V$$



- This is all *only* valid for strong inversion (at 'large' currents)
- $V_{D,Sat}$  increases with larger current (with the  $\sqrt{\quad}$ )


  
# The Diode-Connect MOS

- Consider a MOS with Drain and Gate connected
- $V_{DS} = V_{GS} \rightarrow V_{DS} = V_{GS} > V_{GS} - V_T = V_{DSat}$

→ A diode connected MOS is always in saturation!



$$I_D = K/2 W/L (V_{DS} - V_T)^2 (1 + \lambda V_{DS})$$


(in 'strong inversion')

- Important:

For *any* current  $I_D$ ,  $V_{GS}$  adjust so that this current can flow!



# Illustration: $V_{DS}=V_{GS}$

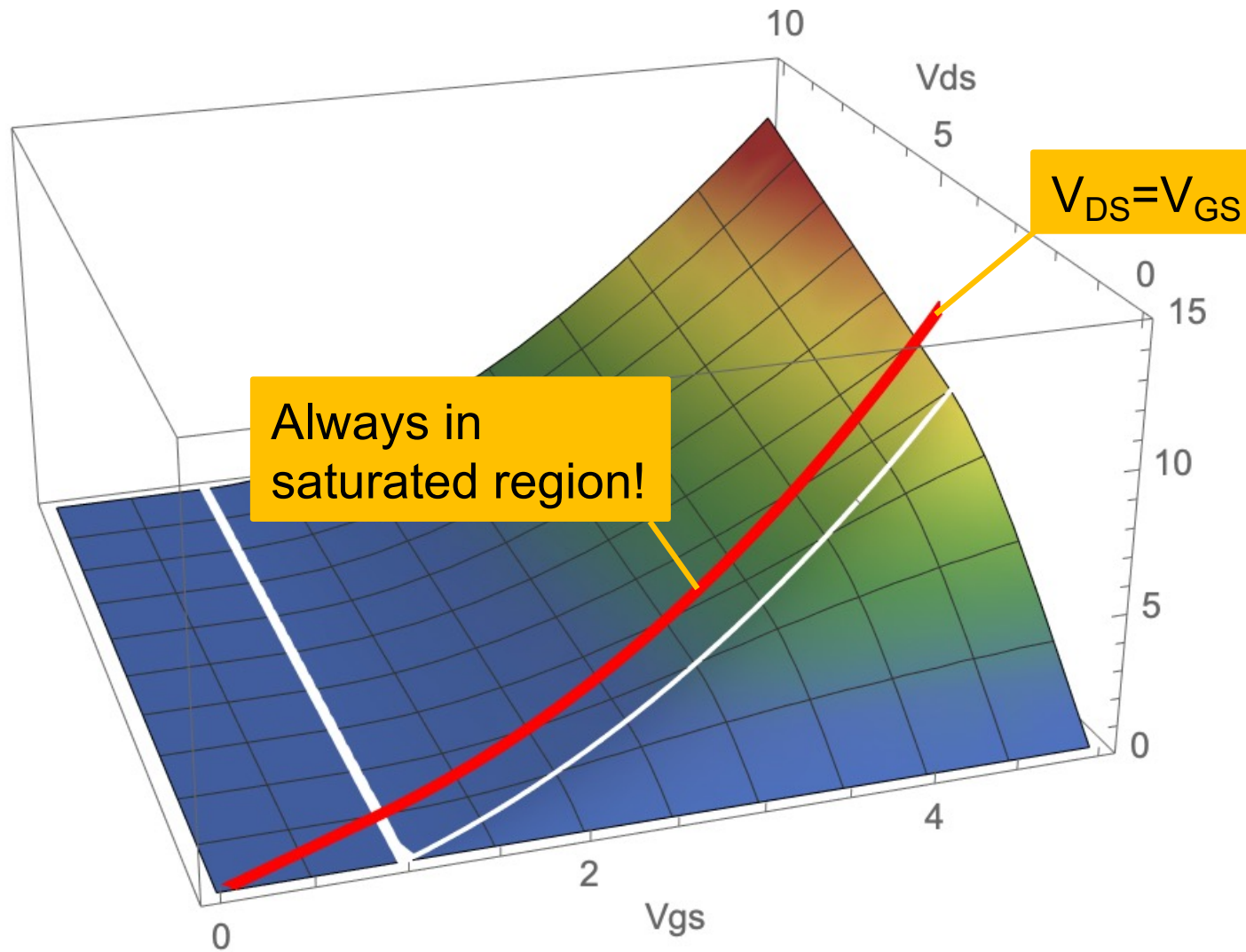



# THE CURRENT MIRROR



# Transistors with same $V_{GS}$

- Consider 2 NMOS with same  $V_{GS}$ :


- Assuming saturation:

- $$I_1 = \frac{K}{2} \frac{W_1}{L_1} (V_G - V_T)^2 (1 + \lambda_1 V_{D1})$$
- $$I_2 = \frac{K}{2} \frac{W_2}{L_2} (V_G - V_T)^2 (1 + \lambda_2 V_{D2})$$

- $$\rightarrow \frac{I_2}{I_1} = \frac{W_2/L_2}{W_1/L_1} \frac{1 + \lambda_2 V_{D2}}{1 + \lambda_1 V_{D1}}$$

- For  $L_1 = L_2$ :

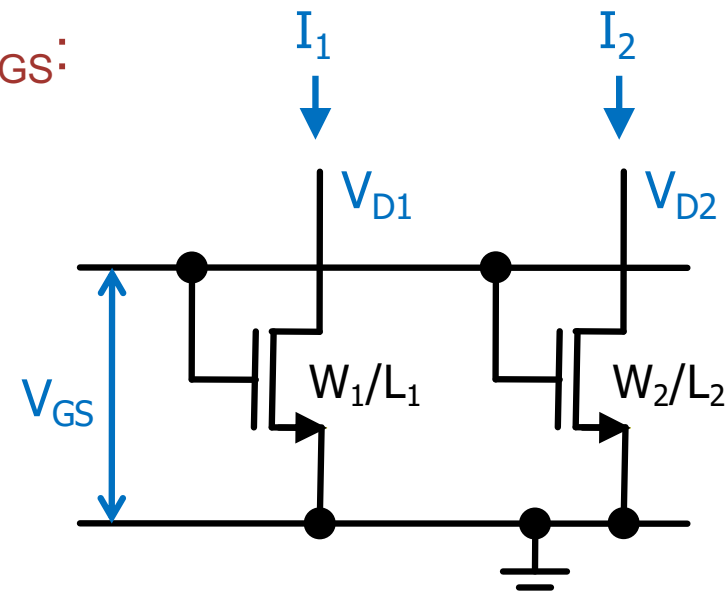- The ratio of input/output current is roughly given by the ratio of the  $W$ s
- The Early effect leads to a ,small' deviation
- The Early effects cancel if  $V_{D1} = V_{D2}$  (for same  $\lambda$ )







 
# The Current 'Mirror'

- First, we assume that  $M_1$  and  $M_2$  are identical
  - $W_1 = W_2, L_1 = L_2$
- Now connect  $M_1$  as a diode
  - $V_G$  adjusts such that  $I_{in}$  flows into  $M_1$
- $M_2$  and  $M_1$  have the same gate voltage  $\rightarrow I_{out} = I_{in}$ 
  - The current is 'mirrored' from the input to the output




- In more detail, Early Effect must be taken into account
  - $I_{out} = I_{in}$  *exactly* only for  $V_D = V_G$  (do you understand why?)


 
# Varying the Output Current

- If  $W_2 \neq W_1$  (assuming still  $L_1=L_2$ ), then  $I_{out} = W_2/W_1 I_{in}$
- $L_1 \neq L_2$  should be avoided because Early Effects (i.e.  $\lambda_s$ ) are different
- Additional MOS can be connected to give further outputs




- The gate voltage of the sources is called a '*Bias*' Voltage
  - It should be 'decoupled' with capacitors to *the source potential* to be 'stable' and noise free.



 
# Large W vs. Multiple MOS

- The *ratio*  $W_2/W_1$  is used for current multiplication
- If this is implemented by MOSs with different layouts, *edge effects* can lead to unknown ratios.
  - To be more precise, the real W of a device is often  $W_{\text{real}} = W_{\text{drawn}} - W_{\text{offset}}$  ( $W_{\text{offset}}$  can have both signs)



 
- Real Ratio  $\neq$  Drawn Ratio!  $\rightarrow$  use *multiple identical* devices!
- For a non-integer ratio  $A/B$ , use  $B$  MOS on diode side and  $A$  MOS on output side. (In practice, add 'dummy' devices for matching)





# The PMOS Mirror

- Here is how a PMOS mirror looks like:


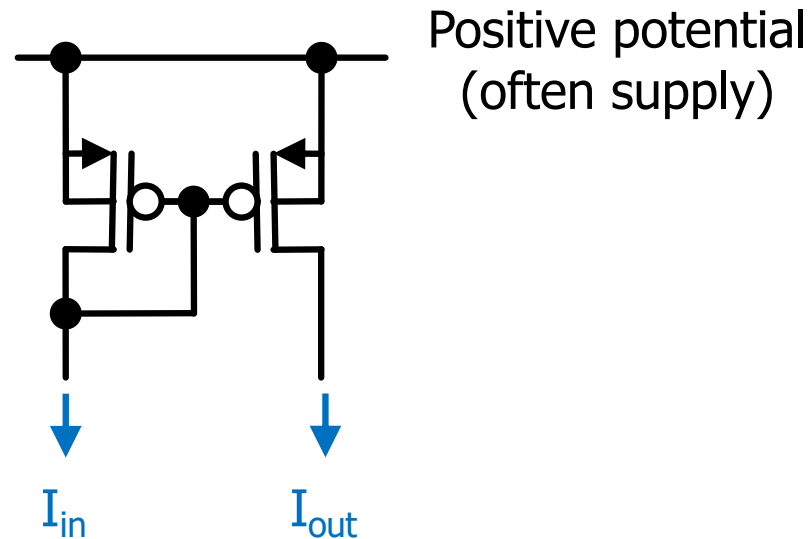


- Same principle and topology.
- Inverted polarities.


 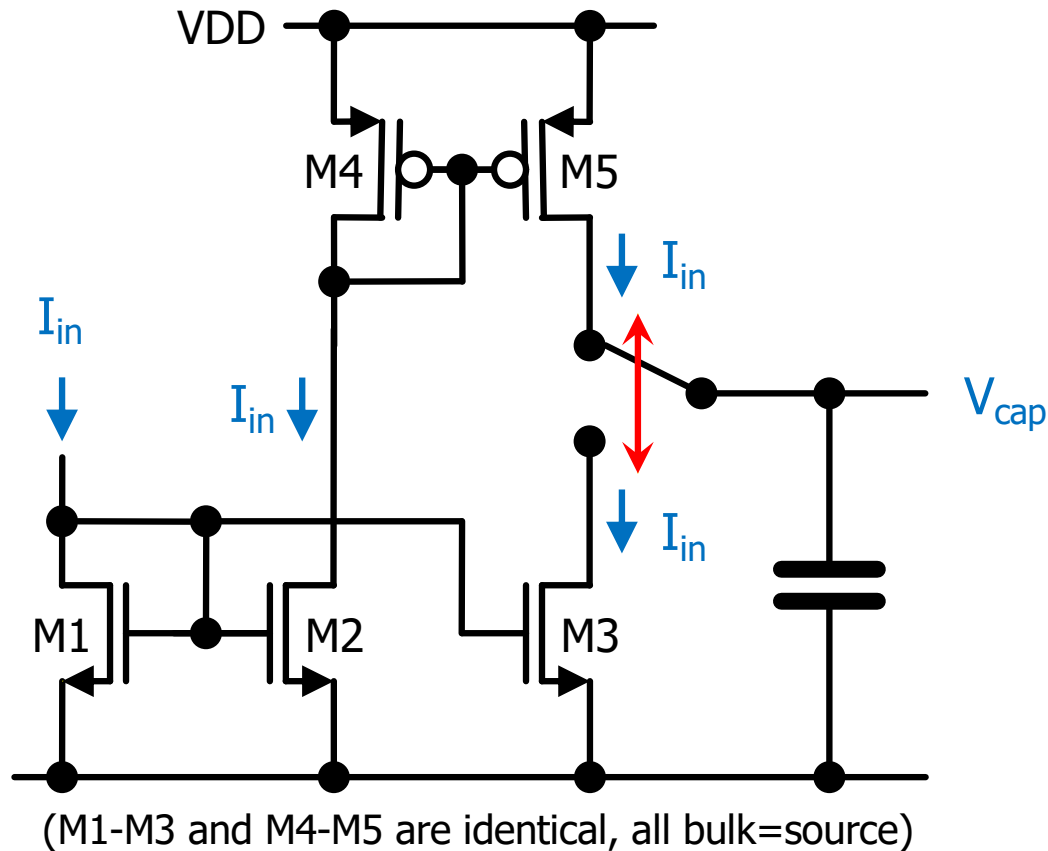
# A Possible Application: Triangular Waveform

- A capacitor is charged / discharged with same current




- Switches: MOS with large W/L controlled by 0/VDD
- Switching could be done by comparing  $V_{cap}$  to a high- and low- level...


 
# Output Resistance

- The Output Resistance  $r_{out}$  of the Mirror is just that of the (output) MOS
- This is obvious from the small signal model
  - The Gate voltage is *constant*, so there is *no small signal*:  $v_{gs} = 0$





- $r_{ds}$  depends on the current and on the geometry (W,L)


 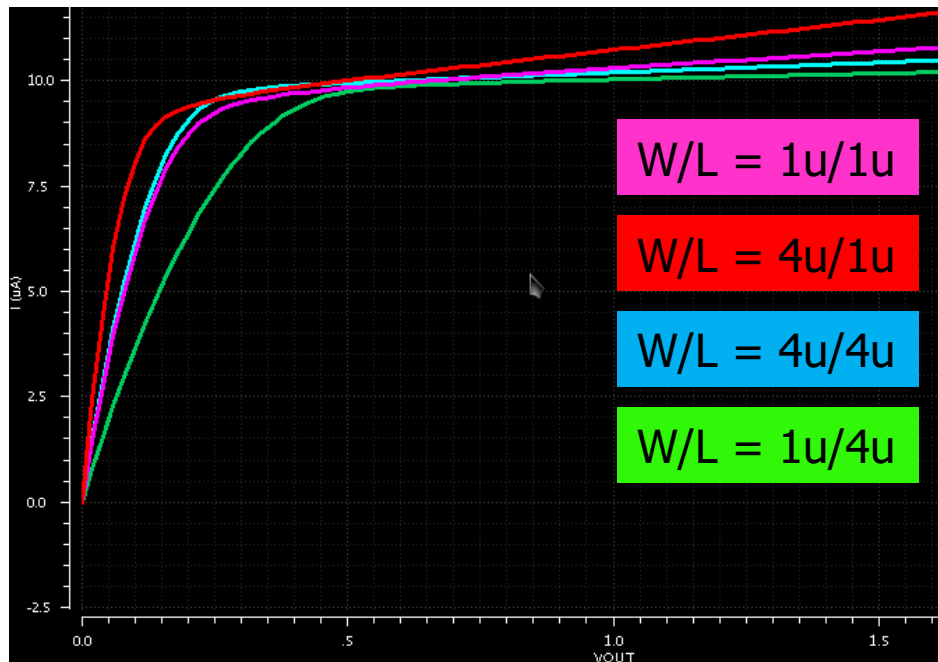
# Good and Bad Mirrors

- Normally, the output MOS of the mirror is used as a *current source*. We therefore want
  - high output resistance  $r_{ds}$  → we need small  $I_D$ , large  $L$
  - low saturation voltage → we need small  $I_D$ , small  $L$ , large  $W$



- Therefore: Good mirrors must have large  $L$  and  $W$ 
  - large  $L$  to increase output resistance
  - large  $W$  to lower saturation voltage




# THE CASCODE




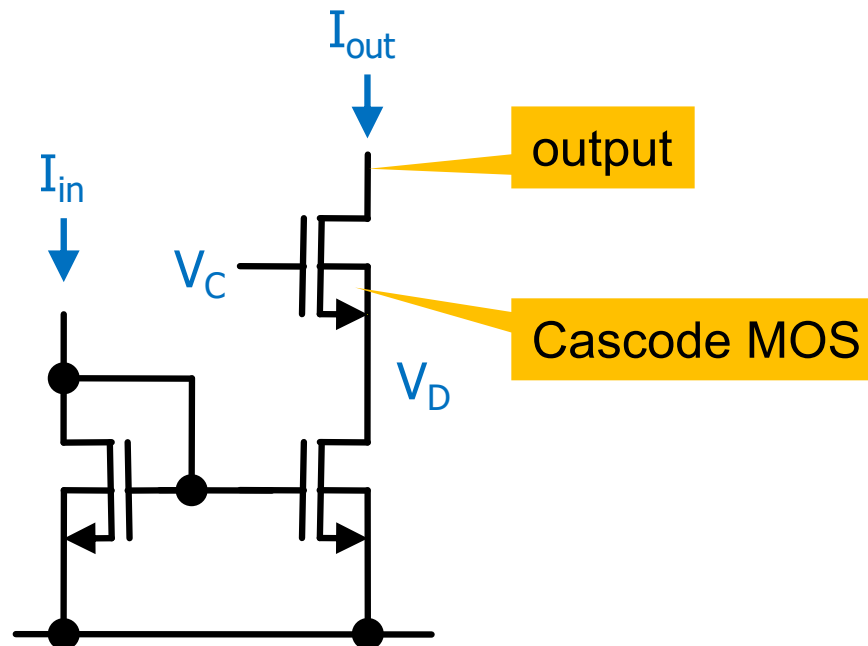
# Improving the Mirror: The Cascode


- The output current in a normal mirror changes, because output voltage = drain voltage
- By inserting another MOS *between* output and drain, the drain voltage is kept (more) constant
  - the output current changes (less)
  - the output resistance is higher 😊
- The upper MOS is called a **CASCODE** (transistor)






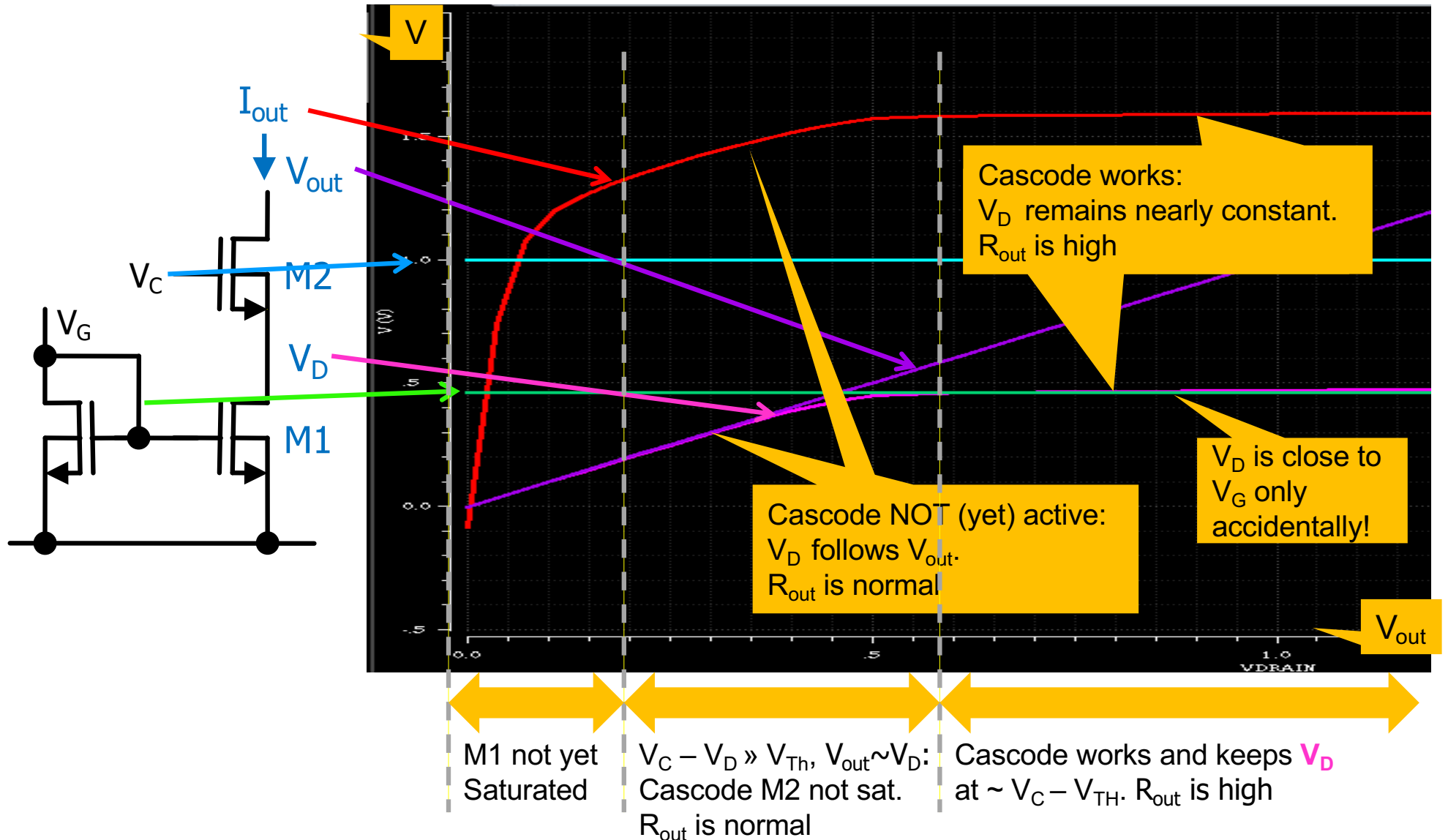
# The Cascoded Current Source in Action

- Simulation for  $V_C = 1V$  (not optimal, see later...)






# Using model 'nmossimple' :

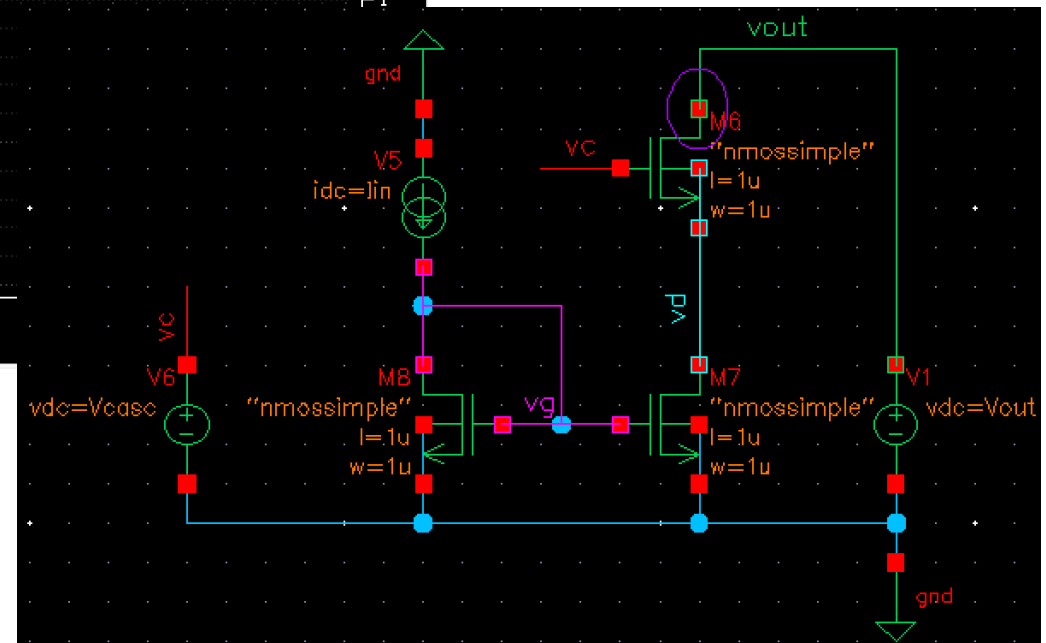 


 
# Crucial: Correctly Biasing the Cascode


- The *gate* voltage of the cascode MOS M2,  $V_C$ , defines the *drain* voltage  $V_D$  of the 'current setting' MOS M1
  - $V_D$  is *roughly one threshold* voltage below  $V_C$
  - More precisely,  $V_D = V_C - V_T - \text{Sqrt}(I_D \cdot 2/K \cdot L/W)$
  - (This holds when Bulk and Source are connected (-), otherwise, the Substrate Effect lowers  $V_D$  even more)
  
- $V_D$  (and thus  $V_C$ ) should be chosen
  - *High enough* to keep M1 'just' saturated
  - *As low as possible* so that  $V_{out}$  can be low
  
- The 'total' saturation voltage at the output for optimal choice is *~ twice* that of M1 (if M1 and M2 have same sizes)





# Simulation: Varying $V_C$


- Sweep  $V_C$  from 0.2...1.8 V:

 



# Zoom of 'Optimum' $V_C$ :


- Sweep 0.7...1.0 V

 


 
## $R_{out}$ and *dynamic range* in more detail

- Look at derivative of output characteristic ( $\partial I_{out} / \partial V_{out} = 1/r_{out}$ )
  - Small is good
- Again, blue (0.8 V) or red (0.9 V) are best...




- Note: Do not believe simulations to better than 50-100 mV!
  - 0.8 V is too close to 'bad' curve for 0.7 V.  $\rightarrow$  Chose 0.9 V



# Output Resistance of Cascoded MOS
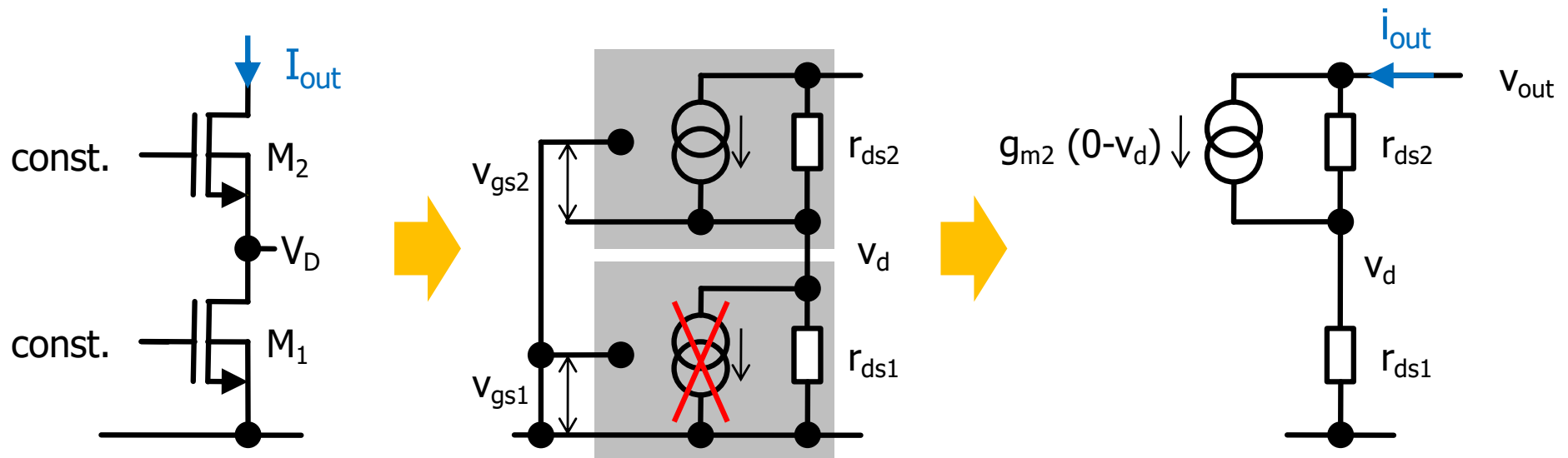
## Small signal analysis

- We only need to consider the output part
- Fixed voltages are equivalent to ground (in small signal!)
- The current source in M1 delivers no current ( $V_{GS} = \text{fix}$ )



## Current sums:

- $i_{\text{out}} = (v_{\text{out}} - v_d)/r_{\text{ds2}} - g_{\text{m2}} v_d = v_d / r_{\text{ds1}} \rightarrow v_d = \dots \rightarrow r_{\text{out}} = v_{\text{out}}/i_{\text{out}}$

$$\rightarrow r_{\text{out}} = r_{\text{ds1}} + r_{\text{ds2}} + g_{\text{m2}} r_{\text{ds1}} r_{\text{ds2}} \rightarrow r_{\text{out}} \cong r_{\text{ds1}} \times (g_{\text{m2}} r_{\text{ds2}})$$





# (The Calculation)

$$\frac{v_{out} - v_d}{r_{ds2}} - g_{m2}v_d = \frac{v_d}{r_{ds1}} \quad \text{= } i_{out}$$

$$\frac{v_{out}}{r_{ds2}} = \frac{v_d}{r_{ds1}} + \frac{v_d}{r_{ds2}} + g_{m2}v_d$$

$$\frac{1}{v_d} = \frac{r_{ds2}}{v_{out}} \left( \frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} + g_{m2} \right)$$

$$r_{out} = \frac{v_{out}}{i_{out}} = \frac{v_{out}r_{ds1}}{v_d} \quad \text{= } v_d / r_{ds1}$$

$$= v_{out}r_{ds1} \frac{r_{ds2}}{v_{out}} \left( \frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} + g_{m2} \right)$$

$$= r_{ds2} + r_{ds1} + g_{m2}r_{ds1}r_{ds2}$$



# Effect of the Cascode

- The output resistance of a cascoded MOS is a factor of  $g_m r_{ds}$  higher than without cascode 😊
- $g_m r_{ds}$  is the 'gain' of the Cascode MOS (as we will see...)
- It is typically 30
  
- The cascode gives a large improvement (in output resistance) for a very 'cheap' cost:
  - One more MOS
  - Loss of *one* saturation voltage (ideally)
  - NO additional power consumption!
- Achieving the same (high) output resistance with a long MOS is very difficult (more space than a second MOS, higher saturation voltage)
  
- → Cascodes are found in *many* places!




# A useful cascode trick

- Generating the 'good' cascode voltage is not so easy...
  - See exercises
- In some technologies, transistors with ***different thresholds*** are available.

- This allows the following circuit:

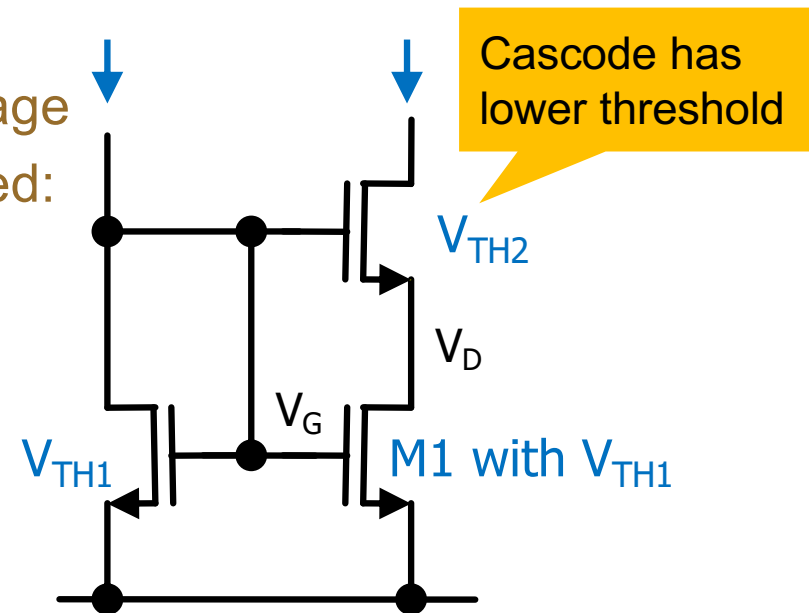- We use the gate voltage  $V_G$  of the mirror *also* as cascode voltage
- For M1 being saturated, we need:  
 $V_D > V_G - V_{TH1}$
- But  $V_D = V_G - V_{TH2} - x$   
where  $x$  depends on current
- The saturation requirement becomes  
 $V_G - V_{TH2} - x > V_G - V_{TH1}$  or  
 $V_{TH2} < V_{TH1} - x$



- With a 'sufficiently low'  $V_{TH2}$ , this works!



## Summary: The Cascoded Current Source

- A cascode MOS stabilizes the drain voltage of the current source
- The output resistance increases by a *factor*  $g_{m2} r_{ds2}$ 
  - This is the 'intrinsic gain' of M2
  - It is typically  $>20$  (depending on geometry and current)
- The cascode bias voltage should be chosen such that the current source is *just above* the *edge* of saturation
- The overall saturation voltage of the cascoded source is  $\sim 2$  times the 'unit' saturation voltage
- For advanced circuits, see the exercises!



# Design Goals for Current Sources

- High output resistance
  - Achieved by large  $L$ , cascode, regulation (see exercise)
- Low saturation voltage
  - Achieved by large  $W$ , optimal biasing
- Matching
  - Same Drain voltages (and of course same geometries)
- Speed (sometimes)
  - small devices (for small capacitances)
  - high current  $\rightarrow$  large  $W/L$



## Ibias ?

- But how do we get the input current?
- There are tricky circuits (Bandgap Reference) which can produce voltages / currents which are rather independent of supply voltage, temperature and component parameters!
- See Lecture 'Advanced Analogue Building Blocks'




# Advanced Current Source Circuits

- See Exercises



# Common Current Mirror Topologies

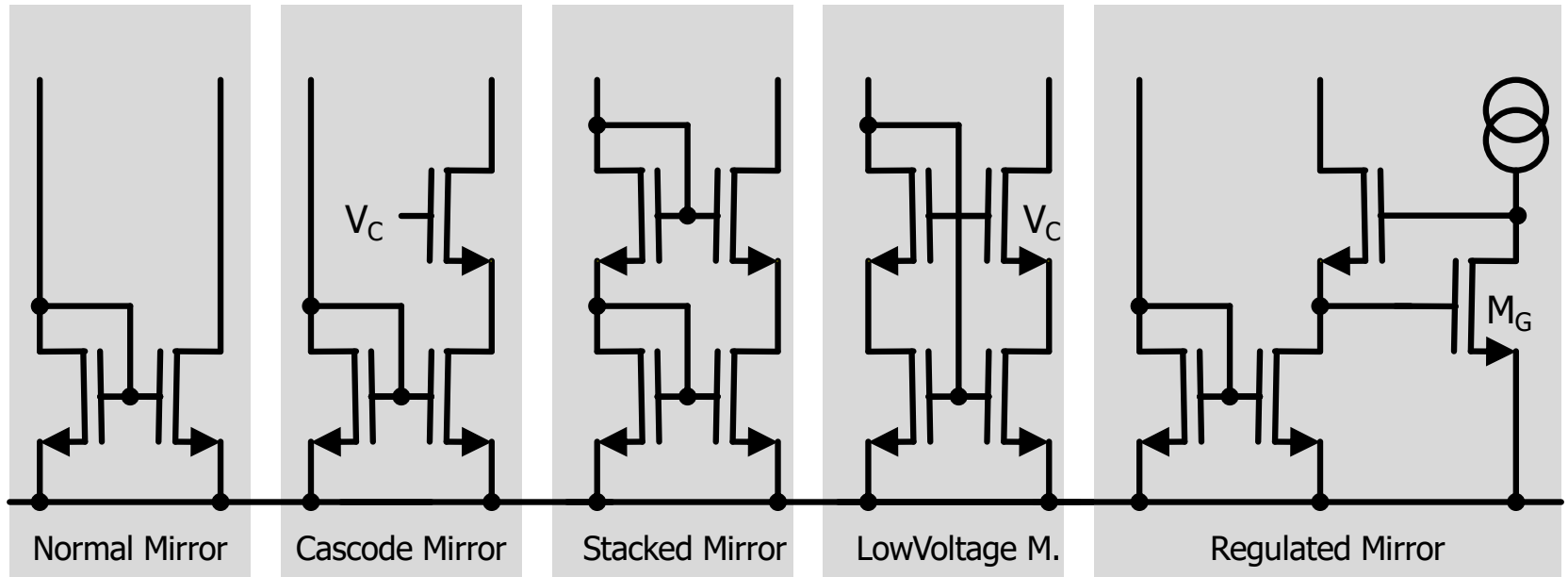

|                |             |                      |                            |                         |   |
|----------------|-------------|----------------------|----------------------------|-------------------------|---|
| $r_{out}$      | $r_{ds}$    | $R_{ds} \times g$    | $R_{ds} \times g$          | $R_{ds} \times g$       | $R_{ds} \times g^2$                                 |
| Best $V_{min}$ | $V_{D,Sat}$ | $2 \times V_{D,Sat}$ | $V_T + 2 \times V_{D,Sat}$ | $2 \times V_{D,Sat}$    | $V_T + 2 \times V_{D,Sat}$                          |
| Matching       | No          | No                   | Yes                        | Yes                     | Yes if $I_{bias} = I_{in}$                          |
| Require $V_C$  | No          | Yes                  | No                         | Yes                     | No  |
| Comment        |             |                      |                            | Fails if $V_C$ too high | May use Low $V_T$ MOS for $M_G$ for lower $V_{out}$ |