





The Differential Pair



The (Differential) Pair – The Principle

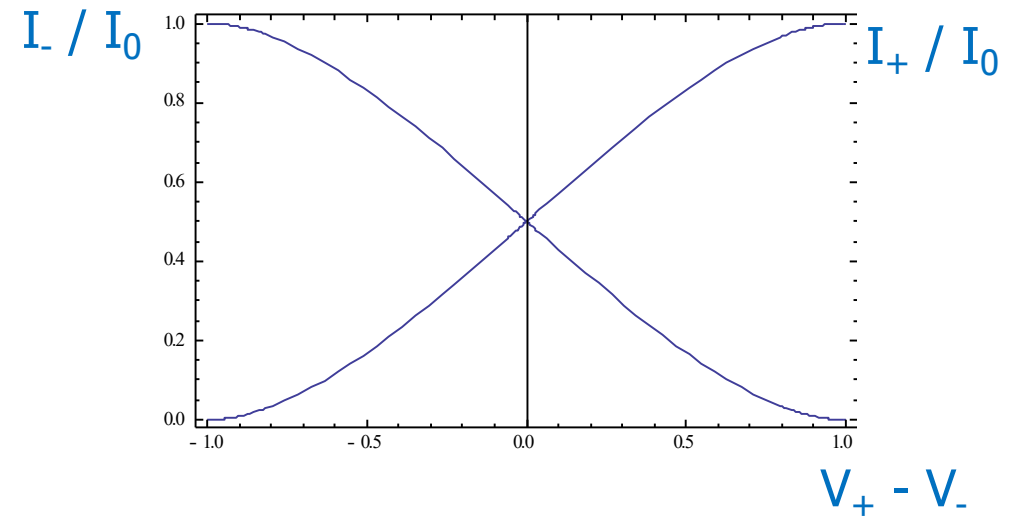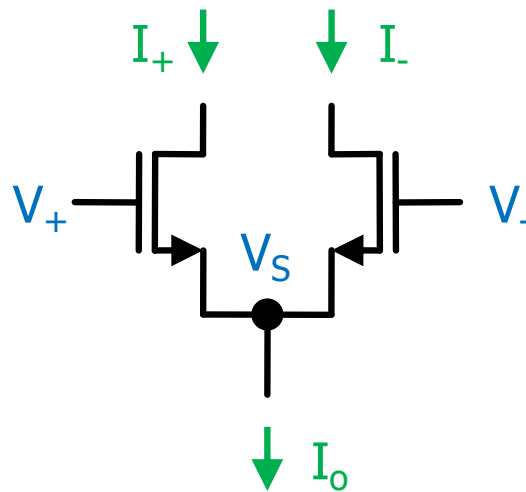- Very often, the *difference* of voltages must be amplified
- The basic circuit are two MOS with ***connected sources***:



- Assume $V_+ = V_-$
 - $\rightarrow V_{GS, \text{left}} = V_{GS, \text{right}} \rightarrow I_+ = I_- = I_0 / 2$
- Assume $V_+ > V_-$
 - $\rightarrow V_{GS, \text{left}} > V_{GS, \text{right}}$
 - $\rightarrow I_+ > I_-$
- Assume $V_+ \gg V_- \rightarrow I_+ \sim I_0, I_- \sim 0$



What is V_S ?

- V_S is (roughly) one threshold voltage below the *higher* input voltage
- It is often called the 'tail' voltage V_{tail} .
- The pair only works for input voltages $> V_{\text{TH}}$
- The tail current is normally provided by a current source which needs additional (saturation) voltage headroom




The Switching Voltage in *Strong* Inversion

- We have $I_D[V_{GS_}] = \beta (V_{GS} - V_{TH})^2$; with $\beta = K/2 \text{ W/L}$
- We have 3 equations for 3 unknowns (I_P , I_N , V_S):

$$I_P == I_D[V_P - V_S];$$

$$I_N == I_D[V_N - V_S];$$


$$I_P + I_N == I_0;$$

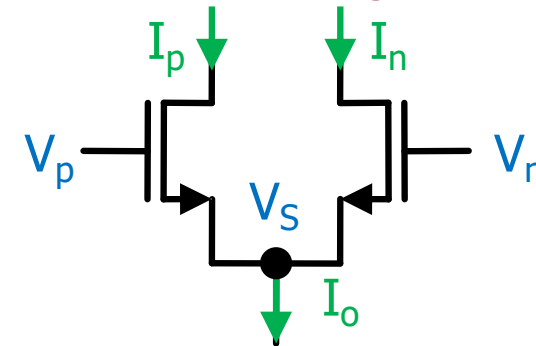

- We get $I_P = \frac{1}{2} \left(I_0 + \sqrt{\beta \Delta V^2 (2 I_0 - \beta \Delta V^2)} \right)$ with $\Delta V = V_P - V_N$

- We switch *completely* for
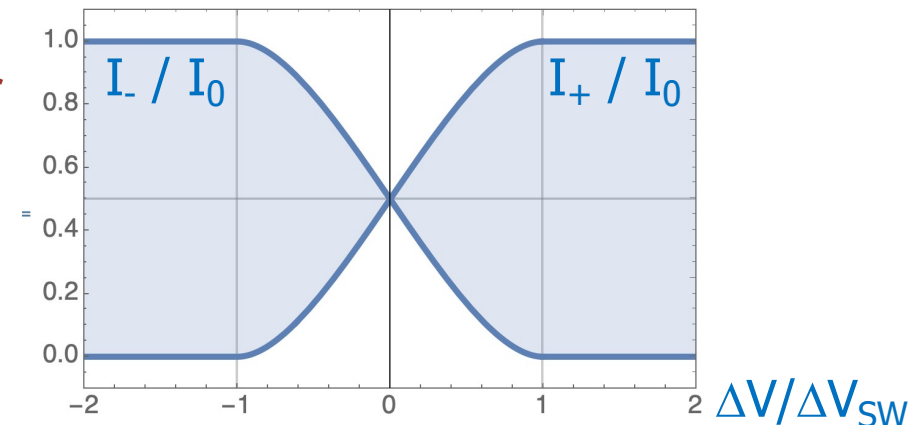
$$\Delta V_{SW} = \frac{\sqrt{I_0}}{\sqrt{\beta}}$$




- Conclusion: In *strong inversion*, pair can be *fully* switched!



The Switching Voltage in *Weak* Inversion

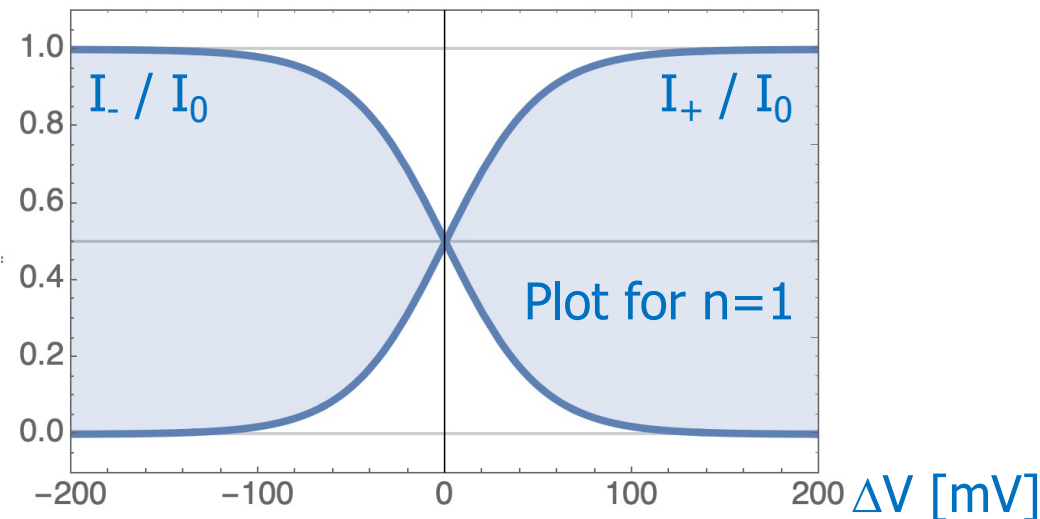- We have $I_D[VGS_-] = \beta \text{Exp}\left[\frac{VGS}{n U_T}\right]$;
- We get $I_P = \frac{I_0}{1 + e^{\frac{\Delta V}{n U_T}}}$ with $\Delta V = V_P - V_N$ and $U_T = 25.6 \text{ mV}$
- We switch in a few U_T , but **never** switch 'really' completely




- Conclusion: In *weak inversion*, pair switches at *small voltages*, but never fully!



The Differential Amplifier


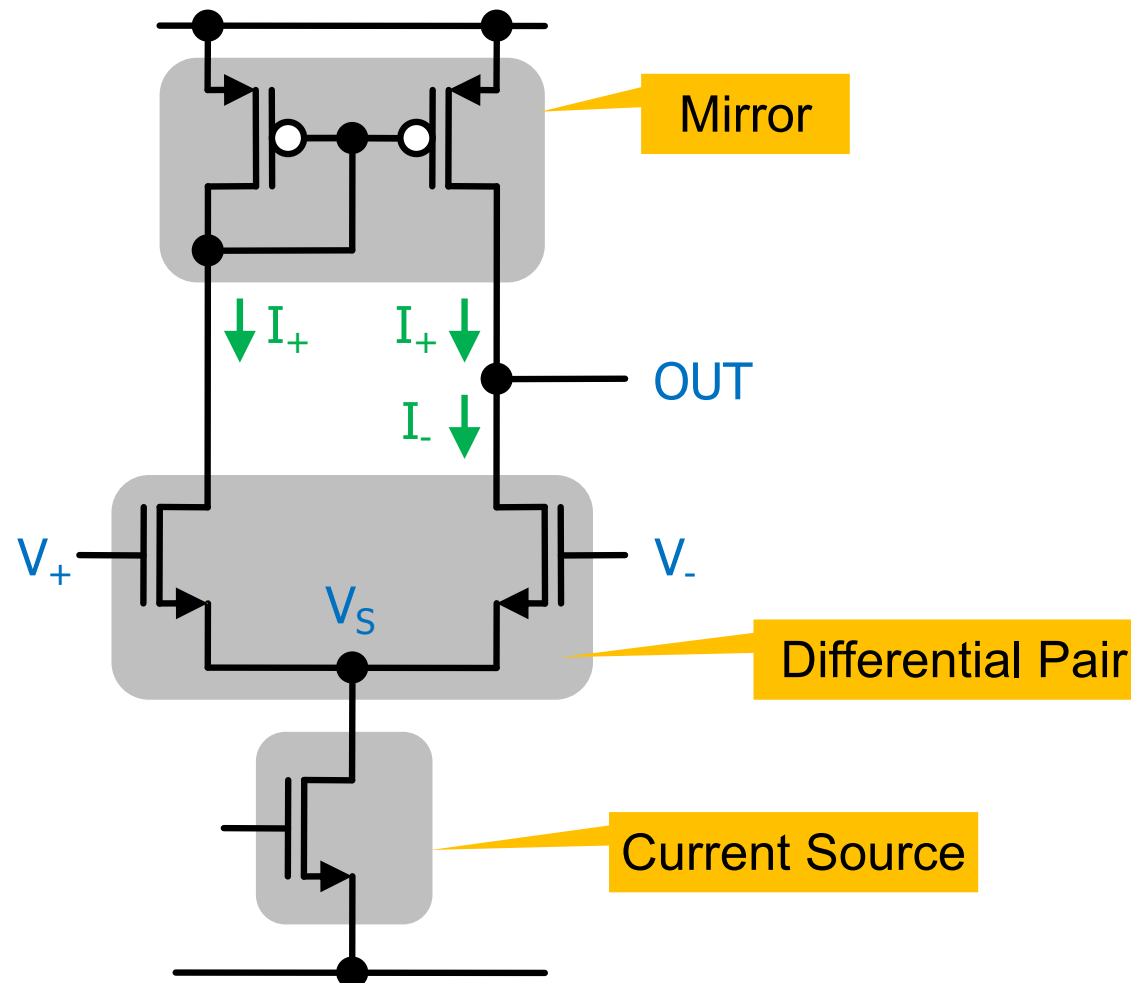
- One 'output' current (I_+) is often mirrored and added to the current of the other side (I_-):





Output *Current* of the Differential Amplifier

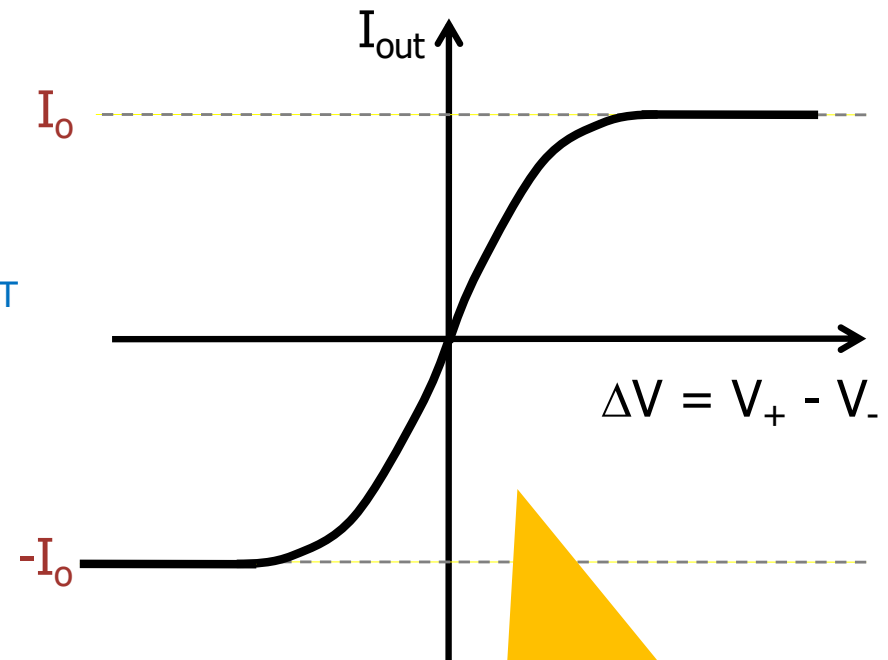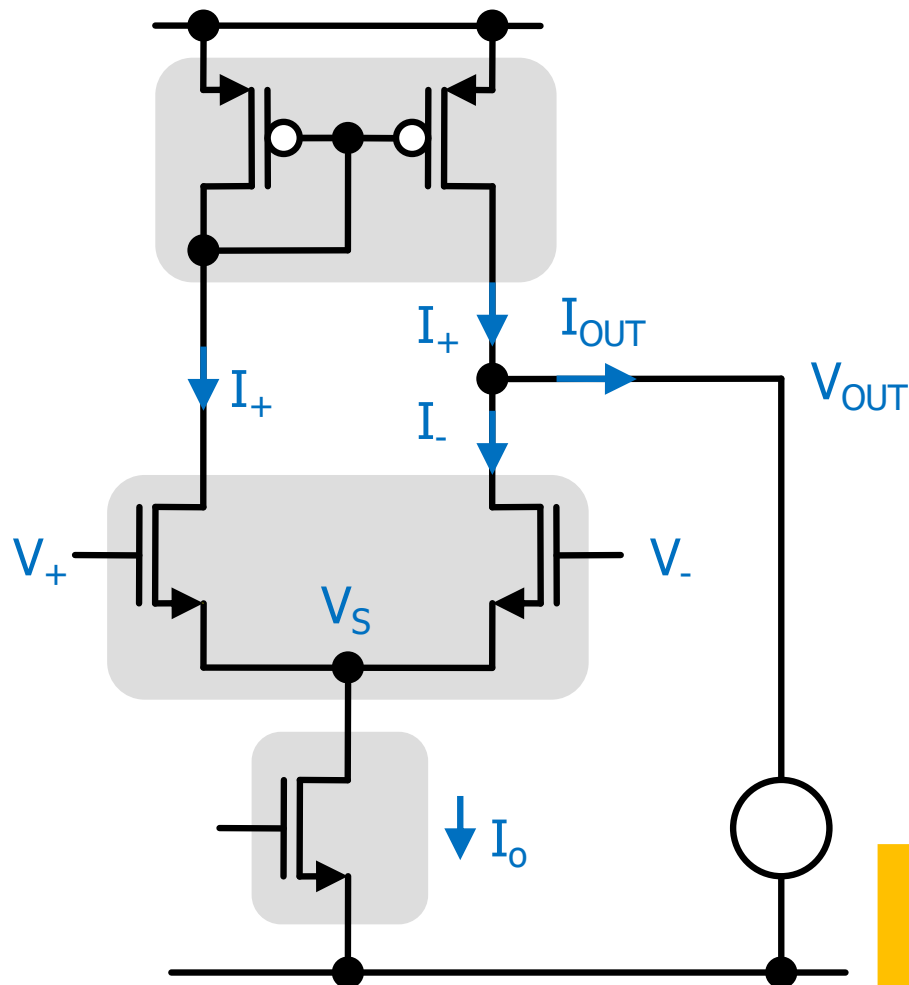- If the output voltage is *fixed*, the *output current* is just $I_+ - I_-$
- The circuit is a ,*Transconductor*' (it converts $\Delta U \rightarrow I$)





This only works if the V_{OUT} is ,good'
... understand what this means! ...



Output *Voltage* of the Differential Amplifier

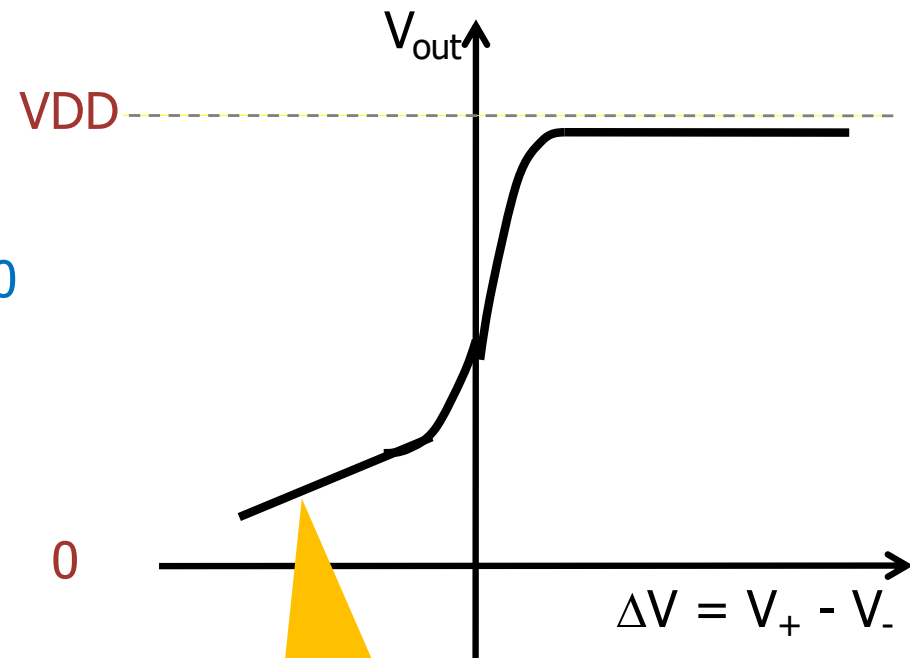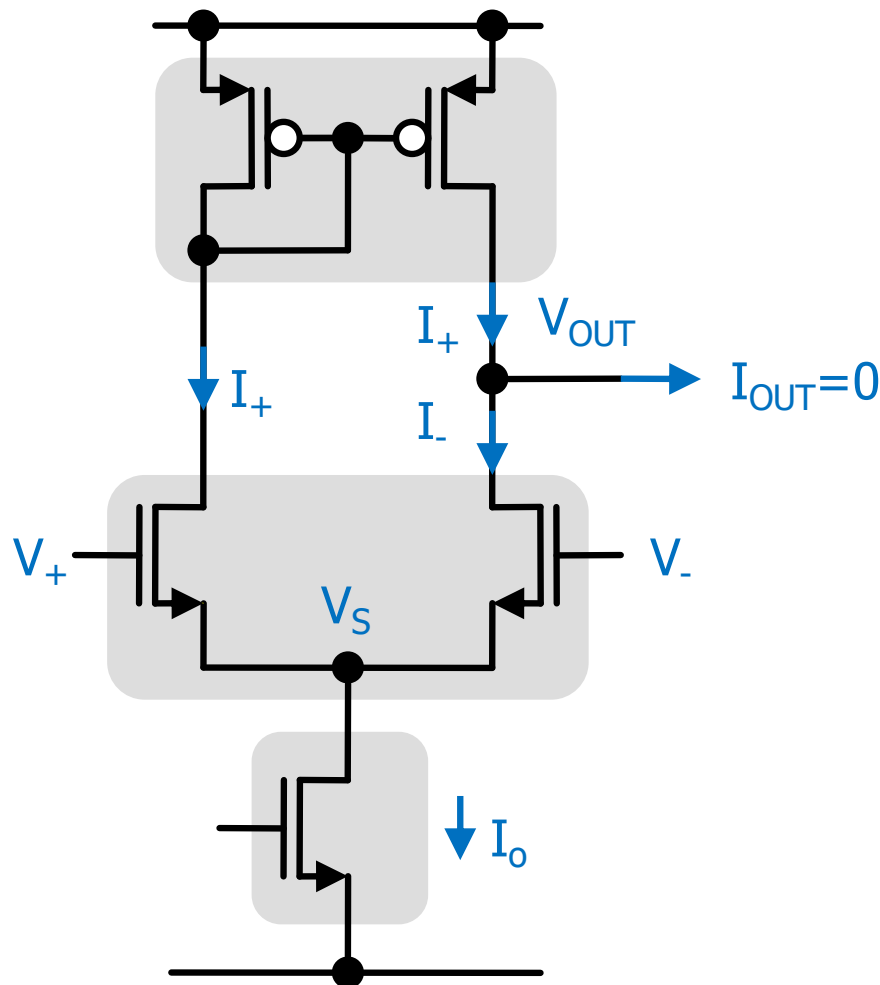- If *no current* flows out of the circuit (the output voltage is left free), we have *voltage* gain (the current $I_+ - I_-$ pulls V_{out} hi/low)





Output cannot go lower than $V_S \sim V_- - V_T$



Simulation

- $V_{DD} = 1.8V$
- $V_N = 1.2V$

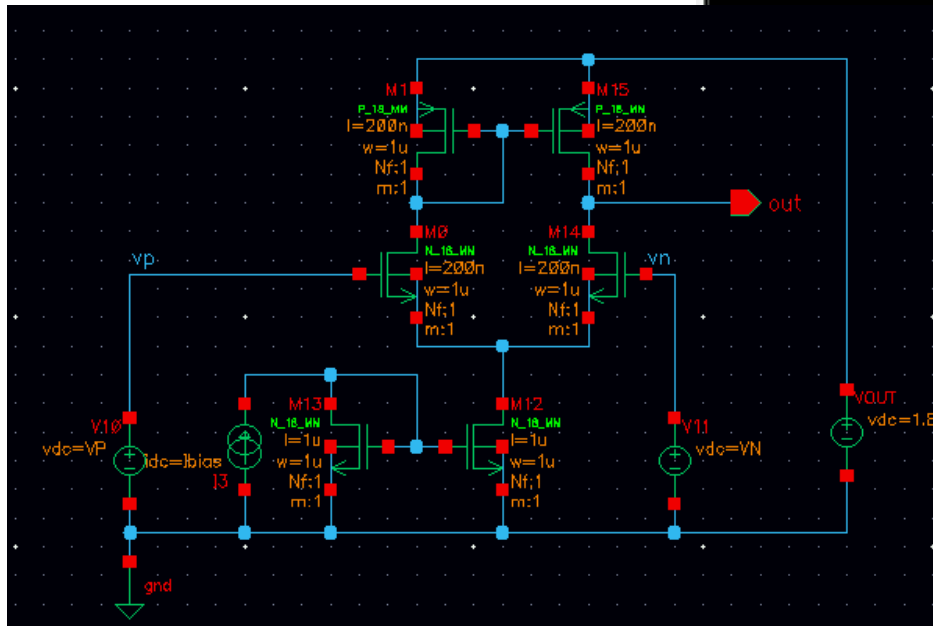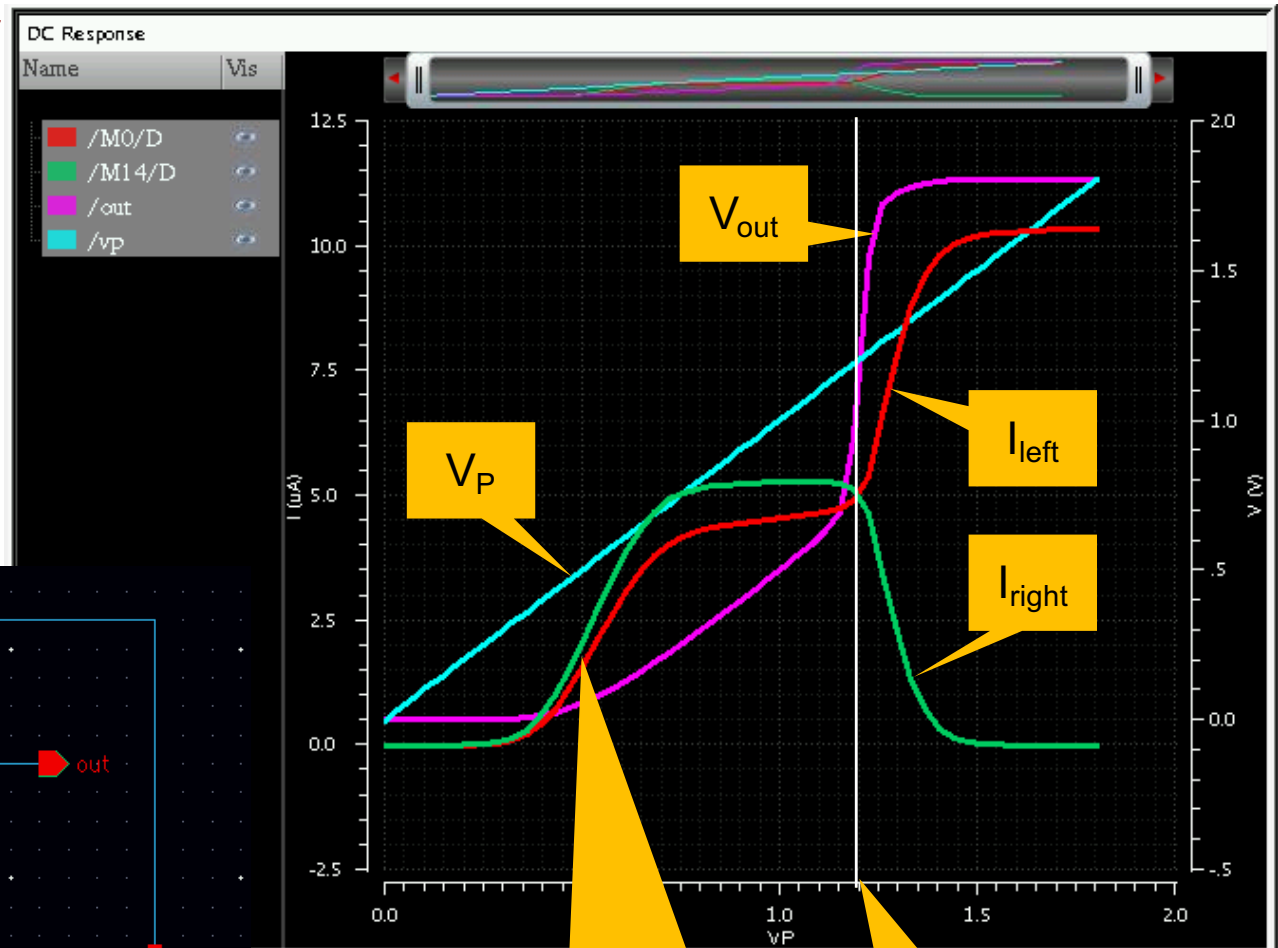

Strange operation
here: I_{right} cannot flow
because output is low


$V_N = 1.2V$



Sweeping V_-

- $V_N = V_- = 0.2, 0.4, \dots 1.6 \text{ V}$

V_{out}

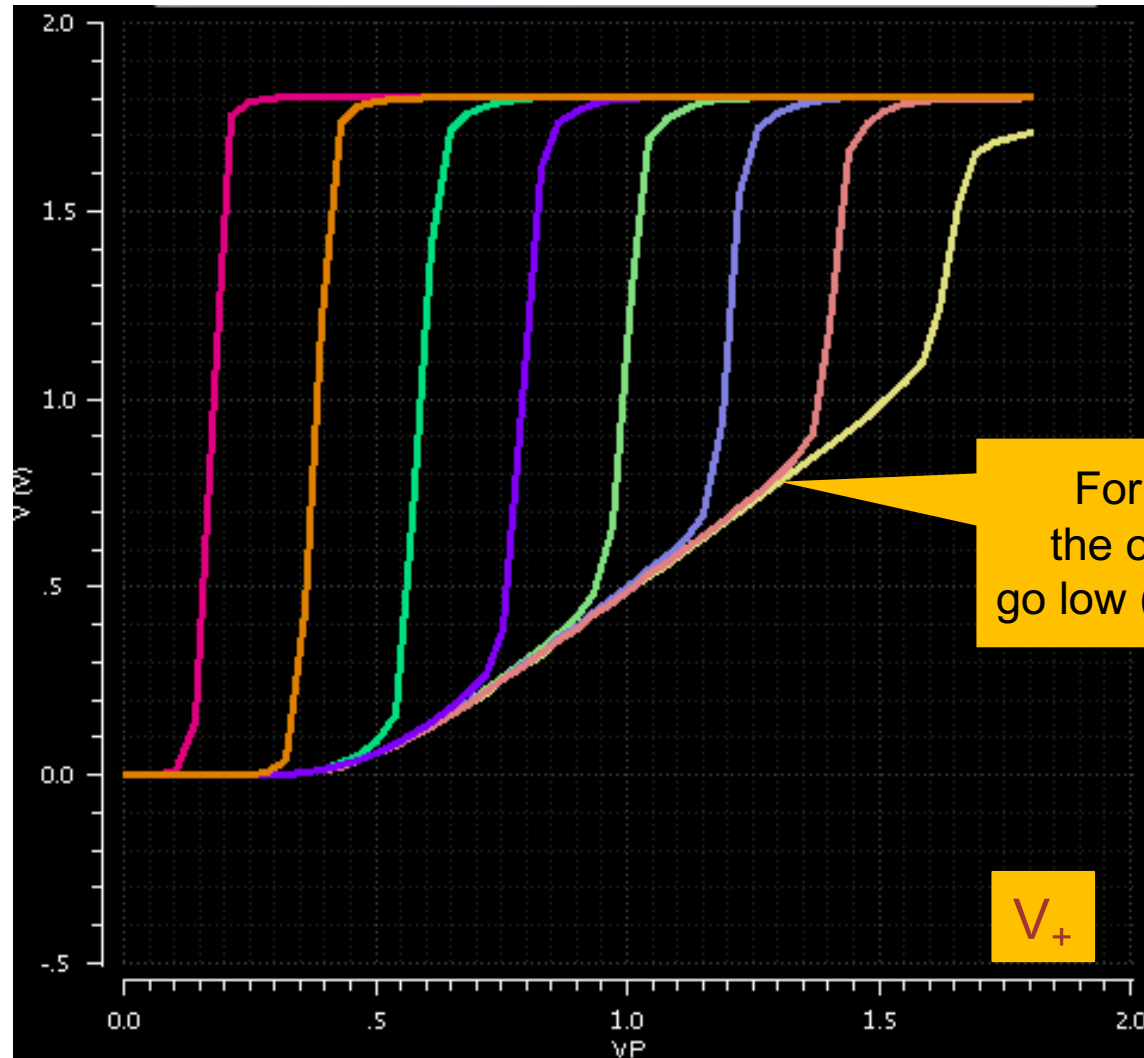

For positive V_- ,
the output cannot
go low (lower than V_S)

V_+



Gain

- What is the (voltage) gain?
- To first order, it is – as before – the g_m of the *input* transistor(s) multiplied with the total impedance at the *output* (i.e. r_{ds} of the current mirror output in parallel to r_{ds} of the diff. pair)
- (The output resistance on the left branch do not matter, because the voltage there is kept nearly constant by the diode connected PMOS upper left...)




Comments

- Understanding the large signal behaviour for very different V_p, V_n is important, but in practical circuits, feedback is often applied so that $V_p = V_n$.
- Another important property is the *common mode input range*. This is limited by the V_{GS} of the input pair and the compliance of the tail current source: An *NMOS* differential pair *does not work* any more at *low* (common mode) input voltage.
- Another property is *common mode gain*, i.e. the change in output voltage if both inputs are changes simultaneously. In an ideal amplifier, common mode gain is 0.
- If the amplifier is loaded with a resistive load, gain drops. (as for the gain stage).
 - A source follower is therefore sometimes added.
 - Stability in feedback circuits is then more tricky. Compensation methods are needed.



More Gain: Diff-Amp with Gain Stage

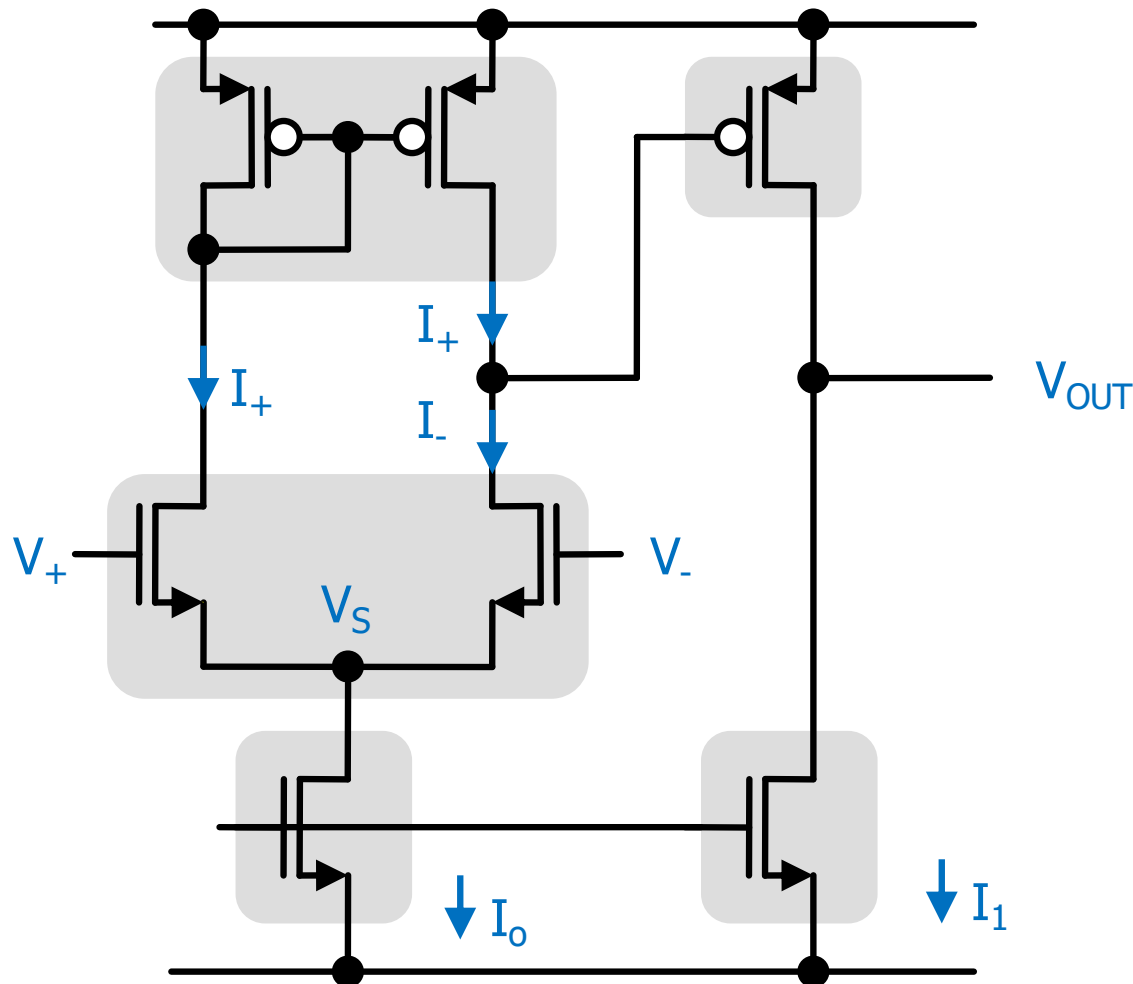- The differential amplifier is often followed by a gain stage
 - This two-stage design has two ,main' poles and may need compensation if used in feedback configuration




- The 'steep' part of the transfer function of the first (differential) stage should coincide with the 'steep' part of the second stage!
- This can be achieved (for 3x equal PMOS) with $I_0 = 2 \times I_1$, so that $I_+ = I_- = I_1$ at the switching point.



Differential Pair + Current Mirror

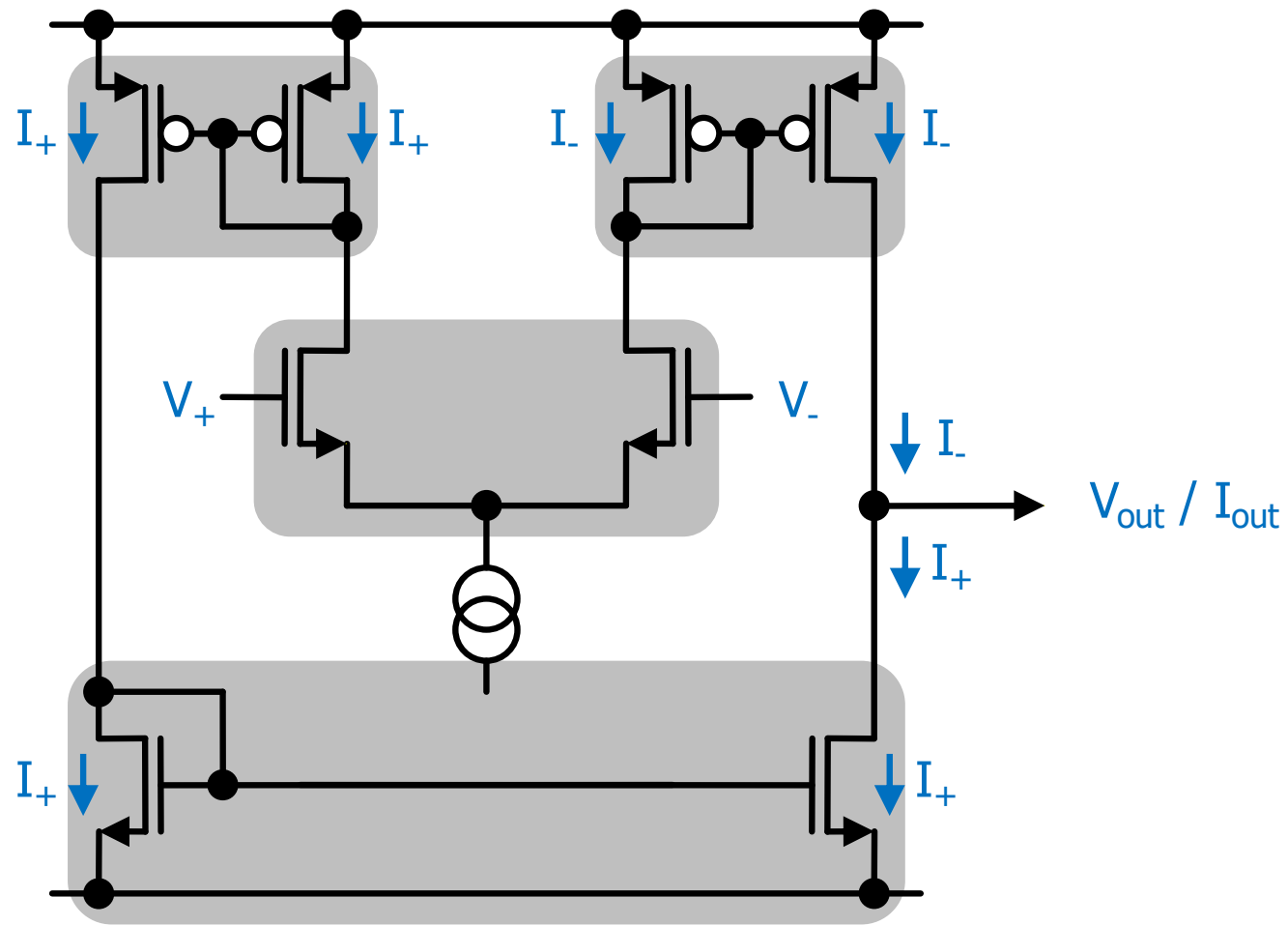- The problem of limited output voltage swing for high input common mode can be solved by mirroring the currents:



- Many topologies are possible, using mirrors and cascodes
- For instance, this 'folded cascode' configuration:

