



Exercise 3: Advances Nets & Multiple Instances

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Exercise 3A: Inverter Chain – Setting Up

- **Create schematic and symbol of an Inverter**
 - Use a minimum size NMOS and a PMOS with minimal length and parameterized width WP
 - Use global nets vddd! and gndd! for the circuit
 - Connect the substrate of the NMOS to global gnd!
 - Connect the well of the PMOS to vddd!
- **Simulate the schematic in a new view**
 - Connect gnd! to gndd! with a $0\ \Omega$ resistor or with a DC source with 0 V.
 - Provide vddd! of 1.8 V
 - Load the circuit with 100 fF or so
 - Provide a square wave input
 - Label your nets 'in' and 'out'
 - Chose WP such that rise and fall times are roughly equal. Use a parametric simulation!
 - Save the simulation state to the cell



Exercise 3A: Inverter Chain – The Chain

- Copy the simulation cell (incl. state) to a new schematic
- Change the schematic so that it contains a chain of 11 inverters. Use advanced nets and multiple instances
 - instantiate you inverters as `linv<10:0>`
 - Decide which inverter is the first in the chain.
 - Find out how to connect the inverter, and how to add the 'in' and 'out' nets
 - Note: You are not allowed to use the same name for single nets ('out') and busses ('out<10:1>')
- Reduce the load capacitor to 1 fF
- Find out the delay between the input 'in' and the output of the last inverter 'out'.
 - Use the available state to start with
- For your understanding: Change the order of the chain, i.e. make the 'other' inverter the first in the chain. Change the signal naming correspondingly.




Exercise 3A: Inverter Chain – An Oscillator

- You can create a 'RING OSCILLATOR' by connecting the output of the chain to the input (remove the source!)

- Try to simulate this
 - you will probably see a constant level between 0V and 1.8V
 - Make sure the oscillation starts by setting an initial condition of 0V or 1.8V to the 1 fF capacitor at the output

- What is the oscillation frequency?
Do you understand how this works?


- Have a look at the simulation netlist

 



Exercise 3B: Voltage Drop in a Large Chip

- A (Pixel) chip consist of N identical circuits in a column
- The pixels are powered by vertical metal traces
- Each pixel consumes a current I_0
- The trace resistance between two cells is R_0 (both supplies)
- **ONLY** the lowermost Pixel 1 is connected to a supply V_S .

 



Exercise 3B: Voltage Drop


- Due to the voltage drop in the R_0 s, the local supply voltages V_i become smaller and smaller from pixel 1 to pixel N
- Calculate the V_i analytically.
 - Hint: calculate the current in each resistor
 - Derive the voltage drop in each resistor
 - Sum up the drops from 1 to N.
- How much has the supply dropped at the topmost pixel?
- Now simulate the structure and confirm your analytical result for $N=100$, $R_0=1\Omega$, $I_0=100\mu\text{A}$, $V_S=2\text{V}$.
 - Obviously, you should use an 'advanced' schematic....



 Exercise 3B: Are you clever ?

- What happens when the topmost pixel N is also connected to VS
 - Where is the largest voltage drop now?
 - How large is it (roughly)?
 - Surprised? Do you understand why?

- Note: Pixel chips usually have connections only on one side, so that many chips can be placed side-by-side to form a larger module.



- Voltage drop is a serious issue which cannot be avoid. Pixel circuitry must be able to 'live with it'