

Solutions to Exercise: Shaper with Unequal Corner Frequencies

PF@SuS@UniHD 2016+

We have $r := \frac{\omega_l}{\omega_h} = \frac{\tau_h}{\tau_l}$

Some Defaults

```
In[122]:= Clear[k, T, R, C];
```

Clear: Symbol C is Protected.

```
In[123]:= $Assumptions = r > 0 && τ > 0 && τh > 0 && τl > 0 &&
ω > 0 && ωh > 0 && ωl > 0 && B > 0 && s > 0 && -3 < Re[k] < 1 && ωCRRC > 0;
```

```
In[124]:= SetOptions[{LogLogPlot, LogLinearPlot, Plot},
{Frame → True, Filling → Axis, ImageSize → 400, PlotLegends → "Expressions"}];
```

1. Transfer Function

```
In[125]:= H[s_] = 1 / (1 + s τl) * s τh / (1 + s τh) /. τl → τh / r /. τh → τ
```

```
Out[125]= 
$$\frac{s \tau}{(1 + s \tau) \left(1 + \frac{s \tau}{r}\right)}$$

```

```
Gain[s_, τ_, r_] = Abs[H[s]] // Simplify (* τ is corner frequency of high pass,
r is ratio between high and low pass *)
```

```
Out[126]= 
$$\frac{r s \tau}{(1 + s \tau) (r + s \tau)}$$


```

For $r = 1$, we have the normal CR-RC filter with equal corners.

For $r < 1$, the $\tau_l > \tau_h$, or $\omega_l < \omega_h$ which is stupid: the low pass starts to drop the signal before the high pass

$r > 1$ is the interesting case where we have a 'trapezoidal' filter shape with a flat plateau.
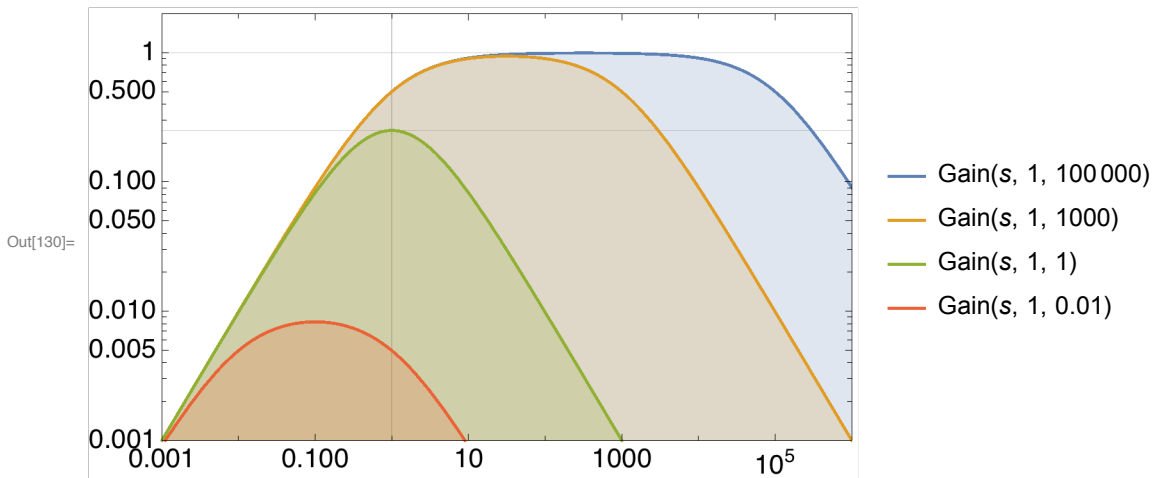
```
In[130]:= LogLogPlot[{Gain[s, 1, 100 000], Gain[s, 1, 1000], Gain[s, 1, 1], Gain[s, 1, 0.01]},
  {s, 0.001, 1000 000}
  , PlotRange -> {{0.001, 1000 000}, {0.001, 2}}, GridLines -> {{1}, {1, 1 / 4}}
```




2. Step Reponse

```
In[131]:= Clear[v];
```

```
v[t_, τ_, r_] = InverseLaplaceTransform[1/s H[s], s, t] // Simplify
```

$$\text{Out[132]} = -\frac{\left(e^{-\frac{t}{\tau}} - e^{-\frac{r t}{\tau}}\right) r}{1 - r}$$
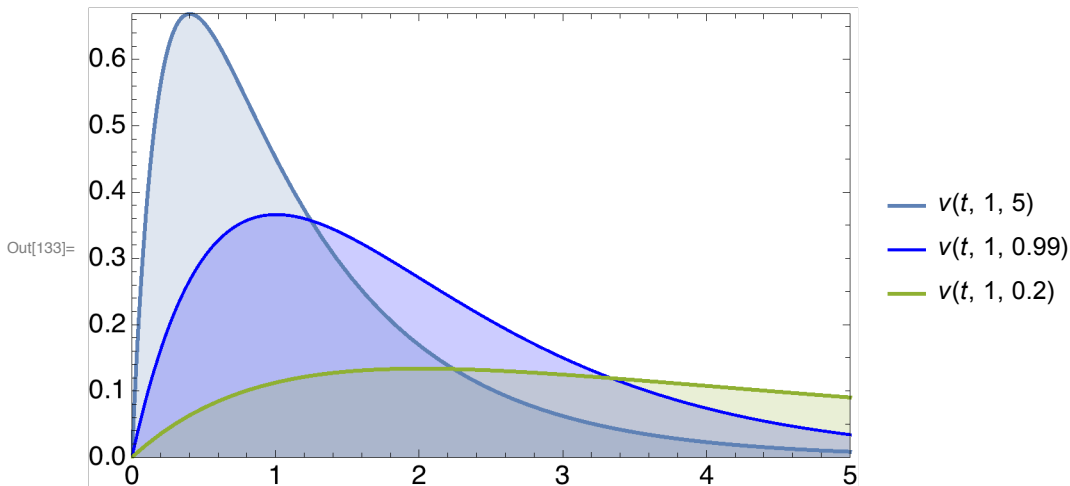
```
In[133]:= Plot[{v[t, 1, 5], v[t, 1, 0.99], v[t, 1, 0.2]}, {t, 0, 5}]
```




3. Peaking Time and Amplitude

```
In[134]:= D[v[t, τ, r], t] // Simplify
```

$$\text{Out[134]} = \frac{r \left(e^{-\frac{t}{\tau}} - e^{-\frac{r t}{\tau}}\right)}{\tau - r \tau}$$

In[135]:= **Clear[tpeak];**

tpeak[τ_, r_] = t /. Solve[D[v[t, τ, r], t] == 0, t] // First // Simplify

 **Solve:** Inverse functions are being used by Solve, so some solutions may not be found; use Reduce for complete solution information.

Out[135]=
$$\frac{\tau \operatorname{Log}[r]}{-1 + r}$$

In[137]:= **vpeak[r_] = v[tpeak[τ, r], τ, r] // Simplify**


Out[137]=
$$r^{\frac{1}{1-r}}$$

This vpeak is a funny formula. What is the limit for this for $r \rightarrow 1$??? It should be our well known $1/e$ for the CR-RC shaper...


In[142]:= **Limit[vpeak[r], r → 1] == $\frac{1}{e}$**

Out[142]= True

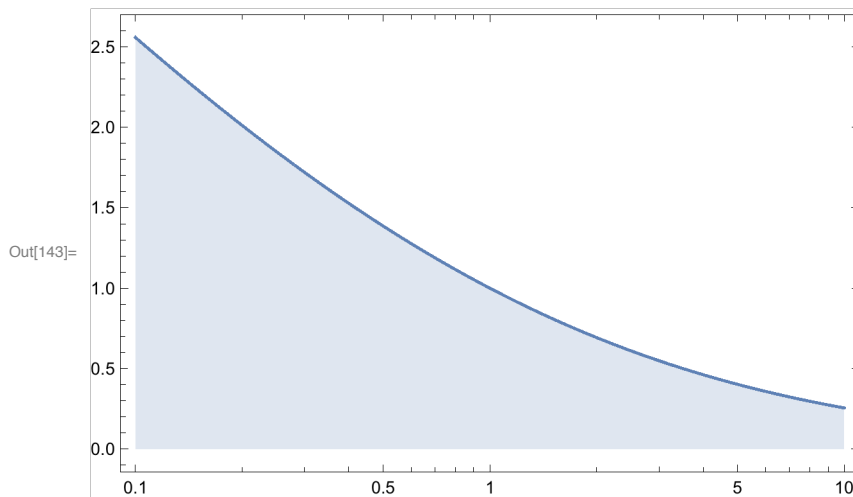In[143]:= **LogLinearPlot[tpeak[1, r], {r, 0.1, 10}]**


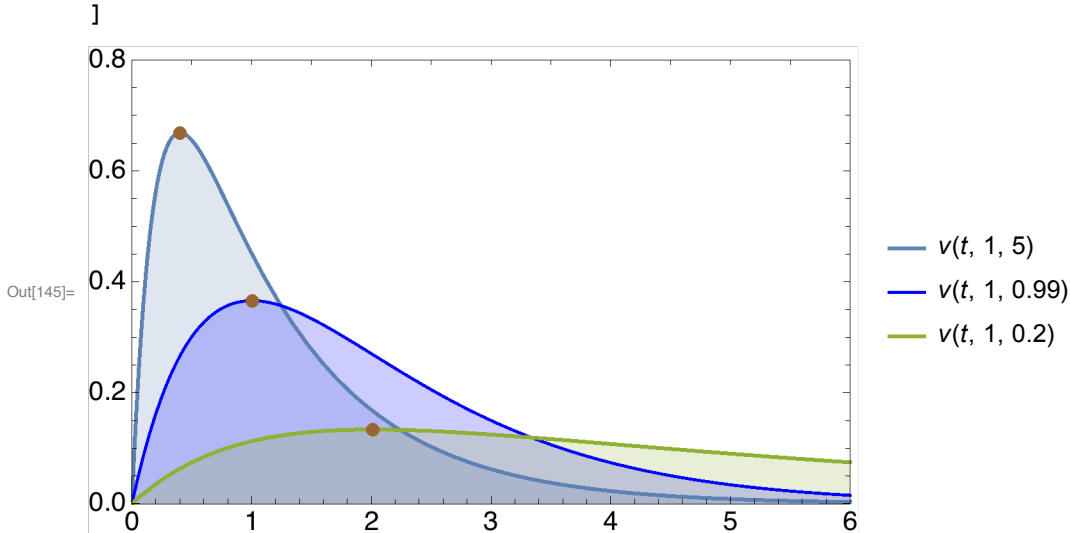
```
Plot[{v[t, 1, 5], v[t, 1, 0.99], v[t, 1, 0.2]}, {t, 0, 6}, PlotRange -> {0, 0.8},
  Epilog -> {PointSize[Large], Brown
    , Point[{tpeak[1, 5], vpeak[1, 5]}]
    , Point[{tpeak[1, 0.99], vpeak[1, 0.99]}]
    , Point[{tpeak[1, 0.2], vpeak[1, 0.2]}]}]
]
```



4. Simple Shaper Limit ($r \rightarrow 1$)

```
In[146]:= Limit[{v[t, τ, r], tpeak[τ, r], vpeak[τ, r]}, r -> 1]
```

$$\text{Out[146]= } \left\{ \frac{e^{-\frac{t}{\tau}} t}{\tau}, \tau, \frac{1}{e} \right\}$$

5. Noise Integral

```
In[147]:= H2[ω_] = H[i ω] Conjugate[H[i ω]] // Simplify
```

$$\text{Out[147]= } \frac{r^2 \tau^2 \omega^2}{(1 + \tau^2 \omega^2) (r^2 + \tau^2 \omega^2)}$$

```
In[149]:= INT[k_] = Integrate[ω^k H2[ω], {ω, 0, ∞}] // FullSimplify
```

(* This is the hard integral *)

(* Note that we have restricted k in the \$Assumptions to $-3 < \text{Re}[k] < 1$, so that the expressions get simpler. If we do not do that, we get conditional expressions *)

$$\text{Out[149]= } \frac{\pi r^2 (-1 + r^{1+k}) \tau^{-1-k} \text{Sec}\left[\frac{k\pi}{2}\right]}{2 (-1 + r^2)}$$

```
In[150]:= Coeff = Table[Limit[INT[k], k -> K], {K, -2, 0}] // Simplify
```

$$\text{Out[150]= } \left\{ \frac{\pi r \tau}{2 + 2 r}, \frac{r^2 \text{Log}[r]}{-1 + r^2}, \frac{\pi r^2}{2 \tau + 2 r \tau} \right\}$$

CoefLatex =

Table[Limit[$\frac{1}{2} \omega^{k+1} \frac{r^{k+1} - 1}{r^2 - 1} \text{Gamma}\left[\frac{1+k}{2}\right] \text{Gamma}\left[\frac{1-k}{2}\right] /. \omega \rightarrow \frac{1}{r \tau}, k \rightarrow K$], {K, -2, 0}] /. r \rightarrow 1/r // Simplify (* For PF: Compare to old LaTeX solution *)

$$\text{Out[151]= } \left\{ \frac{\pi r \tau}{2 + 2 r}, \frac{r^2 \text{Log}[r]}{-1 + r^2}, \frac{\pi r^2}{2 \tau + 2 r \tau} \right\}$$

In[152]= Coeff == CoefLatex (* Check that both are the same *)

Out[152]= True

6. SNR for same peaking time

In[153]= ttrans = Solve[tpeak[τ, r] == tpref, τ] // First

(* Find the τ we need in the general case to keep peaking time at tpref *)

$$\text{Out[153]= } \left\{ \tau \rightarrow \frac{(-1 + r) \text{tpref}}{\text{Log}[r]} \right\}$$

In[154]= XX = $\frac{\text{INT}[k]}{\text{vpeak}[\tau, r]^2} /. \text{ttrans} /. \text{tpref} \rightarrow \frac{1}{\omega_{\text{CRRC}}}$ // FullSimplify

(* XX is INT[] scaled for same amplitude and peaking *)

$$\text{Out[154]= } \frac{\pi r^{\frac{2r}{-1+r}} (-1 + r^{1+k}) \text{Sec}\left[\frac{k \pi}{2}\right] \left(\frac{-1+r}{\text{Log}[r] \omega_{\text{CRRC}}}\right)^{-1-k}}{2 (-1 + r^2)}$$

In[155]= Limit[XX, r \rightarrow 1] (* Lecture case for normal CR-RC-shaper *)

$$\text{Out[155]= } \frac{1}{4} e^2 (1 + k) \pi \text{Sec}\left[\frac{k \pi}{2}\right] \omega_{\text{CRRC}}^{1+k}$$

In[157]= Table[Limit[XX, k \rightarrow K], {K, -2, 0}] // FullSimplify

$$\text{Out[157]= } \left\{ \text{ConditionalExpression}\left[\frac{\pi (-1 + r) r^{\frac{1+r}{-1+r}}}{2 (1 + r) \text{Log}[r] \omega_{\text{CRRC}}}, (-1 + r) \text{Re}\left[\frac{1}{\text{Log}[r]}\right] > 0\right], \right. \\ \text{ConditionalExpression}\left[\frac{r^{\frac{2r}{-1+r}} \text{Log}[r]}{-1 + r^2}, (-1 + r) \text{Re}\left[\frac{1}{\text{Log}[r]}\right] > 0\right], \\ \left. \text{ConditionalExpression}\left[\frac{\pi r^{\frac{2r}{-1+r}} \text{Log}[r] \omega_{\text{CRRC}}}{2 (-1 + r^2)}, (-1 + r) \text{Re}\left[\frac{1}{\text{Log}[r]}\right] > 0\right] \right\}$$

For the moment, I ignore the conditional expression...

In[158]= Limit[%, r \rightarrow 1]

$$\text{Out[158]= } \left\{ \frac{e^2 \pi}{4 \omega_{\text{CRRC}}}, \frac{e^2}{2}, \frac{1}{4} e^2 \pi \omega_{\text{CRRC}} \right\}$$

```
In[159]:= % == 
$$\frac{A^2 \frac{\pi}{4} \left\{ \frac{1}{\omega_{\text{CRRC}}}, \frac{2}{\pi}, \omega_{\text{CRRC}} \right\}}{(A/e)^2} \quad (* \text{ result from lecture slides p.27 } *)$$

```

```
Out[159]= True
```

7. Find Minimum

```
In[160]:= DXX = D[XX, r] // FullSimplify
```

```
Out[160]= 
$$\frac{1}{2 (-1+r)^4 (1+r)^2} \pi r^{\frac{1+r}{-1+r}} \left( \frac{-1+r}{\text{Log}[r]} \right)^{-k} \left( (1+k) (-1+r)^2 (1+r) (-1+r^{1+k}) + \right. \\ \left. r \text{Log}[r] \left( (-1+r) (-1+k+r+k r - r^k (1+k+(-1+k) r)) - \right. \right. \\ \left. \left. 2 (1+r) (-1+r^{1+k}) \text{Log}[r] \right) \right) \text{Sec} \left[ \frac{k \pi}{2} \right] \omega_{\text{CRRC}}^{1+k}$$

```

```
In[161]:= Limit[DXX, r → 1] // FullSimplify
```

```
(* The derivative of XX is zero at r=1 → CR-RC has minimal noise for ALL k *)
```


```
Out[161]= 0
```

```
In[162]:= PP = Table[Limit[XX /. ωCRRC → 1, k → K], {K, -2, 0}] // Simplify
```

```
(* Make an expression with numerical values for plotting *)
```

```
Out[162]= {ConditionalExpression[ $\frac{\pi (-1+r) r^{\frac{1+r}{-1+r}}}{2 (1+r) \text{Log}[r]}$ ,  $(-1+r) \text{Re} \left[ \frac{1}{\text{Log}[r]} \right] > 0$ ], \\ ConditionalExpression[ $\frac{r^{\frac{2r}{-1+r}} \text{Log}[r]}{-1+r^2}$ ,  $(-1+r) \text{Re} \left[ \frac{1}{\text{Log}[r]} \right] > 0$ ], \\ ConditionalExpression[ $\frac{\pi r^{\frac{2r}{-1+r}} \text{Log}[r]}{2 (-1+r^2)}$ ,  $(-1+r) \text{Re} \left[ \frac{1}{\text{Log}[r]} \right] > 0$ ]}
```
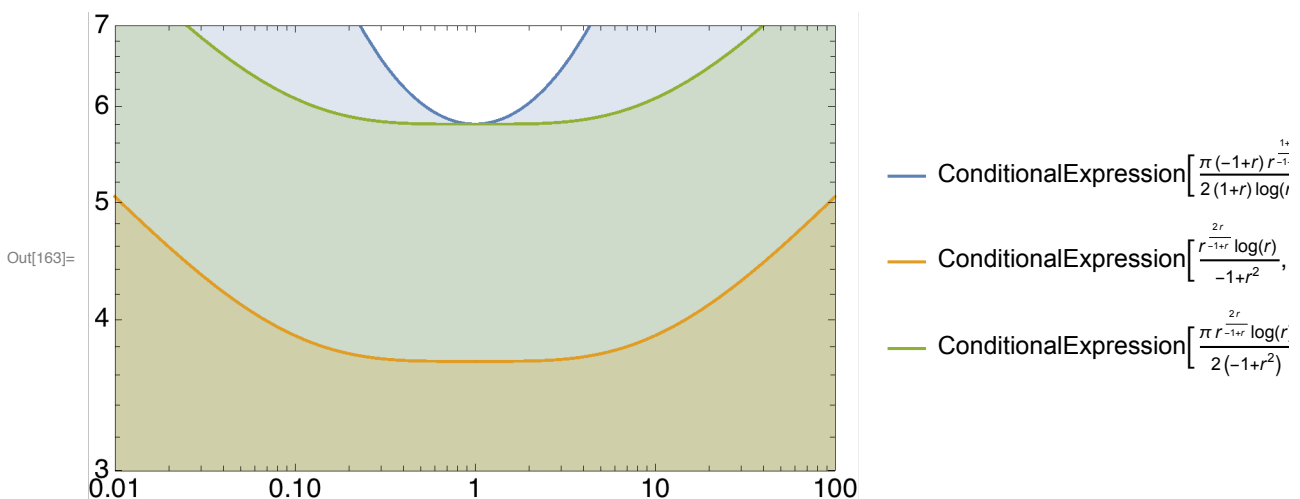
```
In[163]:= LogLogPlot[Evaluate[PP], {r, 0.01, 100}, Filling → Axis, PlotRange → {3, 7}]
```



```
In[164]:= Limit[PP, r → 1]
```

```
Out[164]=  $\left\{ \frac{e^2 \pi}{4}, \frac{e^2}{2}, \frac{e^2 \pi}{4} \right\}$ 
```