



Readout Electronics

P. Fischer, Heidelberg University




We will treat the following questions:

1. How is the sensor modeled ?
2. What is a typical amplifier arrangement ?
3. What is the output signal?
4. How is noise described and what are the dominant contributions?
5. What is the total noise at the output ?
6. How does noise depend on system parameters and how can it be minimized ?
7. What are typical noise figures ?



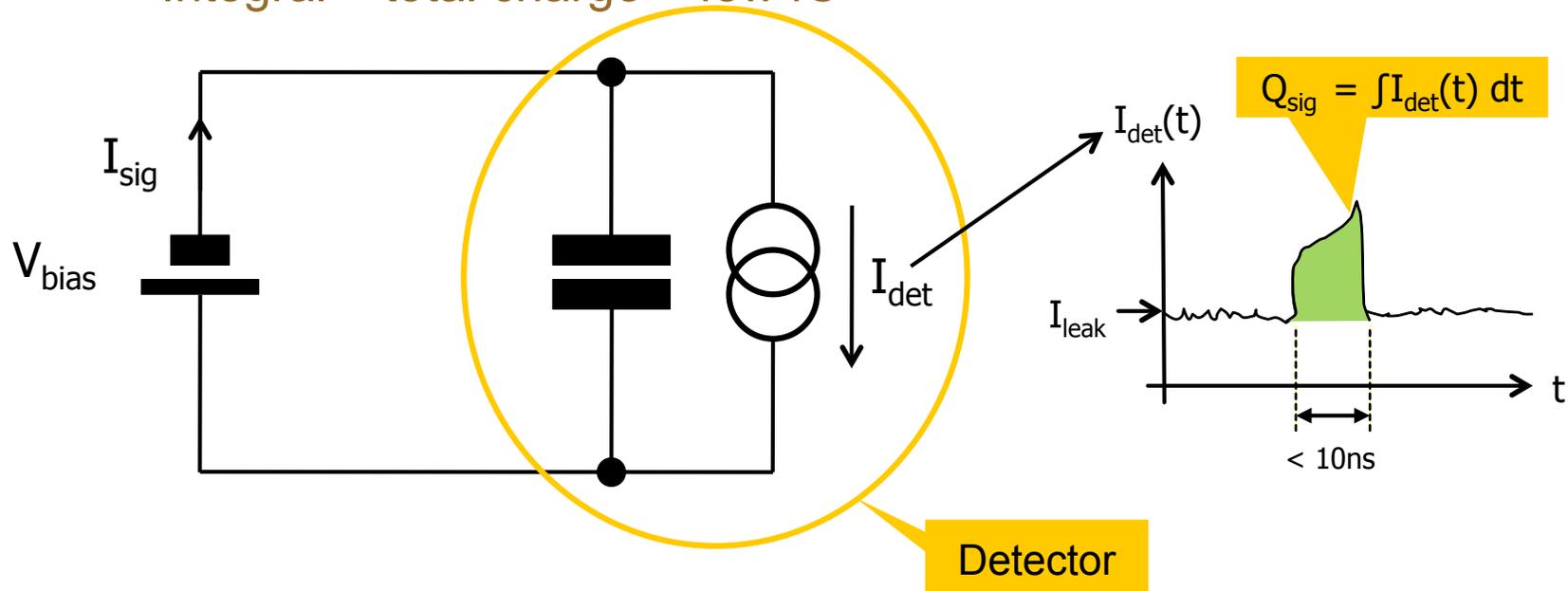1. How is the sensor modeled ?


- By a capacitance in parallel with a signal current source
 - C: few fF (MAPS, SiDC) – some 100 fF (Pixel) – some 10pF (Strips)
 - $I(t)$: depends on charge motion, $O(10\text{ns})$. Maybe leakage!
Integral = total charge = few fC



- Task of the FE Electronics:
 - Fix DC potential of detector on one side
 - Measure signal current / charge



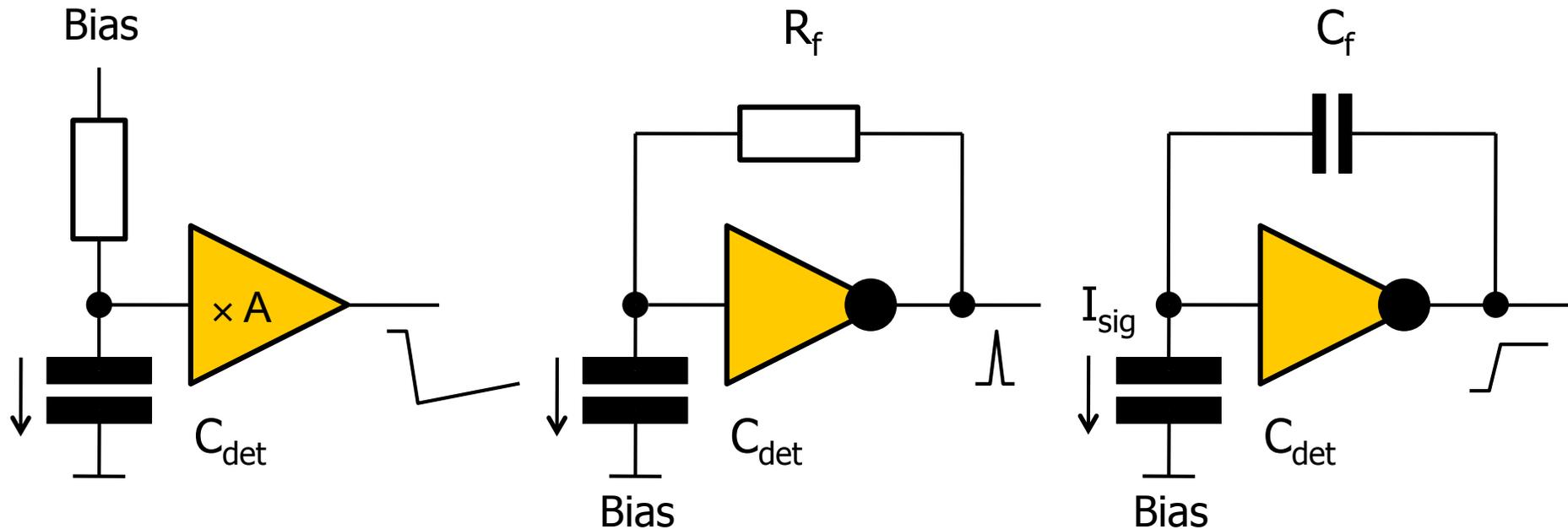2. What are typical amplifier arrangements ?



Voltage Amplifier

$$U_{out} = A Q / C_{det}$$

- step output
- small for large C_{det}
- need to recharge

Current Amplifier

$$U_{out} = I_{sig} R_f$$

- spike output
- independent of C_{det}

Charge Amplifier


$$U_{out} = Q_{sig} / C_f$$

- step output
- independent of C_{det}



Charge Amplifier in more Detail


- The amplifier generates a *virtual ground* at its input
 - This fixes the potential on the second side of the sensor capacitor (the other side is fixed by V_{bias})
 - Note that in most cases this input voltage is not 0V!
- Current (flowing charge) from the sensor cannot stay on C_{det} (because the voltage is fixed) and must flow onto C_f
 - Therefore $Q_{\text{sig}} = \int I_{\text{sig}} dt = Q_f = U_f C_f \rightarrow U_{\text{out}} = -U_f = -Q_{\text{sig}}/C_f$

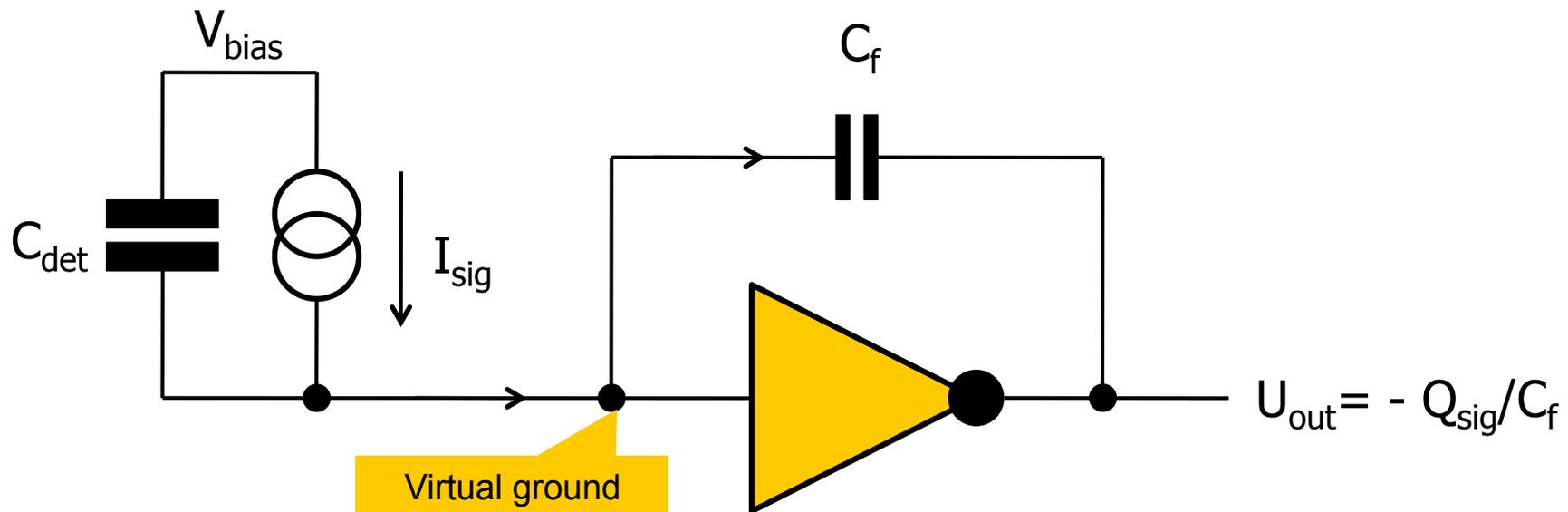




How is the Amplifier Implemented ?

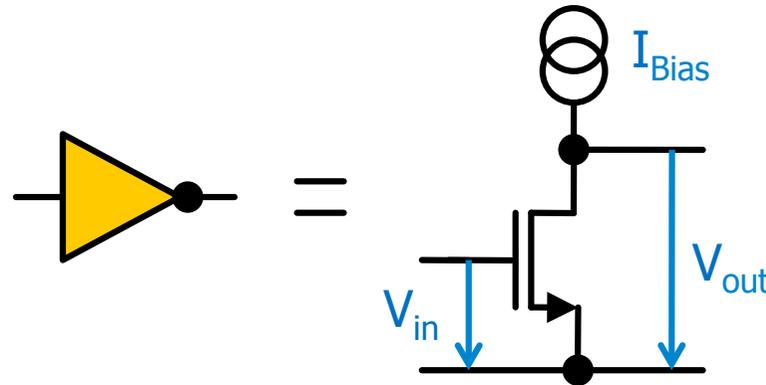- One transistor can be used as an amplifier:



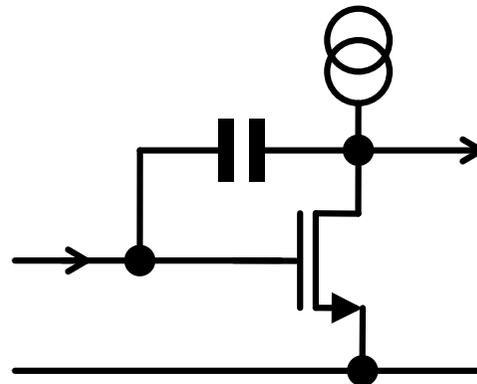- A charge amplifier is then very simple:



- This simple circuit has (often too) low (voltage) gain.
A 'Cascode' is often used to increase the gain to >100



Do we get all the Charge?

- What happens if gain of amplifier is finite?


An inverting amplifier with a feedback capacitor C_f converts an input charge Q_{in} to a voltage. An infinite gain would keep the input at a perfect virtual ground and the output voltage step in this ideal case is $\Delta U_{out} = -Q_{in}/C_f$. If the gain $-v_0$ is finite, however, a small residual voltage remains:

$$\Delta U_{in} = \frac{Q_{in}}{C_{in} + (1 + v_0) C_f}$$

$$C_{eff} = (1 + v_0) C_f \approx v_0 C_f$$

$$\Delta U_{out} = -\frac{Q_{in}}{C_f} \cdot \frac{1}{1 + \frac{1}{v_0} + \frac{C_{in}}{v_0 C_f}}$$

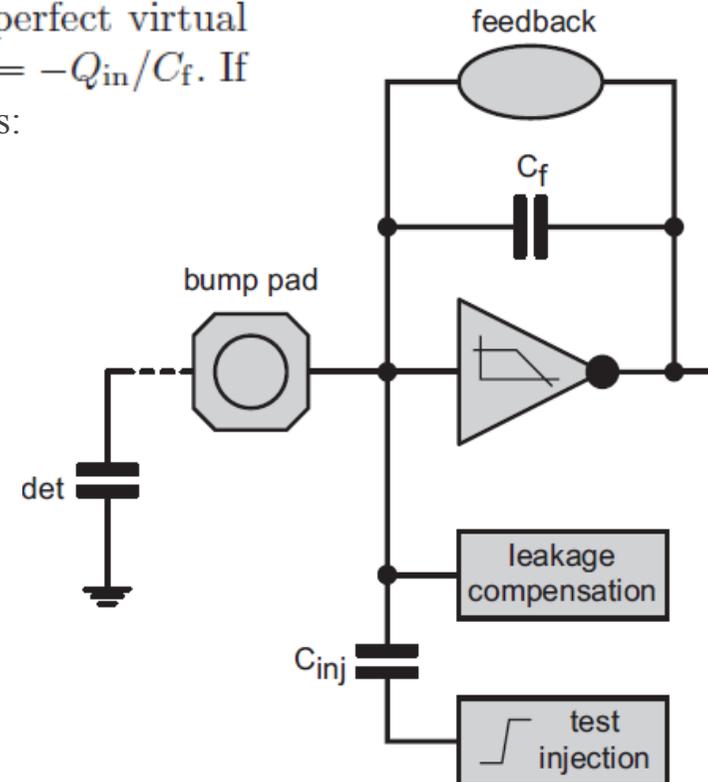
$$C_{eff} \approx v_0 C_f \gg C_{in} = C_{det} + C_{amp} + C_{stray}$$





Classical System have a Filter = Shaper

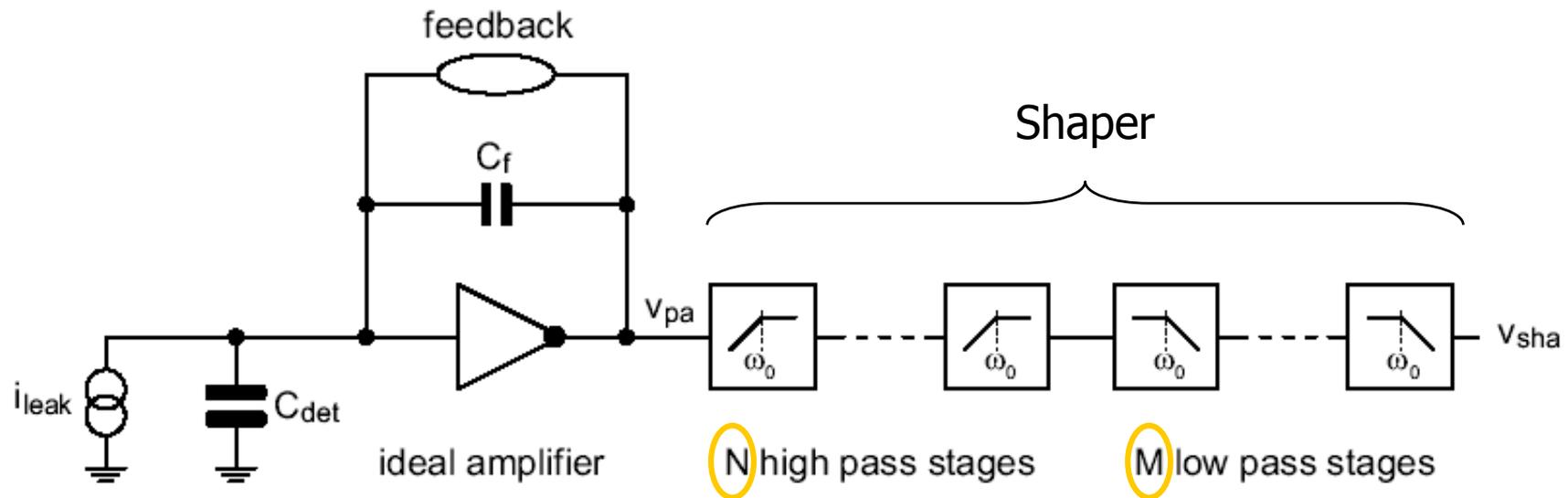- Filter for pulse shaping & noise reduction:
 - *High pass stages* eliminate DC components & low freq. noise
 - *Low pass stages* limit bandwidth & therefore high freq. noise




- Due to its output shape (see later), this topology is often called a ‘Semi Gaussian Shaper’
- Nearly always $N = 1$. Often $M = 1$, sometimes M up to 8




Frequency Behaviour of Shaper

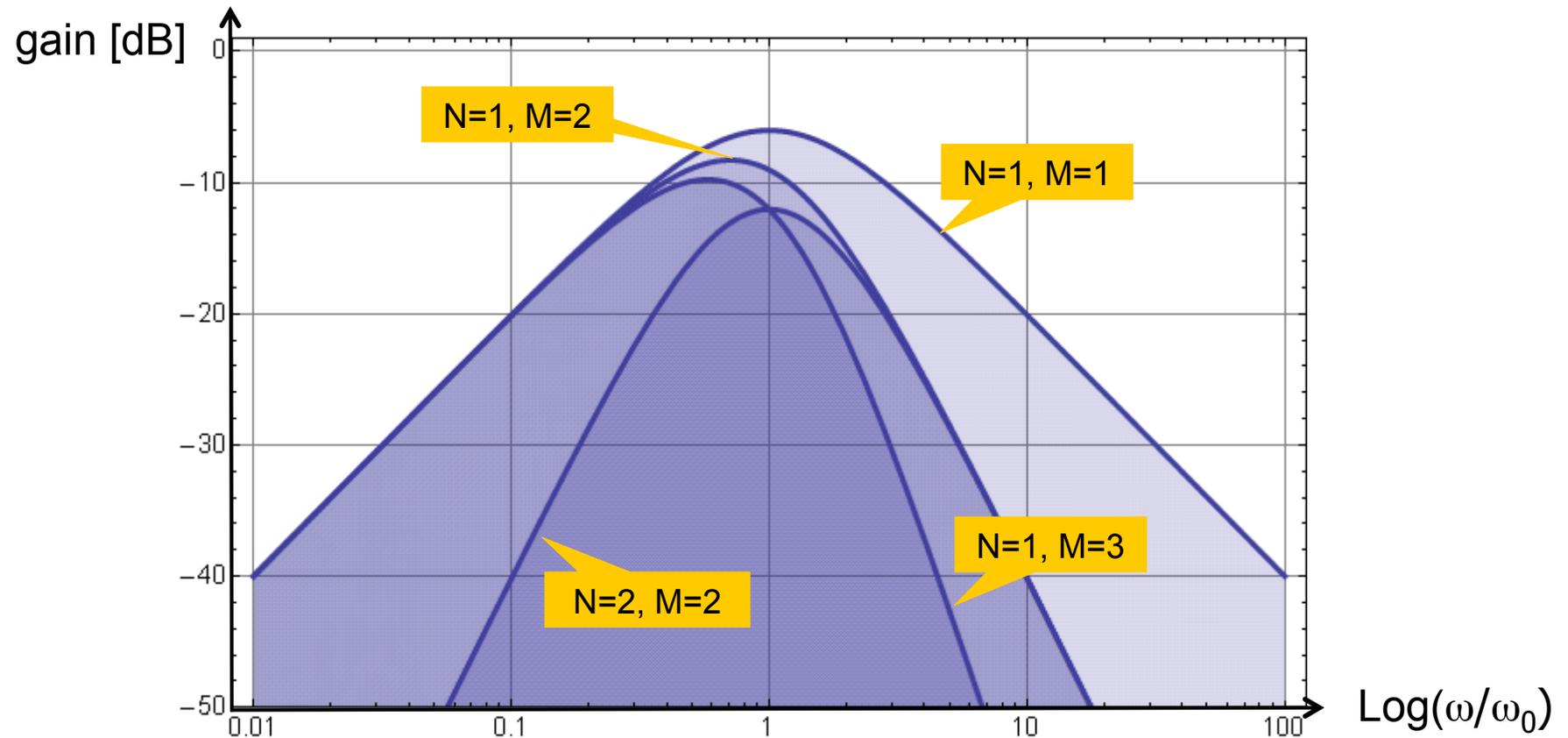- Low and High frequencies are attenuated
- Corner frequency (here: 1) is transmitted best
- Bode Plot (log/log) of transfer characteristic:





3. What is the output signal?

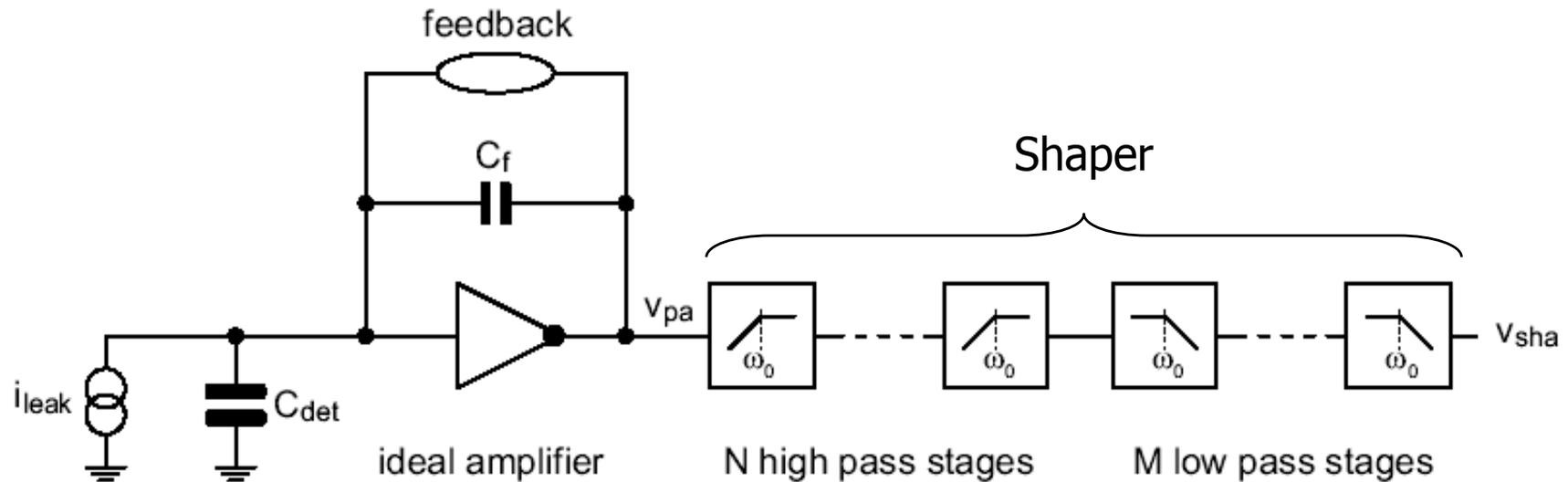

- For a delta current pulse, the output voltage v_{pa} is a step function
- This has a Laplace-Transform $\sim 1/s$
- The transfer functions of the high / low pass stages multiply to:

$$\mathcal{L}^{(N,M)}(s) = \frac{1}{s} \left(\frac{s\tau}{1 + s\tau} \right)^N \left(\frac{1}{1 + s\tau} \right)^M = \frac{\tau^N s^{N-1}}{(1 + s\tau)^{N+M}}$$



Pulse shape after shaper

- The time domain response is the inverse Laplace transform.
- The Laplace integral can be solved with residues:
There is an $(N+M)$ -fold pole at $-1/\tau$

$$\begin{aligned}
 f^{(N,M)}(t) &= \text{Res} \left. \frac{\tau^N s^{N-1} e^{st}}{(1+s\tau)^{N+M}} \right|_{s=-1/\tau} \\
 &= \frac{\tau^N}{(N+M-1)!} \lim_{s \rightarrow -\frac{1}{\tau}} \frac{d^{N+M-1}}{ds^{N+M-1}} \left[\frac{s^{N-1} e^{st}}{(1+s\tau)^{N+M}} \left(s + \frac{1}{\tau} \right)^{N+M} \right] \\
 &= \frac{1}{(N+M-1)!} \left(\frac{t}{\tau} \right)^M \sum_{i=0}^{\infty} \frac{\left(-\frac{t}{\tau}\right)^i}{i!} \frac{(M+i+N-1)!}{(M+i)!} \quad (1.42)
 \end{aligned}$$

- For only ONE high pass section ($N=1$), this simplifies to:

$$f^{(1,M)}(t) = \frac{1}{M!} \left(\frac{t}{\tau} \right)^M e^{-t/\tau} \quad t_{\text{peak}}^{(1,M)} = M\tau = \frac{M}{\omega_0} \quad f_{\text{max}}^{(1,M)} = \frac{1}{M!} \left(\frac{M}{e} \right)^M$$




Reminder (hopefully..): Integration with Residues

This is very simplified!
 The statements are valid under certain conditions only.
 Consult a book on Complex Analysis!

- The *Residue Theorem* states that the line integral of a function f along a closed curve γ in the complex plane is basically the sum of the residues at the *singularities* a_k of f :
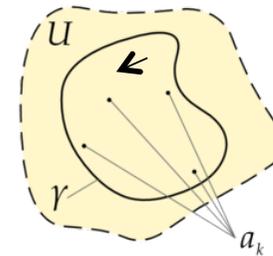
$$\oint_{\gamma} f(z) dz = 2\pi i \sum \text{Res}(f, a_k)$$



Wikipedia

- The *residue* is a characteristic of a singularity a_k
 - For a first order (simple) pole (f behaves \sim like $1/z$ at the pole):

$$\text{Res}(f, c) = \lim_{z \rightarrow c} (z - c) f(z).$$

- For a pole of order n :

$$\text{Res}(f, c) = \frac{1}{(n-1)!} \lim_{z \rightarrow c} \frac{d^{n-1}}{dz^{n-1}} ((z - c)^n f(z)).$$



Example for Integration with Residues

- We want to find $A = \int_{-\infty}^{\infty} \frac{1}{x^2 + 1} dx$.
- The function $f(z) = \frac{1}{z^2 + 1} = \frac{1}{(z + i)(z - i)}$ has poles i and $-i$

- The residue at i is:


$$Res(f, i) = \lim_{z \rightarrow i} f(z)(z - i) = \lim_{z \rightarrow i} \frac{1}{(z + i)} = \frac{1}{2i}$$

- The integral along green curve is then

$$\int_C f(z) dz = 2\pi i Res(f, i) = \pi$$

- When we increase the size of the curve, the contribution of the upper arc vanishes* and the lower line becomes A


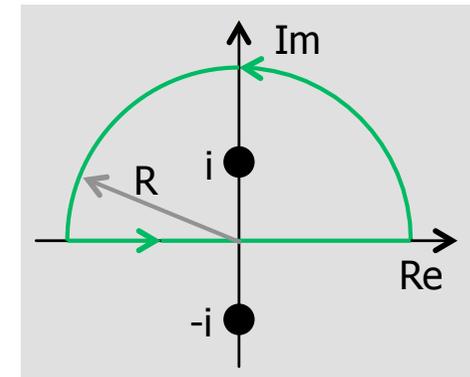
*: the length of the arc rises $\sim R$, but f falls as $1/R^2$





Pulse Shapes for N=1

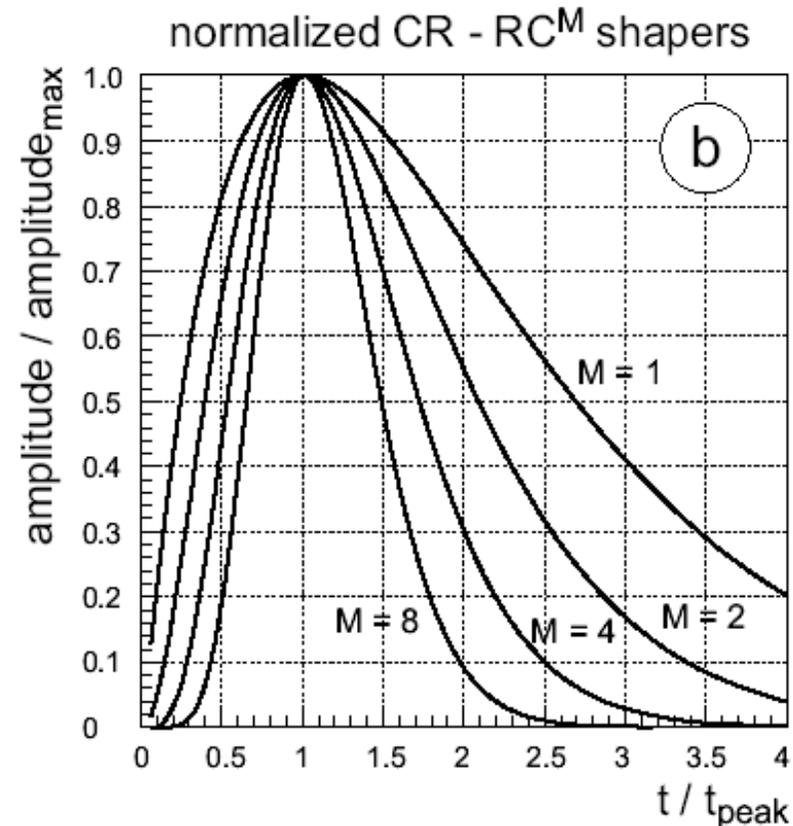
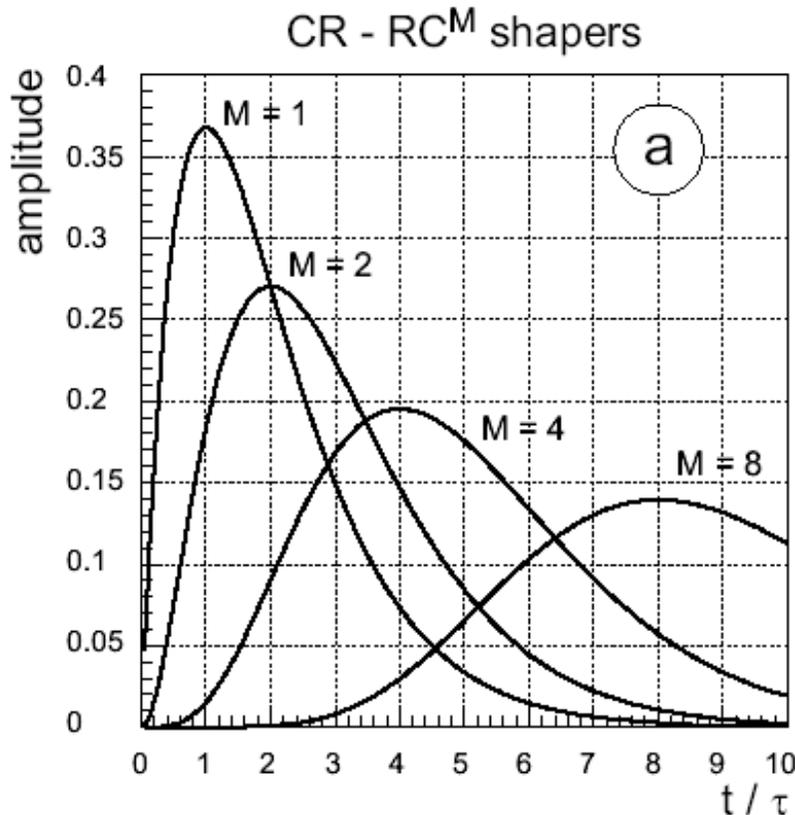
- Pulses from higher order are slower. To keep peaking time, τ of each stage must be decreased
- Right plots shows normalized pulses (same peak amp. & time)
- For high orders, pulses become narrow (width / peaking time), this is good for high pulse rates!






Pulse Shapes for N=2

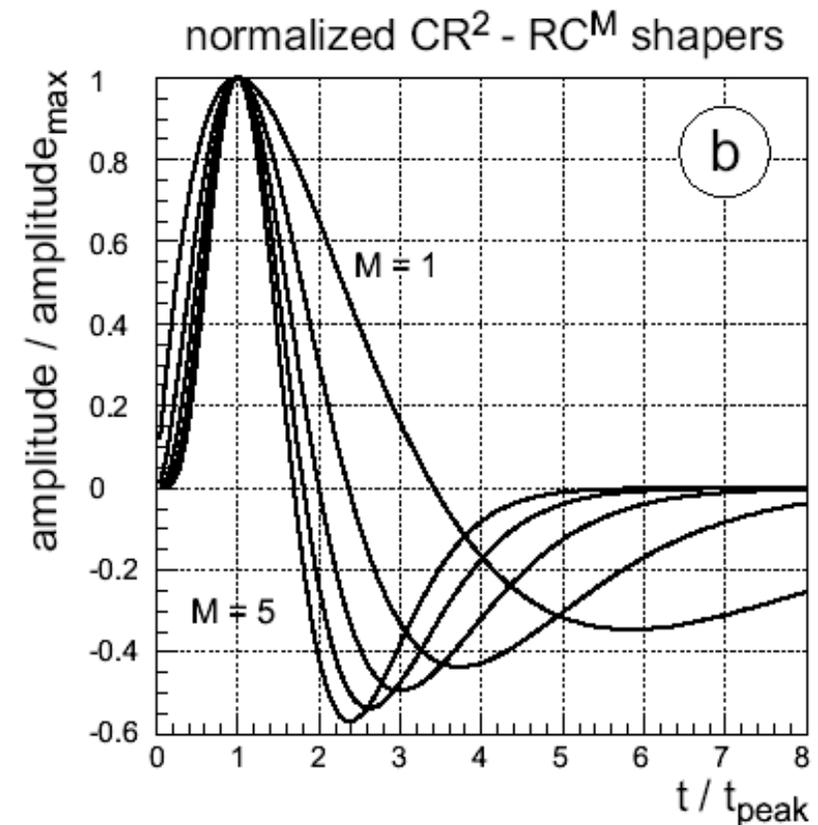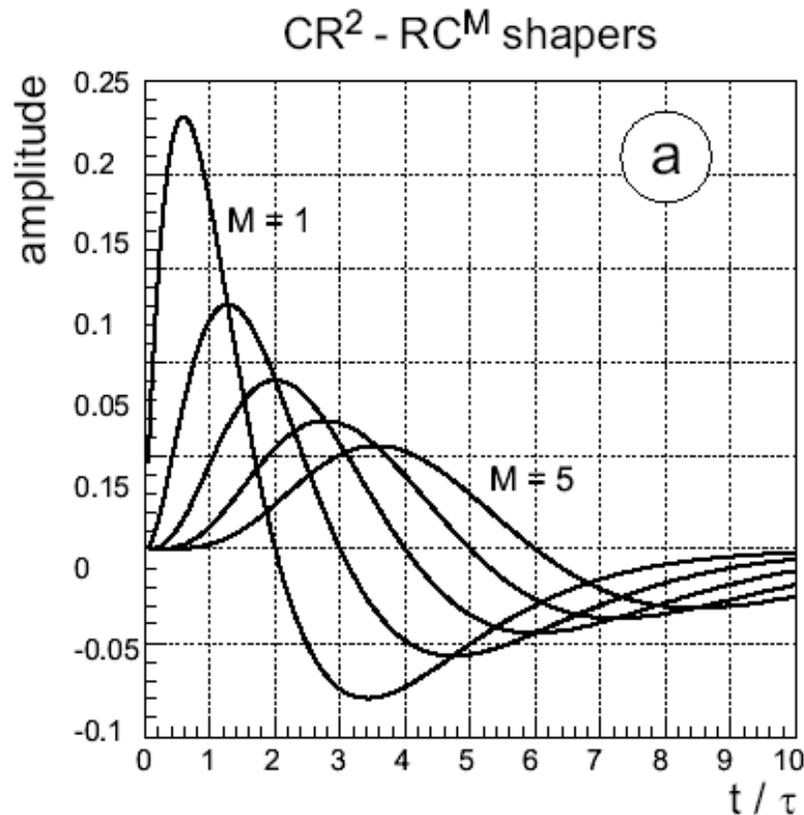- This gives an undershoot which is often undesirable → N=1.
 - But: The zero crossing time is *independent* of amplitude.
It can be used to measure the pulse arrival time with no time walk





4. How is noise described ?

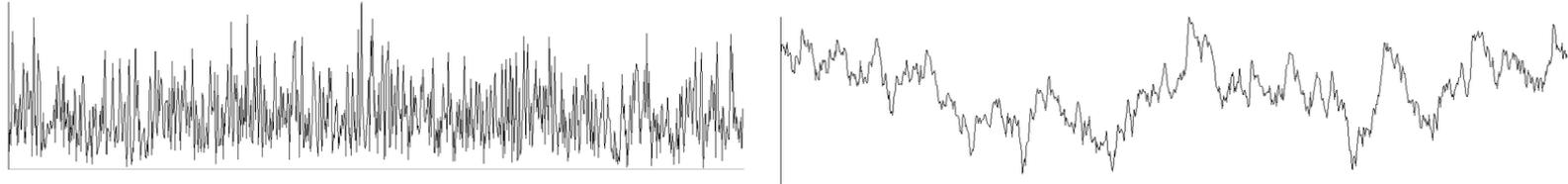


- Noise are random fluctuations of a voltage / current
- The average noise is zero: $\langle \text{sig} \rangle = 0$
- The noise 'value' can be defined as the rms: $\text{noise}^2 = \langle \text{sig}^2 \rangle$
- The fluctuations can have different strength for various frequencies. We therefore describe noise by its *spectral density*, the (squared) noise voltage (density) as a function of frequency. Unit = V^2/Hz (or sometimes $\text{V}/\sqrt{\text{Hz}}$)
- Spectra can be
 - Constant – 'White Noise'
 - $1/f$ – '1/f noise'
 - Drop at high freq. – 'pink noise'



Noise Types

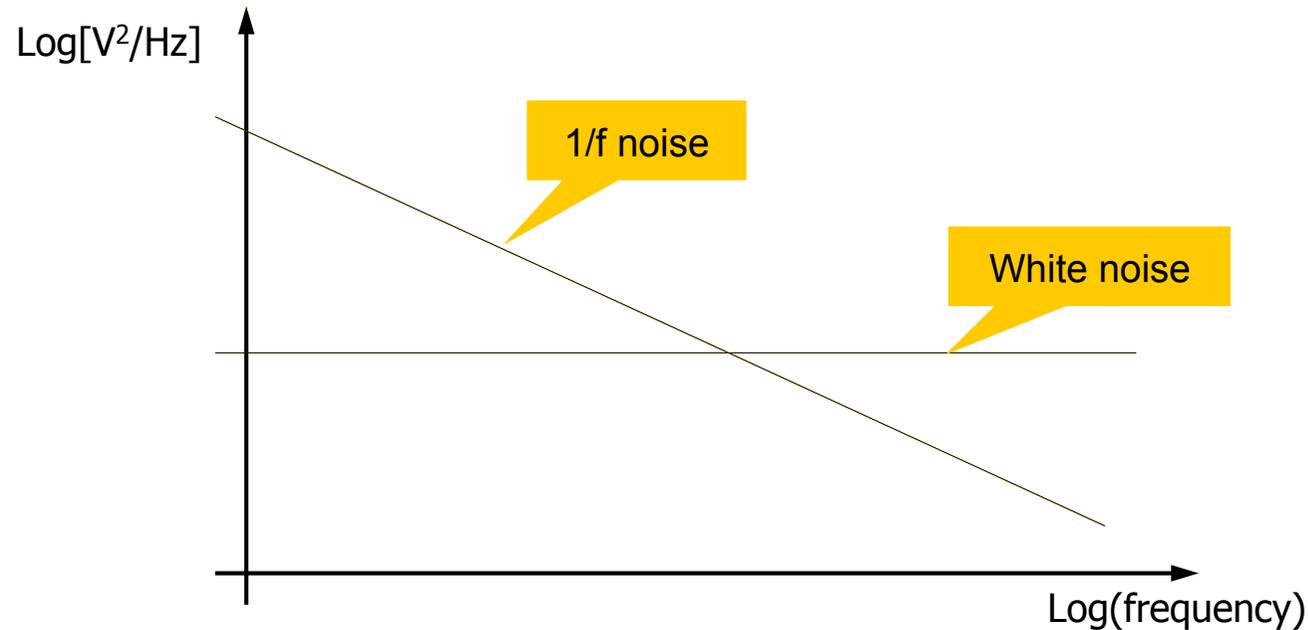- Most common types are
 - *White noise* has constant spectral density
 - The spectral density of $1/f$ is $\sim 1/f$ (or $S(f) \propto 1/f^\alpha$)
- Be careful: one can use frequency ν , to angular freq. ω !



- The rms noise is the integral of the noise spectral density over all frequencies (0 to ∞)



A Closer Look on Thermal Noise

- Problem: a constant spectral density up to infinite frequencies would be infinite noise power.
- Quantum mechanics gives the exact value for the spectral noise density as a function of frequency ν and temperature T :

$$S_{noise}(\nu, T) = \frac{h\nu}{e^{h\nu/kT} - 1} \xrightarrow{h\nu \ll kT} kT$$

- h = Planck's constant = 6.626×10^{-34} Js,
- k = Boltzmann's constant = 1.381×10^{-23} J/K
- For 'low' frequencies ($h\nu \ll kT$), this gives just kT
- The noise starts to drop at $\nu = kT/h \approx 21 \text{ GHz} \times T/K$
 - At room temperature, this is $\sim 5\text{THz}$. The approximation of $S_{noise} = kT$ is therefore valid for all practical circuit frequencies.
- (At very high frequencies, there is an additional 'quantum' noise which rises as $h\nu$)



4. What are the important noise sources ?

- The most important noise sources are:

- *Detector* leakage current (white)
(from charge statistics, 'shot noise')

$$\frac{d\langle i_{\text{leak}}^2 \rangle}{df} = 2qI_{\text{leak}}$$

- Noise in *resistors* (white)
(from thermal charge motion, 'thermal noise')
(mainly in feedback resistor)

$$\frac{d\langle i_{Rf}^2 \rangle}{df} = \frac{4kT}{R_f}$$

or

$$\frac{d\langle v_{Rf}^2 \rangle}{df} = 4kTR_f$$

- Noise in transistors (white and 1/f)
- transistor channel behaves like a resistor
with a reduction of 2/3 due to channel properties

CHECK

(2/3 in strong inversion ... 1/2 in weak inversion)

- thermal (current) noise at output
equivalent to (voltage) noise at gate:

$$\frac{d\langle v_{\text{therm}}^2 \rangle}{df} = \frac{8kT}{3g_m}$$


- 1/f noise mostly expressed as gate
noise voltage:

$$\frac{d\langle v_{1/f}^2 \rangle}{df} = \frac{K_f}{C_{\text{ox}}WL} \frac{1}{f}$$



Noise calculation: Noise sources

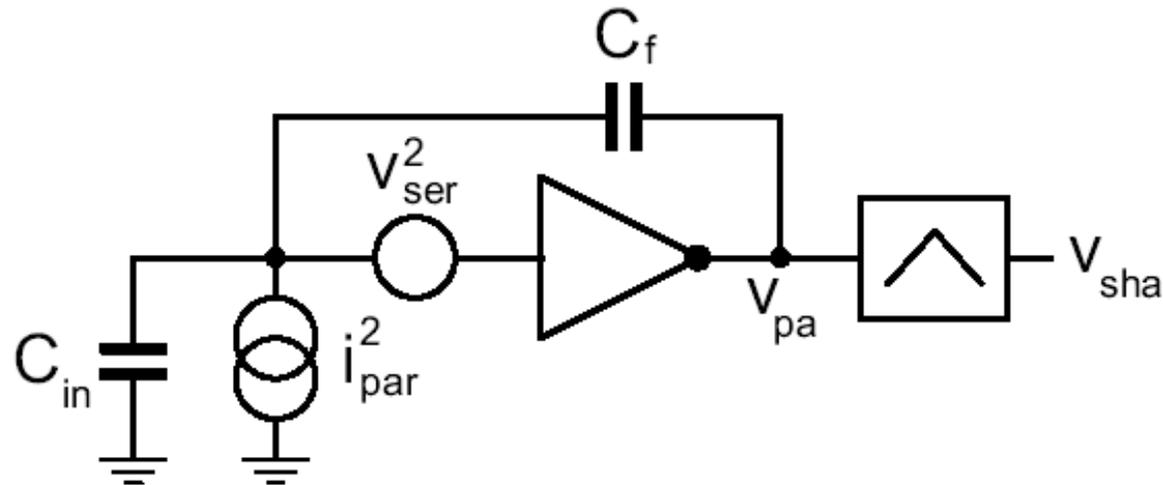- Equivalent circuit with (ideal) amplifier, input capacitance, feedback capacitance and (dominant) noise sources:



- Spectral densities of noise sources:

$$\text{serial noise voltage : } \frac{d\langle v^2(f) \rangle}{df} = V_0 + V_{-1}f^{-1}$$

$$\text{parallel noise current : } \frac{d\langle i^2(f) \rangle}{df} = I_0$$

white (channel) points to V_0

1/f noise (MOS) points to $V_{-1}f^{-1}$

white (leakage) points to I_0



5. What is the total noise at the output ?


- Recipe:
 1. Calculate what effect a voltage / current noise of a frequency f at the input has at the output
 2. For each noise source: Integrate over all frequencies (with the respective densities)
 3. Sum contributions of all noise sources

- This yields the total rms voltage noise at the output

- Then compare this to a 'typical' signal.
It is custom to use *one* electron at the input as reference.



Parallel Noise Current

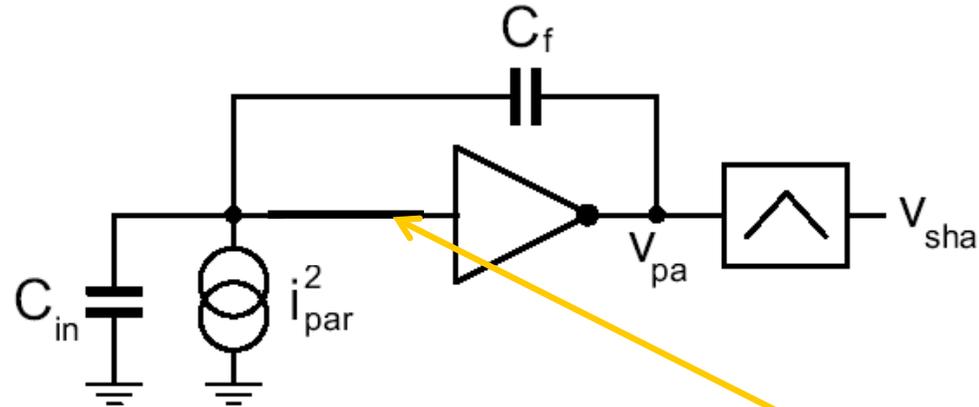


- We assume a perfect virtual ground at the amplifier input
 - No charge can go to C_{in} (voltages are fixed)
 - Noise current must flow through C_f : $v_{out} = i_{in} \times Z_{Cf}$

$$\text{parallel noise : } \frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} = \frac{d\langle i_{par}^2(\omega) \rangle}{d\omega} \frac{1}{(\omega C_f)^2} = \frac{I_0}{2\pi} \frac{1}{(\omega C_f)^2}$$

(note the change of the frequency variable from ν to ω)



Serial Noise Voltage

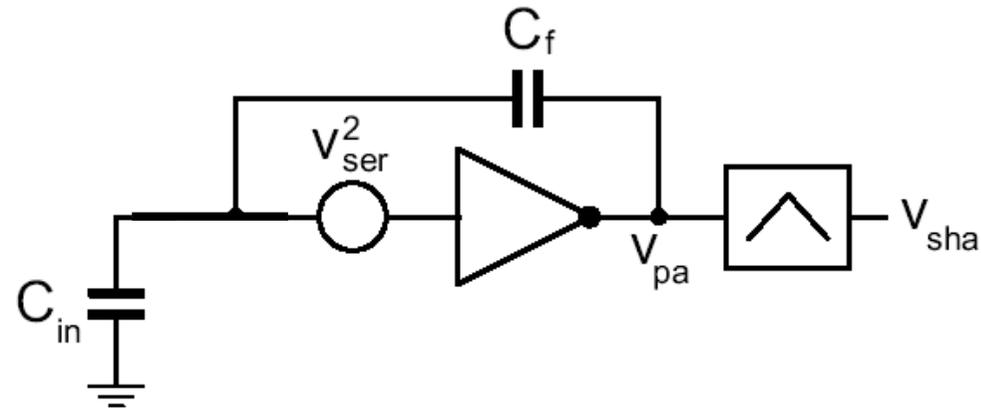

- Output noise is determined by the capacitive divider made from C_f and C_{in} : $v_{ser} = v_{pa} \times Z_{C_{in}} / (Z_{C_{in}} + Z_{C_f})$

or:

$$v_{pa}^2 = v_{ser}^2 \left(\frac{C_{in} + C_f}{C_f} \right)^2$$

Therefore: serial noise : $\frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} \approx \left(V_{-1}\omega^{-1} + \frac{V_0}{2\pi} \right) \left(\frac{C_{in}}{C_f} \right)^2$

$$(C_{in} = C_{det} + C_{preamp} + C_{parasitic})$$



Total *Output* Noise (after the amplifier)

- In total, the output noise can be written as a sum of contributions with different frequency dependence:

$$\frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} = \sum_{k=-2}^0 c_k \omega^k$$

frequency dependence is here

with

$$c_{-2} = \frac{I_0}{2\pi C_f^2}, \quad c_{-1} = V_{-1} \frac{C_{in}^2}{C_f^2} \quad \text{and} \quad c_0 = V_0 \frac{C_{in}^2}{2\pi C_f^2}.$$

leakage
(white)

MOS gate
(1/f)

MOS channel
(white)

from leakage current I_{leak} :

$$I_0 = 2qI_{leak}$$

from transistor channel noise:

$$V_0 = \frac{8}{3} \frac{kT}{g_m}$$

from 1/f noise:

$$V_{-1} = \frac{K_f}{C_{ox}WL}$$



Noise Transfer Function

- (N,M) - Shaper transfer function: $H_{N,M}^2(\omega) = A^2 \frac{\left(\frac{\omega}{\omega_0}\right)^{2N}}{\left(1 + \left(\frac{\omega}{\omega_0}\right)^2\right)^{N+M}}$.

- ‘Filtered’ noise at the output of the shaper:

$$\begin{aligned} \langle v_{\text{sha}}^2 \rangle &= \int_0^\infty H_{N,M}^2(\omega) d\langle v_{\text{pa}}^2(\omega) \rangle = \sum_{k=-2}^0 \int_0^\infty c_k \omega^k H_{N,M}^2(\omega) d\omega \\ &= \frac{A^2}{2} \frac{1}{\Gamma(N+M)} \sum_{k=-2}^0 c_k \omega_0^{k+1} \Gamma\left(N + \frac{k+1}{2}\right) \Gamma\left(M - \frac{k+1}{2}\right) \end{aligned}$$

$$\Gamma(z+1) = z \Gamma(z)$$

$$\Gamma\left(\frac{1}{2}\right) = \sqrt{\pi},$$

- For simplest shaper (N=M=1),
Squared rms noise voltage at the shaper output:

$$\langle v_{\text{sha}}^2 \rangle = A^2 \frac{\pi}{4} \left(\frac{c_{-2}}{\omega_0} + \frac{2}{\pi} c_{-1} + \omega_0 c_0 \right)$$



Calculation of ENC

- The **equivalent noise charge, ENC** is the (rms) noise at the output of the shaper expressed in Electrons input charge, i.e. divided by the ‘charge gain’
- The ‘charge gain’ is (see before): $V_{max} = q/C_f \times A \times 1/e$

charge of 1 electron
(1.6e-19C)

Shaper
dc gain

Peak amplitude
for N=M=1

leakage gives noise
for slow shaping

1/f – noise cannot be
reduced by changing
shaping time

$$ENC_{CR-RC}^2 = \frac{\langle v_{sha}^2 \rangle}{V_{max}^2} = \frac{e^2}{4q^2} \left(\frac{\tau}{2} I_0 + \frac{1}{2\tau} V_0 C_{in}^2 + 2 V_{-1} C_{in}^2 \right)$$

C_{in} is bad for **fast** shaping.
Reducing V_0 requires large g_m



Noise contributions

- Real noise contributions for the coefficients I_0 , V_0 , V_{-1} :

from leakage current I_{leak} : $I_0 = 2qI_{\text{leak}}$

from transistor channel noise: $V_0 = \frac{8 kT}{3 g_m}$

from 1/f noise: $V_{-1} = \frac{K_f}{C_{\text{ox}}WL}$

- For a $0.25\mu\text{m}$ technology ($C_{\text{ox}}=6.4 \text{ fF}/\mu\text{m}^2$, $K_f=33 \times 10^{-25} \text{ J}$, $L=0.5\mu\text{m}$, $W=20\mu\text{m}$) and $C_{\text{in}}=200\text{fF}$, $I_{\text{leak}}=1\text{nA}$ and $\tau=50\text{ns}$, $g_m=500\mu\text{S}$ (typical LHC pixel detector):

$$\left(\frac{\text{ENC}}{e^-}\right)^2 = 115 \cdot \frac{\tau}{10 \text{ ns}} \cdot \frac{I_{\text{leak}}}{1 \text{ nA}} \rightarrow 575$$

$$+ 388 \cdot \frac{10 \text{ ns}}{\tau} \cdot \frac{\text{mS}}{g_m} \cdot \left(\frac{C_{\text{in}}}{100 \text{ fF}}\right)^2 \rightarrow 621$$


$$+ 74 \cdot \left(\frac{C_{\text{in}}}{100 \text{ fF}}\right)^2 \rightarrow 296$$

$\left. \begin{array}{l} \rightarrow 575 \\ \rightarrow 621 \\ \rightarrow 296 \end{array} \right\} \text{ENC}=40 e^-$



Noise vs. Shaping Time

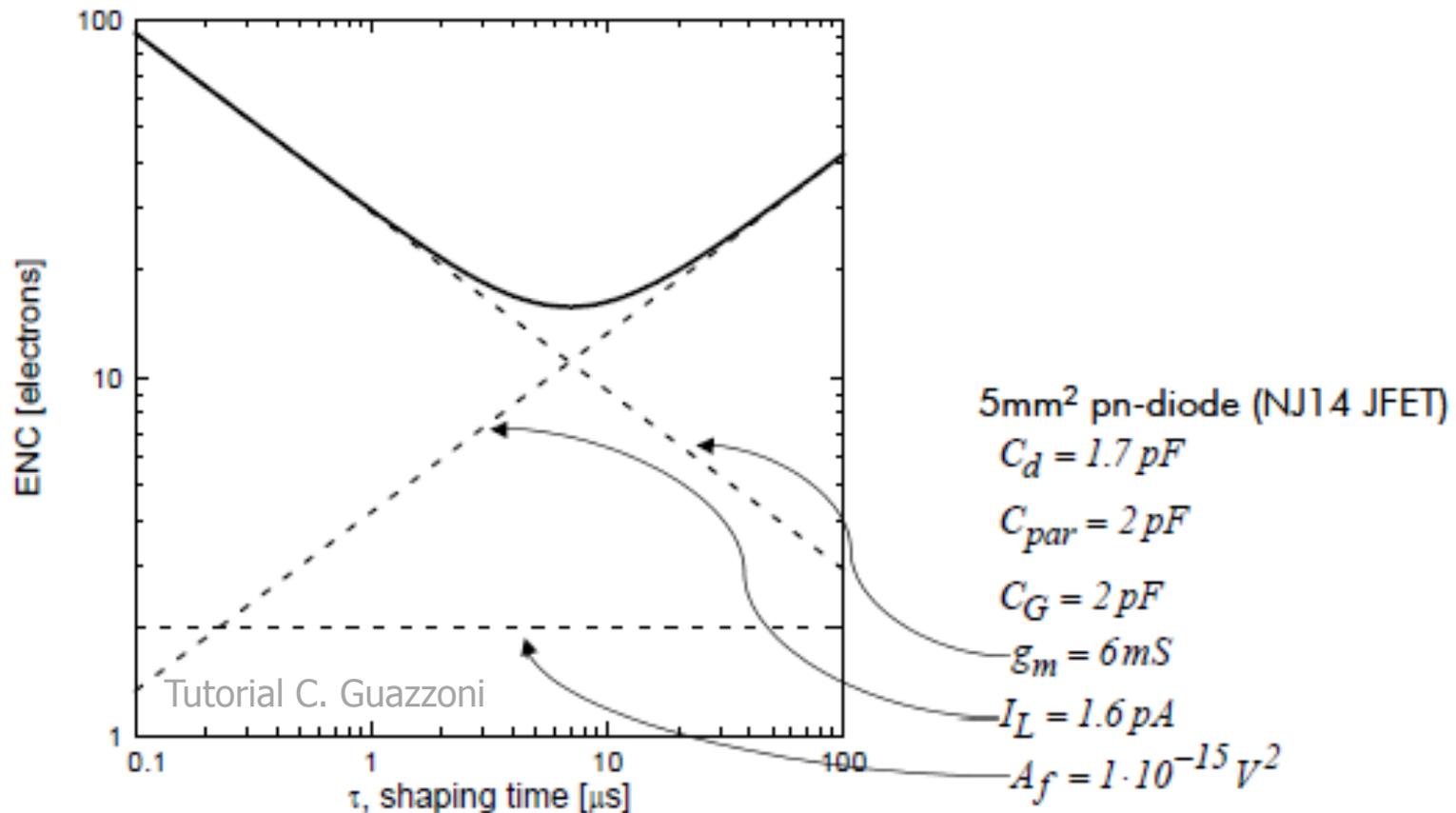
- Long shaping: leakage noise contributes more
- Short shaping: Amplifier white noise, worsened by C_{Det}
- Always: Amplifier 1/f noise, worsened by C_{Det}





Comparison of two Detector Systems

✓ ENC vs. shaping time (τ)

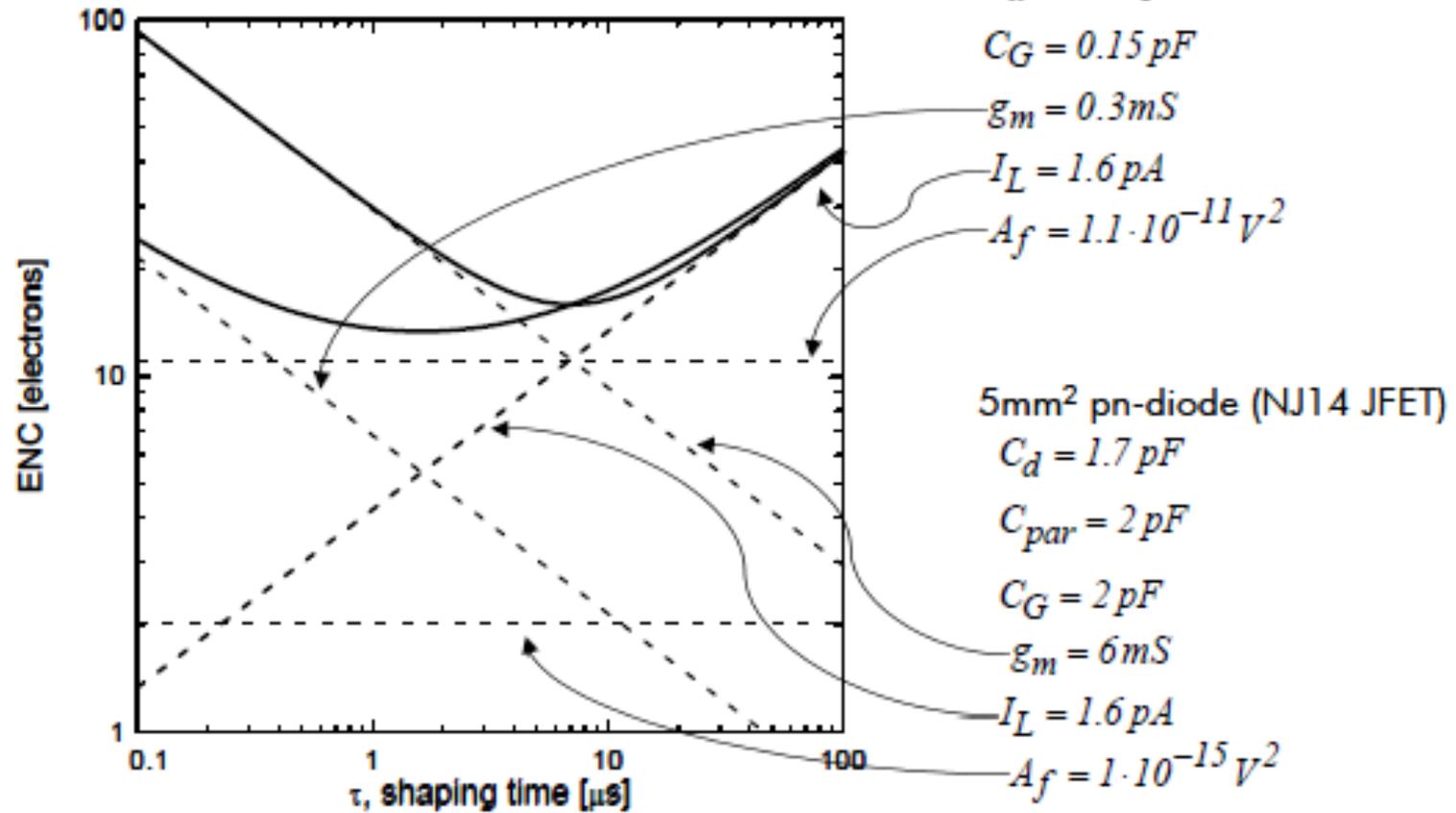



Typical Noise Values

C_{in}	Shaping	Power	Noise	System
10fF	μs	100uW	5	CCD, DEPFET
100fF	μs	40 μ W	30	Slow Pixel
100fF	25ns	40 μ W	100	Pixel (ATLAS)
20pF	200ns	1000 μ W	1000	Strips





Why Do we Need Low Noise ?

- Spectral resolution
- Position resolution (good interpolation, only for 'wide' signals)
- Low noise hit rate (with threshold)
- Good efficiency (with threshold)



How to get g_m ? More power and larger W!

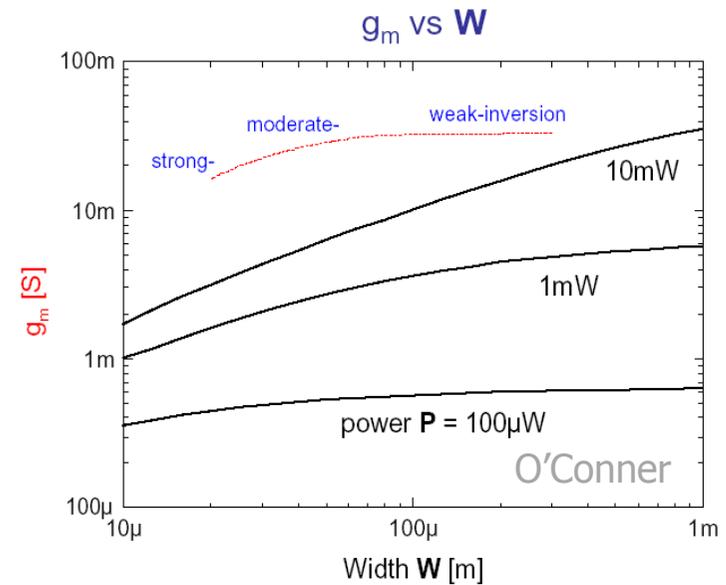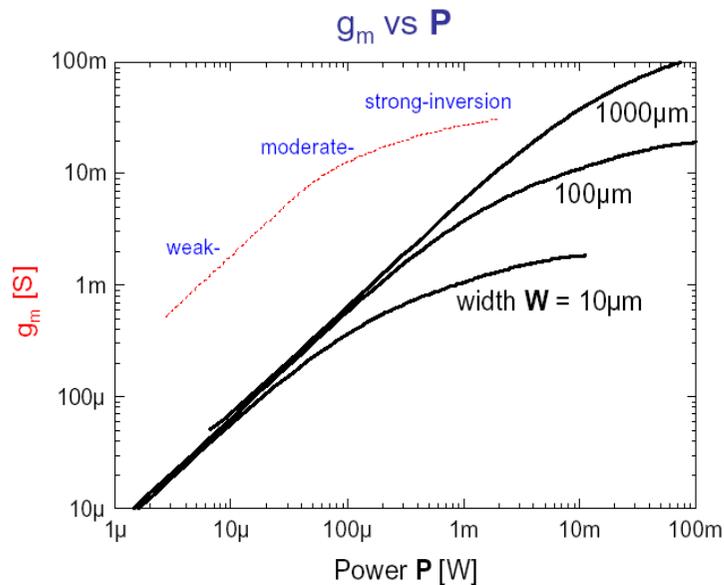- The transconductance g_m of the input MOS is most important. It can be increased by
 - shorter length L (technology limit! short L can add noise)
 - Wider width W works, but increases input capacitance!
 - Increase current works, but increases power consumption





Optimal ENC (Optimal W for each Power value)

Input MOSFET optimization

