 






Design Flow





Levels of Abstraction


This Lecture

  



Design Hierarchy

 
- A chip is subdivided in smaller blocks
 - Described by schematics or hardware description language (HDL)
- At lowest Level:
 - simple logic functions (NAND, MUX) + 'standard cell' layouts
 - Analogue 'full custom blocks'





A real(y deep) Design Hierarchy


 
- The hierarchy has MANY levels
- In our chips: max. 10-15 levels



Pentium P6



Top-Down, Bottom-Up

  


- I believe: both methods have drawbacks
- Try to come from both sides!



 Example: DAC



- Digital Analogue Converter: Binary Code → Current





  1. Schematic and Symbol


- Schematic describes circuit with other cells & transistors
- A ‚symbol‘ of the cell contains all pins
 - It is later used to represent the schematic in the hierarchy





 2. Simulation



- Mostly analogue (for us)
- Models are different for each vendor! Are provided by vendor. Should be verified..
- Optimize circuits
- Results can be used to parameterize the cell.
- For instance, digital cells can be modelled by delay (depending on C_{load} , VDD, Temp,...)
- \Rightarrow digital (VERILOG) Model





Layout, Design Rule Check

 
 
- Layout (mostly by hand) on transistor level
- Check of vendor-given rules with Design Rule Check (DRC) (z.B. conductor widths, spacing,...)
- Design rules are different for each technology!
 - The are collected in a (text) file.





Standard Cells

  - (Digital) standard cells have equal heights and identical (power) connections, so that they can be arranged in rows.
- In technologies with >2 metal layers: routing on top of cells
- 'Optimal' placement of cell is challenging task!
- Wires introduce delays which are not a priori known by simulation!






Special Layout : Bit-Slice


- For repetitive structures: pads are arranged so that touching cells connect correctly
 - compact layout, low delays, best performance

Full Adder



Symbol for 1 bit:

 

Geometry for 1 Bit:

 

4 Bit Adder:

  



Full Chip

- Standard Cells + Full custom cells (here: RAMs, Delays) + Pads ('frame')

