

SPAD CHIP


P. Fischer

Preface

- Grading of the 'VLSI design' will be based on a practical chip design.
- This includes
 - Schematic design
 - Analogue simulations
 - Mixed mode simulation
 - Layout with DRC and LVS
- There will be an opportunity to submit a chip on a real run of the IMS 350nm technology in spring.
- I therefore suggest to make a common design effort (in teams of 2) to produce a full SPAD readout chip.
- These slides document the goal of the design

Goal

 
- We want to solve a real world problem as encountered by a KIP group:
- Photon bursts at known times propagate in an optical fiber. We want to measure the number of photons in each burst. (Bursts are spaced by $\sim 100\text{ns}$)
- Concept: dilute the photon number by sending photons to multiple fibers so that at most 1 photon is left per fiber. Observe each fiber output with one SPAD.



- Preliminary discussions with the users indicate that the SPADs should be arranged in a regular X-Y-grid with $40\mu\text{m}$ pitch (=repetition).



(SPAD Array Geometry)

 - Lateral fiber facet is oval of $< 5 \times 10 \mu\text{m}^2$
- Pitch of splitters is $\sim 40 \mu\text{m}$. Can be adjusted arbitrarily by design.
- Leave $\sim 10 \mu\text{m}$ lateral space for alignment tolerance
- Keep structure symmetric in x and y (assembly freedom, free space concept)
- -> use SPADs of $30 \times 30 \mu\text{m}^2$ in $40 \mu\text{m}$ pitch




SPAD Array and Chip Size

  - Number of SPADs not well defined.
- Odd number preferred to have a clear center SPAD
- Chose 9 x 9 (by chance, this is good for binary adder: $9 \times 9 = 81 = 3 \times 27$)
- Chip needs ~20 Bond pads. Our pitch is $168 \mu\text{m}$.
- Decide on geometry so that fibers can be easily mounted to SPADs
- Keep chip as small as possible to save space




SPAD Readout

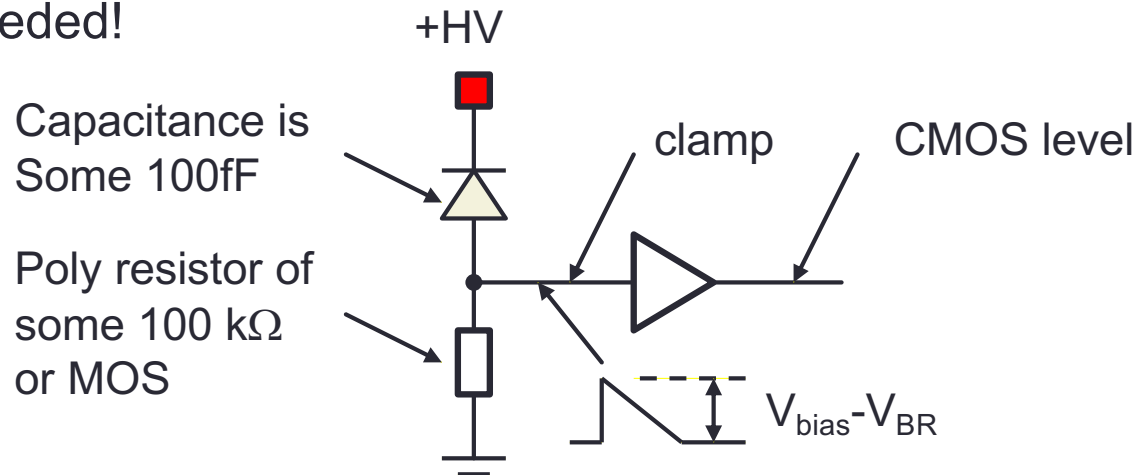- SPADs are reverse biased with positive voltage of $\sim +30\text{V}$
When $V_{\text{bias}} > V_{\text{BR}}$ = 'Break down voltage', photons can trigger an avalanche so that voltage drops back down to V_{BR} .
 - Note: Bond Pad for V_{bias} may **not** have any input protection diodes!!!
 - Note: In order not to destroy following CMOS components, a clamp diode is needed!




- An 'amplifier' is used to produce a CMOS level:
 - No static consumption
 - Low input threshold
 - Fast for rising signal at input

Readout

- We provide the chip with a short GATE signal 
- All *rising edges during* that GATE shall be counted
- We best set flipflops with the rising edge signals (in each of the 9 x 9 channels)
- We then 'count' the number of set flipflops by adding them up.
- Operation should be pipelined, i.e. we can send the next GATE while we add up the previous pattern.
- Chip output is a binary (7 bit) number which occurs with some latency after each GATE

Adder

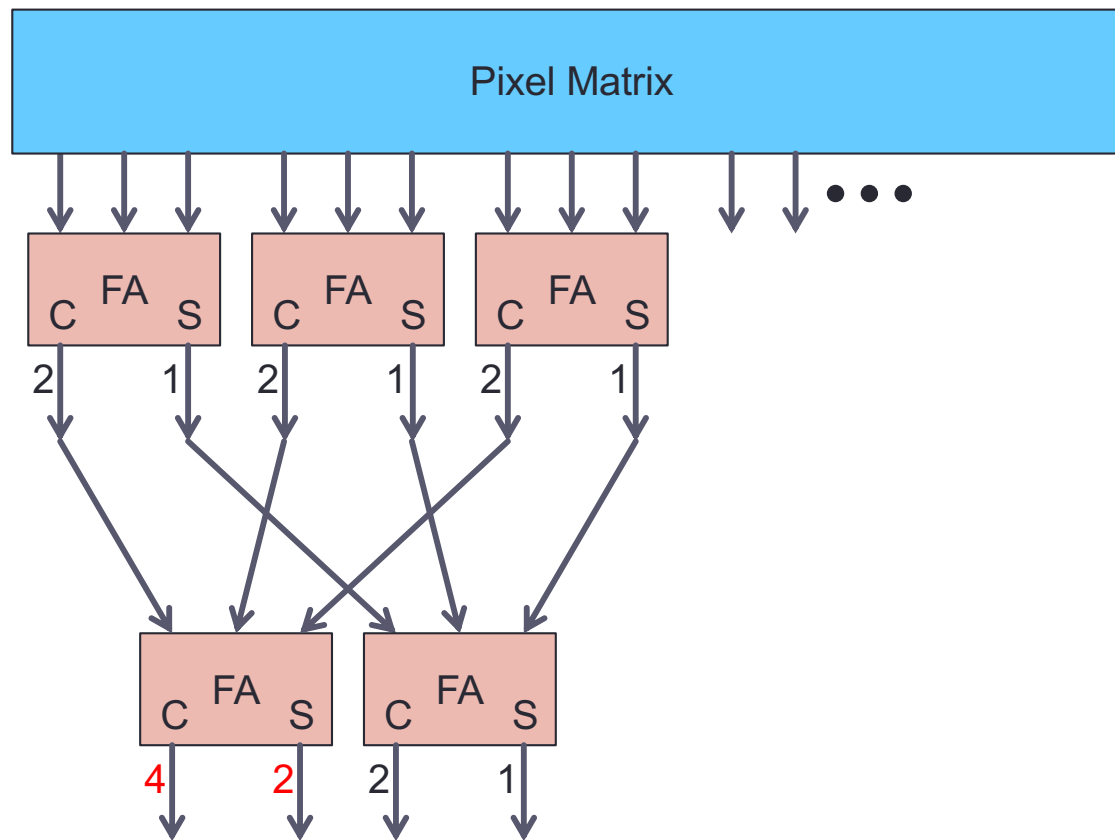- One solution: Add up bits using a tree of full adders



Further Blocks

- We have a PCELL for the SPADs
 - Gap between active areas is $\sim 7\mu\text{m}$
- We can use digital cells from the IMS library, or design our own!
- I suggest to have no buffers in the input cells, so that we do not have to bother about drive strength (but maybe about RC effects!)
- We need a fast output pad to drive the count in a load of, say, 5 pF, in, say, 10 ns.
 - Make sure that pad has no short circuit current in the push-pull driver
 - May use a lower high level to gain speed.

Initial work program

- Think about input circuitry per pixel
- Get acquainted to full adder
- Try out a small adder tree, get a feeling for speed.
 - Use realistic fan-out / fan-in and an estimate for wiring caps.
- Make an overall chip hierarchy
- Count pads