



Graded Exercise VLSI Design WS 22/23:

SAR ADC


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Successive Approximation ADC

- An Analogue – Digital – Converter (ADC) converts an analogue value (here a voltage) into a digital (here binary) code.
- An N bit ADC using the ‘successive approximation’ principle consists of
 - an **N bit DAC** (Digital – Analogue Converter) providing 2^N (voltage) values from (in our case) 0 V to FSR (Full Scale Range)
 - an **analogue comparator**, comparing the ADC input to the DAC output
 - a (clocked, digital) **control logic** which observes the comparator output and generates the DAC input word and the result

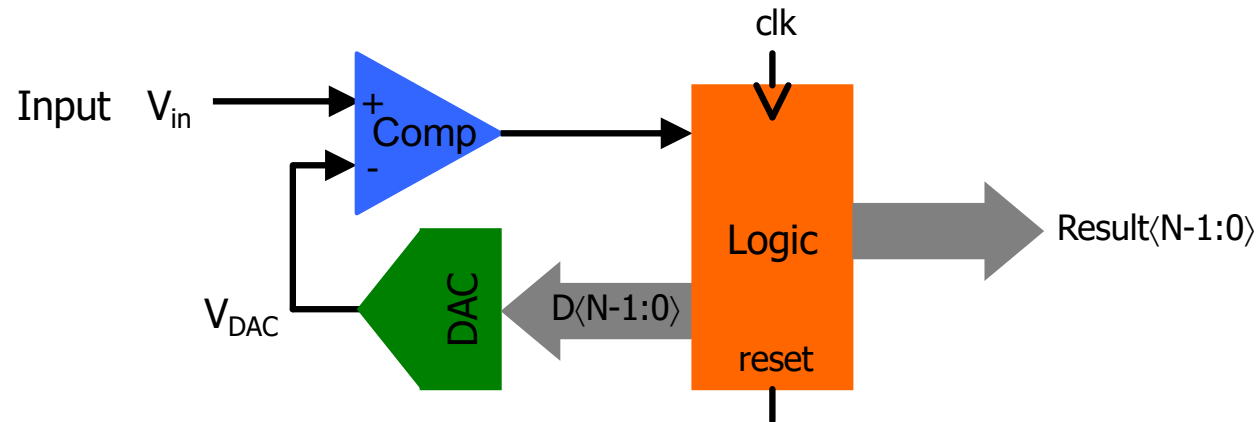




Operation

- The SAR ADC operates in conversion cycles of N clocks
 - We assume that the input voltage V_{in} is constant during the cycle (in practice, a Sample-and-Hold may be required at the input to ‘freeze’ a changing value)
- At the start of a cycle, the logic sets the DAC to $\frac{1}{2}$ FSR
 - The comparator then finds out whether the input V_{in} is larger or smaller than $\frac{1}{2}$ FSR
- At the next clock edge, the logic inspects the comparator output. This is the most significant bit (MSB) of the result.
 - If $V_{in} < \text{FSR}/2$, the logic sets the DAC to $\frac{1}{4}$ FSR
 - If $V_{in} \geq \text{FSR}/2$, the logic sets the DAC to $\frac{3}{4}$ FSR
- At the next clock edge, the next bit is extracted, and the DAC interval is again reduced by half, etc.
- With each clock, the difference between V_{in} and V_{DAC} is reduced to half and one more output bit is generated



The Comparator

 - We use a very simple comparator with
 - a (PMOS) differential pair
 - followed by a (NMOS) gain stage







The Comparator

- The comparator is biased with a ‘not too short’ PMOS current source NP1 ($L \sim 1\mu\text{m}$).
 - Generate the bias voltage p_{bias} by a current mirror!
 - Use a current of – for instance – $10\mu\text{A}$.
 - For the sake of simplicity, generate the input current to the mirror with a resistor to ground.
- The second stage must be biased with *half the current* of the first stage so that its threshold is set to the condition $V_+ = V_-$. Try to understand why!
 - This is achieved by using two PMOS for NP1, one for NP2
- This comparator can handle voltages at its inputs from (just) ground up to some positive voltage, but not up to VDD.
 - Why does it help to connect the bulks of the pair to VDD?
- We will therefore restrict the voltage range FSR of our ADC (and thus of the DAC) to this maximal value



The DAC

- We use a voltage divider made out of many equal resistors R_A with 2^N taps to generate all possible voltages.
 - Because $FSR < VDD$, we have an additional resistor R_B
- We then use analogue switches to implement a $2^N \rightarrow 1$ MUX which selects one of the voltages, depending on the DAC input code.
 - The MUX may be implemented as a binary tree (a), or using one switch and a decoder per resistor (b)

  



THE GRADED EXERCISE



Task and Criteria for Grading

- In this exercise you should
 - Understand the SAR principle
 - Produce a well structured schematic hierarchy of the design
 - Provide analogue simulations of Comparator and DAC
 - Write a simple Verilog module for the control logic
 - Make a mixed mode simulation which shows correct conversion of a low, a medium and a high input voltage
 - Make 'nice', DRC and LVS error free layouts of Comparator and DAC

- These points should be documented in a short write-up with
 - a text describing your design decisions
 - text and screenshots of the simulation results, answering at least the question raised in the following
 - screenshots and explanations of your schematics layouts

- Use $N = 5$ or 6 Bit



Exercise 1: Understanding the SAR principle

- Write down the DAC output codes for the conversion sequences of some input voltages.
- Define an algorithm to generate the new DAC control word in the i -th step of the conversion.
- You may want to write a small program to check that your algorithm works



Exercise 2: Simulating the Comparator

- Show that the comparator works:
 - Set one input to a fixed voltage V_1 and sweep (DC or transient) the other input from a bit below V_1 to a bit above V_1 .
- Find out and understand for which voltage range of V_1 the comparator works (at decent speed)
 - Try to extend the range as much as you can be sizing the transistors.
 - Make sure $V_1 = \text{GND}$ is ok!
 - This fixes the FSR
- Check the speed:
 - The ‘precision’ of the comparator must only be $\sim \text{FSR} / 2^N$.
 - We can therefore define a figure of merit for ‘speed’ as the reaction time for a step input of this size around the threshold.
 - Does speed increase for higher bias current?
 - This speed sets your maximum clocking frequency!!!



Exercise 2 cont.: Simulating the Comparator

- Input offset and common mode effects:
 - Does the comparator really switch *exactly* at $V_- = V_+$?
 - Understand what happens!
 - Does this 'input offset' depend on the absolute input voltage level (The 'common mode input voltage') ?

- For our application, the input offset should be smaller than the LSB of our DAC...
 - What is the general effect of input offset on the transfer characteristic of the ADC ?



Exercise 3: Simulating the DAC

- Chose the resistors such that the current in the DAC is not too high (compared to what?)
- Find arguments for the type of decoder to use and implement the schematic
 - What type of MOS can be used for the switches? Or should you better use transmission gates?
- Simulate (best with a mixed mode simulation) that the decoder works as expected
- How long does it take to stabilize the output voltage for a large voltage step?
 - How does this depend on a load capacitance?
 - Which factors / components limit the speed? How?
 - Is the speed sufficient (compared to the comparator speed) when the capacitive load by the comparator is connected ?



Exercise 4: The full ADC

- Write a Verilog module for the SAR algorithm and simulate the full ADC
 - Make sure in your simulation that the input voltage is stable during one conversion

- Simulate several input voltages in one simulation
 - You may stimulate the input with a piecewise linear voltage source pwl, or superimpose voltages of several vpulse sources

- You may check that the ADC does *not* work any more if you run it too fast.
 - You could add an extra capacitance to the DAC output to artificially slow it down.



Exercise 5: Layout

- Make the layout of the DAC (with switches) such that
 - The resistance value can be changed easily without the need to re-do large parts
 - The number of bits can be changed easily later
- The layout of the DAC should
 - be reasonably compact
 - Not have an extreme aspect ratio, i.e. should be roughly square