



SPADIC v0.3 and v1.0


Self-triggered Pulse Amplification and Digitization asIC



Tim Armbruster tim.armbruster@ziti.uni-heidelberg.de FEE/DAQ Meeting @ FIAS (Frankfurt) November 2010

1. Latest Chip Architecture (v0.3)

Block Diagram of Current ASIC

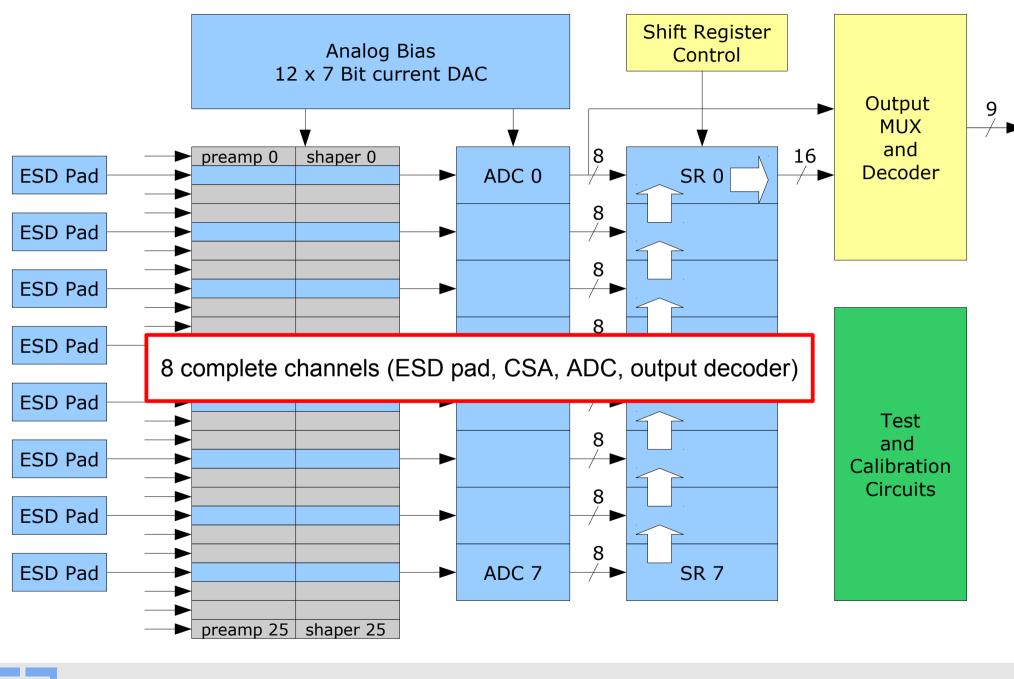


Nov. 2010 F

.0 FEE/DAQ Meeting - Tim Armbruster

LS Schaltungstechnik & Simulation

Reminder: Preamplifier/Shaper Circuit

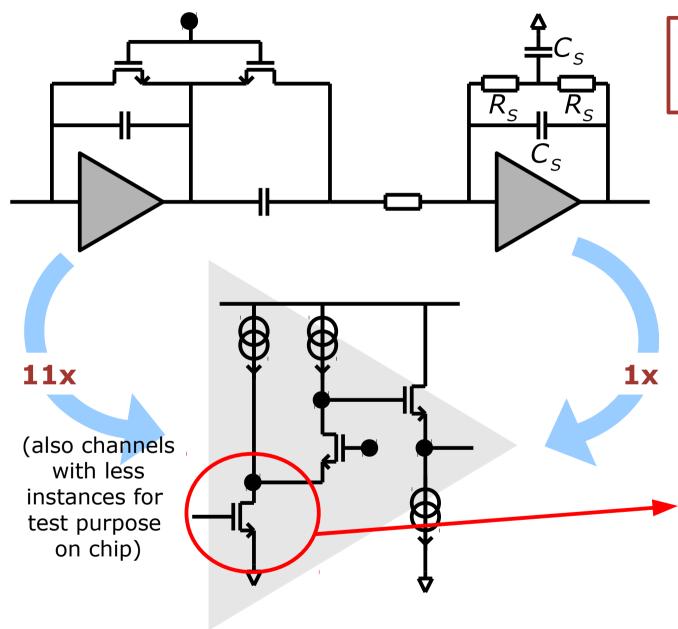

$$H(s) \approx \frac{A_{DC}}{\left(1 + sR_{S}C_{S}\right)^{2}}$$

- O'Connor FB
- 2nd order shaper
- Shaping time: 82 ns
- Unified amplifier cell
- N-MOS input
- ≈ 3.6 mW/channel


New:

- Scaled lengths of input NMOS (180, 250, 320, 390, 460nm)
- Re-Layout of input NMOS: The (long) gate-fingers have been cut into smaller pieces to decrease gate resistance

4


Reminder: Algorithmic ADC Design

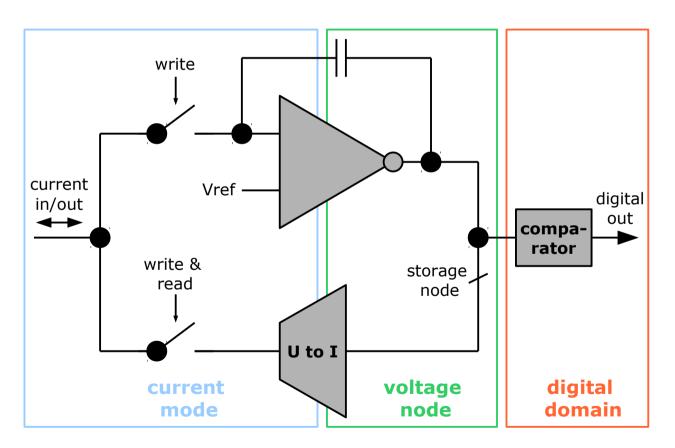- 8 (scaled) pipeline stages, therefore 9 Bit design, 7.5 Bits effective so far
- Algorithmic working principle ("1.5 redundant Bits" / conversion step)
- 25 MSamples/s, layout only 130x120 μm², power consumption 4.5 mW
- Core unit: Novel current storage cell:






Current Test-Chip: Layout

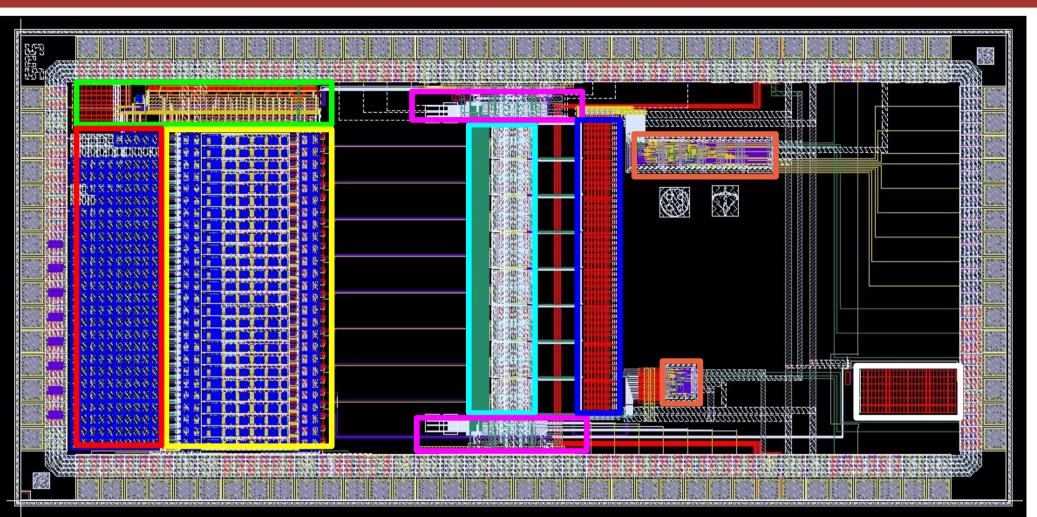

Bias circuitry (12 current DACs) 26 preamp/shaper channels Detector capacitors (5pF per block) 8 pipelined ADCs ADC control + bias 5.2 kBit shift register matrix Control + readout/decoder logic blocks Test circuits




Typical Analog Shaper Pulse

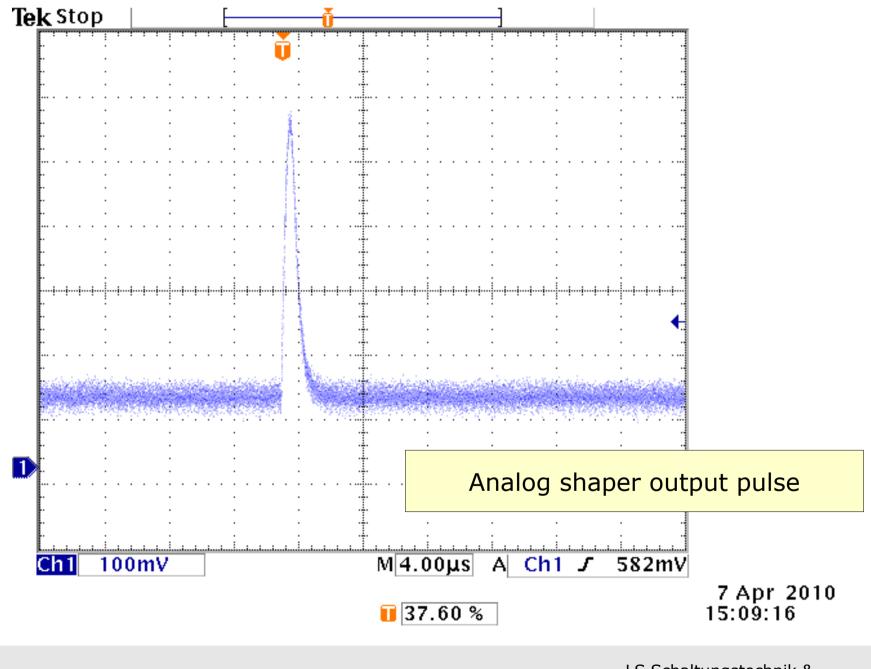


Nov. 2010 FEE/DAQ Meeting - Tim Armbruster

LS Schaltungstechnik & Simulation

Preamp/Shaper Noise

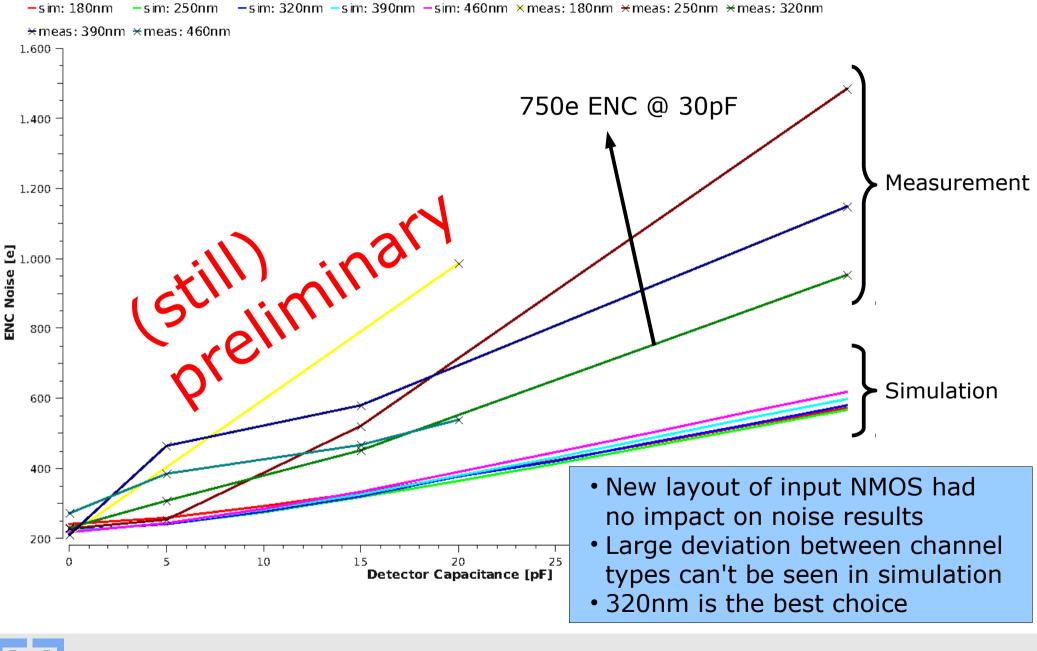


Characteristic ADC Curve

 

ADC's DNL and INL

– DNL Differential Non-Linearity

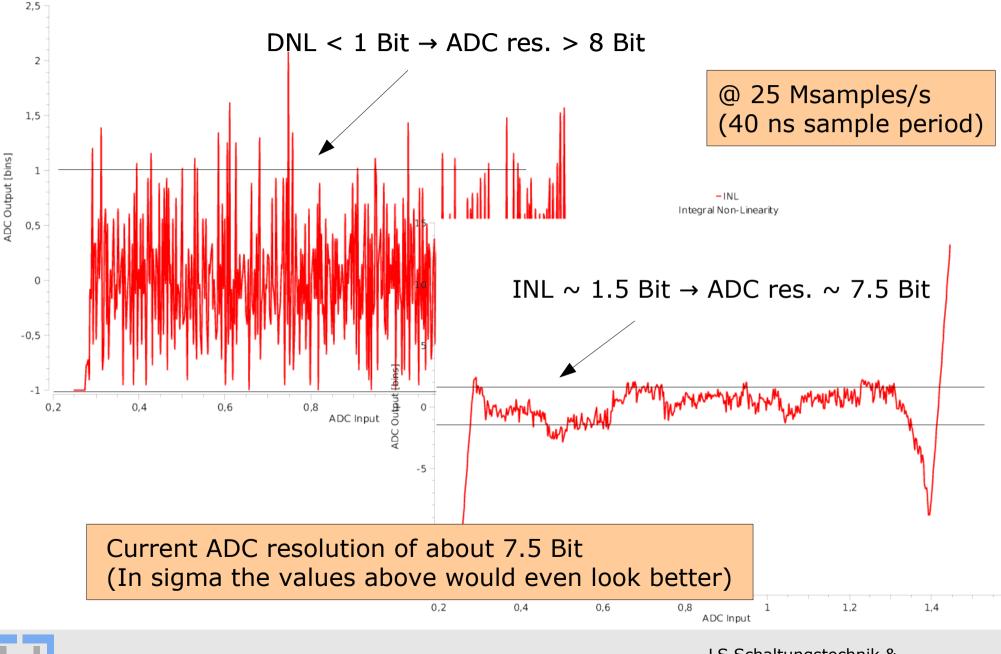


Nov. 2010 FEE/DAQ Meeting - Tim Armbruster

LS Schaltungstechnik & Simulation 1,6

First (yet noisy) digitized pulses

-Fit - hit - Fit - hit -

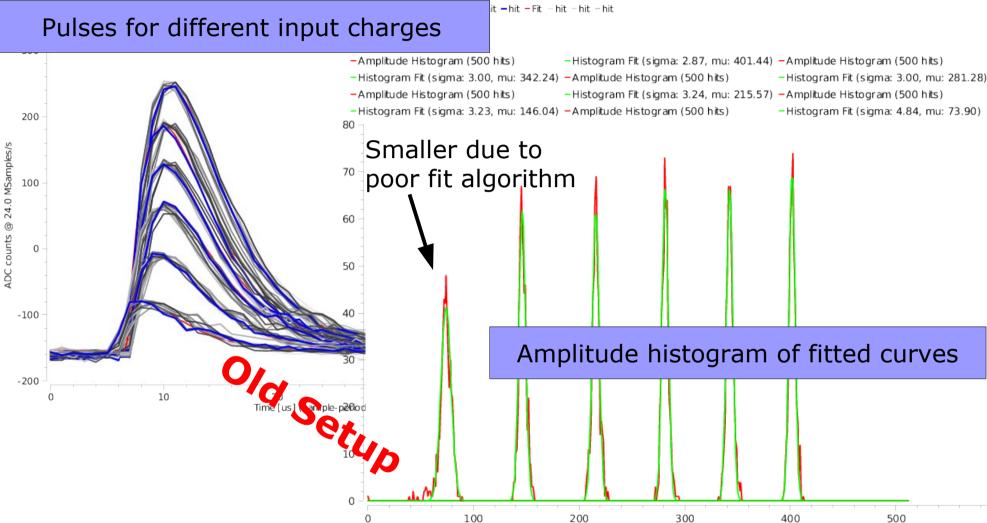


Pulses with new setup look even much smoother (see next slides), but no measurement available yet :-(




600

11

(Old) Pre-Testbeam Setup

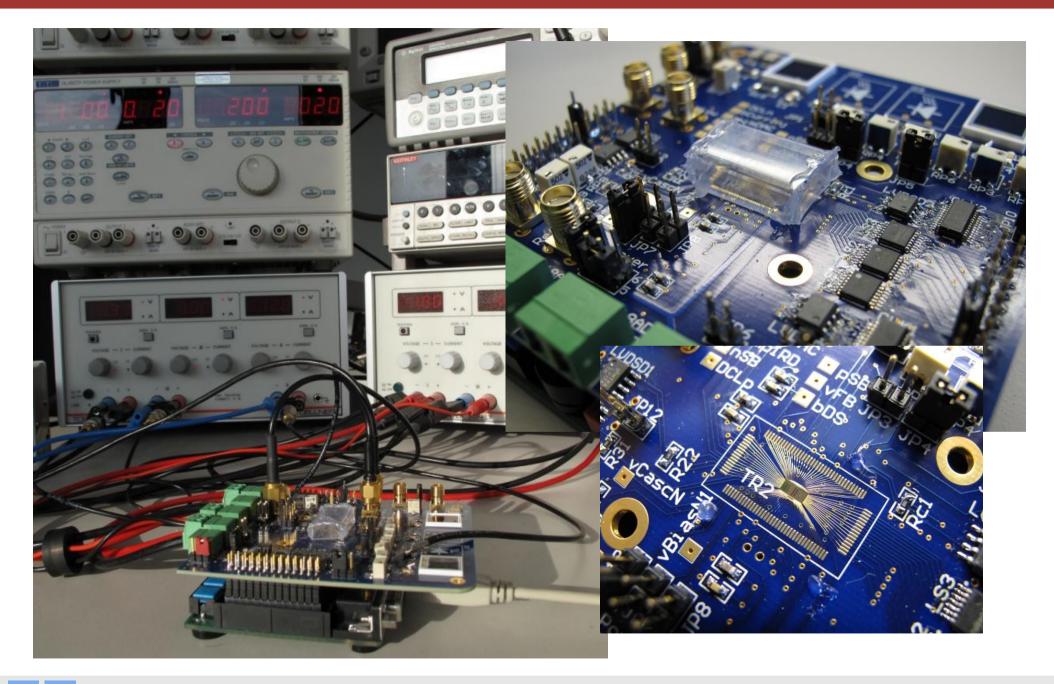

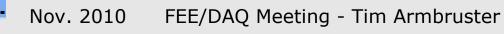


2. Testbeam Setup

Testbeam Setup Overview

- "Old" chip (Spadic v0.3) but ...
 - New front-end PCB
 - Low-noise layout, several smaller improvements
 - Harwin ZIF connector compatible (same connector type as in ALICE TRD)
 - New FPGA readout controller (Susibo)
 - Virtex 5, 2MB SRAM, FTDI (USB 2.0), EEPROM(s), ...
 - New firmware
 - High readout rate of up to 8k events/s (368 Byte/event)
 - Package based protocol
 - New Features like local time-stamp, external event-id extraction (sync-t), ...
 - New Software-Library
 - Provides abstract functions like (dis-)connect(), readNextPackage(), status(), ...
 - Necessary for integration in DABC framework
 - New stand-alone readout client (hitclient)
- Beamtime target: 8 completely running Setups (8 channels each)
 - Last-minute point landing, also the Susibo was "just in time"
 - A lot of problems with assembly and bonding

=> Finally 8 setups worked (most of the beam-time only 6 were run in parallel)


SPADIC plugged on Susibo

 




Nov. 2010 FEE/DAQ Meeting - Tim Armbruster

Setup in Lab

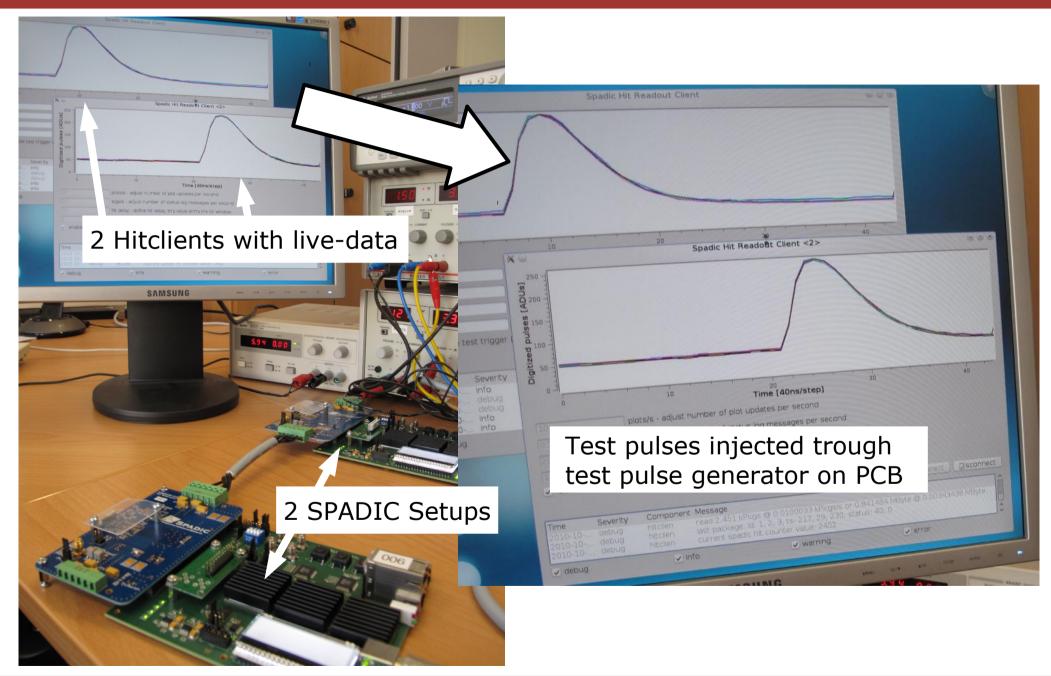

Hitclient Screenshot

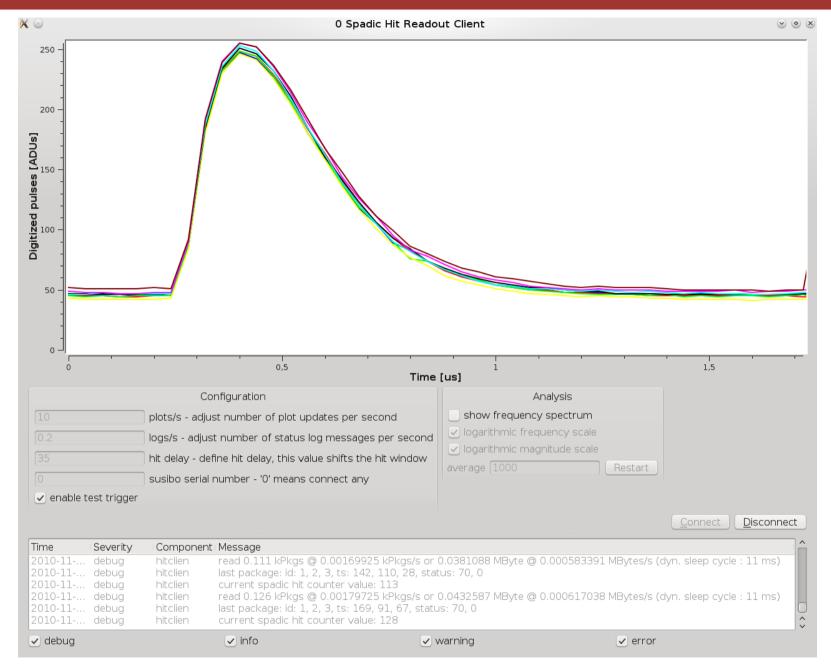





Sorry, problem with my digi-cam :-(



Münster's TRD-SPADIC Setup

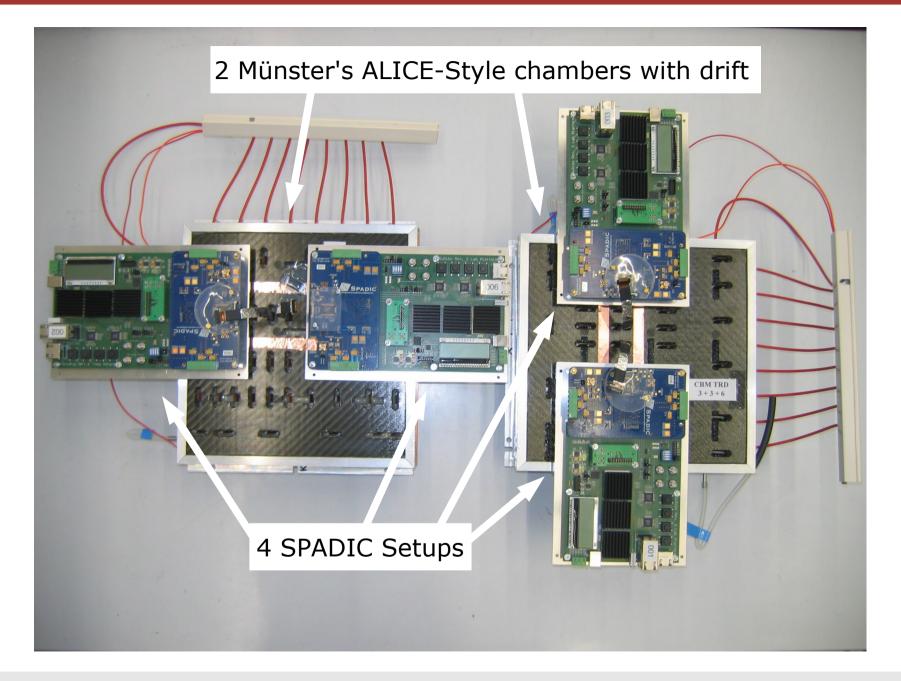

 

Sorry, problem with my digi-cam :-(




3. First Testbeam Results

- Bad :-(
 - Many problems with pickup (external noise) a lot of effort was necessary to reduce the different kinds of oscillation to a tolerable minimum

- Even after "optimization" some boards still showed strong oscillations


- (Due to known reasons) the chip's configuration was very unstable a lot of reconfigurations/restarts were necessary
- Strange baseline-shift (DC-level) of shaper outputs if detectors were connected AND the ADCs were running (yet there was no time to investigate this)
- Good :-)
 - 8 Spadic/Susibo setups finished just in time
 - Successful integration of Spadic software library into DABC (thanks to Sergey and Jörn)
 - External triggering-scheme worked well
 - Finally 6 working Spadic setups in parallel (4 x Münster, 2x Frankfurt)
 - A lot of nice hits could be recorded (but also some ugly)

Go4 Spadic online event

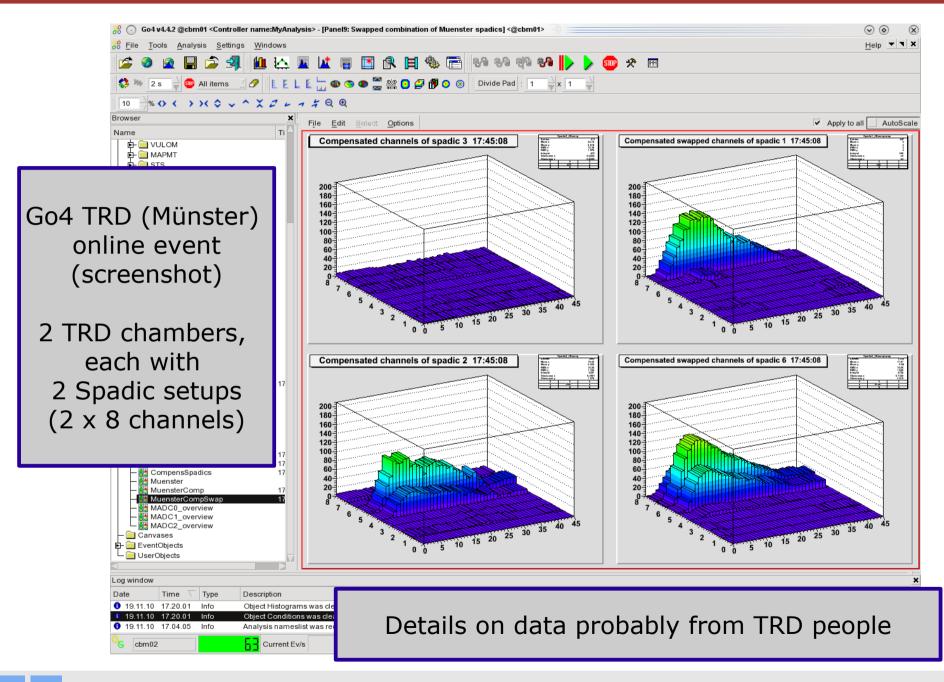

4. Towards SPADIC v1.0

Status of Development

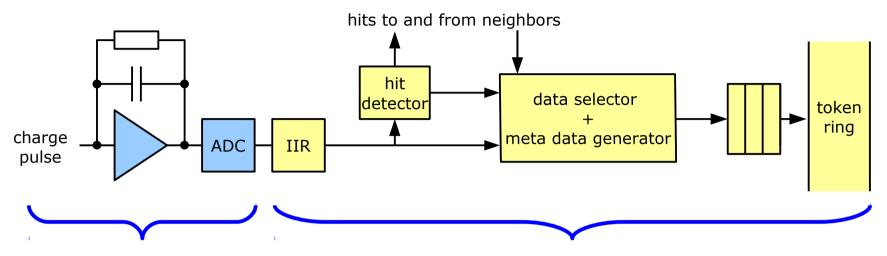


Analog Parts: Preamp, Shaper and ADC

- Several test-ASICs successfully designed and tested
- Working 8 channel readout setup (for testbeam as well as for chamber tests)
- Overall design concept mostly settled down
- A lot of parameters must be fixed soon

Digital Parts: IIR filter, hit detector, feature extraction (?), package generator, neighbor logic, token ring, interface protocol (Frank Lemke), ...


- First design proposal of data flow and control concept finished
- 1st Verilog iteration of most blocks available and simulated
- Michael Krieger, diploma student, working on IIR filter (ion-tail cancellation, ...)
- But: Still a lot of work to do ...

Conceptual Data Flow Diagram

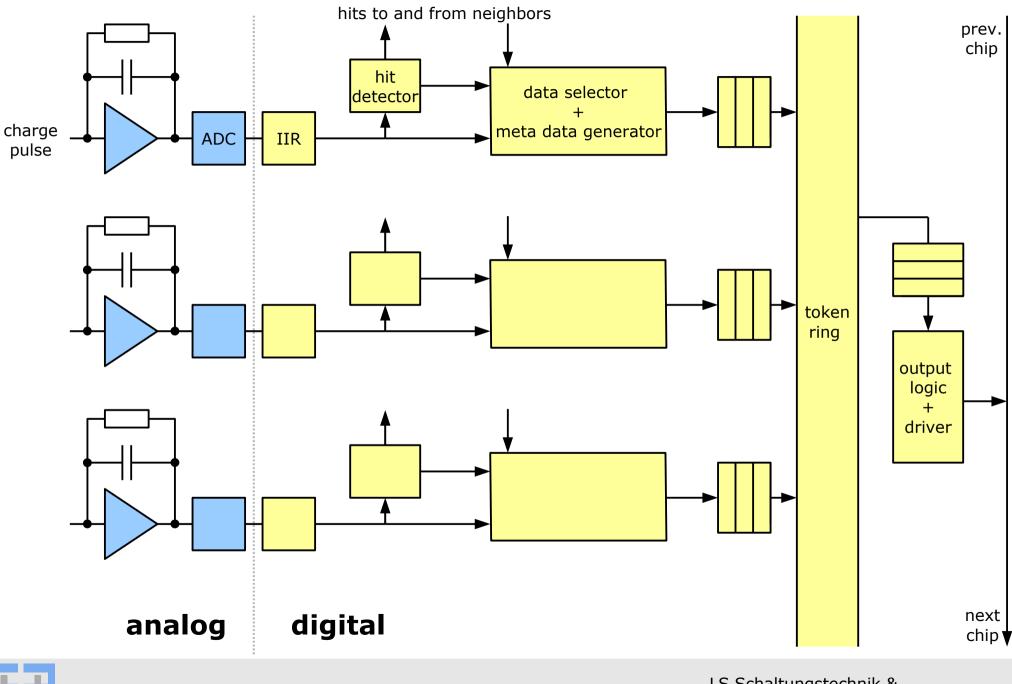

Nov. 2010 FEE/DAQ Meeting - Tim Armbruster


Spadic 1.0: Preamplifier / Shaper

 

- Charge sensitive preamplifier (CSA)
 - Single ended, N-MOS input
 - Input protection
 - Switchable polarity
 - Switchable # amplifier cells
- Shaper
 - 2nd order, PZ-cancellation, 82 ns
 - Switchable shaping-time
 - Increased order
- Both
 - 750e ENC @ 30 pF, 3.8 mW
 - Switchable gain




Spadic 1.0: ADC

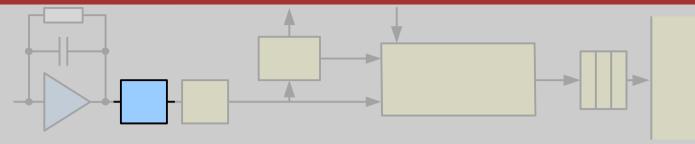

- Pipeline ADC, continuously running
 - Current-mode algorithmic ADC
 - 9 Bit design, 7.5 Bit effective
 - Up to 25 Msamples/s
 - 4.5 mW / rad-tolerant
 - Slightly better resolution (~ 8 Bit)
 - High resolution (> 8 Bit), possible but very expensive in terms of man-power, power consumption, chip area, ...
 - Improved DC-Level / baseline adjustment mechanism

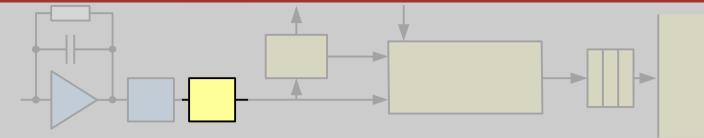
Spadic 1.0: Infinite Impulse Response Filter (IIR)



- IIR Filter / data pre-processing
 - Michael Krieger's diploma thesis
 - Simulation framework developed
 - 10-14 Bit multiplier + adder
 - Ion-tail cancellation
 - Baseline correction
 - Higher order shaping
 - (Simple) additional ideas ???




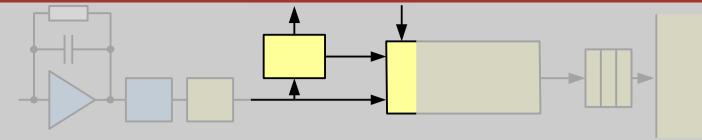Spadic 1.0: Hit Detector and Neighbor Trigger




- Digital hit detector
 - Digital hit extraction logic
 - Different hit extraction schemes (threshold, double threshold, pulse length, ...)
 - 1th order Verilog, simulation works
- Neighbor readout logic
 - Automatic readout of neighbor channels
 - Trigger signal across chip edges
 - 1th order Verilog, simulation works

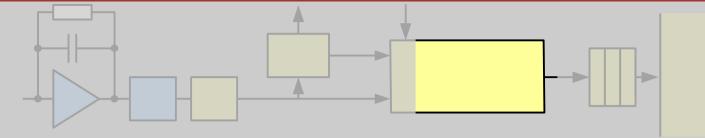Spadic 1.0: Meta Data Generator and Package Builder



- Meta Data Generator
 - Local and external time-stamp extraction
 - Hit type extraction (internal, neighbor, ...)
 - Channel #, Chip ID, ...
 - 1th order Verilog, simulation works
- Package builder
 - Generation of hit package including meta and hit data
 - 1th order Verilog, simulation works


Spadic 1.0: Output Interface

 

- Output Interface
 - FIFO package buffer
 - Need access to some UMC 018 SRAM generator
 - Token ring inter-channel network
 - Sophisticated deterministic latency output protocol (Frank Lemke)
 - CBM DAQ compatible !!!
 - Serializer
 - Output driver



Digital Hit Detector and Package Builder

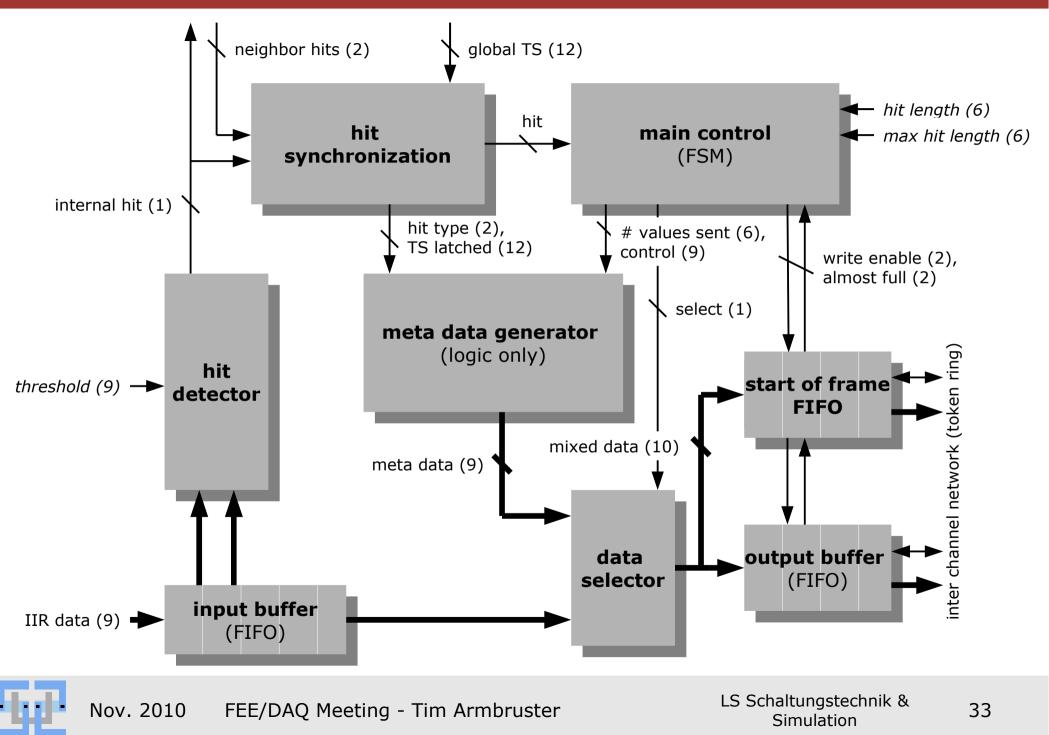

Chip Concept




Planned feature Possible feature

- Features on chip-level
 - 32 channels / chip (maybe 64)
 - Several test mechanisms (test injection, analog signal access, ...)
 - On-chip bias circuitry (current DACs + diodes)
 - A lot of global and local configuration registers
 - Maskable channels
 - Power consumption / channel: analog ~ 10mW, digital ??? \rightarrow power limit?
 - Data: LVDS inputs / outputs only
 - Additional channel as global reference to eliminate systematic disturbances (e.g. pick-up)



If Spadic also goes for RICH people ...

 

- Necessary adjustments of Spadic 1.0 concept for RICH (Ring Imaging Cherenkov)
 - Much smaller input gain (max. 1.6 pC / hit) → switchable preamp/shaper gain
 - − Negative input charge \rightarrow bidirectional input stage
 - − Very good time resolution ~ 2ns → sophisticated feature extraction on-chip or offline
 - Is this time resolution achievable (40 ns sampling period)?
 - Energy feature extraction \rightarrow on-chip (preferred) or offline (?)
 - Opt: more than 32 channels (>= 64)
- List not too long, but I'm already busy → additional man-power on the horizon?


Some estimated numbers:

- 32 channels / chip
- 250 kHz maximum event rate / channel (one hit every 4 µs)
- 8 Bit ADC resolution
- 10 samples / event <= we need to further investigate here
- 12 Bit time-stamp / event (epoch length 164 µs @ 25MSamples/s ADC speed)
- 5 Bit channel ID

$$R_{chip} = \underbrace{\frac{250 \, k \, events}{channel \cdot s}}_{hit \, rate chip} \cdot \underbrace{32 \, channels}_{hit \, rate chip} \cdot \underbrace{\frac{8 \, bit}{sample}}_{hit \, data} \cdot \underbrace{\frac{10 \, samples}{event}}_{hit \, data} + \underbrace{\frac{17 \, bit}{event}}_{time-stamp+ID} = \frac{776 \, Mbit}{s}$$

- => Conservative estimation: <u>about 12 Bytes / (hit + channel)!</u>
- => Planned output protocol from computer architecture group (Ulrich Brüning and Frank Lemke) foresees two links per chip with 500 Mbit/s each
- Note: Epoch counter + forward error correction overhead <u>not considered here!</u>

Floor Plan Proposal

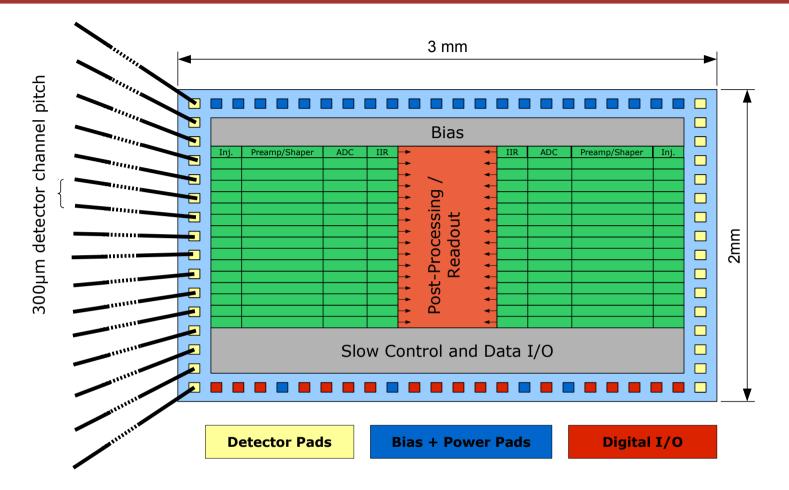

- 3 x 2 mm² estimated die size
- 32 channels, 80µm pitch, (mostly) symmetric layout for low(er) IR-drops
- Detector connection-pads on two sides (chips will probably be attached to back of detectormodule, this relaxes routing/spacing)

5. Future of the Test-Beam-Setup

Spadic User Community


- (Potential) users of the "Spadic Test-Beam" setup
 - **IKF, Frankfurt** currently making first steps (2 boards)
 - Uni Münster currently making first steps (2 boards)
 - **JINR Dubna** showed interest in using the setup for their chambers
 - RICH, GSI readout of the photomultipliers with Spadic just as a proof of principle and to get familiar with the setup (usage of course not as a working horse)
- Other planned "Spadic Test-Beam" setup activities
 - Readout of some strip diodes from Johann (GSI) as a proof of principle and to measure some spectra
 - GSI would like to gather bonding-experience with some Spadic chips
- => To a certain limit, I would like to improve the current setup and ...
 - ... add some additional features (e.g. include a sync-t trigger generator)
 - ... stabilize the readout
 - ... re-iterate the front-end PCB (remove some little bugs, optimize the detector connectivity, consider some external advice, add footprint for strip diode, ...)

But all this strongly depends on available man-power and willingness to cooperate!

 6. Next steps and timetable

Next Step: Iterate over Specification

- I've started a Spadic 1.0 specification file
- Everybody concerned should help interating it
- We need to fix all basic numbers before the chip development starts




- We still need to understand ...
 - ... the strange baseline shift ...
 - ... the high sensitivity to pick-up noise (PCB, chip or detector problem?) ...
- We probably should gather some more experience by ...
 - ... reading out some silicon strip detector ...
 - ... (maybe) reading out the RICH photodiodes ...
 - ... further improving the setup (see need to understand) ...

... **before** we finish the Spadic 1.0 development.



Timetable

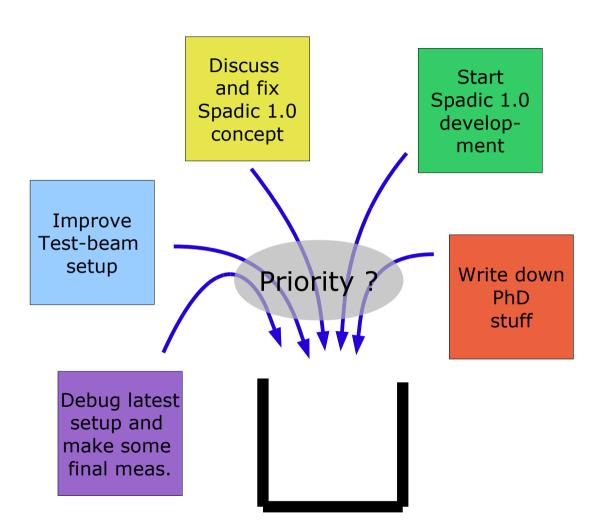

- A lot of different tasks
- I need to decide when to start writing down my PhD (plan was to start at beginning of 2011)
- A **very** optimistic estimation for the submission of Spadic 1.0 is middle of 2011
- A priority list, working packages and a timetable must soon be defined
- The focus should go as soon as possible to the Spadic 1.0 development!

5. Summary and Outlook

Summary and Outlook

Status of the latest setup:


- 8 working Spadic v0.3 / Susibo setups
- Successful integration in CBM test-beam environment
- Promising results in lab and from test-beam but also open problems
- A lot of interest in using the current setup from different groups

Status of Spadic 1.0 design concept

- Complete design concept available
- Analog part (except for some improvements) conceptually completed
- Most digital building blocks still in a very early design phase
- Many features still need to be discussed
- Design kick-off as early as possible in 2011

Next Steps:

 - Improve latest setup and gather more experience with chambers and silicon
- Discuss and fix specification
- Focus on Spadic 1.0 development



Self triggered Pulse Amplification and Digitization asIC

You want to use this logo? Feel free to do so! Get it at http://cbm.uni-hd.de/daq/more/spadic/logo/