



# Exercise: Simulating a Diode



Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg


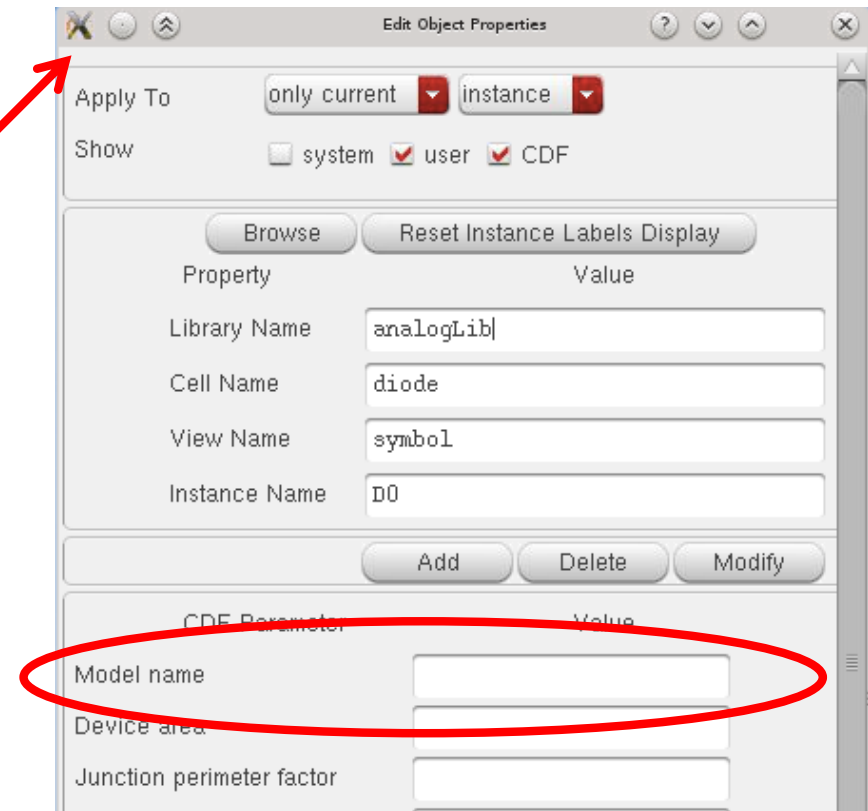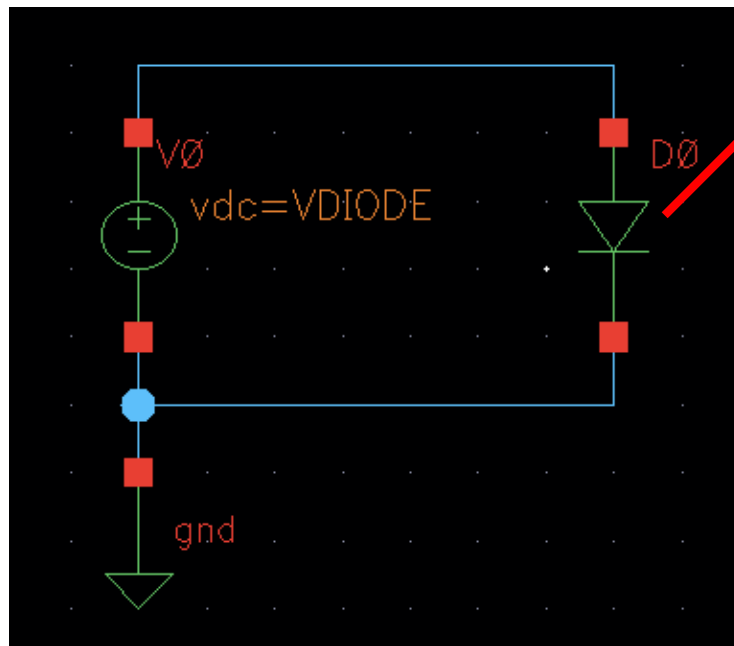
# 1. Defining a Model

- Create the following schematic.
  - The diode is taken from `analogLib`
  - Note that NO model is associated to this 'generic' diode






# Trying a DC simulation

- Simulate (DC!) the diode current for  $V_{DIODE} = 0 \dots 1V$ 
  - An error occurs:

'No model given'

```
Error found by spectre during hierarchy flattening.
ERROR (CMI-2119): D0: Instance (of type diode) requires the use of a model.
```

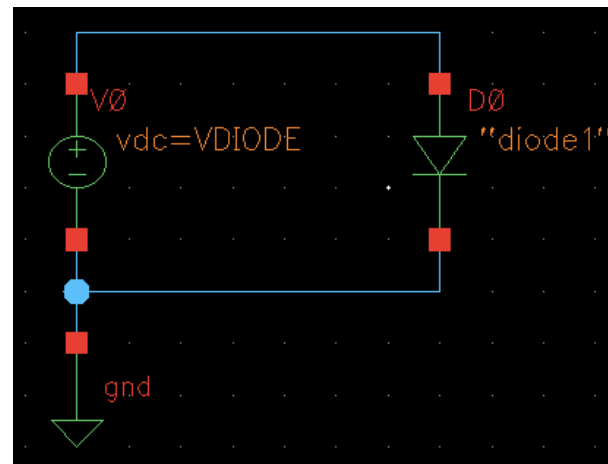- Now assign a model with name 'diode1' to the diode:



- Run the simulation again:


'model given, but not defined / found'

```
Error found by spectre during circuit read-in.
ERROR (SFE-23): "input.scs" 36: The instance `D0' is referencing an undefined model
```


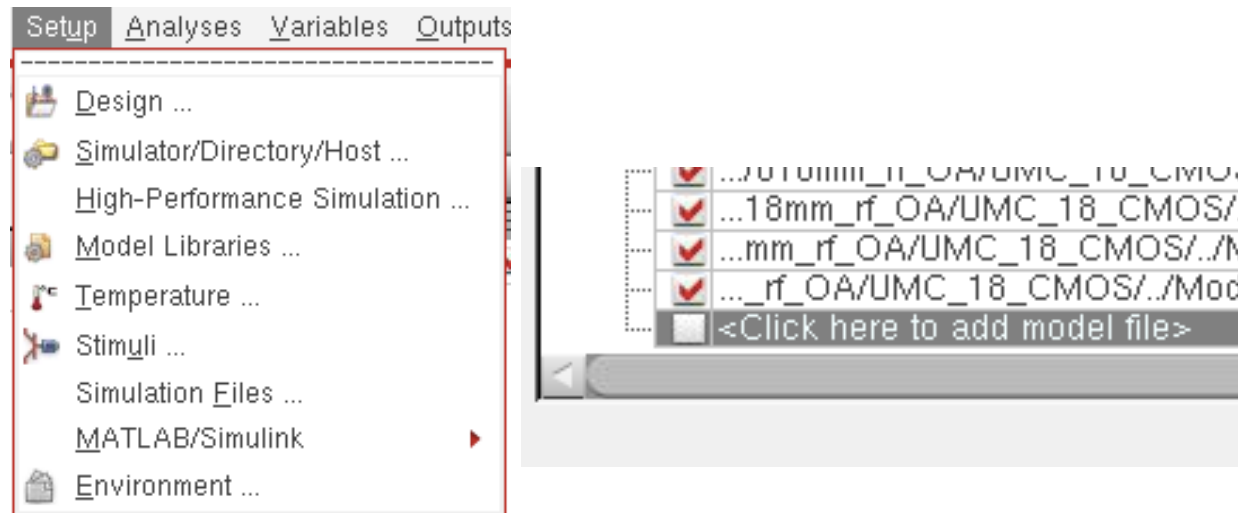
# Defining a Model

- Create a text file `MyDiode.lib` with the following model definition:
  - `.MODEL diode1 d IS=1e-08 RS=1 CJO=1e-11 VJ=0.7 M=0.5`
- The simulator needs to know about this file:
  - In `Setup->Model Libraries...`, add your file `MyDiode.lib`.



- Run the simulation again.
- Does the current increase exponentially? Try a log current scale! Sweep only to 0.4V! Why does  $I(U)$  become linear?




## 2. Different Models

- Instantiate a second diode with another model 'diode2'
- Add model 'diode2' to your `MyDiode.lib`. Change for instance `IS` to `2e-8`.
- Simulate and compare the two diode currents (best in log scale)
  
- **ATTENTION / NOTE:**
  - The simulator tries to be efficient and caches the models. If you just change `MyDiode.lib`, the change is not seen. There are (at least) 2 tricks to make sure the new model is used:
    - every time you change the model, use a *different model name* (and update the model name in the schematic)
    - Save `MyDiode.lib` under a *different file name* and include that new file in the model directory dialogue.


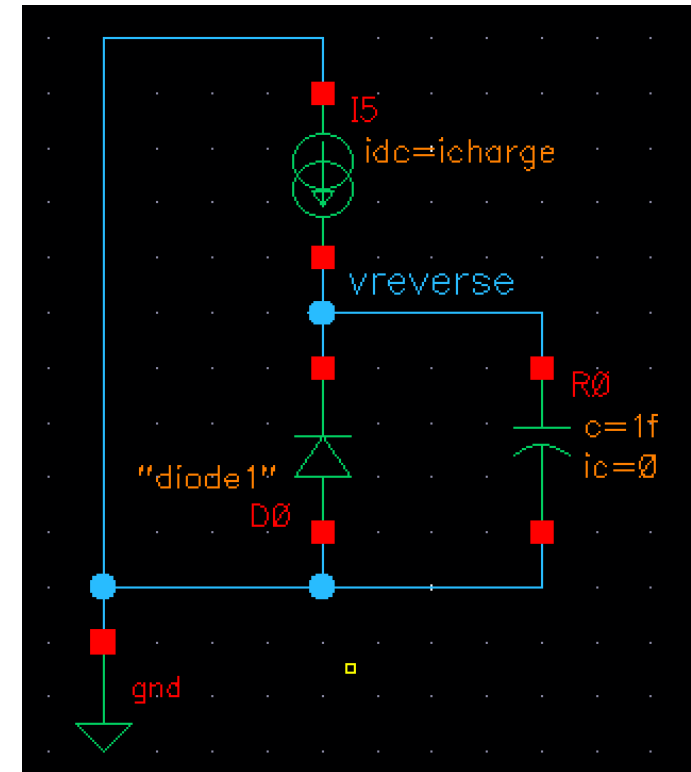
## 3. Capacitance


- To see the effect of the diode capacitance, you can charge it with a constant current *icharge*.
  - Make sure the polarity is such that the diode is in reverse bias
  - You can define the start voltage with a very small (1 fF) capacitor in parallel to the diode with an initial condition.
  
- Find a good value for *icharge* for your transient simulation
- Observe how the diode voltage increases with time. From the slope (calculator tool!), determine the capacitance
- Observe how the capacitance varies with voltage (time)
- Compare to what you expect from the model




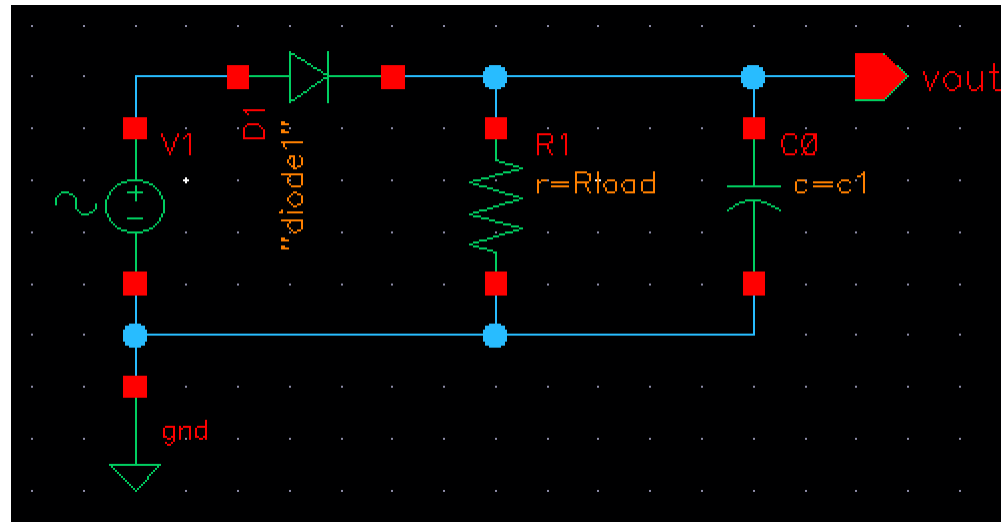
## 4: A Simple Rectifier

- Alternating voltages can be converted to 'dc' with a 'rectifier':






- Make a transient simulation (50 Hz, 10 V,  $R_{load}=1k\Omega$ ,  $C1=0$ )
  - Compare  $v_{in}$  and  $v_{out}$ . Observe the small difference in voltage. Where does it come from? How does that change with  $R_{load}$ ?
  - Now set  $c1$  to 1  $\mu F$ . Observe how  $v_{out}$  stays positive even in the negative phases of  $v_{in}$ . How does this work?
  - What are the effects of changing  $R_{load}$  and changing  $c1$ ?
  - Which  $C$  is needed to keep  $V_{out} > 8V$  for  $R_{load}=1k\Omega$ ? Calculate!



# 5: Full Wave Rectifier

- The full wave rectifier ('Graetz') uses 4 diodes to utilize the negative half-wave as well:

- make a Schematic

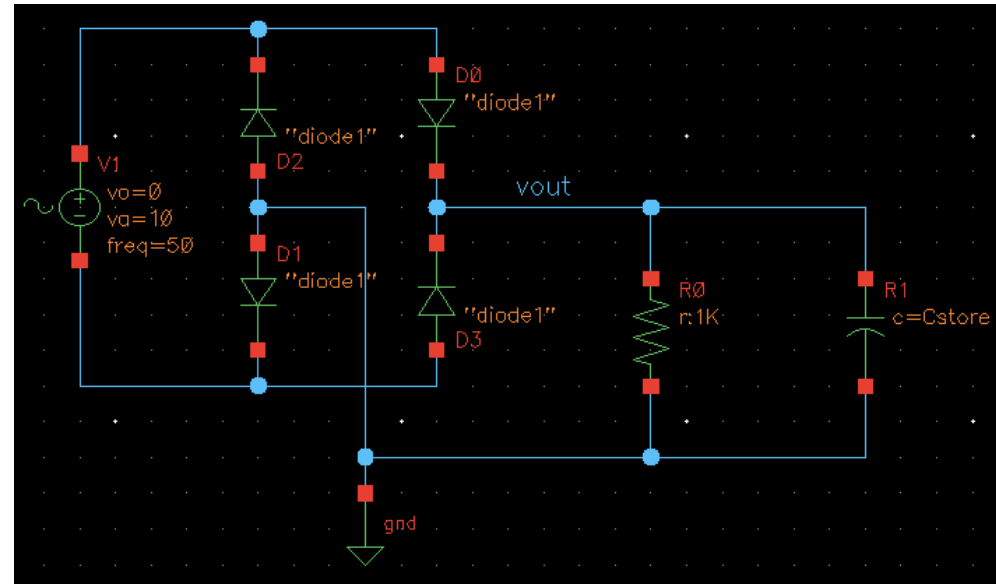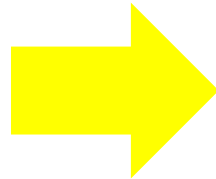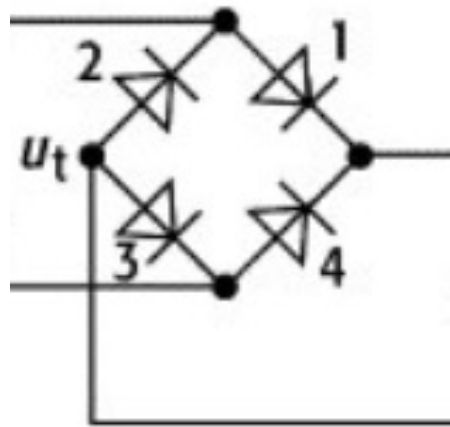


- How does  $V_{out}$  look like for  $C_{store} = 0$
- How does the circuit work?
- What is the peak amplitude? Why?
- What  $C_{load}$  do you need to guarantee  $V_{out} > 8V$ ? Calculate!




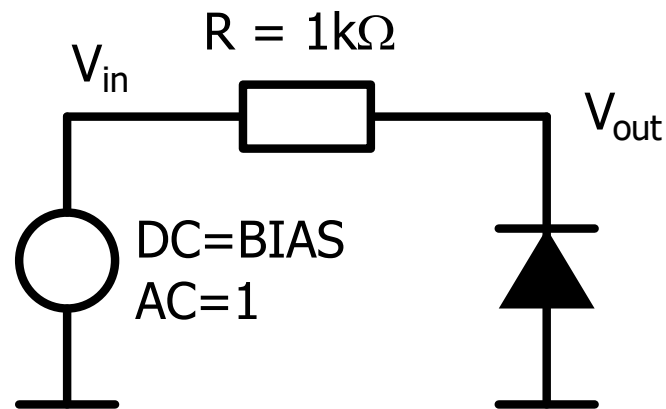
## Exercise 6: Operation Point

- A voltage dependent capacitance is part of the diode model.
- Implement the following circuit:



```
.MODEL diode1 d
+IS=1e-08 RS=0.05 N=1.5 EG=0.6
+XTI=0.05 BV=50 IBV=5e-08 CJO=1e-11
+VJ=0.7 M=0.5 FC=0.5 TT=1e-09
```

- Make an AC sweep from 1M to 1G or so for  $BIAS = 1V$ 
  - What is the corner frequency?
- Change  $BIAS$  to 10V or 0.5V
  - Does the corner frequency change?
  - Is it changing in the right 'direction'?