



# Exercise: Time Domain

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg




# Exercise 1

- A filter is made up of a
  - low-pass
  - an ideal unity gain buffer
  - a high-pass with same corner frequency as the low-pass
- What is the time response of this filter to a unit step ?
- Calculate and Simulate!


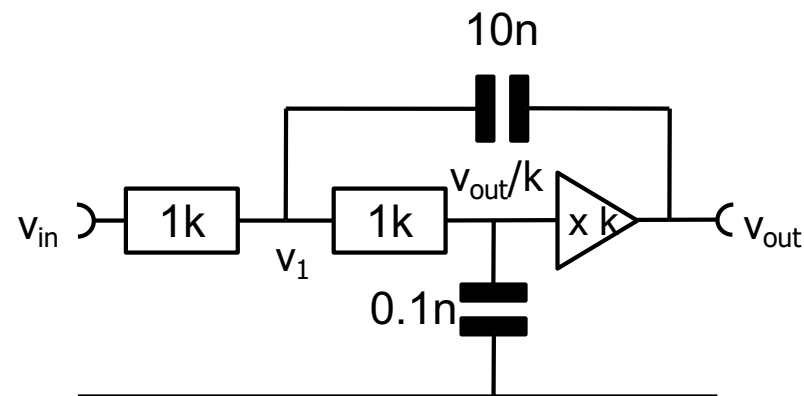
## Exercise 2

- Derive  $H[s]$  for the following active filter
  - The (ideal) voltage amplifier has gain  $k$



- For which  $k$  do you get a divergence ?
- What is the step response for  $k=1$  ?
- Simulate the circuit and compare quantitatively.