



Exercise: Current Mirrors


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



 Exercise: Dynamic Regulation


- Draw a diode connected NMOS
 - Use a 'simple' MOS model
 - Connect a large ,extra' capacitance (say, 1pF) to the gate with an *initial condition* of 0 V
 - Set the initial condition ('IC') in the properties of the capacitor
 - Send a small current I_{in} (e.g. 1 μ A) into the ,diode'
 - Perform a transient simulation
 - Estimate / calculate a reasonable max. time!
 - Observe the Input = Gate = Drain Voltage
-
- Use different initial conditions (0...1.8V, Parametric sweep!)
 - *Understand* how the equilibrium point is reached!
 - Why is settling much faster for a more positive start ?
 - Vary I_{in} . What changes? Why?





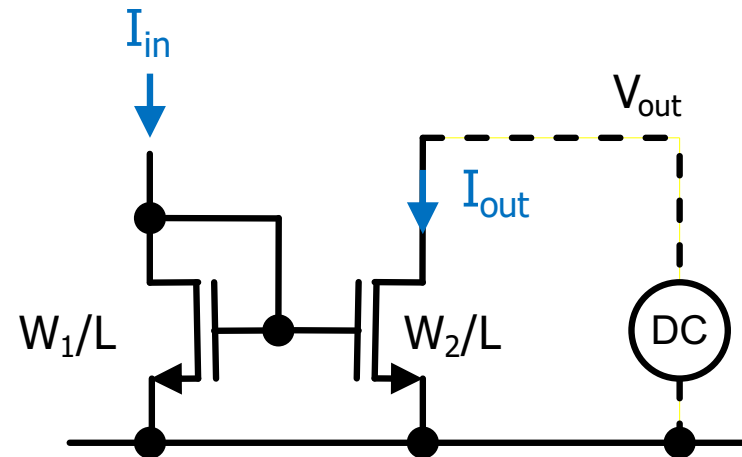Exercise: A First Mirror

- Draw the following *current mirror*, with $W_1 = W_2 = 1\mu\text{m}$.
Use for instance $L = 0.5\mu\text{m}$ and $I_{\text{in}} = 10\mu\text{A}$



- Sweep the output voltage V_{out} and observe the current I_{out} .
 - When is $I_{\text{out}} = I_{\text{in}}$ *exactly*? Why?
 - Try another input current, change W_2 !
- For fixed I_{in} , W_1, W_2 , vary L (same in both MOS). Explain
 - Explain what you see! Compare output slopes and saturation voltages. (See P.15 in lecture slides on mirror)
- Use the 'nmossimple' and the 'nmos' models and compare



Exercise: PMOS Mirror

- Draw a PMOS Mirror
- Simulate the output characteristics



Exercise: Triangle Generation


- Simulate the triangle generator from p.13 ('mirror' slides)
 - Use a supply voltage of 2V.
- Chose for instance a capacitor of 1pF and a current of 10μA
 - Start with a capacitor voltage of 0.5V (initial condition)
- For the switches, use can use the 'switch' element from analogLib.
 - You must set the 'close' voltage high than the 'open' voltage.
- Drive the two 'coils' with signals from two vpulse sources of suitable frequency. The two signals must be complementary.

- What slew rate (dU/dT) do you expect?



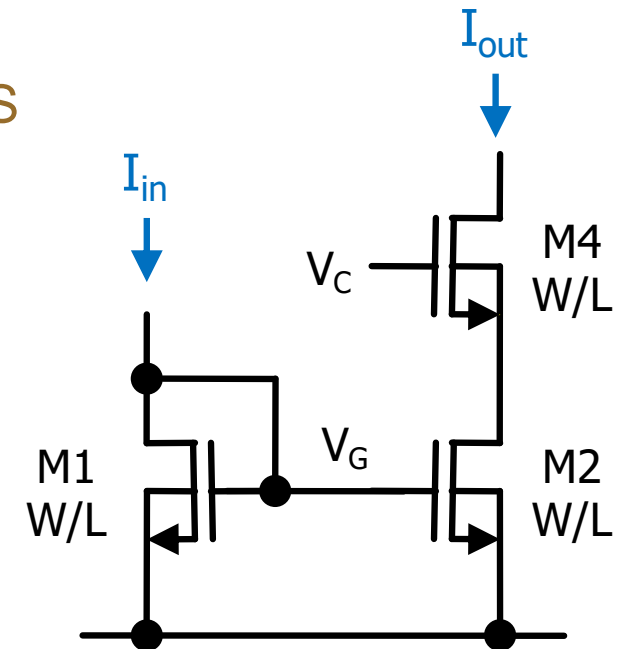Exercise: A Better Mirror

- The output current varies with V_{out} (i.e. the output resistance is not infinite) due to the Early Effect in M2.
- Try the following circuit:
 - Connect bulk and source in all MOS
 - Start with $V_C = 1.2V$
 - Use $I_{in} = 1\mu A$
- Sweep V_{out}
 - How is the output resistance now? (You may simulate the 'simple' mirror of the previous exercise in parallel for comparison)
- *Calculate* the small signal output resistance!
 - You only need to consider M2 and M4 (because V_G is constant)
- Vary V_C (from 0V to 1.8V) and see what happens
 - What is the 'ideal' V_C ?






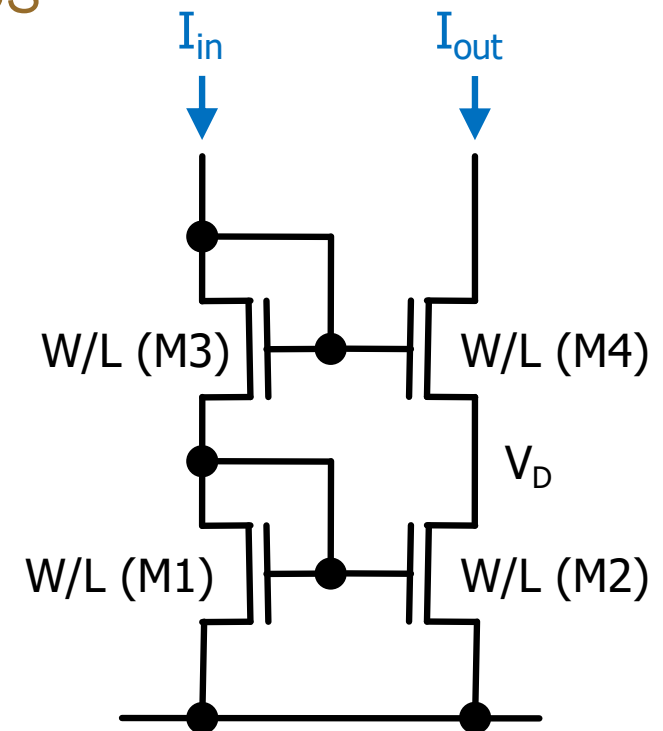Exercise: A Mirror with Better Matching

- Unfortunately, the previous circuit does NOT reproduce I_{in} exactly. Why?
- Try this circuit (which does not need V_C and more):
 - Connect bulk and source in each MOS
 - It is called the 'stacked mirror'

- Sweep V_{out}
 - Do currents match?
 - What is r_{out} ?
 - Where is the saturation ?




- What is the drain voltage V_D of M2? Is that optimal?



 Exercise: The Low Voltage Mirror


- In the stacked mirror of the previous exercise, the drain voltage V_D of the current source M2 is fixed by the diode connection of M1.
- This is simple, but provides a *too high* voltage (by $\sim V_T$!)
- The following circuit connects the diode differently:
 - Understand that the gate voltage V_G still stabilizes to the 'correct' level!
 - We now need to find V_C
 - Sweep V_C from 0.4 to 1.4V in steps of 0.2V
 - What is a good choice?
 - Why do very low voltages fail (check V_G !)
 - What happens at high voltages? Why? (this is tricky to understand... Look at V_{D1} ...)
 - Note that the 'best' V_C depends in I_{in}





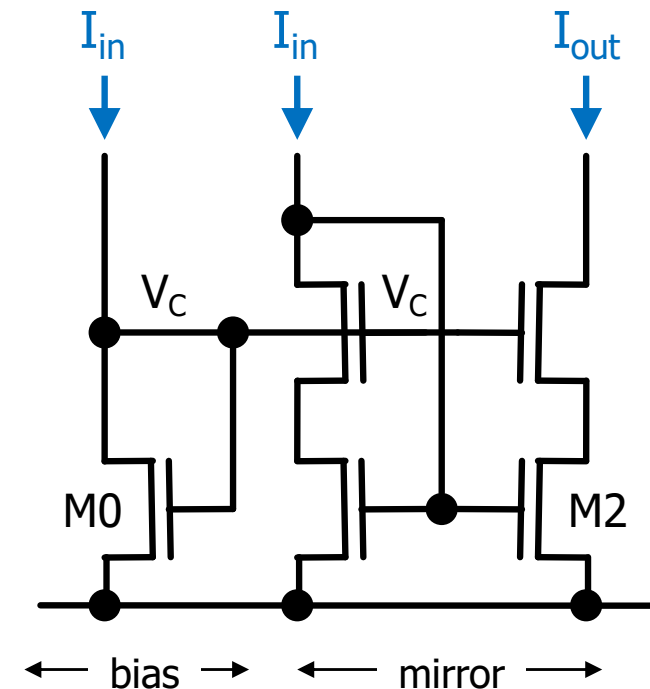Exercise: The Low Voltage Mirror

- The required optimal cascode voltage V_C can be generated *automatically* by a diode connected MOS M0 with different geometry than the others:
 $(W/L)_0 = k (W/L)_{\text{others}}$
- We assume that we have a second input current I_{in} available (both I_{in} s are equal)



- *Calculate* k so that M2 is just saturated.
 - Use the *large signal* model in strong inversion with no Early effect
- Simulate the circuit




Exercise: An *Even* Better Mirror

- The key trick is obviously to keep the drain voltage of M2 very constant irrespective of the output voltage.
- This can be done with an active circuit (with an amplifier):
 - Amp amplifies the difference of the two input voltages by A_0
 - Where is the positive/negative input for stable operation?
 - Simulate the circuit. Use a voltage controlled voltage source vcvs from the analogLib for Amp with $A_0=1000$

- *Calculate* the output resistance!

 - This topology is called the *Regulated Mirror*





Exercise (Advanced): Implementing the Regulated Mirror

- The amplifier in Ex. 7 can be implemented by a gain stage
- Simulate such a circuit!
- You can use a Spice current source in the regulation amplifier to start with...
- Explain why V_D is not optimal. Can you use a transistor with low threshold?
- You could also cascode in the gain stage...

