



Exercise: CAM - Part 1


Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



SRAM Cell

- Create the symbol of a SRAM cell

 


- Pins should be: **Bit**, **BitB**, **Word**
- Make a schematic
 - Use global nets vdd! and gnd! for the supplies
 - Use minimal lengths for the NMOS
 - Use WNWRITE for the write NMOSs, WNINV for the others
 - Use WPINV and LPINV for the PMOSs
 - Start with $W=0.44\mu\text{m}$ for all MOS and min. length PMOS.



Simulating ONE SRAM cell

 - Create the following schematic SIM_SRAM



- Use wide (10 μm), minimum length MOS for driving
- You can use a VCVS for the inverter
- Create control signals which
 - Write 0 to the SRAM, then read it back. Then try writing 1.
 - You can create a signal with multiple pulses by stacking vpulses
 - Use for instance 5ns for precharge



Simulating MULTIPLE cell

- Add a second SRAM cell
 - You also need a further control signal Word2

- Create signals for the following sequence
 - Write 0 to the first RAM cell
 - Write 1 to the second RAM cell
 - Read back the first cell
 - Read back the second cell

 - Make a drawing of the signals on paper first!
 - Work e.g. in steps of 5 ns

- Add additional capacitance to the bit lines until the circuit stops working




Transistor Dimensions

- Play with the dimensions of the transistors
- Find out in which ranges the cell works
- Add an OFFSET of 0.1V to one of the inverters in the SRAM cell (using a VDC source) and repeat the above exercise.



CAM Cell

 - Starting from the SRAM cell, make a CAM cell



- Add a **Match** signal
- Use minimal length NMOS with WNMATCH
- Simulate the cell in schematic SIM_CAM:
 - Write 0 as before
 - Precharge the match line
 - Present comparison data at the bit lines (once matching, once mismatching)



Layout

- In the layout
 - Word and Match shall run horizontally
 - the two bit lines vertically
 - Power can go either way
 - No not put substrate or NWEELL contacts in each CAM cell
 - Use only M1 - M3

- Before going in layout details, investigate on a paper various options for component and bus placement
 - Make sure cells can be placed directly adjacent to each other (maybe flipped or mirrored)
 - Try to minimize the NWEELL area (and spacings) required
 - Keep your findings on 'good' (or 'bad') transistor sizes in mind!

- Do it!