



Graded Exercise VLSI Design WS24/25:

Binary Multiplier

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



The Task

- In this exercise, you should create a full custom implementation of a digital **binary multiplier** circuit
 - The input are two N bit binary numbers A, B, i.e. bus signals $A\langle N-1:0\rangle$ and $B\langle N-1:0\rangle$
 - We restrict ourselves to positive values, i.e. $A \geq 0$, $B \geq 0$
 - The result is a 2N bit wide SUM vector
 - You may choose $N=4\dots 8$. If you work systematically, there is nearly no extra effort for larger N.
- We will implement the multiplier as a very simple ‘array multiplier’. This is not very efficient, there are much more clever implementations (‘Wallace Tree’, ‘Booth Encoding’)
- You should do
 - A hierarchical schematic
 - Analog simulations of basic elements
 - A Mixed Mode Simulation of the full multiplier
 - A nice, compact layout which is DRC and LVS clean.



How Multiplication Works

- Multiplication of integers can be done with the 'school' method.
- One input number (here $A=13$) is multiplied with all digits of B (here 1234) -> 'partial products'
- The partial products are added, respecting digit position
- The summing can create overflows (carry) from a lower to a high digit position


A	B		
<u>13</u>	x	<u>1234</u>	
		52	← 13 x 4
		39	← 13 x 30 = 13 x 3, shifted 1 to the left
		26	← 13 x 200 = 13 x 2, shifted 2 to the left
		<u>13</u>	← 13 x 1000 = 13 x 1, shifted 3 to the left
Carry		1 1	
Sum:		16042	

↑
'partial product'



Multiplication With Binary Numbers

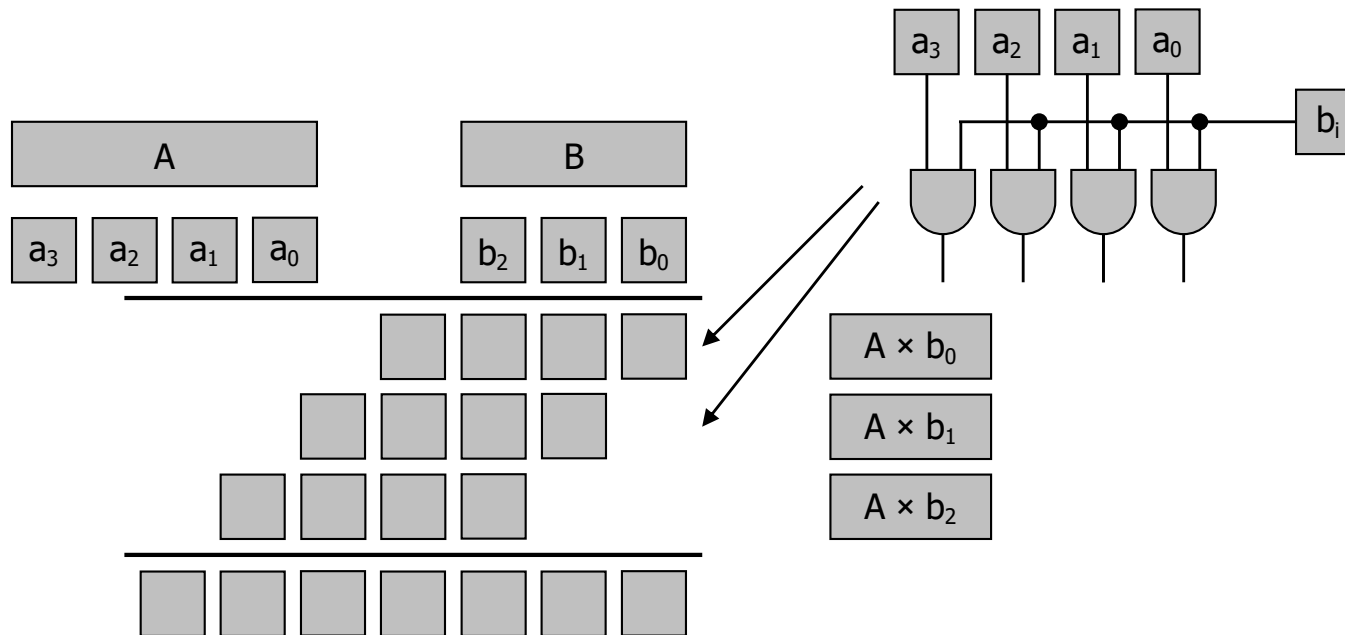
- In binary, digits can only take 0/1, so the row multiplication is trivial:
 - $A \times 0 = 0$
 - $A \times 1 = A$
- We need just an AND gate on all bit positions!





Summing Up

 - Adding up the upper 2 rows requires a digital adder
- This is made up from **full adder circuits**:



C_{in}	b	a	C_{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- A carry signals propagates from the least significant digit to higher digits
- The first position has no carry-in, so a Half Adder can (could) be used.
- The sum is then added to the next row etc.
- Overall, N-1 rows of adders are required.



The Full Adder

- You can learn about digital logic in the slides of ‘Digitale Schaltungstechnik’ in WS21/22
 - Slides ‘Kombinatorik und Flipflops’, p15ff.
- There are many ways to make a full adder:
 - You find an efficient transistor level implementation of a full adder in the slides
 - You can also make it from two half adders
 - Or you use basic gates



1. Schematic

- Make schematics+symbols of the AND gate and the Full Adder.
- You may also make a schematic/symbol of an adder bit with the AND in front.
- Make a schematic+symbol of an N bit adder. It may be clever to have a 'normal' input and an input which is 'ANDed' with a control bit. Use bus notation to keep the schematic simple!
- Assemble the multiplier from the adders and some more stuff. Use bus notation!



(Optimizations)

- To optimize the circuit a bit you could
 - Use a NAND instead of the AND and handle the inverted signal somehow 'later'
 - Similarly live with inverting Full Adders
 - Use only a Half Adder at the first position

- As mentioned, there are more efficient ways to add up all the bits, see 'Wallace Tree', 'Dada-Tree',...



2. Analogue Simulation

- Simulate the basic cells.
 - Check that behavior is correct for all bit combinations.
- Simulate the adder for some values of X, Y
- What is the worst case speed (when a carry propagates fully through the chain) ?




3. Mixed Mode Simulation

- Check with a mixed mode simulation that the adder works correctly for some random numbers.
- Check the full multiplier for some ‘typical’ cases and for random numbers.
- How long does it need in a worst case until the result is complete. What is the ‘critical path’?



 4. Layout

- Make a compact layout of the FullAdder. Arrange the pins, power, ... such that you can place cells next to each other.
- Make the layouts of all cells in the schematic hierarchy.
- Try to make the top cell rectangular by placing the adders under each other (not shifted, as shown left)



- The layout must be DRC and LVS clean



Report

- Provide a document (10-15 pages) with
 - A summary of the task and how you solved it.
 - Explanations on how the circuits work, why you chose them as they are, and how you set up the hierarchy
 - Schematics (just screen shots), using a decent hierarchy with some explanations
 - Simulation results (function, speed) with explanations
 - Results of the mixed mode simulation + Verilog code
 - A 'nice' layout (screenshots). Explain your reasonings.



Bonus

- For a very good grade
 - your description should be complete and decently formatted
 - Schematics should be tidy
 - You may simulate transistor speed corners to see how slow the circuit can get in the worst case.
 - Layout should be rather compact (most space occupied by MOS)
 - You could implement an adder of variable size as a PCELL, similarly for the full multiplier, so that you can instantiate a NxM multiplier.
 - You may have a look at the Wallace Tree concept, explain how that works and why it is clever.